

# ELL 101: INTRODUCTION TO ELECTRICAL ENGINEERING

## Tutorial Problem Set 2

1. Find the current  $I$  for the circuit shown in figure 1

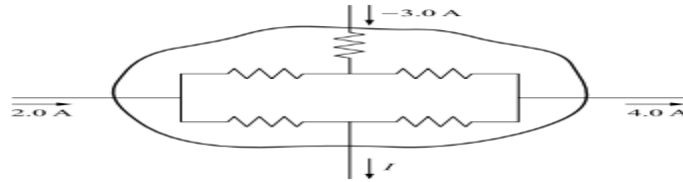


Fig. 1

2. Use branch currents in the network shown in Fig. 2 to find the current supplied by the 60-V source.

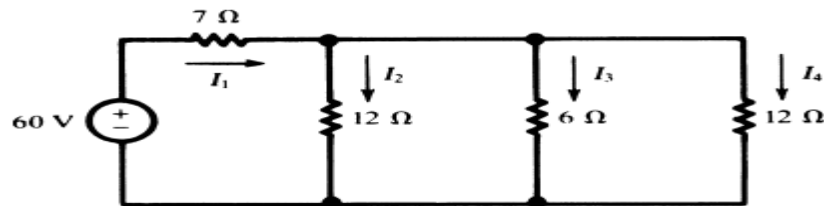


Fig. 2

3. Find the unknown voltage  $V_1$  in the circuit of Fig. 3.

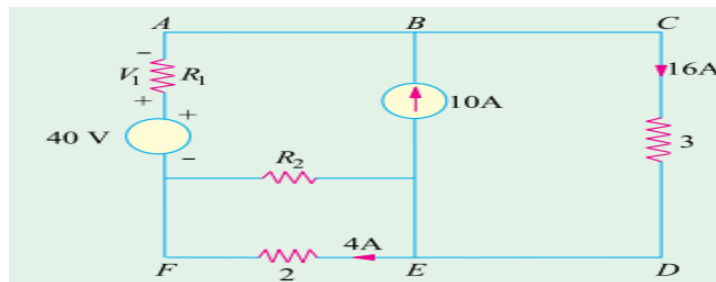


Fig. 3

4. What is the voltage  $V_S$  across the open switch in the circuit of the given figure?

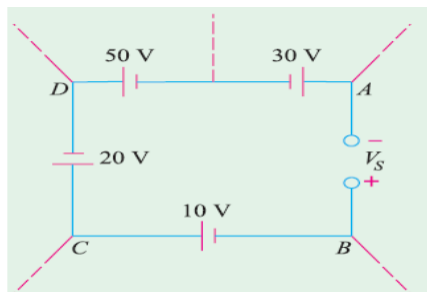


Fig. 4

5. Find the value of unknown voltage in the given circuit

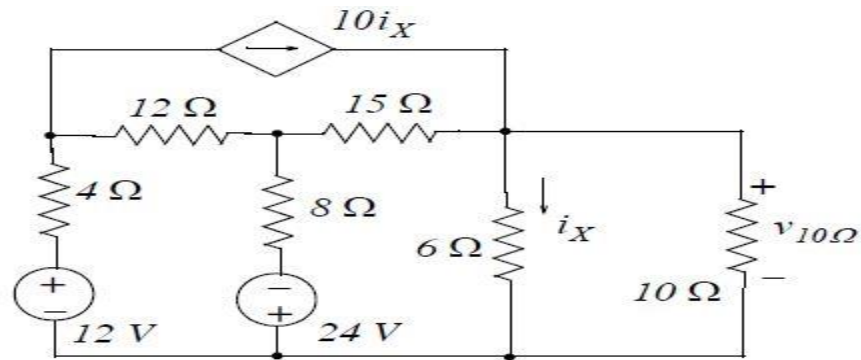


Fig. 5

6. Determine the voltage labeled  $v$  in the circuit of the figure shown below.

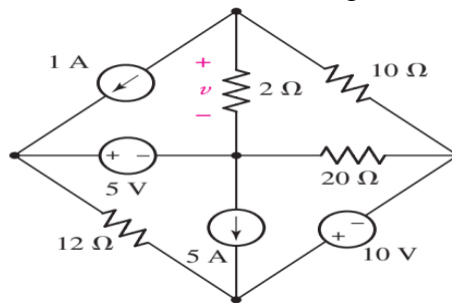


Fig. 6

7. For the circuit shown in the following figure, determine the value of the voltage labelled  $v_1$  and the current labeled  $i_1$ .

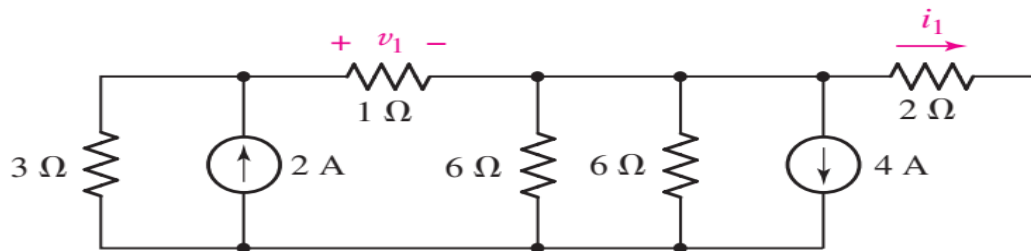


Fig. 7

8. Determine the voltage  $v$  as labeled in the following figure, and calculate the power supplied by each current source.

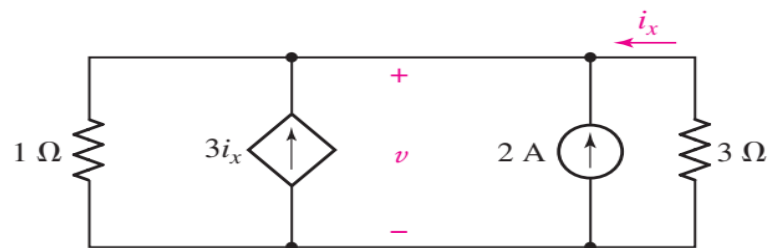


Fig. 8

9. The voltage  $V$  shown in the figure below is:

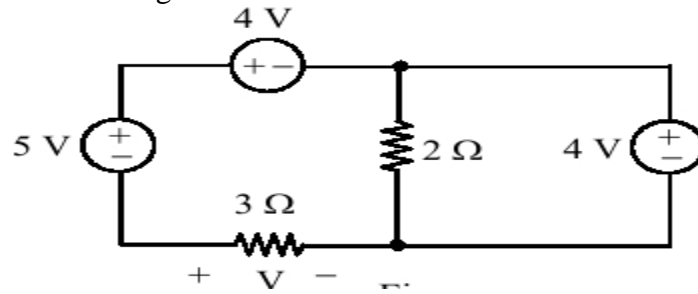


Fig. 9

10. The circuit shown in Fig. 14 is a voltage divider, also called an attenuator. When it is a single resistor with an adjustable tap, it is called a potentiometer, or pot. To discover the effect of loading, which is caused by the resistance  $R$  of the voltmeter  $VM$ , calculate the ratio  $V_{out}/V_{in}$  for (a)  $R = \infty$ , (b)  $1\text{ M}\Omega$ , (c)  $10\text{ k}\Omega$ , and (d)  $1\text{ k}\Omega$ .

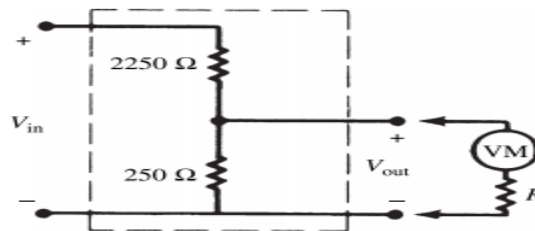


Fig. 10

11. Find the value of  $V$  in the given circuit

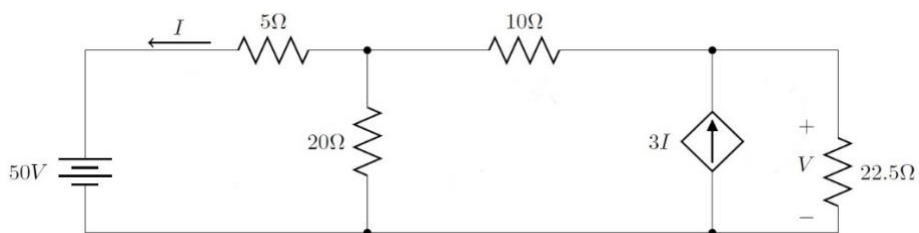


Fig. 11

12. Find the value of  $I_1$  in the given circuit

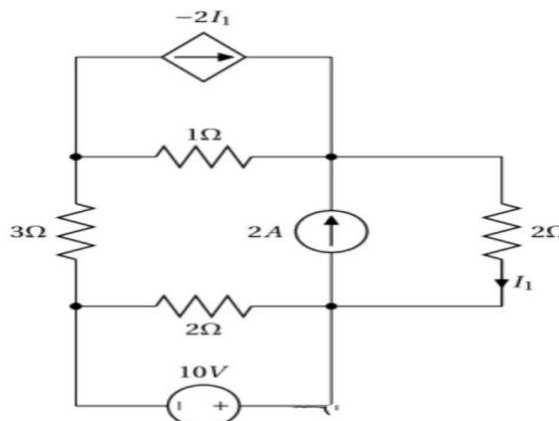


Fig. 12

13. Find the value of current  $I_1$ ,  $I_2$ ,  $I_3$ .

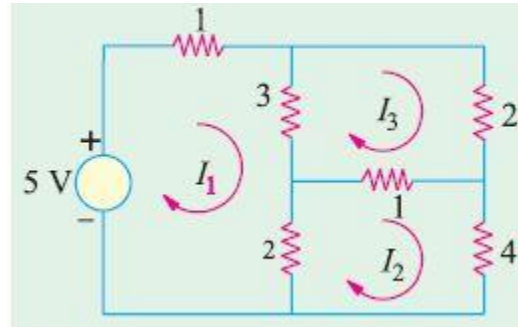


Fig. 13

14. Determine numerical values for each of the three mesh currents as labeled in the circuit diagram of following figure

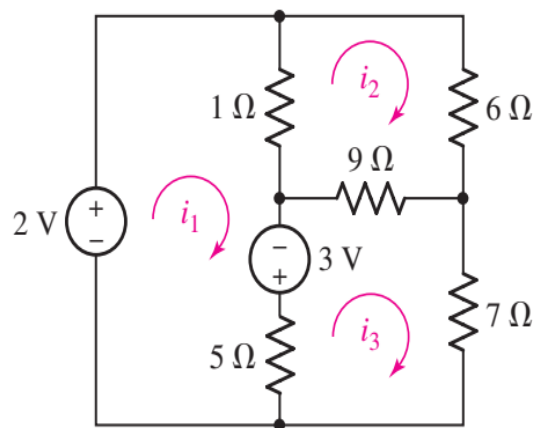


Fig. 14

15. For the circuit of following figure, determine the mesh current  $i_1$  and the power dissipated by the  $1\ \Omega$  resistor.

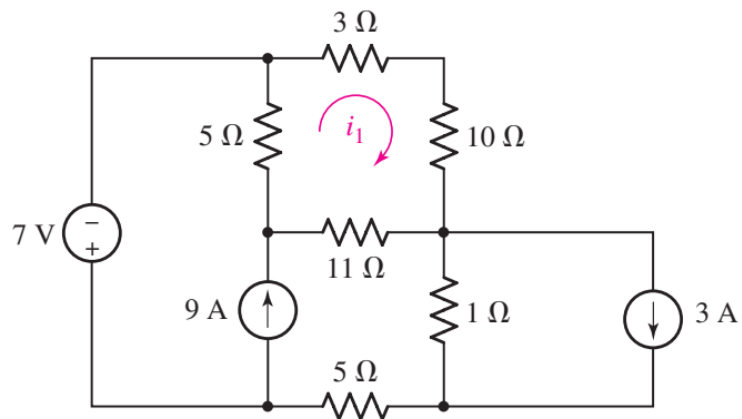


Fig. 15

16. Calculate the mesh currents  $i_1$  and  $i_2$  for the circuit shown in the figure below:

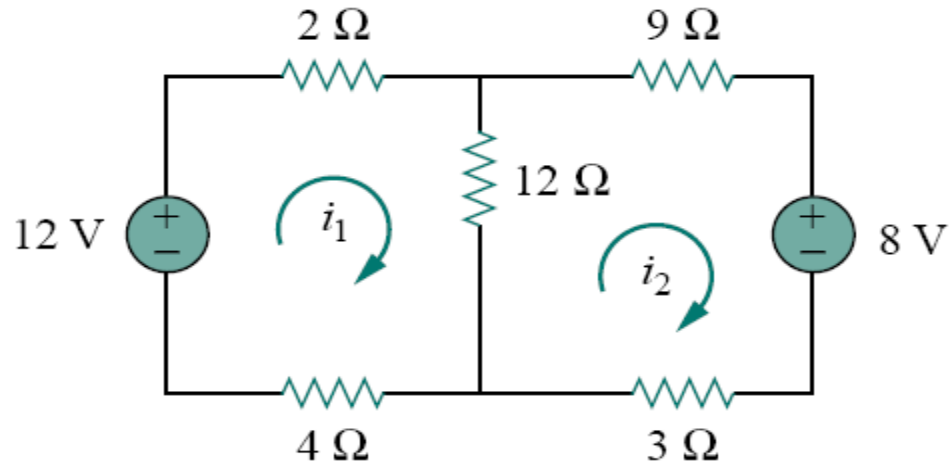


Fig. 16

17. For the circuit shown in Fig.17, find the branch currents  $I_1$ ,  $I_2$  and  $I_3$  using mesh analysis.

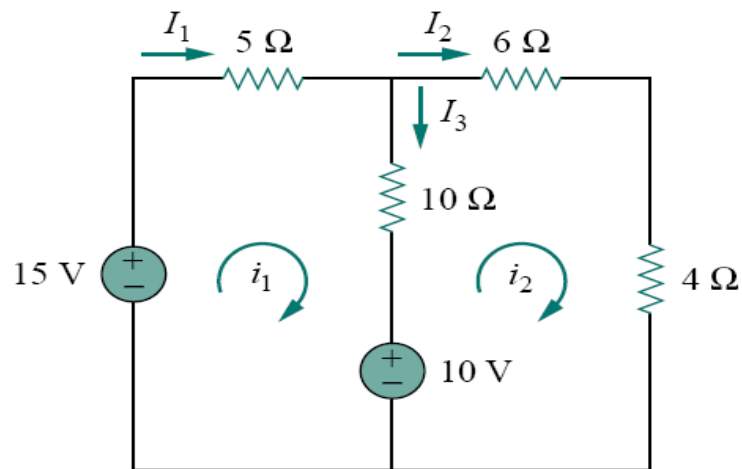


Fig. 17

18. Find the voltage  $V_{ab}$  in the network shown in Fig. 18.

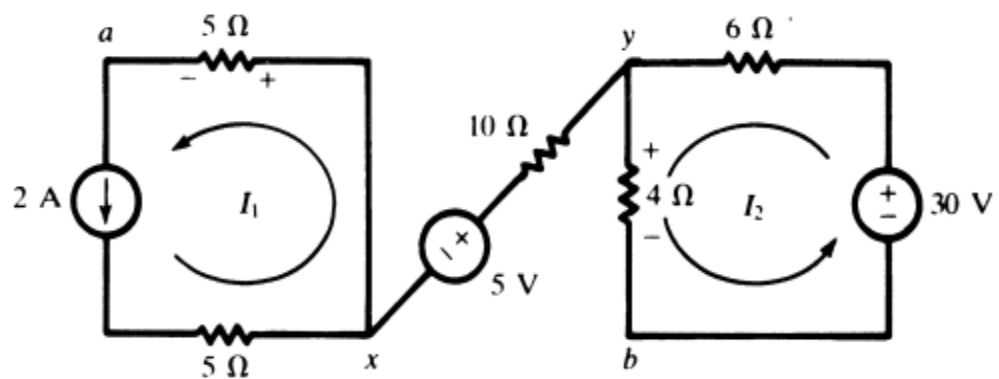


Fig. 18

19. Obtain the total power supplied by the 60-V source and the power absorbed in each resistor in the network.

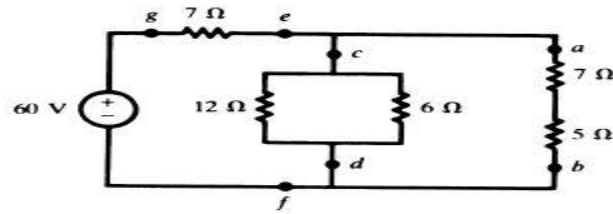


Fig. 19

20. For the network shown in Fig. 20, find  $V_s$  which makes  $I_0 = 7.5$  mA.

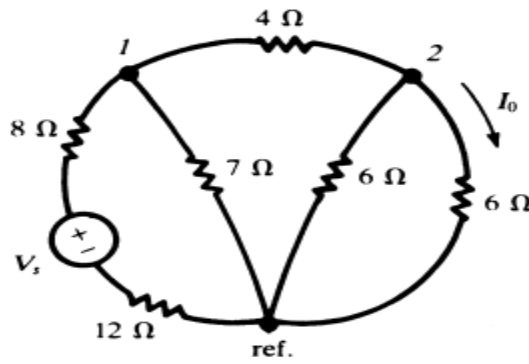


Fig. 20