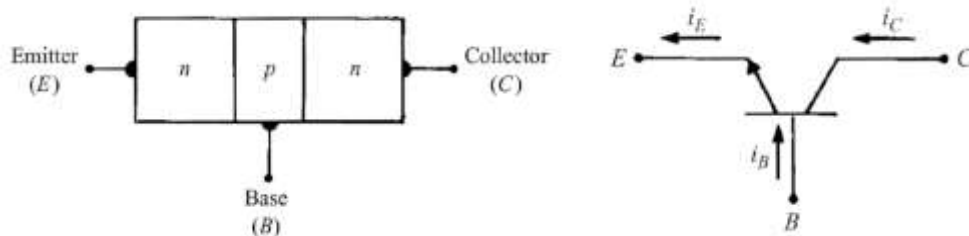


## Tutorial Sheet

### Bipolar Junction Transistor

- In a npn transistor,  $10^8$  holes/ $\mu\text{s}$  move from the base to the emitter region while  $10^{10}$  electrons/ $\mu\text{s}$  move from the emitter to the base region. An ammeter reads the base current as  $I_B = 16\mu\text{A}$ .

a) Determine the emitter current  $I_E$  and the collector current  $I_C$ .



b) For the previous example, find the  $\alpha$  and  $\beta$ , if the leakage currents are considered negligible, and the described charge flow is constant.


Given data: npn transistor,  $I_B = 16\mu\text{A}$ ,  $I_E = 1.618\text{mA}$ ,  $I_C = 1.602\text{mA}$

- A BJT has  $\alpha = 0.99$ , Base current,  $I_B = 25\mu\text{A}$ , Leakage current,  $I_{CBO} = 200\text{nA}$


Find the following parameters:

- DC collector Current
- DC emitter Current
- % Error in the emitter current when the leakage current is neglected.

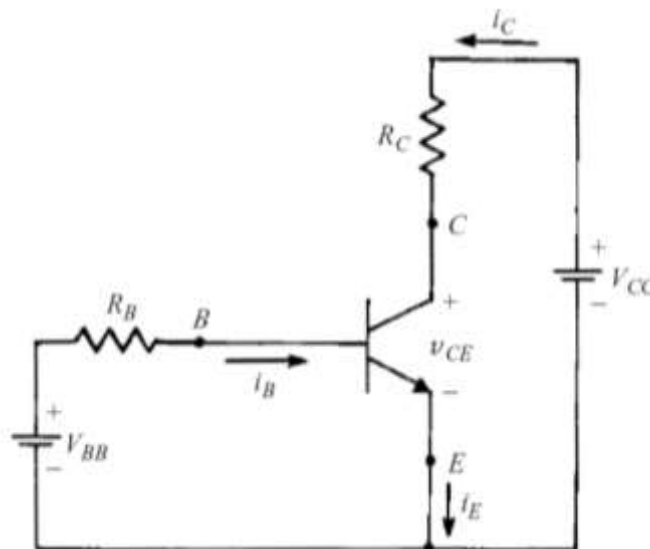
- In the circuit of Figure,  $\beta = 100$ ;  $I_{BQ} = 20\mu\text{A}$ ,  $V_{CC} = 15\text{V}$  and  $R_C = 3\text{k}\Omega$ . If  $I_{CBO} = 0$ , find (a)  $I_{EQ}$  b)  $V_{CEQ}$ . (c) Find  $V_{CEQ}$  if  $R_C$  is changed to  $6\text{k}\Omega$  and all else remains the same.



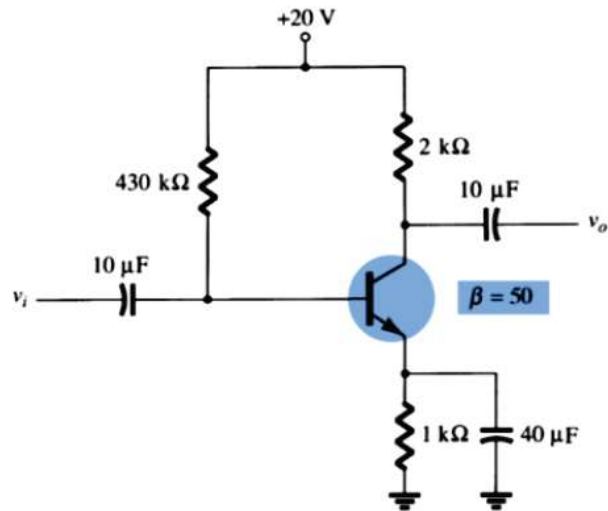- For the emitter bias circuit shown below, determine collector current  $I_C$  (in mA). Assume  $V_{BE} = 0.7\text{V}$



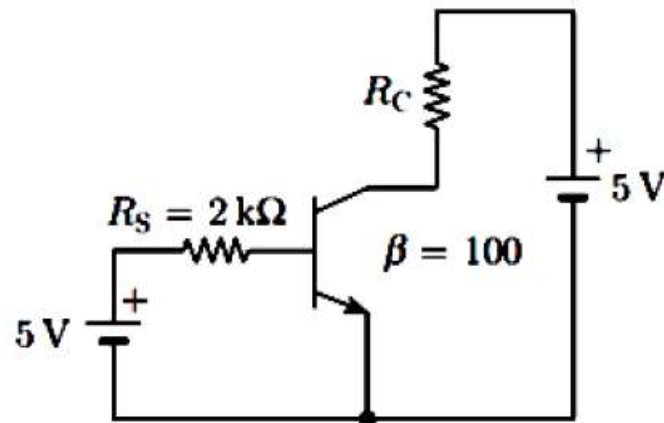5. The transistor in the given circuit should always be in the active region. Take  $V_{CE(\text{Sat})} = 0.2 \text{ V}$ ,  $V_{BE} = 0.7 \text{ V}$ . What is the maximum value of  $R_c$  in  $\Omega$  which can be used?



6. In the circuit of given figure  $V_{CC} = 12 \text{ V}$ ,  $V_S = 2 \text{ V}$ ,  $R_C = 4 \text{ k}\Omega$ , and  $R = 100 \text{ k}\Omega$ . The Ge transistor is characterized by  $\beta = 50$ ;  $I_{CEO} = 0$ , and  $V = 0.2 \text{ V}$ . Find the value of  $R$  (in  $\text{k}\Omega$ ) that just results in saturation if the capacitor is replaced with a short circuit.  $V_{BE}$  for germanium transistor =  $0.3 \text{ V}$

