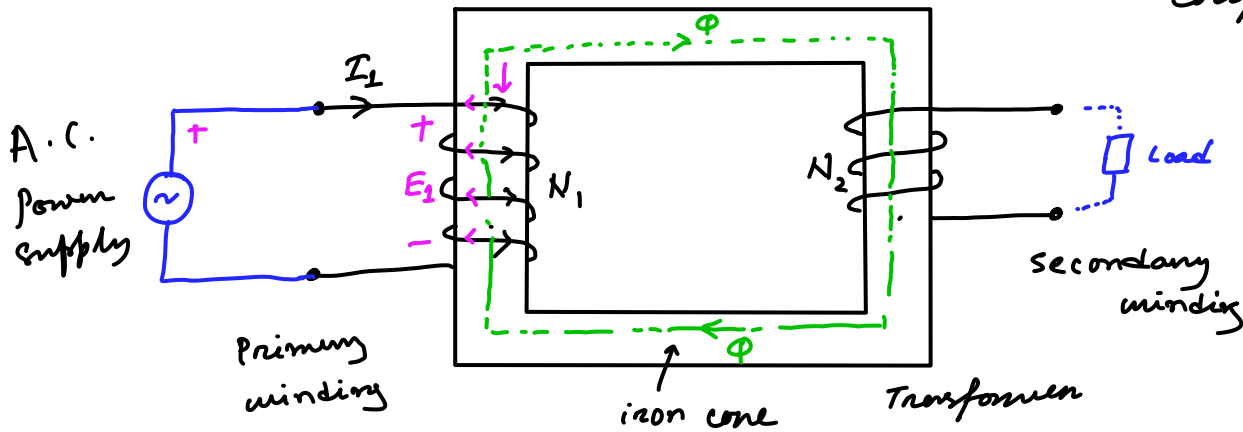


TRANSFORMER

↓
Magnetic circuit
↓

It transfers energy/power from one electric circuit to another, which are magnetically coupled.



(Fig-1)

- Connect transformer primary winding to an A.C. source
- The flux

$$\Phi = \frac{\mathcal{F}}{R_{\text{total}}} = \frac{N_1 I_1}{R_c}$$

- The nature of flux is also time-varying since I_1 is time varying.
- Ideal Transformer (Assumptions)
 - The resistance of the winding is neglected.
 - There is no leakage flux. The flux produced are all inside the core.

→ B is linear function of H

$$B = \mu_0 H \quad \Rightarrow \quad \phi \text{ is linear with } \mathcal{F}$$

* → There is no core-loss (no eddy current loss & no hysteresis loss)

$$I_1 = I_{\max} \sin \omega t \quad \text{where } \omega = 2\pi f$$

$$\phi = \phi_{\max} \sin \omega t \quad \left(\sin \phi = \frac{V}{R} \right) \quad \text{frequency } 50 \text{ Hz}$$

Emf in primary side (we have kept secondary open)

$$e_1 = -N_1 \frac{d\phi}{dt}$$


$$= -N_1 \omega \phi_{\max} \cos \omega t$$

$$= \underbrace{N_1 \omega \phi_{\max}}_{E_{\max}^1} \sin(\omega t - \pi/2)$$

R.M.S. value of primary side emf

$$E_1 = \frac{E_{\max}^1}{\sqrt{2}} = \frac{2\pi f N_1}{\sqrt{2}} \phi_{\max}$$

$$E_1 = \sqrt{2} \pi f N_1 \phi_{\max}$$

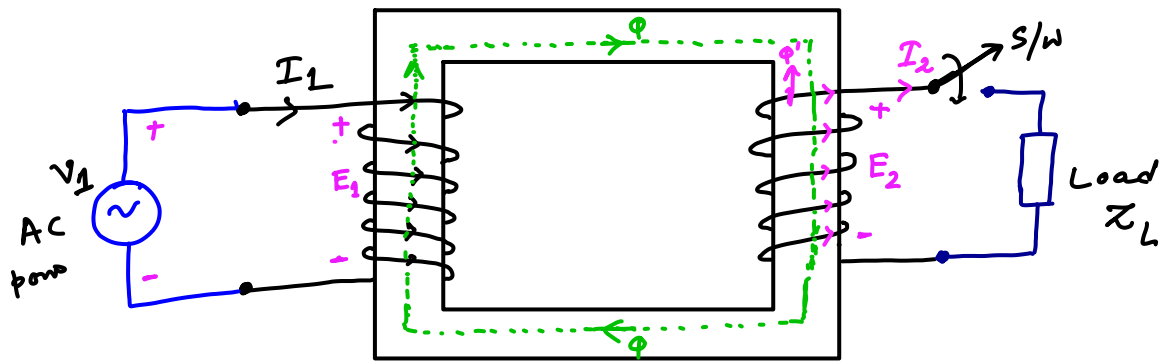

(Fig - 2)

Secondary side emf

$$\begin{aligned}
 e_2 &= -N_2 \frac{d\phi}{dt} \\
 &= -N_2 \omega \phi_{\max} \cos \omega t \\
 &= \underbrace{N_2 \omega \phi_{\max}}_{E_{\max}^2} \sin(\omega t - \pi/2)
 \end{aligned}$$

Secondary side emf

$$\text{R.M.S. } E_2 = \frac{E_{\max}^2}{\sqrt{2}} = \sqrt{2} \pi f N_2 \phi_{\max}$$

$$E_2 = \sqrt{2} \pi f N_2 \phi_{\max}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \Rightarrow E_2 = \left(\frac{N_2}{N_1} \right) E_1$$




- When $N_1 < N_2$ (Step-up transformer)
- when $N_2 < N_1$ (Step-down transformer)

$$I_1 = I_{\max} \sin \omega t$$

$$\phi = \phi_{\max} \sin \omega t$$

$$E_1 = E_{\max}^2 \sin(\omega t - \pi/2)$$
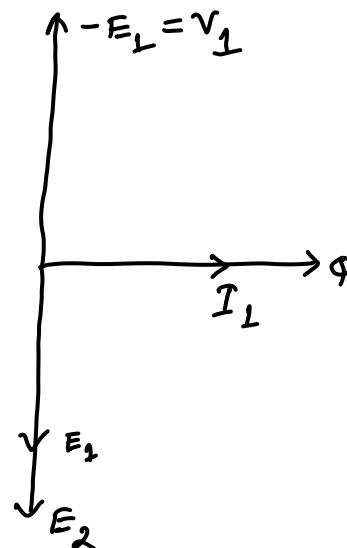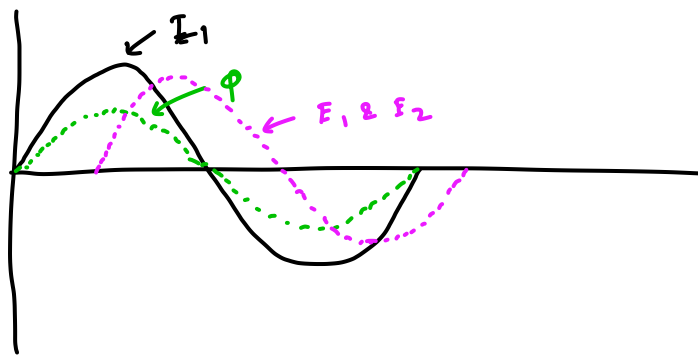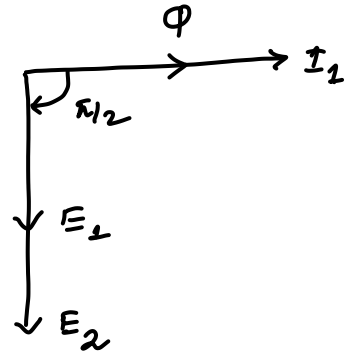
$$E_2 = E_{\max}^2 \sin(\omega t - \pi/2)$$



• By neglecting the resistance of the winding

$$V_1 = E_1$$

$$E_1 = \sqrt{2} \pi f N_1 \Phi_{\max}$$

- For ideal transformer (windings resistance is neglected)

$$V_1 = E_1 = \sqrt{2} \pi f N_1 \Phi_{\max}$$

$$\Phi_{\max} = \frac{V_1}{\sqrt{2} \pi f N_1}$$

- The flux in the core is completely determined by V_1 , f , N_1 .

- As long as the applied/supplied voltage remains const., the flux in the core will also remain const.

→ After closing S/W

Under Load - connected condition

- A secondary current I_2 will flow, which is determined by the load.

↓

- A flux Φ' will create to oppose the existing flux Φ in the core.

- Since $\Phi_{max} = \frac{V_1}{\sqrt{2} \pi f N_1}$,

↓

the flux Φ in the core will remain const. as long as V_1 is const.

- Sim $\Phi = \frac{N_1 I_1}{\mathcal{R}_c}$ $\Phi' = \frac{N_2 I_2}{\mathcal{R}_c}$,

↓

To maintain const. flux Φ in the core,
there will be more current flow
from primary side I_1'

$$I_1 = I_\phi + I_1'$$

↓

to magnetize
the core

↓

to maintain
flux Φ in the core

Load component of
primary current.

- In an ideal transformer,

$$I_1 = I_1' \quad \text{as } I_\phi \text{ is neglected in comparison to } I_1'.$$

- To maintain the const flux in the core the mmf of both side must be balanced.

$$N_1 I_1' = N_2 I_2 \quad \phi = \frac{N_1 I_1}{\mathcal{R}} \quad \phi' = \frac{N_2 I_2}{\mathcal{R}}$$

from ideal transf \Rightarrow $N_1 I_1 = N_2 I_2$

$$\Rightarrow I_1 = \left(\frac{N_2}{N_1} \right) I_2$$


$$E_2 = \left(\frac{N_2}{N_1} \right) E_1$$

$$\frac{E_2}{I_1} = \frac{E_1}{I_2} \Rightarrow E_2 I_2 = E_1 I_1$$

- The volt-ampere of primary side is equal to the volt-amp. in secondary side.

$$e_2 i_2 = e_1 i_1$$
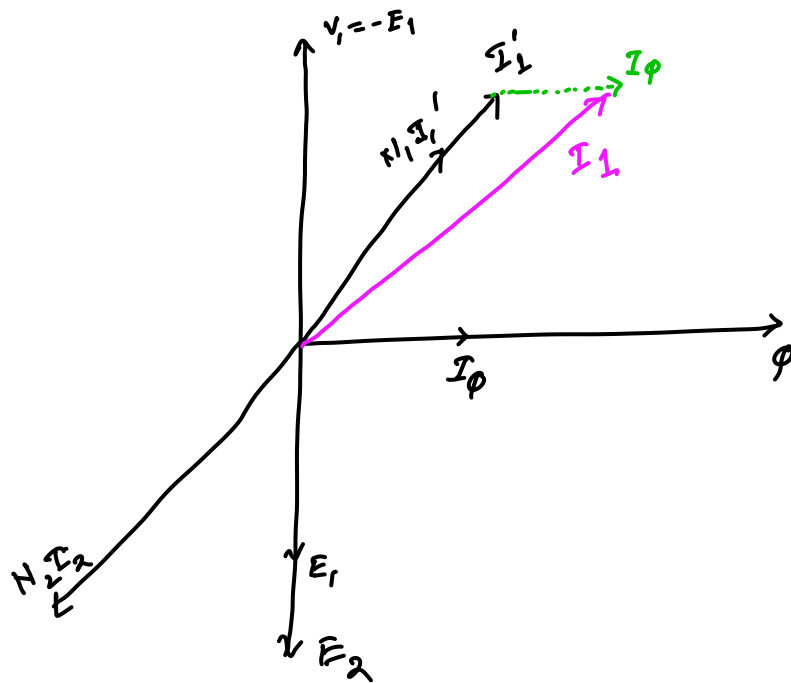
$$v_1 i_1 = v_2 i_2 \quad \text{for ideal transformer}$$



$$N_1 I_1' = N_2 I_2$$

$$I_1 = I_\phi + I_1'$$

- For an ideal transformer :
The instantaneous power at primary & secondary will remain equal.