

# ELL101: INTRODUCTION TO ELECTRICAL ENG.



## Nodal Analysis

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik, Harshan Jagadeesh


Department of Electrical Engineering, IITD

1

## Nodal Analysis
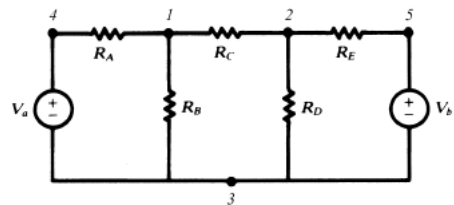
### Introduction

- Popularly known as Node Voltage Analysis
- It is a technique used to find the voltages at the nodes of the circuit
- It is based upon KCL
- It results in system of linear equations that can be solved for unknown voltages
- Number of node voltages = Number of nodes – 1




Source: M. Nahvi and J. A. Edminister, *SCHAUM's Outline: Electric Circuits*, McGRAWHILL Edu., 2018.

2

## Nodal Analysis
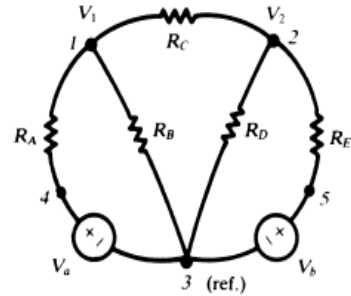
### How to Apply Nodal Analysis

- Identify the nodes available in the circuit
- Identify the node that can be assigned as the reference node
- Assign the voltage to all the other nodes
- Apply the KCL at each node to get the equations
- Solve the equations to get the values of voltage




Source: M. Nahvi and J. A. Edminister, *SCHAUM's Outline: Electric Circuits*, McGRAWHILL Edu., 2018.

3

## Nodal Analysis

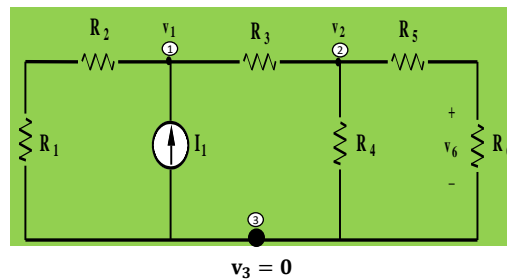Example 1: Use nodal analysis to form voltage relations for the given circuit



Step 1: The given circuit has three nodes

Step 2: The lowermost node has been taken as reference node and its voltage has been set zero

Step 3: All the other nodes had been assigned an unknown voltage

4

## Nodal Analysis

Step 4: Apply KCL at node 1:

$$I_2 + I_3 = I_1$$


$$\Rightarrow \frac{V_1}{R_1 + R_2} + \frac{V_1 - V_2}{R_3} = I_1 \quad (1)$$

Step 5: Apply KCL at node 2:

$$I_4 + I_5 = I_3$$

$$\Rightarrow \frac{V_2}{R_4} + \frac{V_2}{R_5 + R_6} = \frac{V_1 - V_2}{R_3} \quad (2)$$

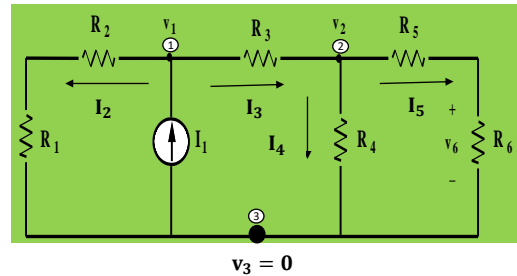
Solving the above equations we can get the value of Voltages  $V_1$  and  $V_2$



5

## Nodal Analysis

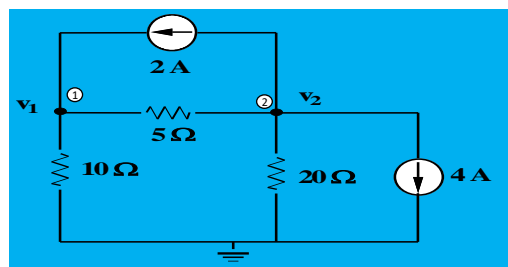Example : Find the values of unknown voltages  $V_1$  and  $V_2$  in the given circuit




KCL at node 1

$$\frac{V_1}{10} + \frac{V_1 - V_2}{5} = 2$$

KCL at node 2
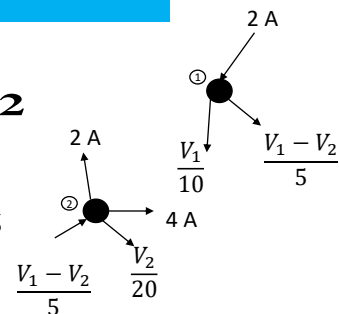
$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} = -6$$



6

## Node Analysis

Equation at node 1 can be simplified to

$$3V_1 - 2V_2 = 20 \quad (1)$$

Equation at node 2 can be simplified to

$$5V_2 - 4V_1 = -120 \quad (2)$$

Solving (1) and (2) we get the values of unknown voltages as

$$V_1 = -20 \text{ and } V_2 = -40$$


7

## Nodal Analysis


### Various cases in Nodal Analysis

**Case 1:** Voltage source in the circuit (connected with the reference node)

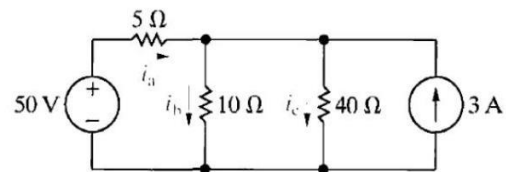Example: Use nodal analysis to find the value of unknown currents



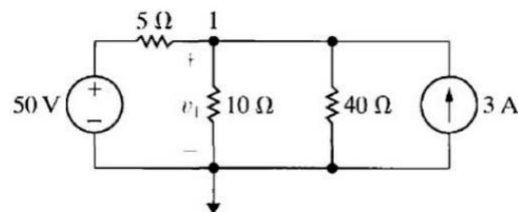Assigning voltages to the different nodes




8
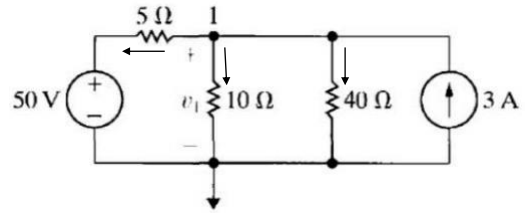
## Nodal Analysis

Applying KCL at node 1

$$\frac{v_1 - 50}{5} + \frac{v_1}{10} + \frac{v_1}{40} - 3 = 0$$



Solving the above equation we get  $v_1 = 40\text{V}$

Now, using the above value of  $v_1$  we can find  $i_a$ ,  $i_b$ , and  $i_c$  as


$$i_a = -(v_1 - 50) / 5 = 2\text{A} ; i_b = v_1 / 10 = 4\text{A} ; i_c = v_1 / 40 = 1\text{A}$$

9

## Nodal Analysis

**Case 2:** When there is voltage source (not connected with reference node)

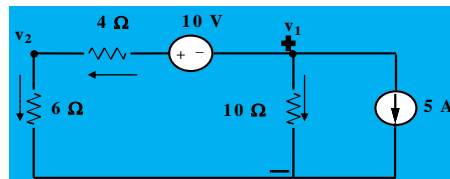Example: Find the values of unknown voltages in the given circuits



$$\text{KCL at } V_1: \frac{V_1}{10} + \frac{V_1 + 10 - V_2}{4} = -5$$

$$\text{KCL at } V_2: \frac{V_2}{6} + \frac{V_2 - 10 - V_1}{4} = 0$$

10

## Node Analysis

Equation at  $V_1$  can be simplified to

$$7V_1 - 5V_2 = -150 \quad (1)$$

Equation at  $V_2$  can be simplified to

$$5V_2 - 3V_1 = 30 \quad (2)$$

Solving (1) and (2) we get the values of unknown voltages as


$$\mathbf{V_1 = -30V \text{ and } V_2 = -12V}$$

11

## Nodal Analysis

**Case 3:** Supernode (Voltage source between two nodes without any resistance)

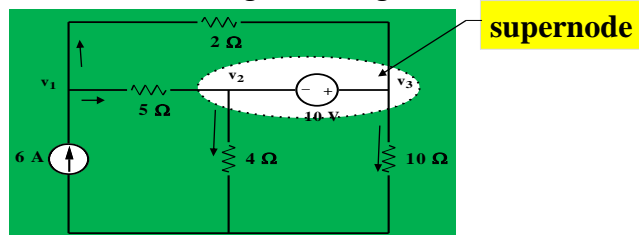Example: Find the values of unknown voltages in the given circuit



$$\text{KCL at } V_1 \quad \frac{V_1 - V_2}{5} + \frac{V_1 - V_3}{2} = 6$$

$$\text{KCL at Supernode} \quad \frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_3}{10} + \frac{V_3 - V_1}{2} = 0$$

12

## Node Analysis


Equation at  $V_1$  can be simplified to

$$7V_1 - 2V_2 - 5V_3 = 60 \quad (1)$$

Equation at supernode can be simplified to

$$9V_2 - 14V_1 + 12V_3 = 0 \quad (2)$$

$$V_2 - V_3 = -10 \quad (3)$$

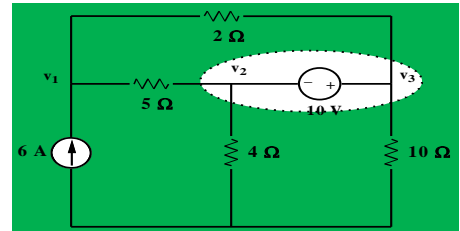

Solving (1), (2) and (3) we get the values of unknown voltages as

$$V_1 = 30V, V_2 = 14.29V \text{ and } V_3 = 24.29V$$

13


## Nodal Analysis

**Case 4:** When dependent sources are present

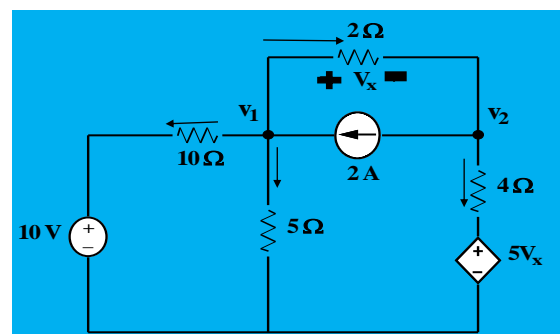Example: Find the unknown voltages

$$\text{KCL at } V_1 \quad \frac{V_1 - 10}{10} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 2$$

$$\text{KCL at } V_2 \quad \frac{V_2 - V_1}{2} + \frac{V_2 - 5V_x}{4} = -2$$



14

## Node Analysis

Equation at  $V_1$  can be simplified to


$$8V_1 - 5V_2 = 30 \quad (1)$$

Equation at  $V_2$  can be simplified to

$$3V_2 - 2V_1 - 5V_x = -8 \quad (2)$$

Also,

$$V_x = V_1 - V_2 \quad (3)$$

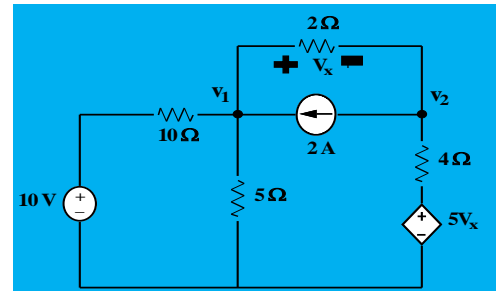


Solving (1), (2) and (3) we get the values of unknown voltages as

$$V_1 = 6.9V \text{ and } V_2 = 5.03V$$

15
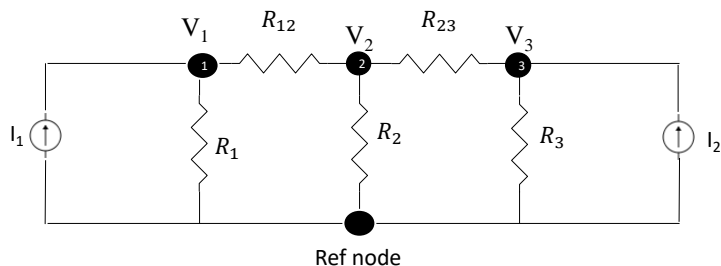
## Matrix Based Nodal Analysis

- Apply nodal analysis to find the values of  $V_1, V_2, V_3$



Need three equations to find the values of three node voltages.


16


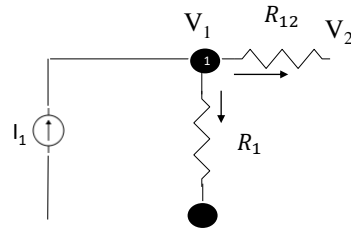
## KCL at Node 1

$$I_1 = \frac{V_1 - V_2}{R_{12}} + \frac{V_1}{R_1}$$

$$V_1 \left( \frac{1}{R_{12}} + \frac{1}{R_1} \right) - \frac{V_2}{R_{12}} = I_1$$




17
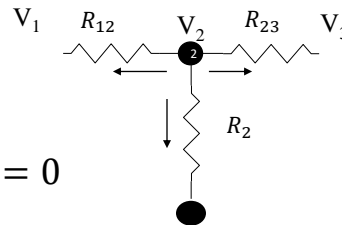
## KCL at Node 2


$$\frac{V_2 - V_1}{R_{12}} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_{23}} = 0$$

$$-\frac{V_1}{R_{12}} + V_2 \left( \frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{R_{23}} \right) - \frac{V_3}{R_{23}} = 0$$



18

## KCL at Node 3

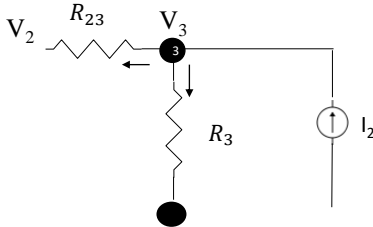

$$\frac{V_3 - V_2}{R_{23}} + \frac{V_3}{R_3} = I_2$$

$$-\frac{V_2}{R_{23}} + V_3 \left( \frac{1}{R_{23}} + \frac{1}{R_3} \right) = I_2$$

19

## System of Equations

- Node 1:


$$V_1 \left( \frac{1}{R_{12}} + \frac{1}{R_1} \right) - \frac{V_2}{R_{12}} = I_1$$

- Node 2:

$$-\frac{V_1}{R_{12}} + V_2 \left( \frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{R_{23}} \right) - \frac{V_3}{R_{23}} = 0$$

- Node 3:
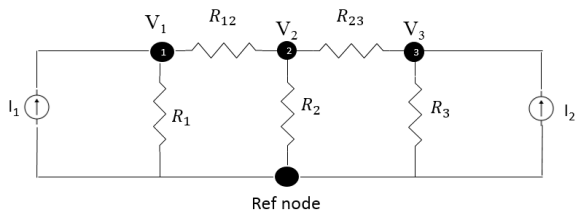
$$-\frac{V_2}{R_{23}} + V_3 \left( \frac{1}{R_{23}} + \frac{1}{R_3} \right) = I_2$$



The left side of the equation:

- The node voltage is multiplied by the sum of *conductances* of all resistors connected to the node.
- Other node voltages are multiplied by the conductance of the resistor(s) connecting to the node and subtracted.

The right side of the equation:

- The right side of the equation is the sum of currents from sources entering the node.

20

## Matrix Notation

- The three equations can be combined into a single matrix/vector equation

$$\begin{bmatrix} \left(\frac{1}{R_{12}} + \frac{1}{R_1}\right) & -\frac{1}{R_{12}} & 0 \\ -\frac{1}{R_{12}} & \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{R_{23}}\right) & -\frac{1}{R_{23}} \\ 0 & -\frac{1}{R_{23}} & \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

- The equation can be written in matrix-vector form as

$$\mathbf{AV} = \mathbf{I}$$

- The solution to the equation can be written as  $\mathbf{V} = \mathbf{A}^{-1}\mathbf{I}$

21

## Matrix Inversion

- Given the 2x2 matrix A

$$\mathbf{A} = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

- The inverse of A is

$$\mathbf{A}^{-1} = \frac{1}{ad - bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

22

Example : Find the values of unknown voltages  $V_1$  and  $V_2$  in the given circuit

$$\begin{bmatrix} \frac{1}{10} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{20} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{3}{10} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{4} \end{bmatrix}^{-1} \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{1}{\frac{3}{40} - \frac{1}{25}} \begin{bmatrix} \frac{1}{4} & \frac{1}{5} \\ \frac{1}{5} & \frac{3}{10} \end{bmatrix} \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{200}{7} \begin{bmatrix} -\frac{7}{10} & \frac{7}{10} \\ \frac{14}{10} & -\frac{10}{10} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -20 \\ -40 \end{bmatrix}$$

