
# COL216 Computer Architecture


Pipelined Processor design – Controller, Data forwarding 21st February 2022

# 5 Stage Pipeline

 


# Controllers for different design styles


# Controller for single cycle DP

 


# Controller for multi-cycle DP

 


# Controller for pipelined DP

 


# Controller for single cycle DP

 


# Controller for multi-cycle DP

 


# Controller for pipelined DP

 


### Extending inter-stage registers

 


# Controlling inter-stage registers

 

# Stalling instructions

 

# Inserting bubbles

 

### Dependence check logic

Condition to be checked:

Operand of instruction in RF stage is a register in which instruction in ALU stage or DM stage is going to write

ID/EX.RW = 1 and


(IF/ID.Rn=ID/EX.Rd or IF/ID.Rm=ID/EX.Rd)

EX/Mem.RW = 1 and

(IF/ID.Rn=EX/Mem.Rd or IF/ID.Rm=EX/Mem.Rd)

We need to ensure that instruction in RF stage actually reads Rn and/or Rm (not taken care here)

#### Dependence check

 


```
ID/EX.RW = 1 and

(IF/ID.Rn = ID/EX.Rd or


IF/ID.Rm = ID/EX.Rd)
```

#### Dependence check

 


EX/Mem.RW = 1 and (IF/ID.Rn = EX/Mem.Rd or IF/ID.Rm = EX/Mem.Rd)

# Data forwarding paths

 


# Data forwarding path P1

 


# Control for forwarding path P1

fwdA = 1 ifEX/Mem.RW = 1 and EX Mem **WB** EX/Mem.Rd = ID/EX.Rn EX/Mem ID/EX Mem/WB reader writer fwdA rd ad DM fwdB fwdC Path P1 Path P2 Path P3


# Data forwarding path P2

 


# Control for forwarding path P2

 


# Data forwarding path P3

 

# Control for forwarding path P3

 

# Stalling with data forwarding

 

# Thanks