

ELL101: INTRODUCTION TO ELECTRICAL ENG.



Mesh Analysis

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik, Harshan

Jagadeesh

Department of Electrical Engineering, IITD

1

MESH ANALYSIS


Introduction

- Popularly known as Mesh Current Analysis
- It is a technique used to find the currents circulating around a loop or mesh with in any closed path of a circuit
- It is based upon KVL
- It results in system of linear equations that can be solved for unknown currents
- Number of mesh currents = Number of Branches – Number of nodes + 1


2

Mesh Analysis

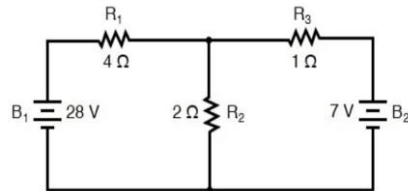Example: Apply the Mesh Analysis to get the values of current for the given circuit



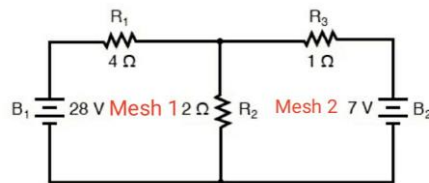
- Step 1: Identify the number of meshes in the circuit




3

Mesh Analysis

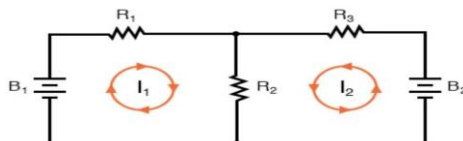- Step 2: Assign the current value to each mesh



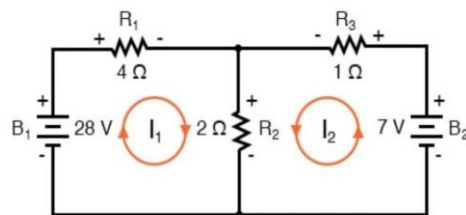- Step 3: Apply the KVL to form the linear equations




4

Mesh Analysis

Applying KVL at both the loops we get

$$\text{Mesh 1: } 4I_1 + 2(I_1 + I_2) = 28$$
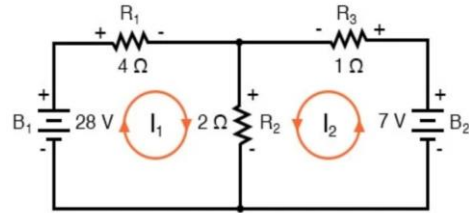
$$\text{Mesh 2: } 2(I_1 + I_2) + I_2 = 7$$



- Step 4: Solving the equation to get the values of current

$$\text{Mesh 1: } 6I_1 + 2I_2 = 28$$

$$\text{Mesh 2: } 2I_1 + 3I_2 = 7$$


Answer: $I_1 = 5\text{A}$; $I_2 = -1\text{A}$

5


Mesh Analysis

Various Cases in Mesh Analysis

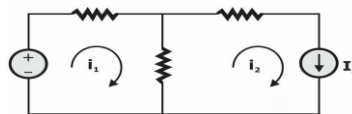Case 1: When current source exist in one mesh only



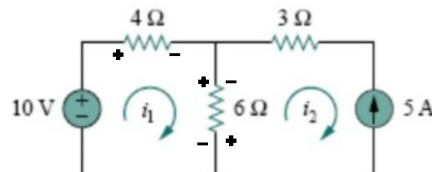Example: Find the current for the given circuit



$$\text{Mesh 1: } 4i_1 + 6(i_1 - i_2) = 10$$


$$\text{Mesh 2: } i_2 = -5\text{A}$$

Using the above equations we get the value of i_1 as: $i_1 = -2\text{A}$


6

Mesh Analysis

Case 2: Supermesh

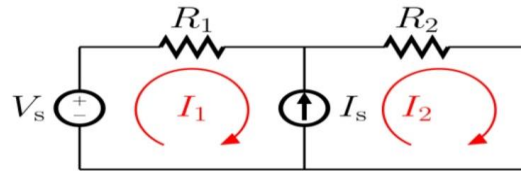

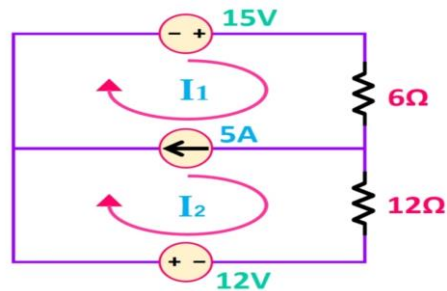Example: Find the currents for the given circuit





7

Mesh Analysis

Solution:

Step 1: Apply the supermesh

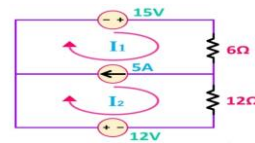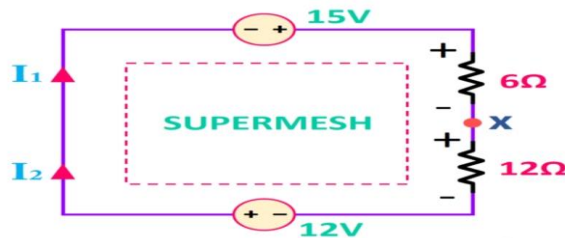

Step2: Apply KVL in supermesh to form the linear equation

$$\text{Supermesh: } 6I_1 + 12I_2 = 27$$


$$\text{Equation at Current source: } I_1 - I_2 = 5$$

Solving both the equation we get the values as: $I_1 = 29/6$, $I_2 = -1/6$


8

Mesh Analysis

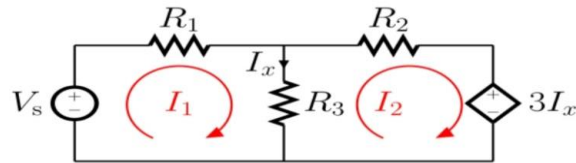Case 3: When Dependent source is there in the mesh



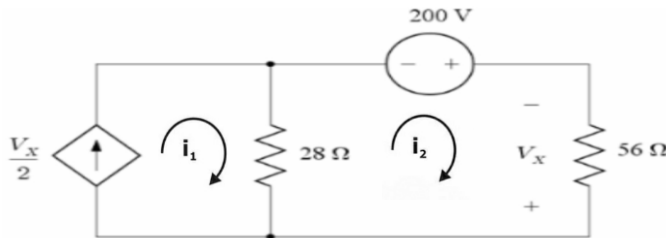Example: Find the currents in the given circuit



9

Mesh Analysis


Solution: Apply Ohm' law to find the value of V_x in terms of I_2

$$V_x = -56 I_2 \quad (1)$$

Apply KVL in both the mesh to form the equation

$$I_1 = V_x/2 \quad (2)$$
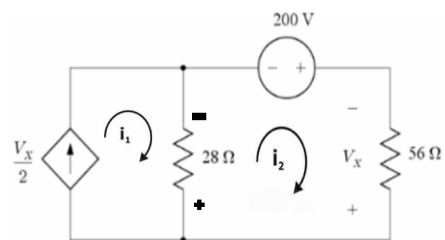
$$56 I_2 + 28(I_2 - I_1) = 200 \quad (3)$$



Solving these equations we get the value of I_1 and I_2 as: $I_1 = -200/31$, $I_2 = 50/217$

10

Mesh Analysis

Applying KVL in mesh 2:


$$-10i_1 + 20i_2 + 4i_0 = 0 \quad (1)$$

At point A using KCL we get:

$$i_0 = i_1 - i_2 \quad (2)$$

Using (1) and (2) we get:

$$i_1 = (16/6) i_2 \quad (3)$$

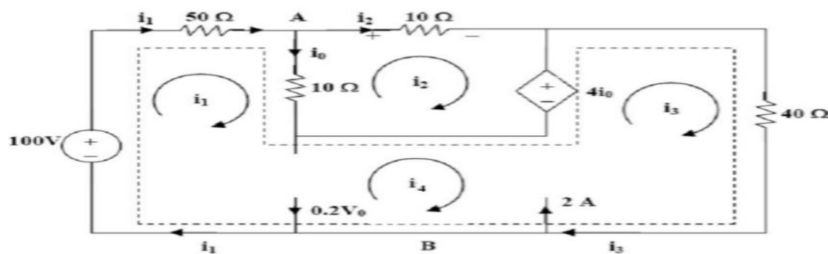

13

Mesh Analysis

In Supermesh

$$i_1 = (16/6) i_2$$

$$50 i_1 + 10(i_1 - i_2) - 4i_0 + 40i_3 = 100 \quad (4)$$

Using $i_0 = i_1 - i_2$ (4) can be simplified to

$$28 i_1 - 3i_2 + 20i_3 = 50 \quad (5)$$


Also, $i_3 - i_4 = 2$ and $-i_4 + i_1 = 0.2 v_0$

But, $v_0 = 10i_2$ which gives us

$$i_3 = 2 + (2/3) i_2 \quad (6)$$


Solving, (1) - (6) we get $i_2 = 0.11764$ A

We get, $i_0 = 0.196$ A

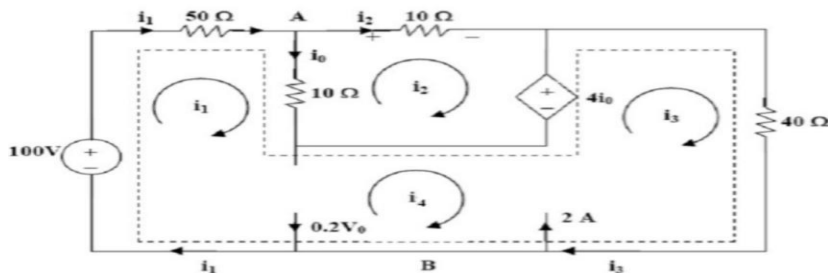

14

Matrix Analysis

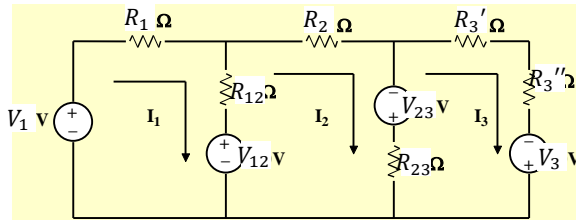

- Apply KVL:


Mesh 1: $R_1 I_1 + R_{12}(I_1 - I_2) = V_1 - V_{12}$

Mesh 2: $R_{12}(I_2 - I_1) + R_2 I_2 + R_{23}(I_2 - I_3) = V_{12} + V_{23}$

Mesh 3: $R_{23}(I_3 - I_2) + R_3' I_3 + R_3'' I_3 = V_3 - V_{23}$

15

Simplifying

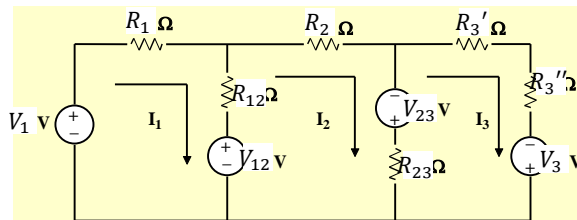

Mesh 1: $(R_1 + R_{12})I_1 - R_{12}I_2 + 0I_3 = V_1 - V_{12}$

Mesh 2: $-R_{12}I_1 + (R_{12} + R_2 + R_{23})I_2 - R_{23}I_3 = V_{12} + V_{23}$

Mesh 3: $0I_1 - R_{23}I_2 + (R_3' + R_3'' + R_{23})I_3 = V_3 - V_{23}$

Matrix Form:

$$\begin{bmatrix} (R_1 + R_{12}) & -R_{12} & 0 \\ -R_{12} & (R_{12} + R_2 + R_{23}) & -R_{23} \\ 0 & -R_{23} & (R_3' + R_3'' + R_{23}) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 - V_{12} \\ V_{12} + V_{23} \\ V_3 - V_{23} \end{bmatrix}$$


$$\mathbf{RI} = \mathbf{V}$$

$$\Rightarrow \mathbf{I} = \mathbf{R}^{-1}\mathbf{V}$$

16

Loop Analysis

Find currents in all resistances

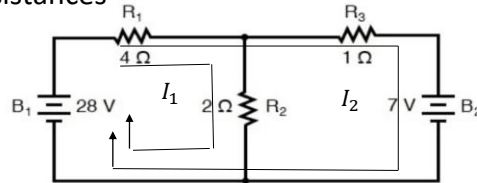

Apply KVL:

$$\text{Loop 1: } R_1(I_1 + I_2) + R_2 I_1 = B_1$$

$$\text{Loop 2: } R_1(I_1 + I_2) + R_3 I_2 = B_1 - B_2$$

Simplifying:

$$\text{Loop 1: } (R_1 + R_2)I_1 + R_1 I_2 = B_1$$

$$\text{Loop 2: } R_1 I_1 + (R_1 + R_3)I_2 = B_1 - B_2$$

Solving:

$$I_1 = \frac{R_3 B_1 + R_1 B_2}{(R_1 + R_2)(R_1 + R_3) - R_1^2}$$

$$I_2 = \frac{(R_1 + R_2)B_2 - R_2 B_1}{R_1^2 - (R_1 + R_2)(R_1 + R_3)}$$

Solution:

$$I_1 = 4A$$

$$I_2 = 1A$$

Currents:


$$R_1 \rightarrow I_1 + I_2 = 5A$$

$$R_2 \rightarrow I_1 = 4A$$

$$R_3 \rightarrow I_2 = 1A$$

17

Applicability

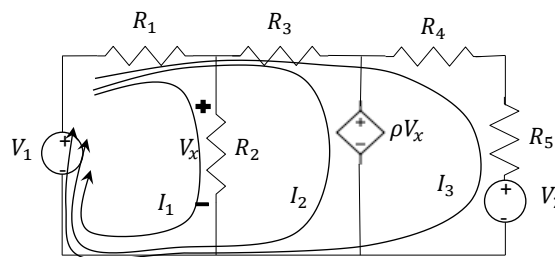

Applying KVL:

$$\text{Loop 1: } R_1(I_1 + I_2 + I_3) + R_2 I_1 = V_1$$

$$\text{Loop 2: } R_1(I_1 + I_2 + I_3) + R_3(I_2 + I_3) = V_1 - \rho V_x$$

$$\text{Loop 3: } R_1(I_1 + I_2 + I_3) + R_3(I_2 + I_3) + (R_4 + R_5)I_3 = V_1 + V_2$$

$$\text{Note that } V_x = R_1 I_1$$

18