

# COL215L: Digital Logic & System Design

## Lecture 3: CMOS Circuits (Cont.)



M. Balakrishnan  
CSE@IITD


August 13, 2021

Vireshwar Kumar  
CSE@IITD

# Digital Logic

- Any system
  - Storage
  - Computation
  - Communication
- Implementation of any system
  - Digital logic (0-1)
- Realization of digital logic
  - Transistors for controlling voltages that we interpret as 0 or 1

# Digital Logic and Voltage Values

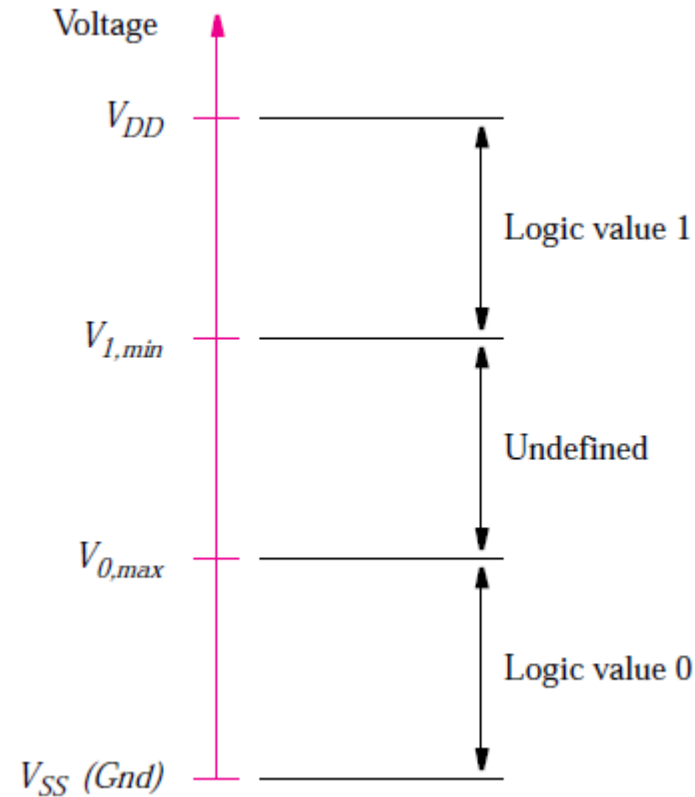


Mapping of digital logic and voltage values [Brown & Vranesic].

# Realizing the Mapping


- Metal Oxide Semiconductor Field-effect Transistor (MOSFET)
  - n-channel MOSFET (NMOS)
  - p-channel MOSFET (PMOS)
- Complementary MOS (CMOS)
  - Circuits using both NMOS and PMOS

# NMOS

- Drain
- Source
- Gate


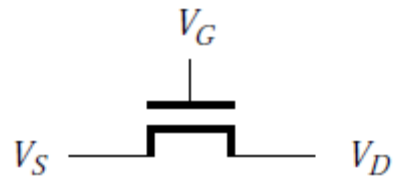


NMOS [Brown & Vranesic].

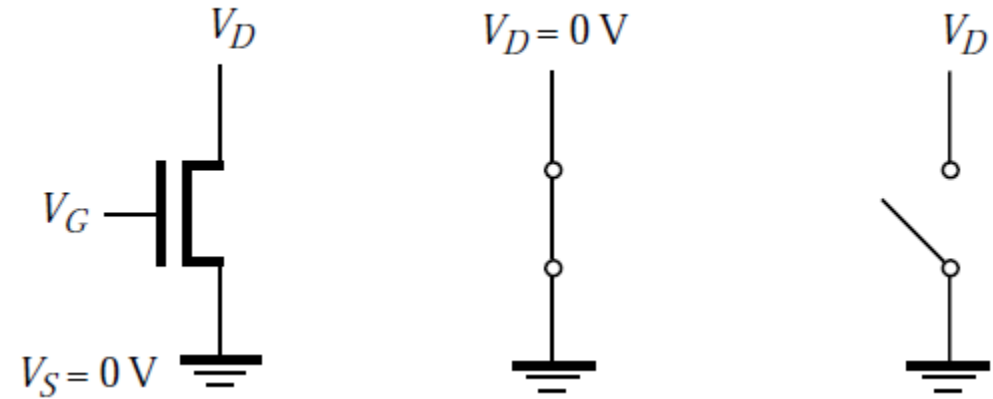


NMOS logic circuit [Brown & Vranesic].

# PMOS

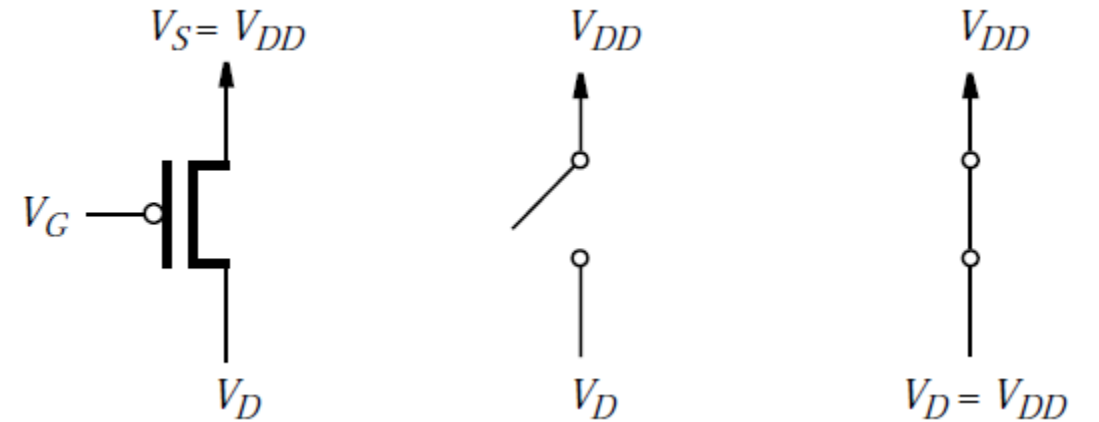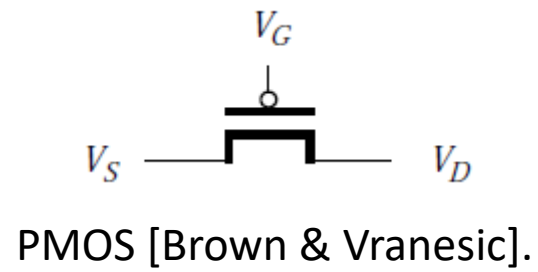

PMOS logic circuit [Brown & Vranesic].

# Realizing NOT using NMOS

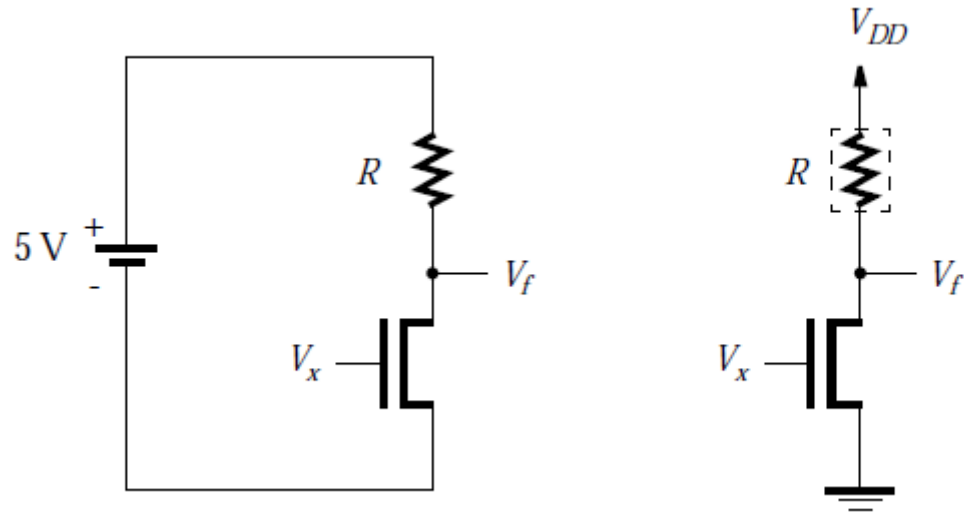


NOT Circuit [Brown & Vranesic].



Representation.

# Realizing NAND using NMOS

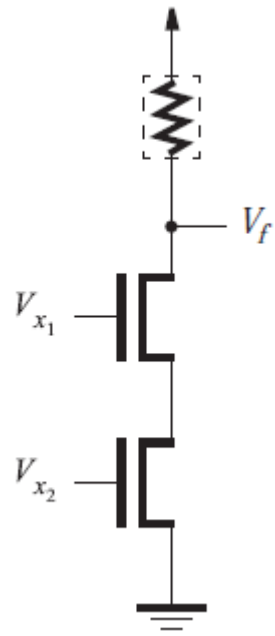


NAND Circuit [Brown & Vranesic].




Representation



# Realizing logic gates using CMOS

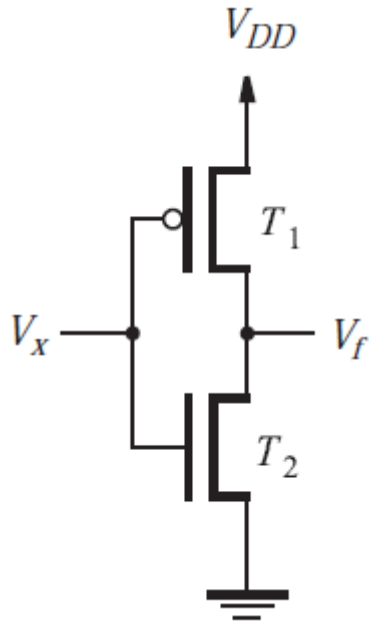


NOT circuit [Brown & Vranesic].

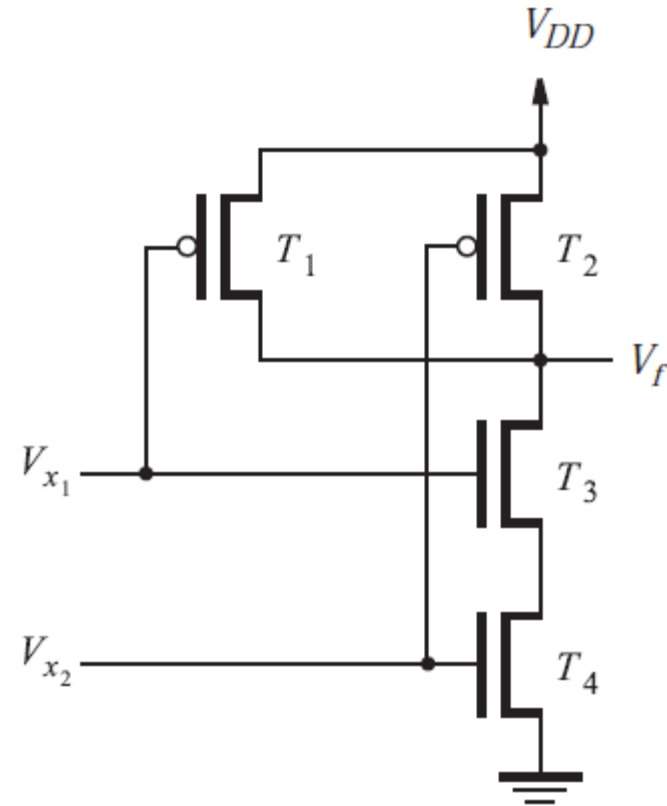

NAND circuit [Brown & Vranesic].

# Programmable Logic Array (PLA)

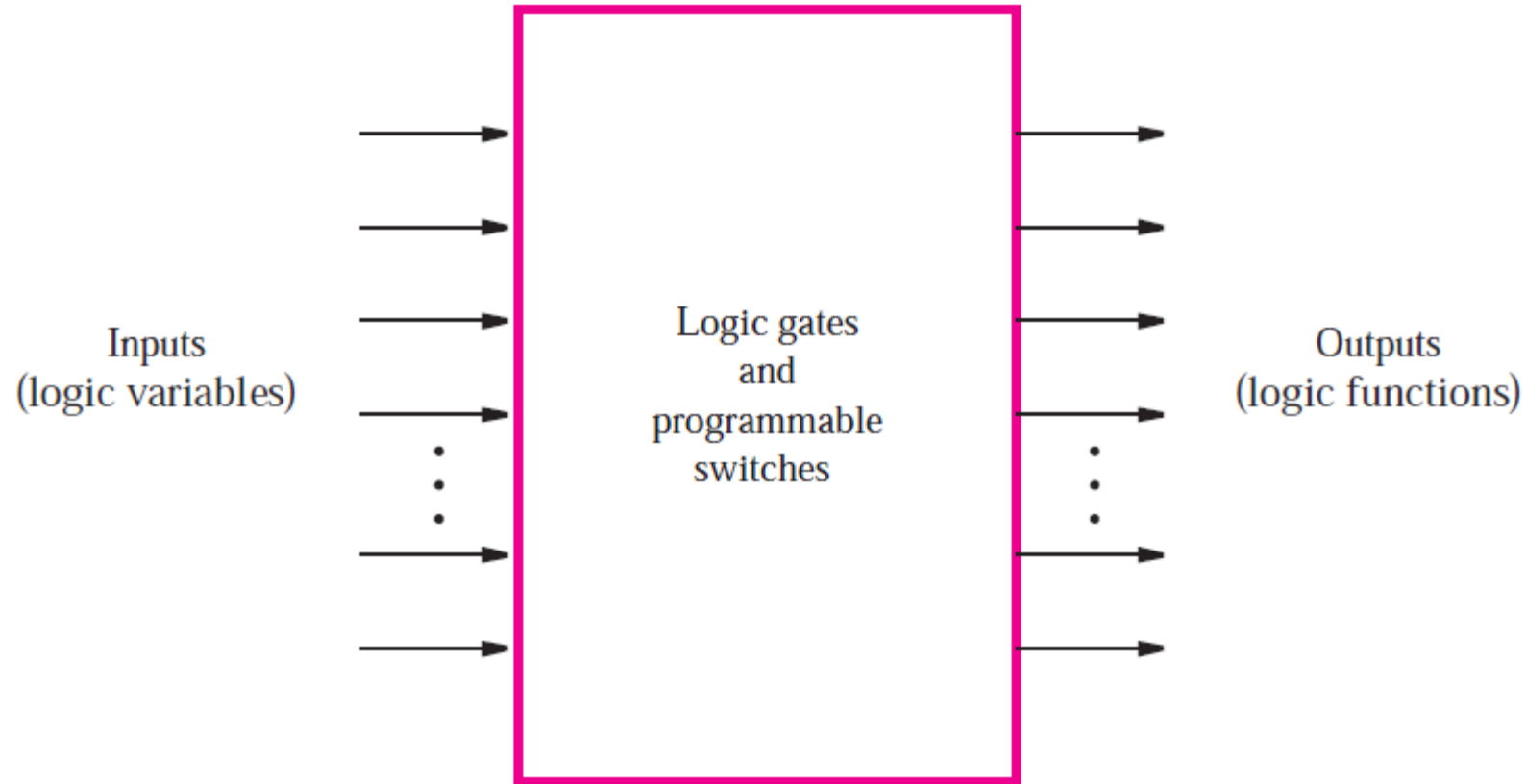

PLA [Brown & Vranesic].