



# ELL100: INTRODUCTION TO ELECTRICAL ENGG.


## Lecture 22: Semiconductor Diode Circuits

Instructor: Debanjan Bhowmik

Reference: Donald Neamen's 'Electronic Circuit Analysis'  
Chapter 2 (Diode Circuits)
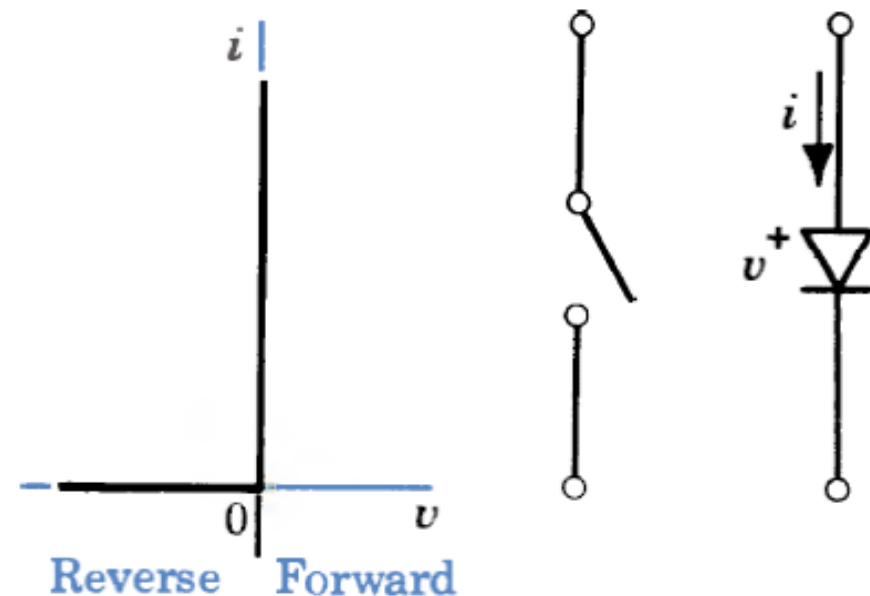
# Ideal and Practical Diode

- An **ideal diode** has a infinite diffusion, and zero drift.
- Presents
  - Zero resistance in forward bias
  - Infinite resistance in reverse bias.




Like a switch

Wednesday, August 29, 2018


Ideal diode
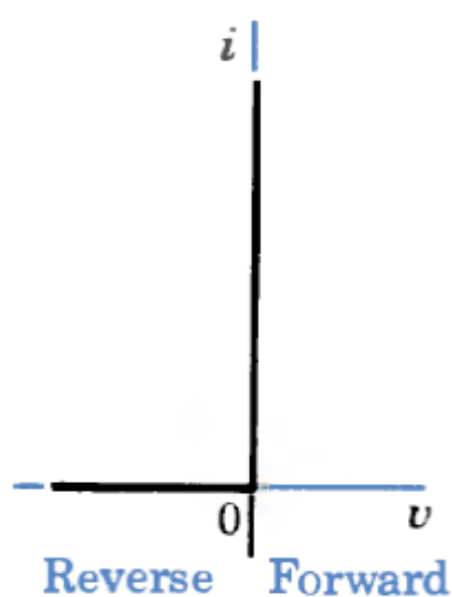
# Ideal and Practical Diode


- An **ideal diode** *acts like a switch*.
- A **practical diode** has a nonlinear I-V characteristics.
  - Current-voltage relations



Ideal diode

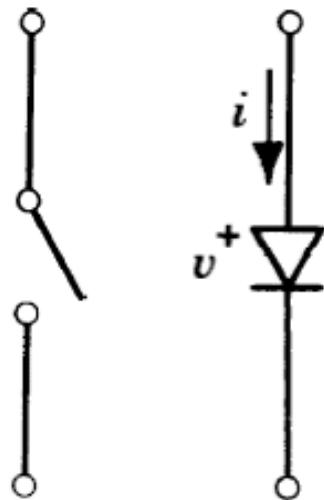

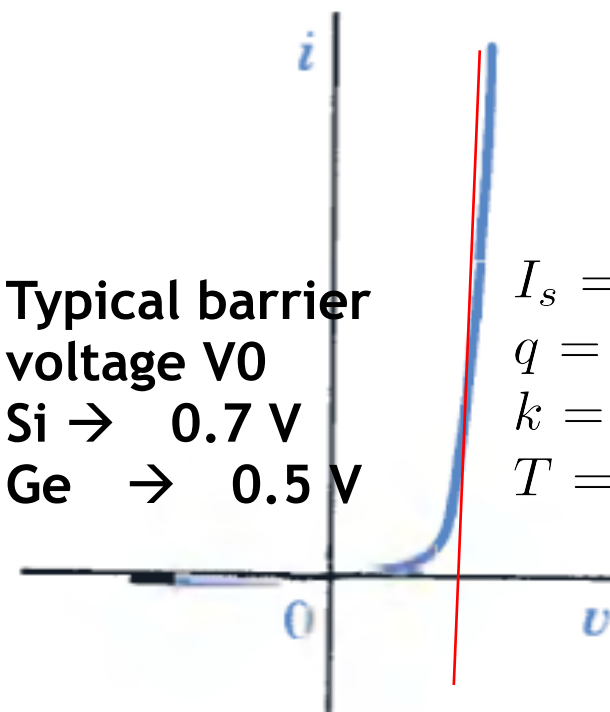Typical barrier  
voltage  $V_0$   
Si  $\rightarrow$  0.7 V  
Ge  $\rightarrow$  0.5 V




Practical Diode

$$i = I_s \left( e^{\frac{qV}{kT}} - 1 \right)$$

$I_s$  = Reverse saturation current.  
 $q$  = Charge of electron  
 $k$  = Boltzmann Const.  
 $T$  = Junction temperature in K

# Ideal and Practical Diode

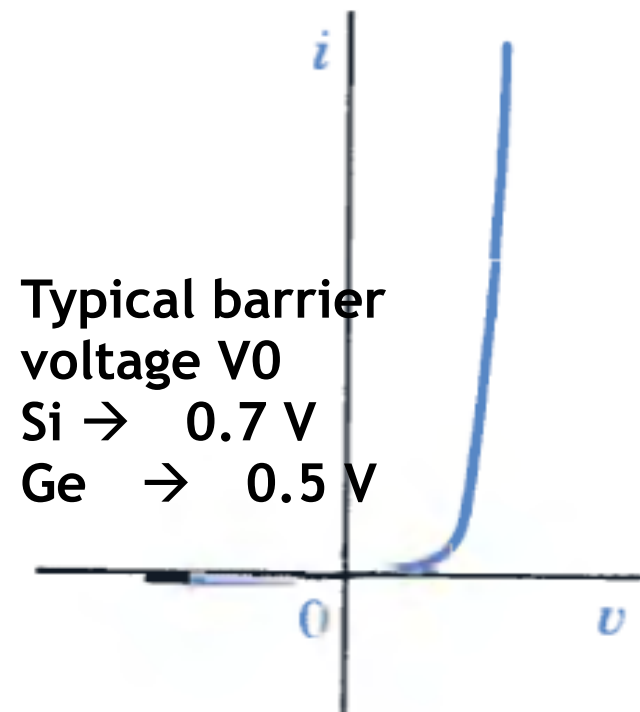


## Practical Diode:

under forward bias: potential across it is almost 0.7 V (Si), current depends on the circuit.

under reverse bias: potential across it can be anything (negative quantity), current is almost 0

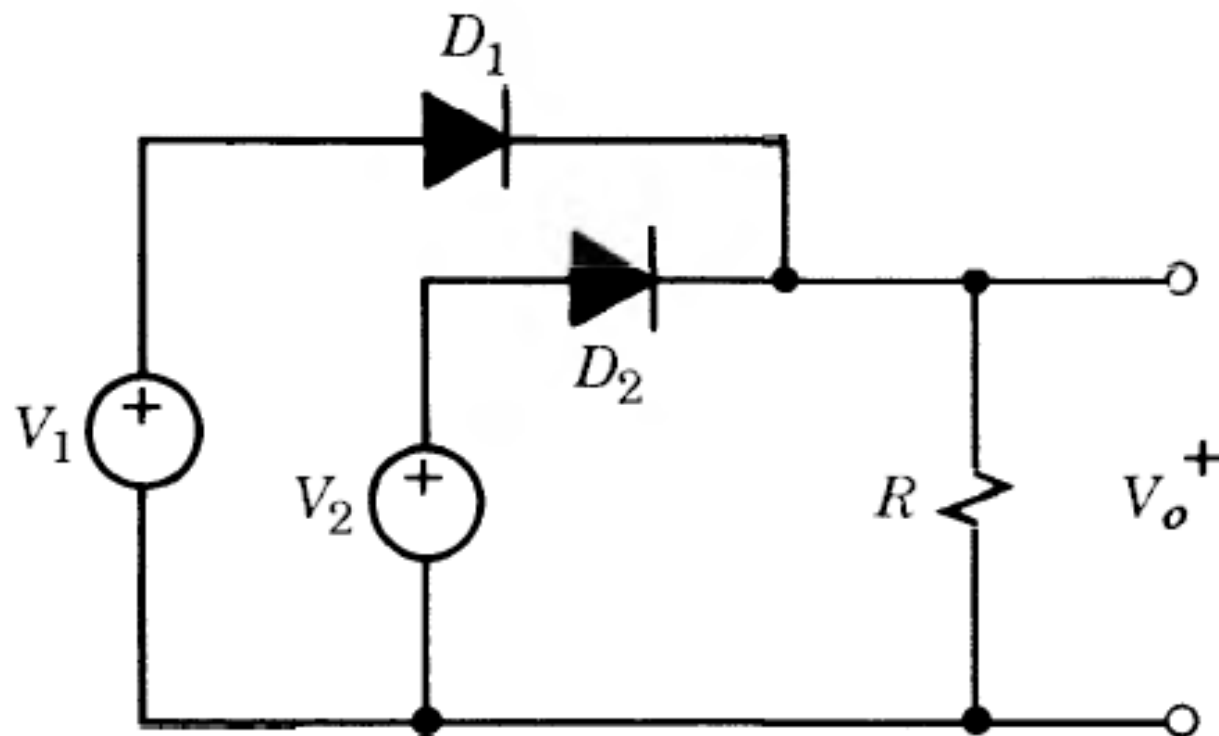
# Example 1

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Determine  $V_o$ .


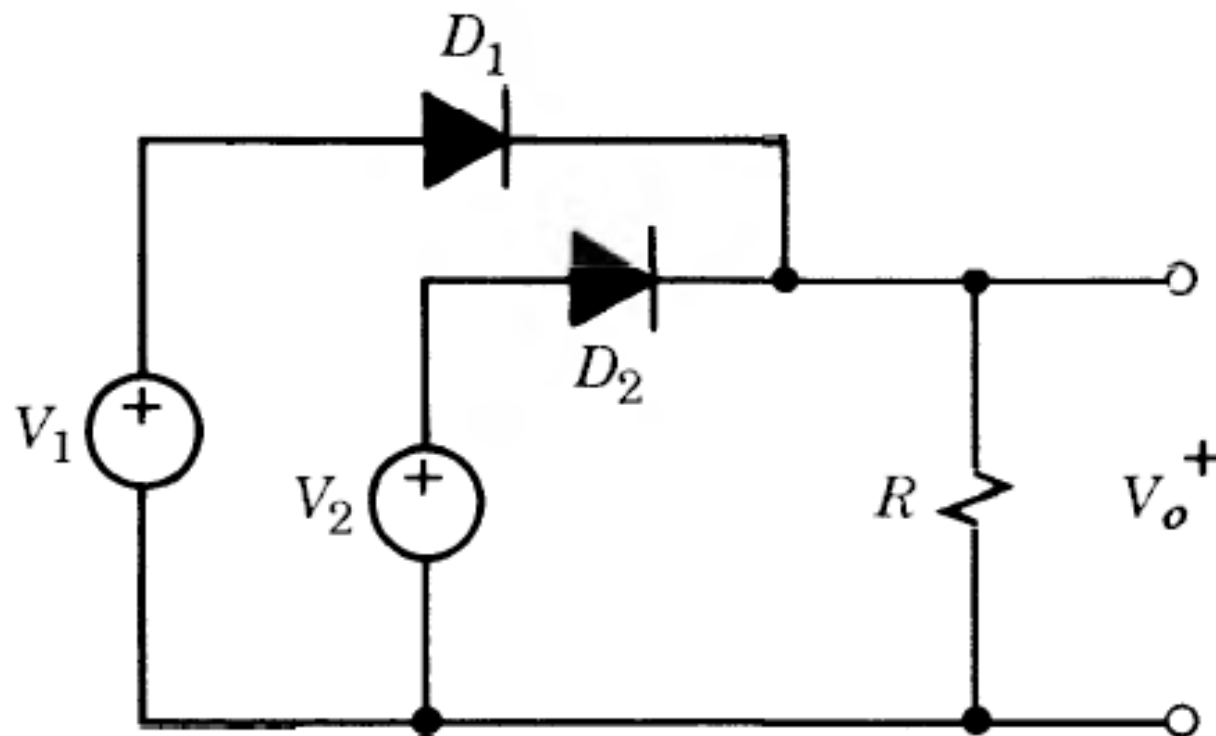
# Example 1

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is  $0.7\text{ V}$ .

Now there are four situations corresponding to the forward/reverse biasing of the two diodes.

$D_1 \rightarrow \text{FB}$ ,  $D_2 \rightarrow \text{RB}$  ( $5 > V_o > 0$ )

Possible

$D_1 \rightarrow \text{RB}$ ,  $D_2 \rightarrow \text{RB}$  ( $0 < 5 < V_o$ )

Possible


$D_1 \rightarrow \text{FB}$ ,  $D_2 \rightarrow \text{FB}$  ( $5 > 0 > V_o$ )

Possible

$D_1 \rightarrow \text{RB}$ ,  $D_2 \rightarrow \text{FB}$  ( $5 < V_o < 0$ ) No
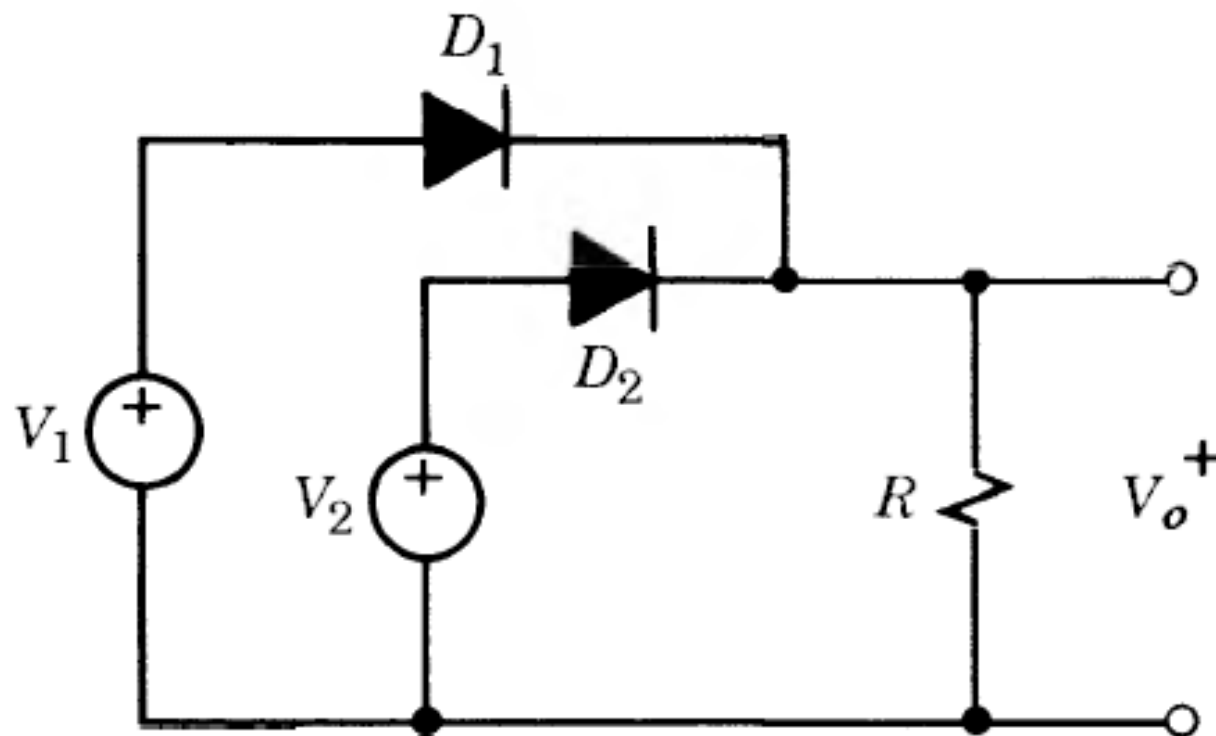
# Example 1

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is  $0.7\text{ V}$ .

Now there are four situations corresponding to the forward/reverse biasing of the two diodes.

**$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{RB} (5 > V_o > 0)$**

**Possible**

$V_o = 5 - 0.7 = 4.3\text{ V}$

$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{RB} (0 < 5 < V_o)$

Possible


$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{FB} (5 > 0 > V_o)$

Possible

~~$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{FB} (5 < V_o < 0)$  No~~
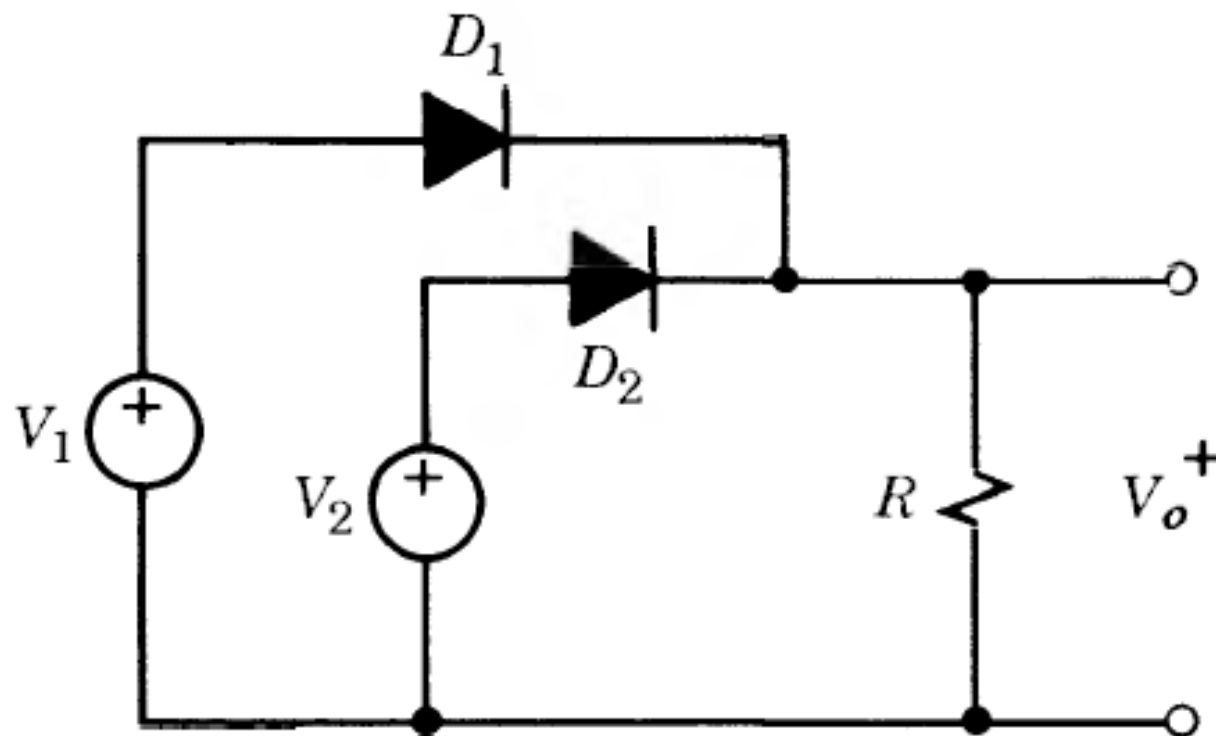
# Example 1

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is  $0.7\text{ V}$ .

Now there are four situations corresponding to the forward/reverse biasing of the two diodes.

$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{RB} \ (5 > V_o > 0)$

Possible

$V_o = 5 - 0.7 = 4.3\text{ V}$

$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{RB} \ (0 < 5 < V_o)$

Possible

$V_o = 0$  and  $> 5\text{ !!}$

$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{FB} \ (5 > 0 > V_o)$


Possible

~~$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{FB} \ (5 < V_o < 0)$  No~~


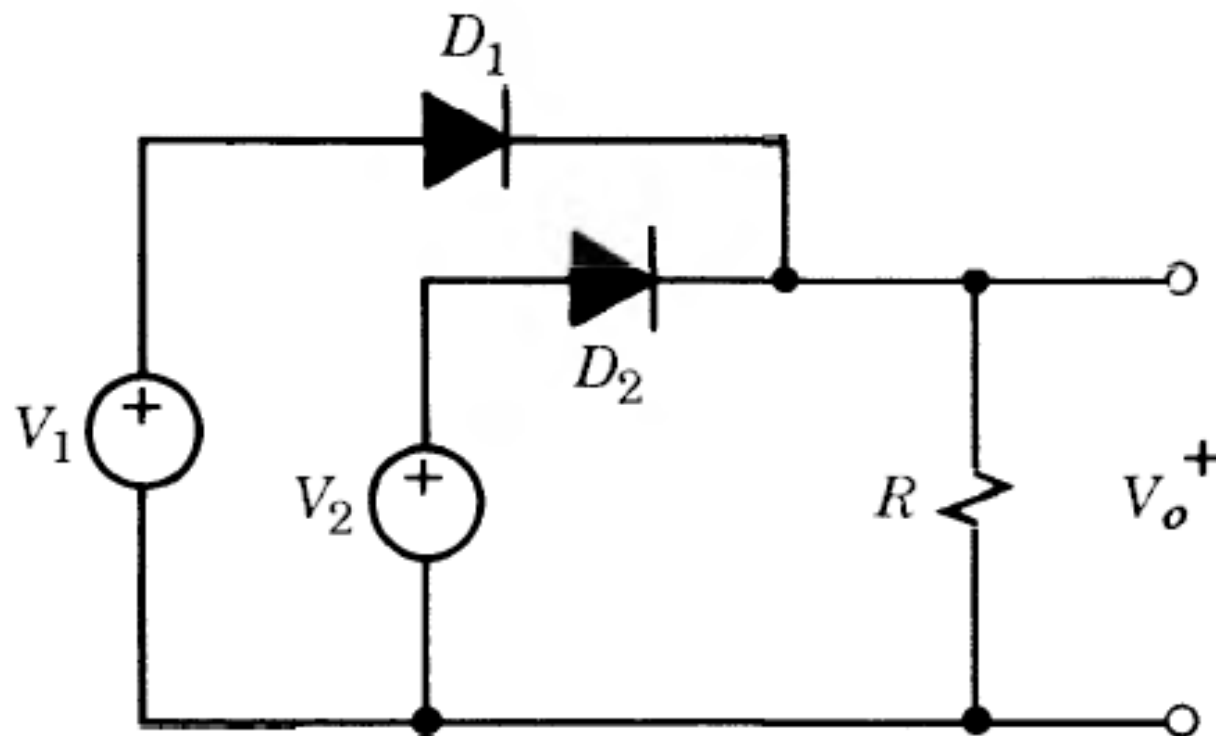
# Example 1

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is  $0.7\text{ V}$ .

Now there are four situations corresponding to the forward/reverse biasing of the two diodes.

$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{RB} \ (5 > V_o > 0)$

Possible

$$V_o = 5 - 0.7 = 4.3\text{ V}$$

~~$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{RB} \ (0 < 5 < V_o)$~~

~~Possible~~

**$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{FB} \ (5 > 0 > V_o)$**


**Possible**

$$V_o = 5 + 0.7; V = 0 + 0.7 !!$$

~~$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{FB} \ (5 < V_o < 0)$  No~~
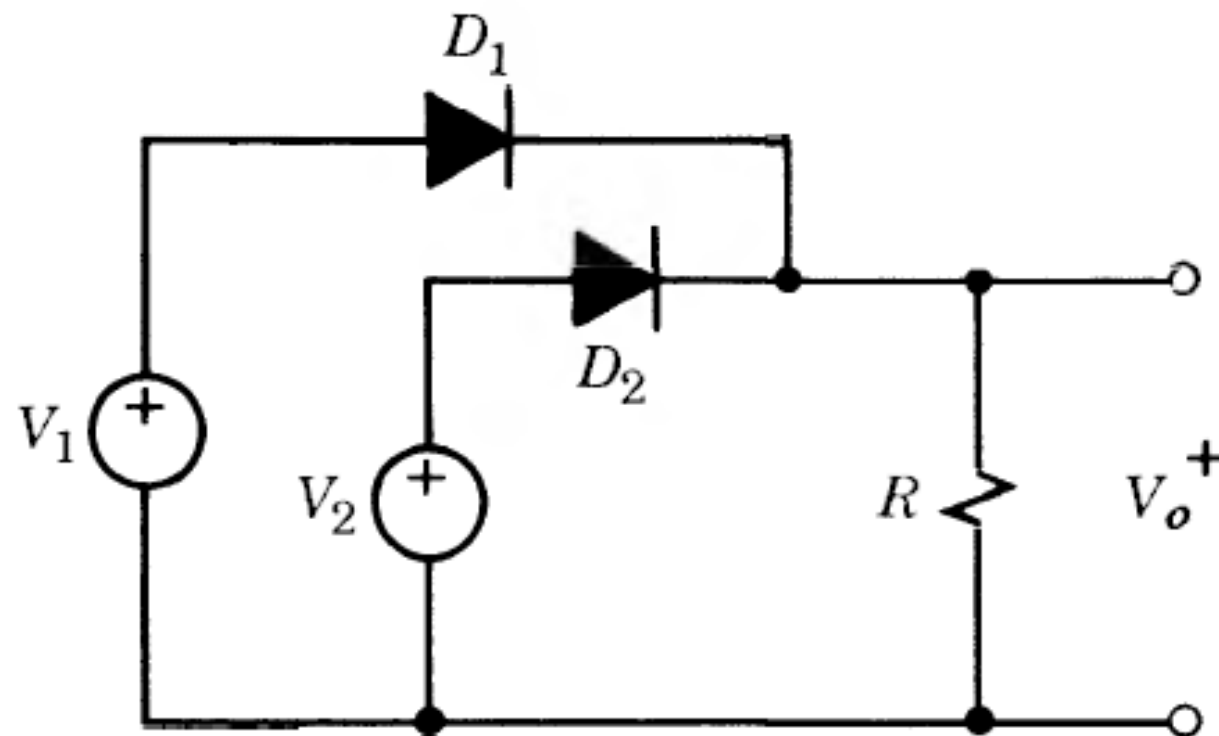
# Example 1

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is  $0.7\text{ V}$ .

Now there are four situations corresponding to the forward/reverse biasing of the two diodes.

$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{RB} \quad (5 > V_o > 0)$

Possible

$$V_o = 5 - 0.7 = 4.3\text{ V}$$

~~$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{RB} \quad (0 < 5 < V_o)$~~

~~Possible~~


~~$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{FB} \quad (5 > 0 > V_o)$~~

~~Possible~~

~~$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{FB} \quad (5 < V_o < 0)$  No~~

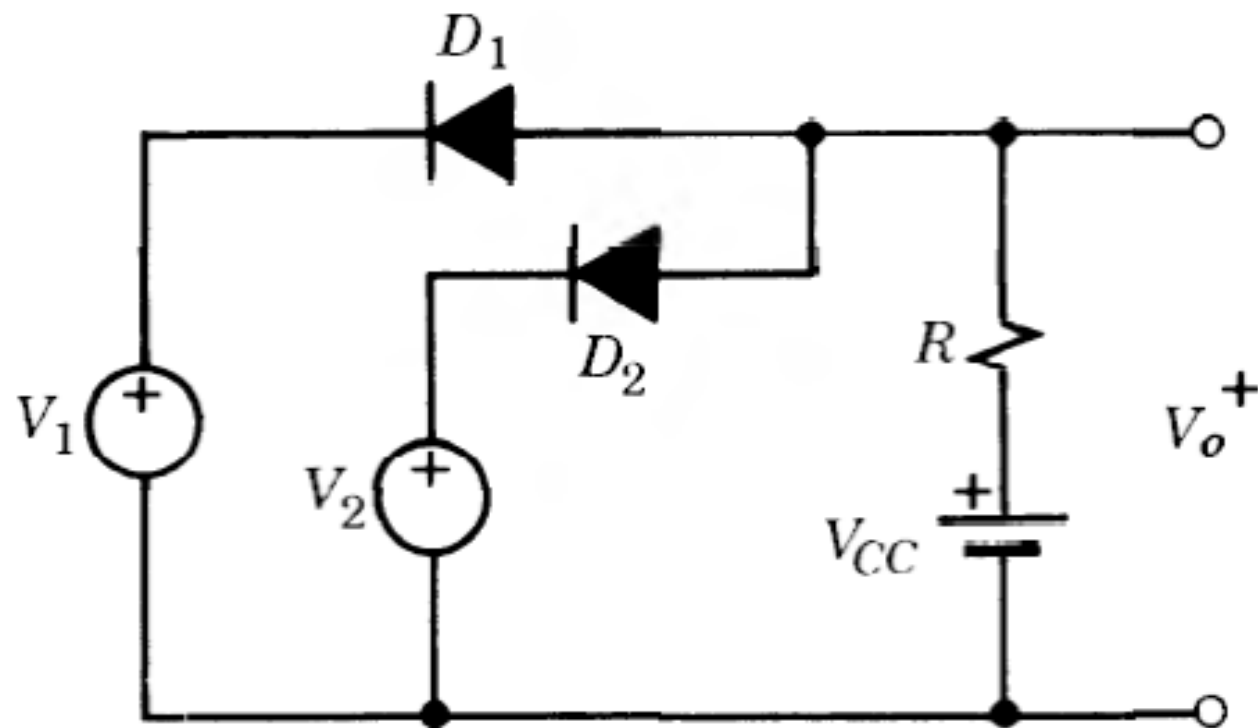
## Example 2

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$  and  $V_{CC} = 6\text{ V}$ . Determine  $V_o$ .


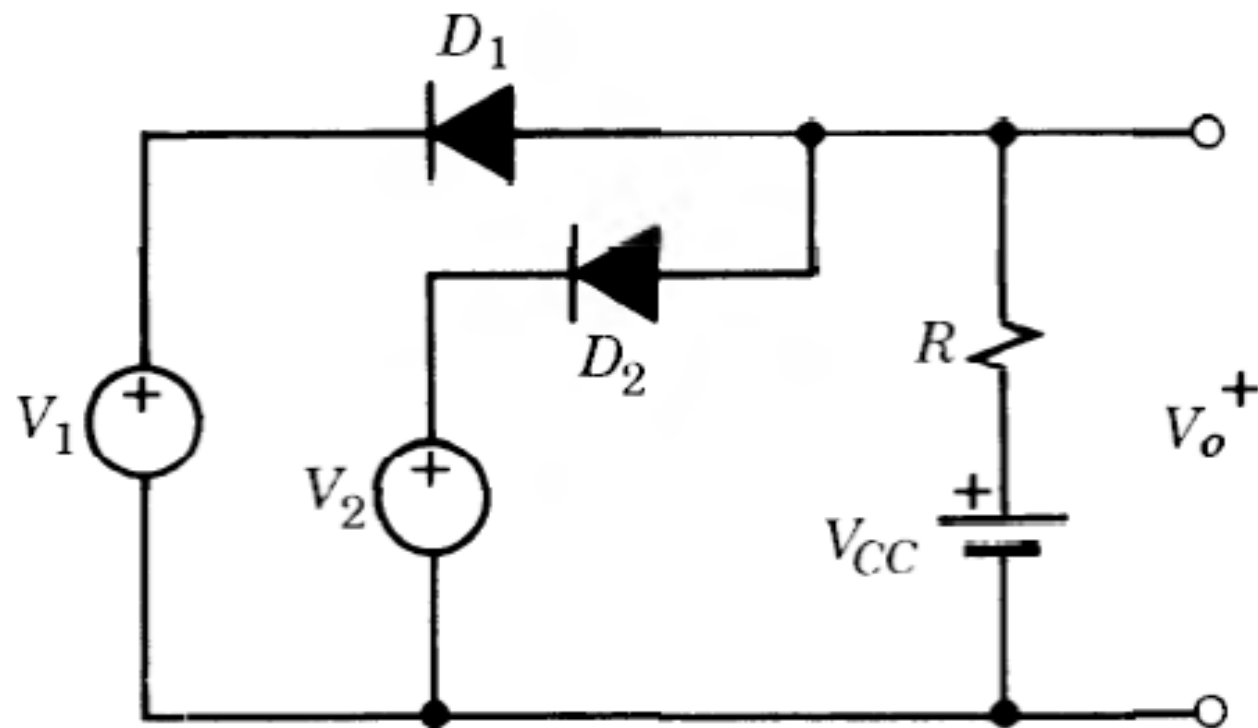
## Example 2

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$  and  $V_{CC}=6\text{ V}$  Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is  $0.7\text{ V}$ .


$D_1, D_2 \rightarrow \text{FB } 6 > V_o > (5, 0)$

But then there is conflict of  $V_o = 5 - 0.7$  or  $0 - 0.7$ .

$D_1, D_2 \rightarrow \text{RB } 6 < V_o < (5, 0)$  NOT Possible
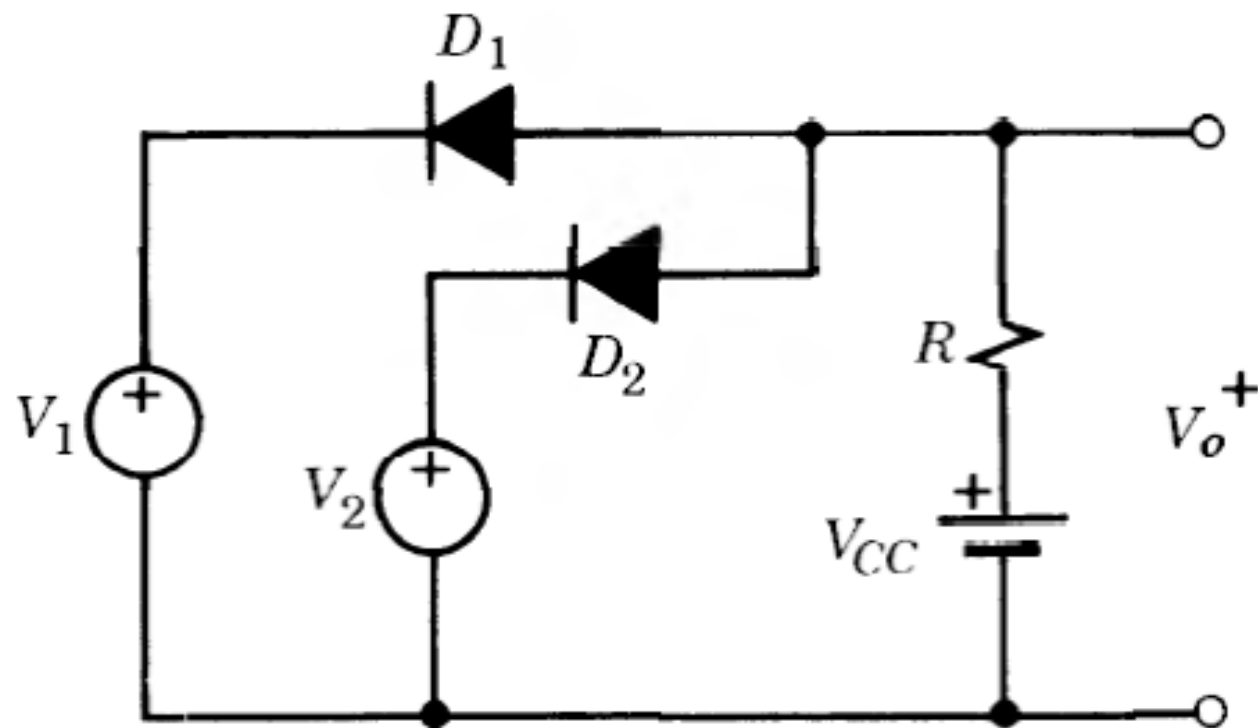
## Example 2

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$  and  $V_{CC}=6\text{ V}$  Determine  $V_o$ .




Since it is a Silicon diode, barrier voltage is 0.7 V.

~~$D_1, D_2 \rightarrow \text{FB } 6 > V_o > (5, 0)$~~

$D_1, D_2 \rightarrow \text{RB } 6 < V_o < (5, 0)$  NOT Possible
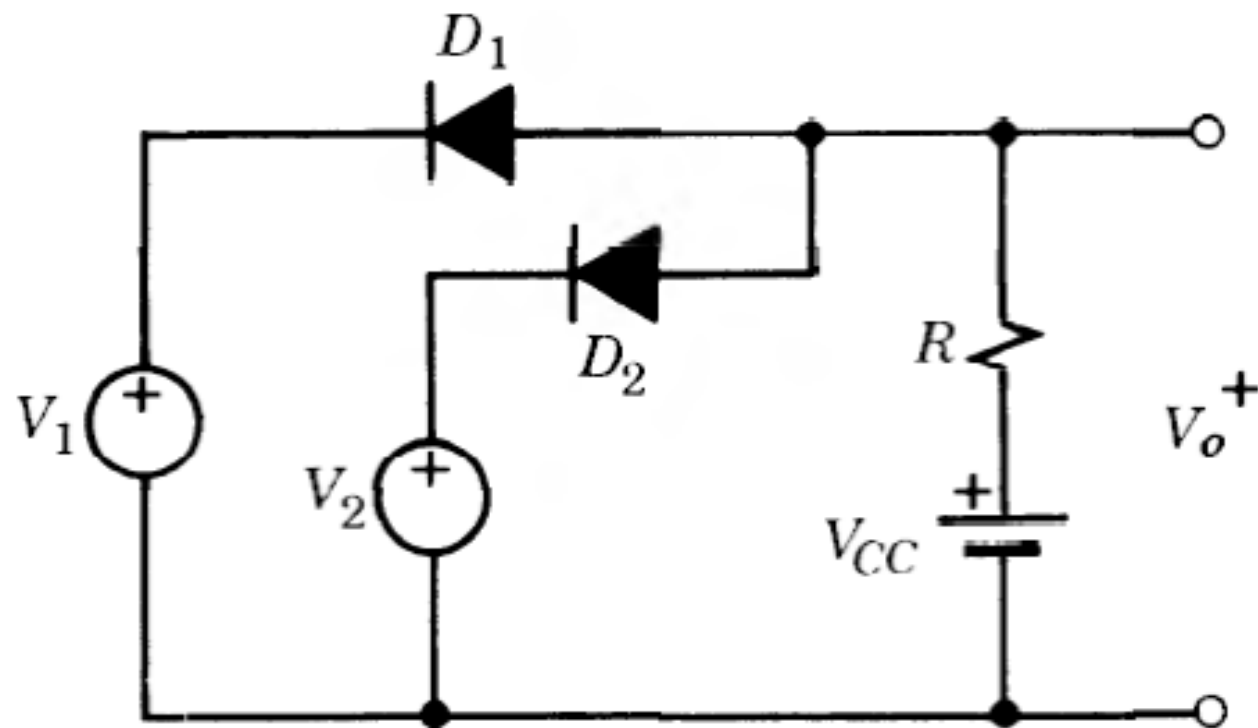
## Example 2

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$  and  $V_{CC}=6\text{ V}$  Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is 0.7 V.


~~$D_1, D_2 \rightarrow \text{FB } 6 > V_o > (5, 0)$~~

~~$D_1, D_2 \rightarrow \text{RB } 6 < V_o < (5, 0)$  NOT Possible~~

$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{RB } 0 > V_o > 5$  NOT Possible
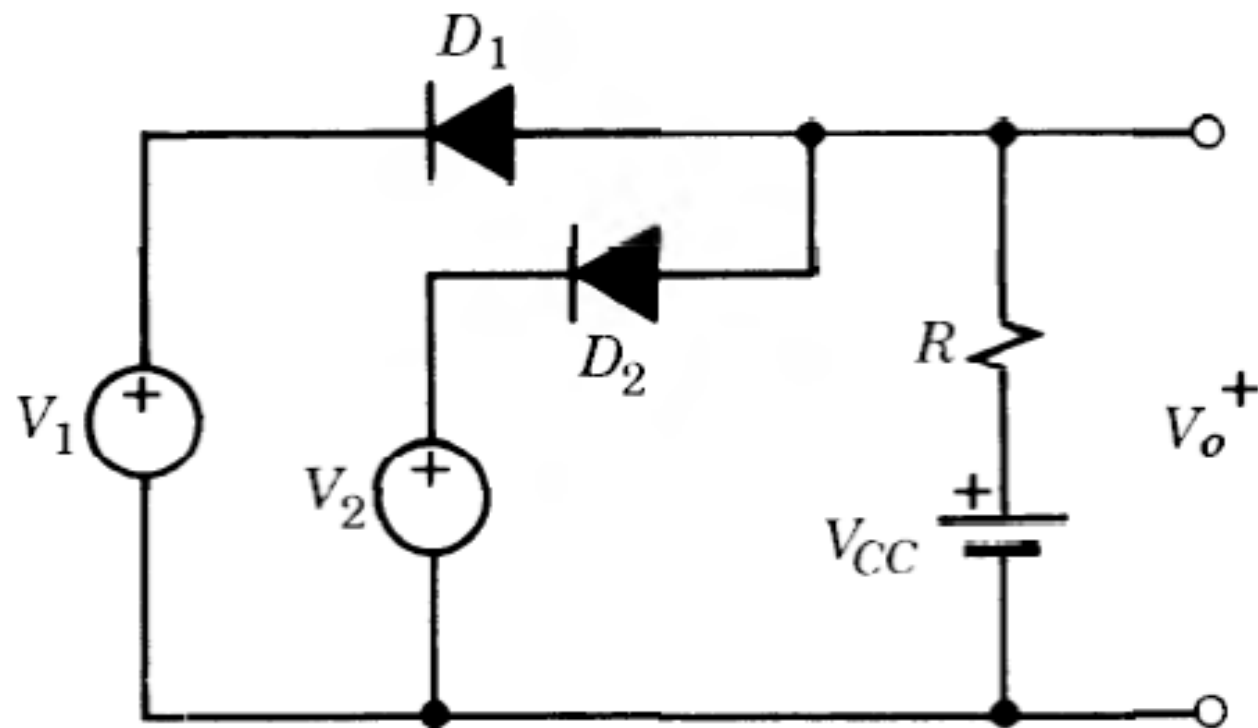
## Example 2

- Consider the **Si** diode in the circuit. Let  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$  and  $V_{CC}=6\text{ V}$  Determine  $V_o$ .



Since it is a Silicon diode, barrier voltage is  $0.7\text{ V}$ .

~~$D_1, D_2 \rightarrow \text{FB } 6 > V_o > (5, 0)$~~

~~$D_1, D_2 \rightarrow \text{RB } 6 < V_o < (5, 0)$  NOT Possible~~

~~$D_1 \rightarrow \text{FB}, D_2 \rightarrow \text{RB } 0 > V_o > 5$  NOT Possible~~

$D_1 \rightarrow \text{RB}, D_2 \rightarrow \text{FB } 0 < V_o < 5$


$$V_o = 0 + 0.7 = 0.7\text{ V}$$

Current flowing through  $D_1 = 0$

Current flowing through  $D_2 = (V_{CC} - V_o) / R$
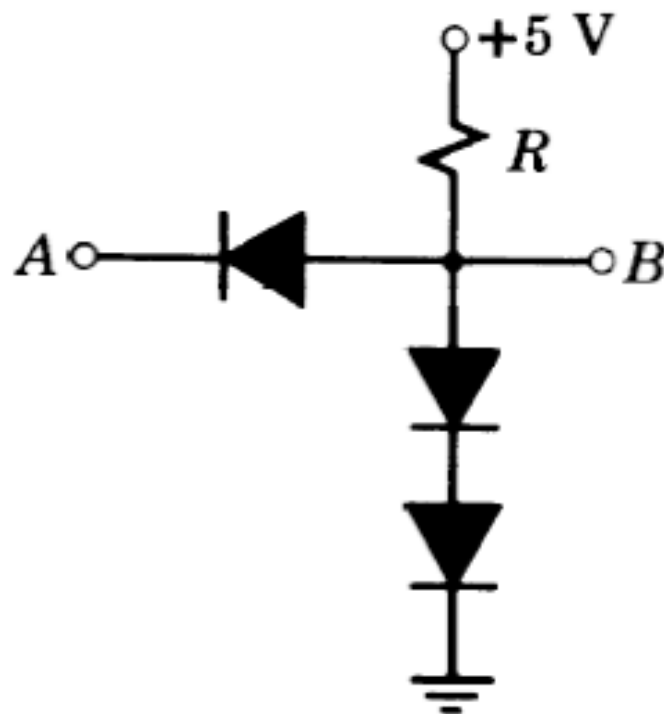
## Example 3


- Consider the circuit with silicon diodes.  
Determine  $V_B$ , when  $V_A = 2\text{ V}, 1\text{ V}, 0\text{ V}, -1\text{ V}$




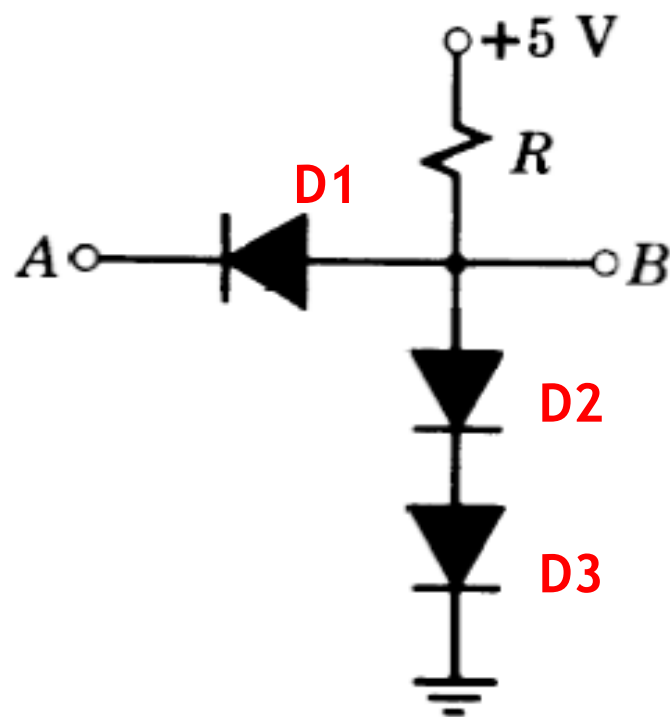
# Example 3


- Consider the circuit with Silicon diodes.  
Determine  $V_B$ , when  $V_A = 2\text{ V}, 1\text{ V}, 0\text{ V}, -1\text{ V}$



	D2,D3→FB	D2,D3→RB
D1→RB		$V_b < \min(V_a, 0)$ $V_b = ???$
D1→FB		
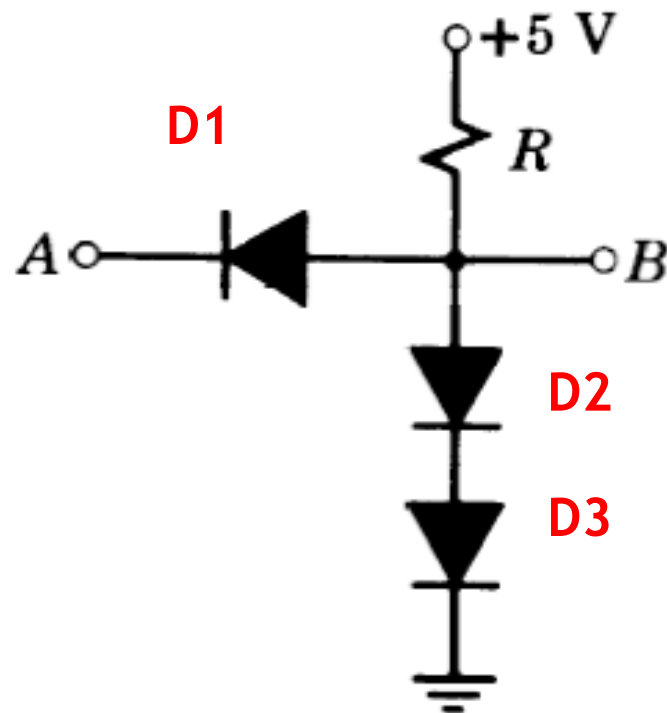
# Example 3

- Consider the circuit with Silicon diodes.  
Determine  $V_B$  when  $V_A = 2\text{ V}, 1\text{ V}, 0\text{ V}, -1\text{ V}$




	D2,D3→FB	D2,D3→RB
D1→RB	$V_a > V_b > 0$ $V_b = 0 + 2 \times 0.7 = 1.4\text{ V}$	$V_b < \min(V_a, 0)$ $V_b = ???$
D1→FB		

$V_a = 2\text{ V}, V_b = 1.4\text{ V}$
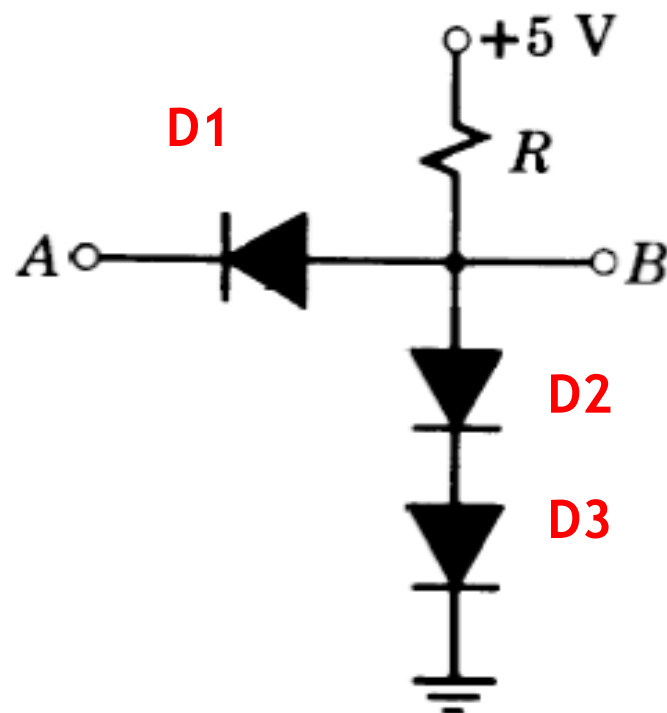
# Example 3

- Consider the circuit with Silicon diodes.  
Determine  $V_B$  when  $V_A = 2\text{ V}, 1\text{ V}, 0\text{ V}, -1\text{ V}$



	D2,D3→FB	D2,D3→RB
D1→RB	$V_a > V_b > 0$ $V_b = 0 + 2 \times 0.7 = 1.4\text{ V}$	$V_b < \min(V_a, 0)$ $V_b = ???$
D1→FB	$V_b > V_a, V_b > 0$ $V_b = \min(V_a + 0.7, 1.4)$	


$$V_a = 2\text{ V}, V_b = 1.4\text{ V}$$

$$V_a = 1\text{ V}, V_b = \min(1.7, 1.4) = 1.4\text{ V}$$

$$V_a = 0\text{ V}, V_b = \min(0.7, 1.4) = 0.7\text{ V}$$
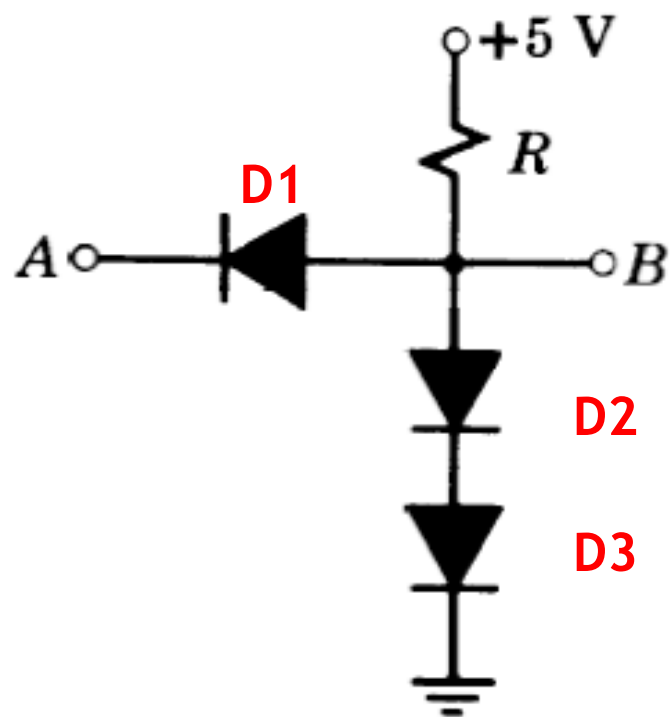
# Example 3

- Consider the circuit with Silicon diodes.  
Determine  $V_B$ , when  $V_A = 2\text{ V}, 1\text{ V}, 0\text{ V}, -1\text{ V}$



	D2,D3→FB	D2,D3→RB
D1→RB	$V_a > V_b > 0$ $V_b = 0 + 2 \times 0.7 = 1.4\text{V}$	$V_b < \min(V_a, 0)$ $V_b = ???$
D1→FB	$V_b > V_a, V_b > 0$ $V_b = \min(V_a + 0.7, 1.4)$	$V_a < V_b < 0$ $V_b = V_a + 0.7$

$$V_a = 2\text{ V}, V_b = 1.4\text{ V}$$


$$V_a = 1\text{ V}, V_b = \min(1.7, 1.4) = 1.4\text{ V}$$

$$V_a = 0\text{ V}, V_b = \min(0.7, 1.4) = 0.7\text{ V}$$

$$V_a = -1\text{ V}, V_b = -0.3\text{ V}$$
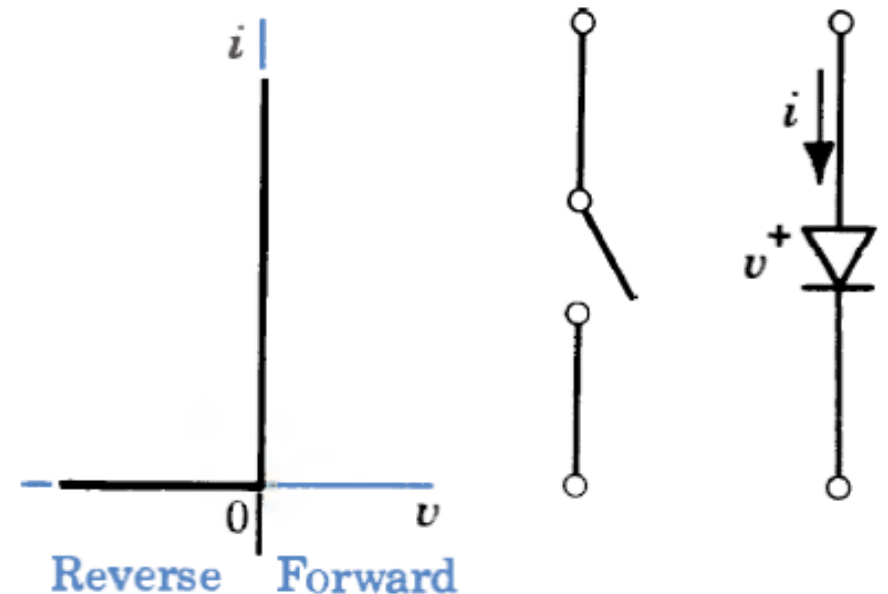
# Diode as a Switch

- A diode (ideally) acts as a switch.
- This property can be used in a variety of circuits.
  - AC-DC Conversion : Rectifier
  - Peak Detection, DC Restoration : Clamper
  - Wave Shaping : Clipper




# Rectifier


- Rectification : Conversion of an alternating current to unidirectional, but pulsating current by using a nonlinear element (like diode).
- Type :
  - Half-Wave Rectifier : Utilizes only one half of an AC signal for conversion.
  - Full-Wave Rectifier : Uses both halves of an AC signal for conversion
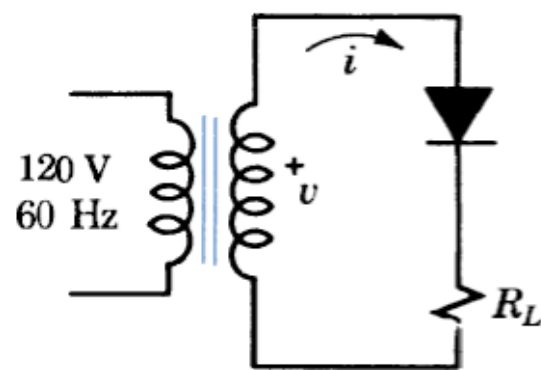
# Half-Wave Rectifier (HWR)


- A Half-wave rectifier circuit uses a single diode to recover one HALF of an AC signal.




(a) Wiring diagram

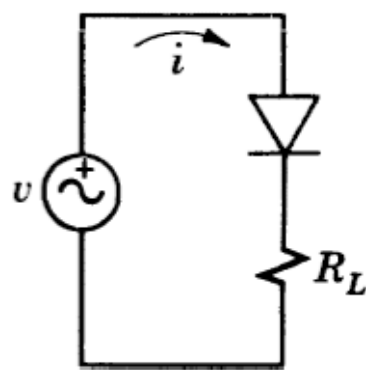

(b) Circuit model

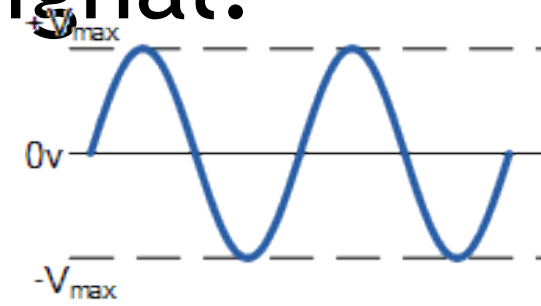

Input Waveform

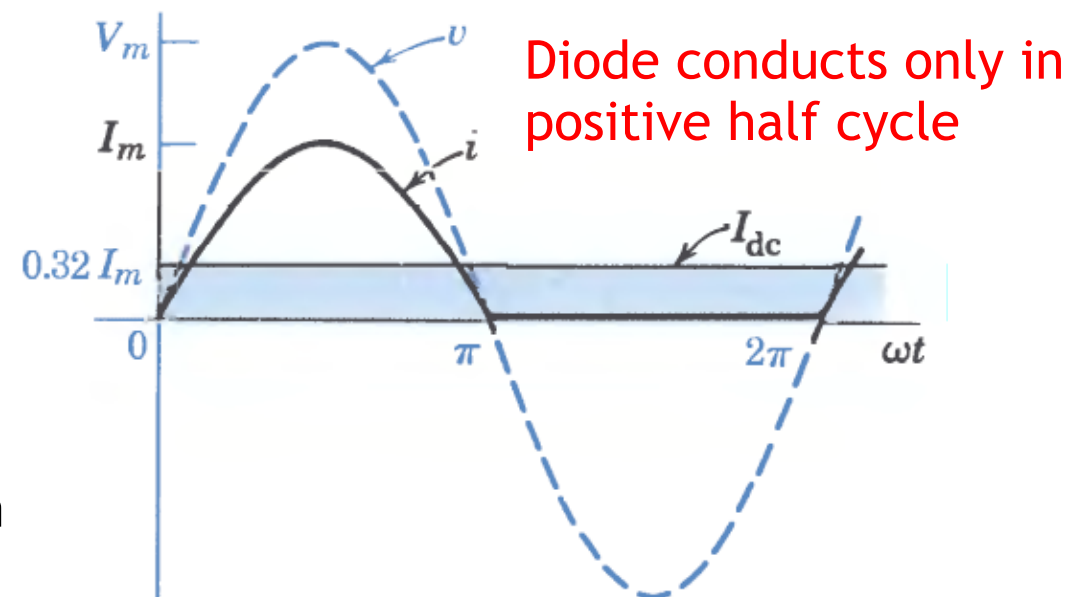

Output Waveform

# HWR : DC/Average Value



- Assuming ideal diode

$$\begin{aligned} i &= \frac{v}{R_L} = \frac{V_m \sin \omega t}{R_L} \quad \text{for } 0 \leq \omega t \leq \pi \\ &= 0 \quad \text{for } \pi \leq \omega t \leq 2\pi \end{aligned}$$

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i \, d(\omega t) = \frac{1}{2\pi} \int_0^{\pi} \frac{V_m \sin \omega t}{R_L} \, d(\omega t) + 0$$

$$= \frac{V_m}{\pi R_L} = \frac{I_m}{\pi}$$
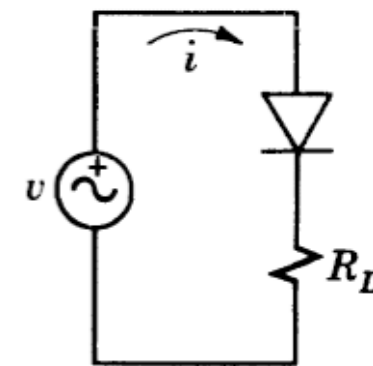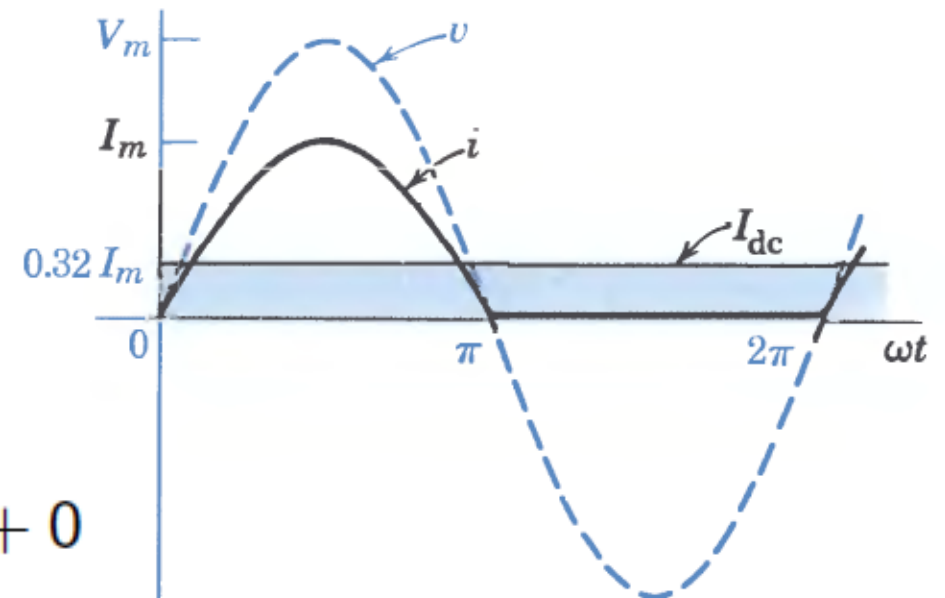
$$V_{dc} = \frac{V_m}{\pi} \quad \text{Approx. 32\%}$$







# Full-Wave Rectifier (FWR)

- Is there a way to utilize BOTH halves of the AC signal to produce a unidirectional output voltage/current?

- Bridge Rectifier :
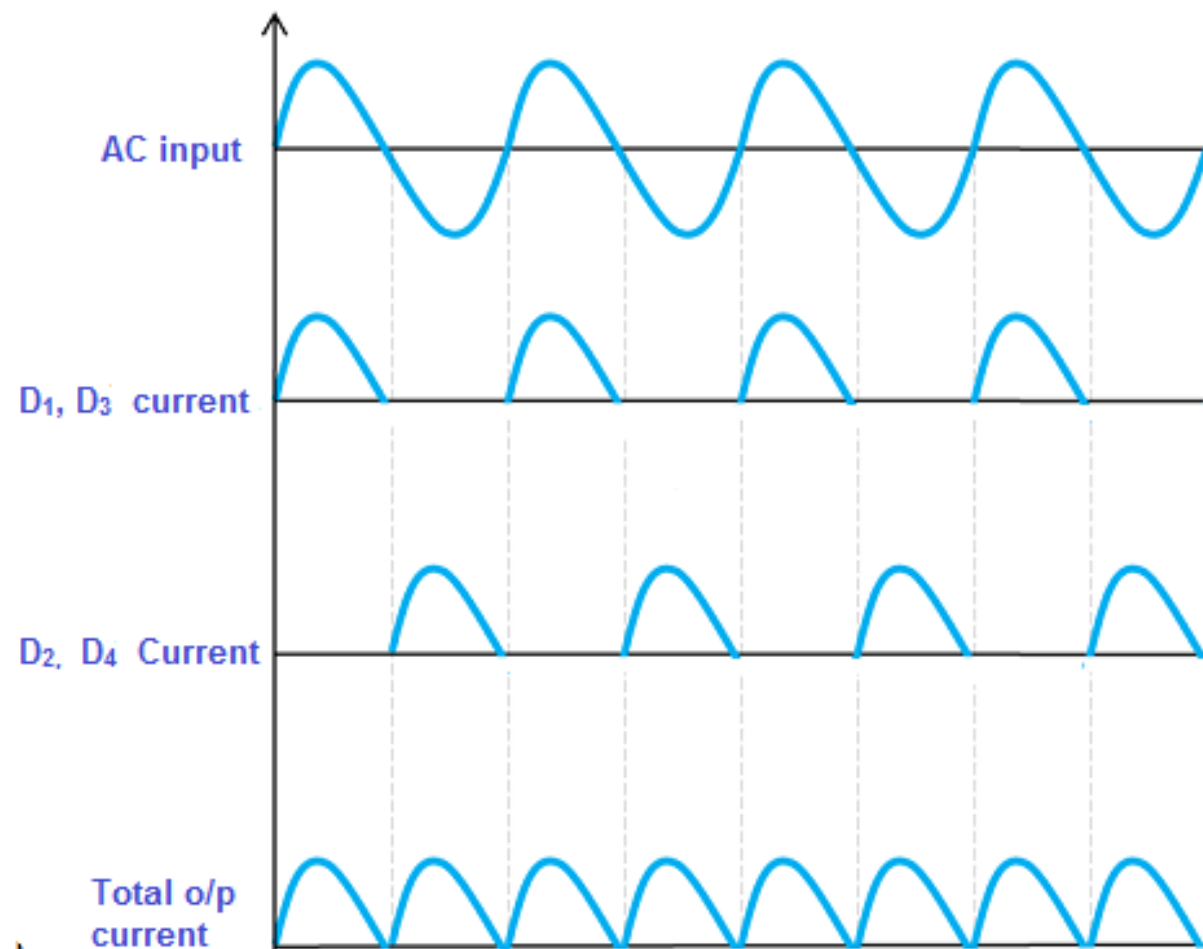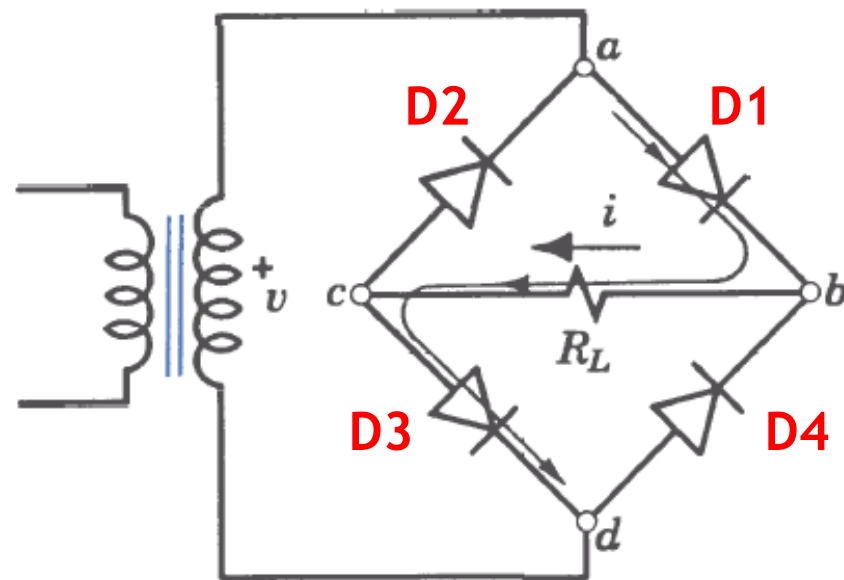
$$V_{DC} = \frac{2}{\pi} V_m \approx 64\% \text{ of } V_m$$



Friday, August 31, 2018



+ve 1/2 cycle of V : Diodes D1 and D3 conduct: D2 and D4 are off (a-b-c-d)  
 -ve 1/2 cycle of V : Diodes D2 and D4 conduct: D1 and D3 are off (d-b-c-a)

# Full-Wave Rectifier (FWR)

- Bridge Rectifier has some disadvantages.
  - Needs 4 diodes
  - Power is always dissipated in 2 of the diodes (in series with the load).

# Full-Wave Rectifier (FWR)

- FWR with centre-tapped transformer :

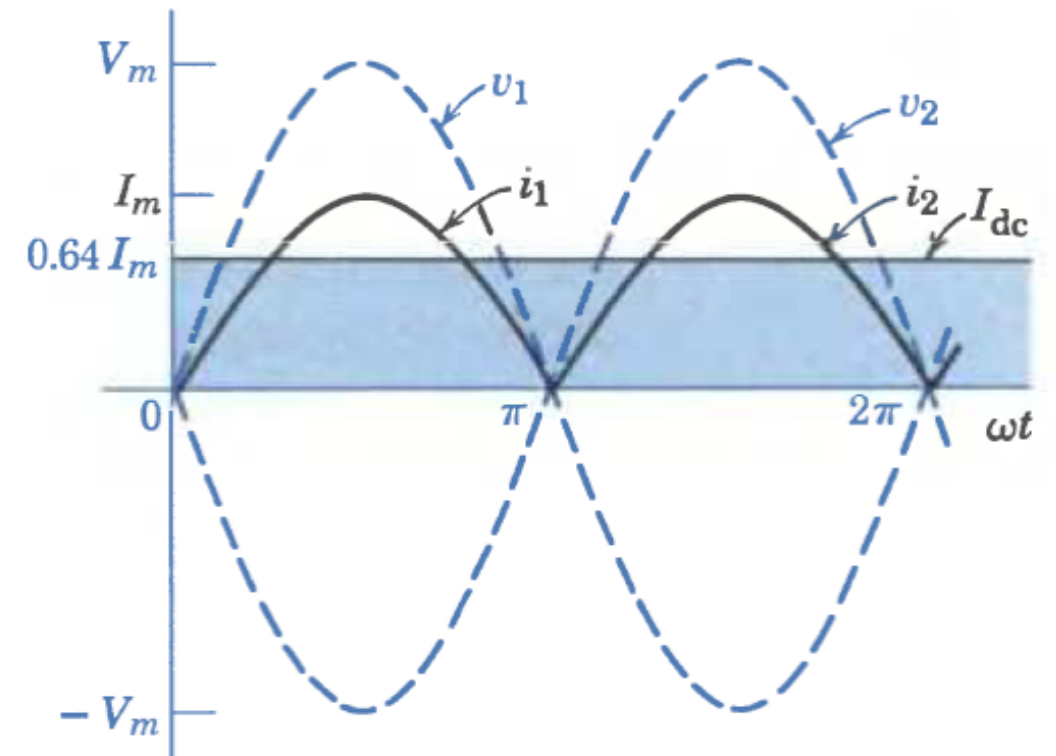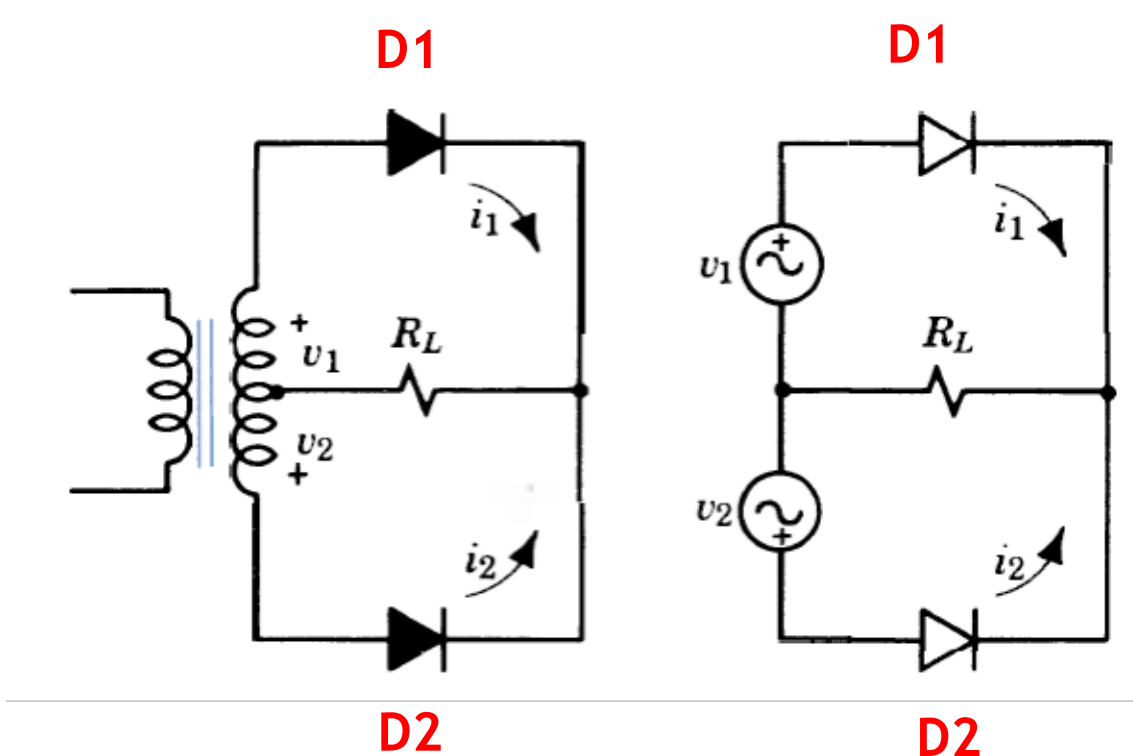

+ve 1/2 cycle of  $v$  :  $D_1$  conducts and  $D_2$  is off  
 -ve 1/2 cycle of  $v$  :  $D_2$  conducts and  $D_1$  is off

$$V_{dc} = \frac{2}{\pi} V_m$$

$$v_{1,2} = V_m \sin(\omega t \pm \pi/2 + \phi)$$

$V_m$  is the maximum OUTPUT Voltage

# FWR – Comparison


Full wave bridge rectifier	Full wave rectifier with center tap transformer
4 diodes required	2 diodes required
More power dissipation	Less power dissipation
Less expensive transformer	More expensive transformer required
Lower operating efficiency	Higher operating efficiency

# Signal Filtering


- In both HWR and FWR, the output voltage varies from 0 to  $V_{max}$ .
- This variation between max and min voltage is called 'ripple voltage'. Undesirable.
- Filter : Removes these pulsations and improves the DC component.
- Capacitor Filter : Connect a Capacitor across the rectifier to reduce ripple.
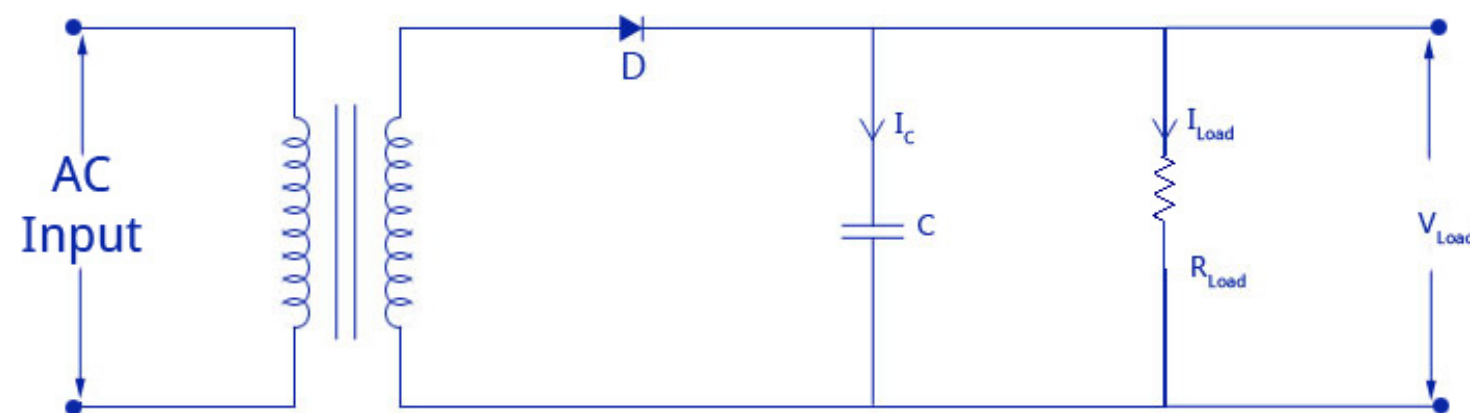
# Capacitor Filter with Rectifier (HWR)

- With the capacitor, the voltage across the load 'decays' slowly



# Capacitor Filter with Rectifier (HWR)

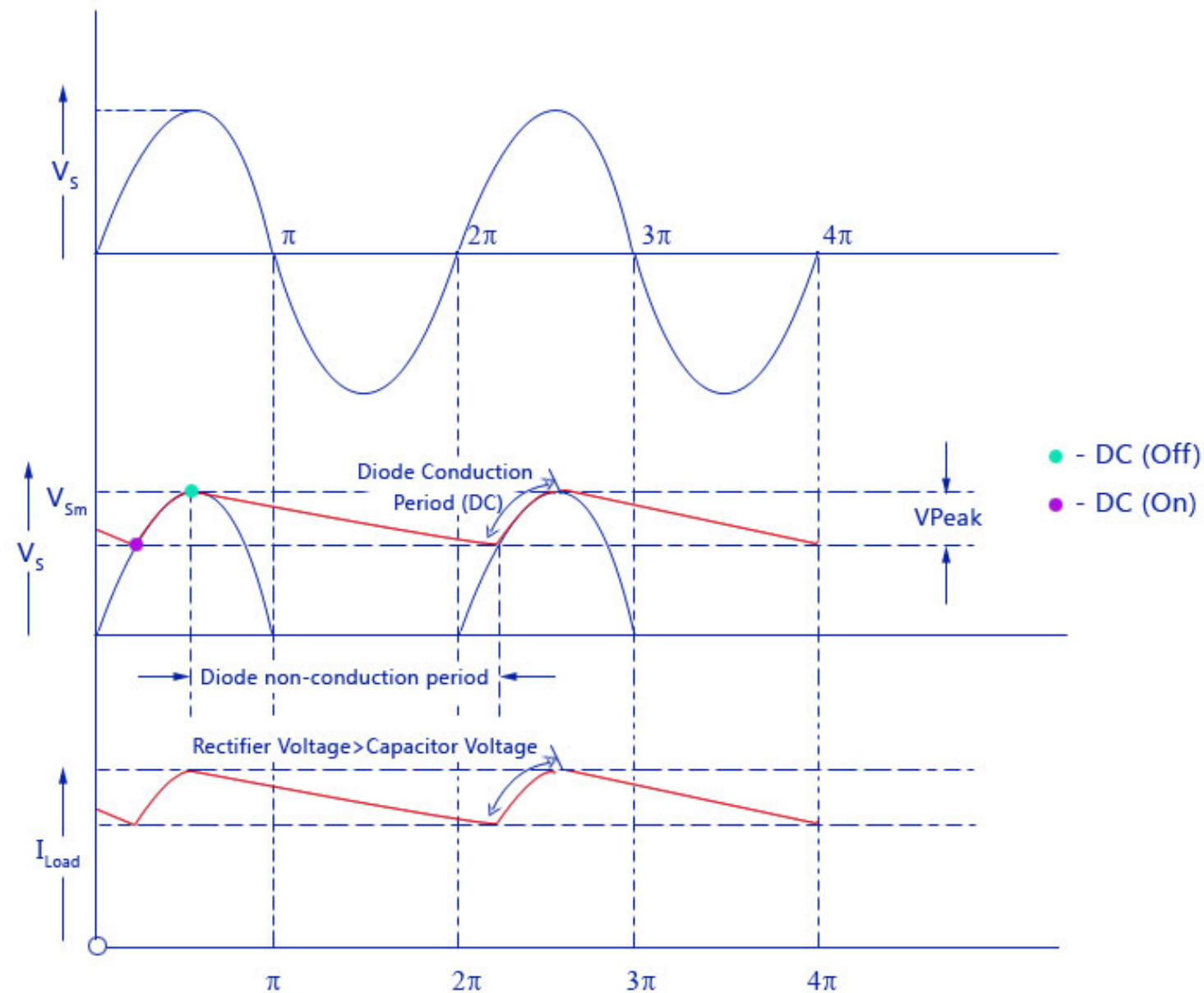


$$\tau = R_L C \gg T$$

Output Voltage remains almost constant


$$\begin{aligned}
 V_r &= \frac{\Delta q}{C} \approx \frac{I_{dc} T}{C} \\
 &= \frac{I_{dc}}{fC} = \frac{V_{dc}}{f R_L C}
 \end{aligned}$$

# Capacitor Filter with Rectifier (FWR)

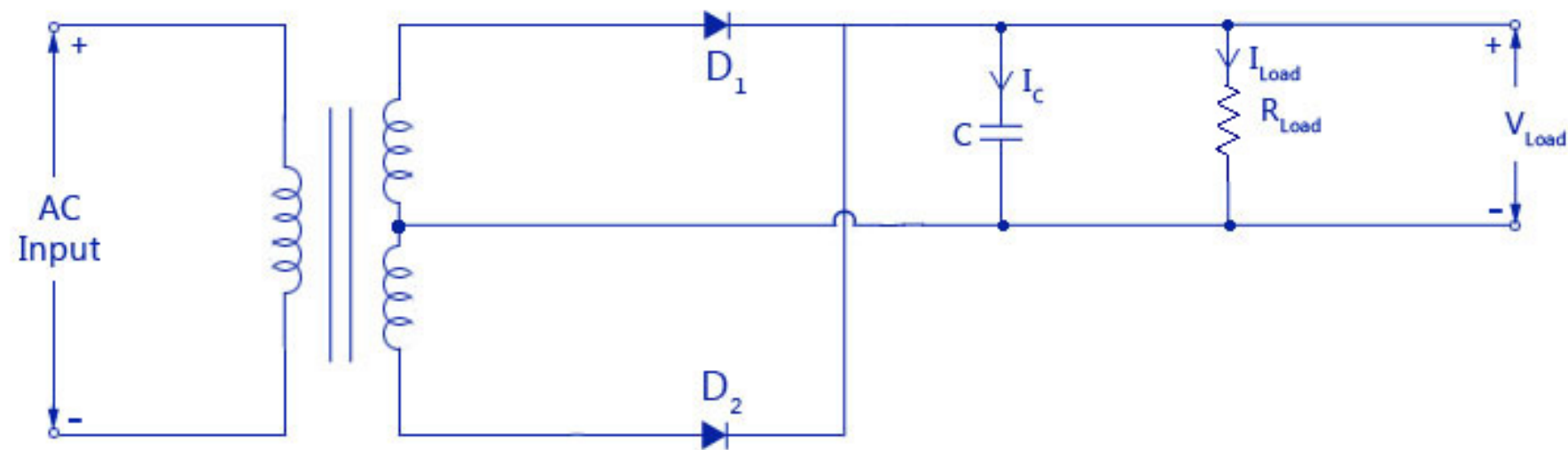



# Capacitor Filter with Rectifier (FWR)

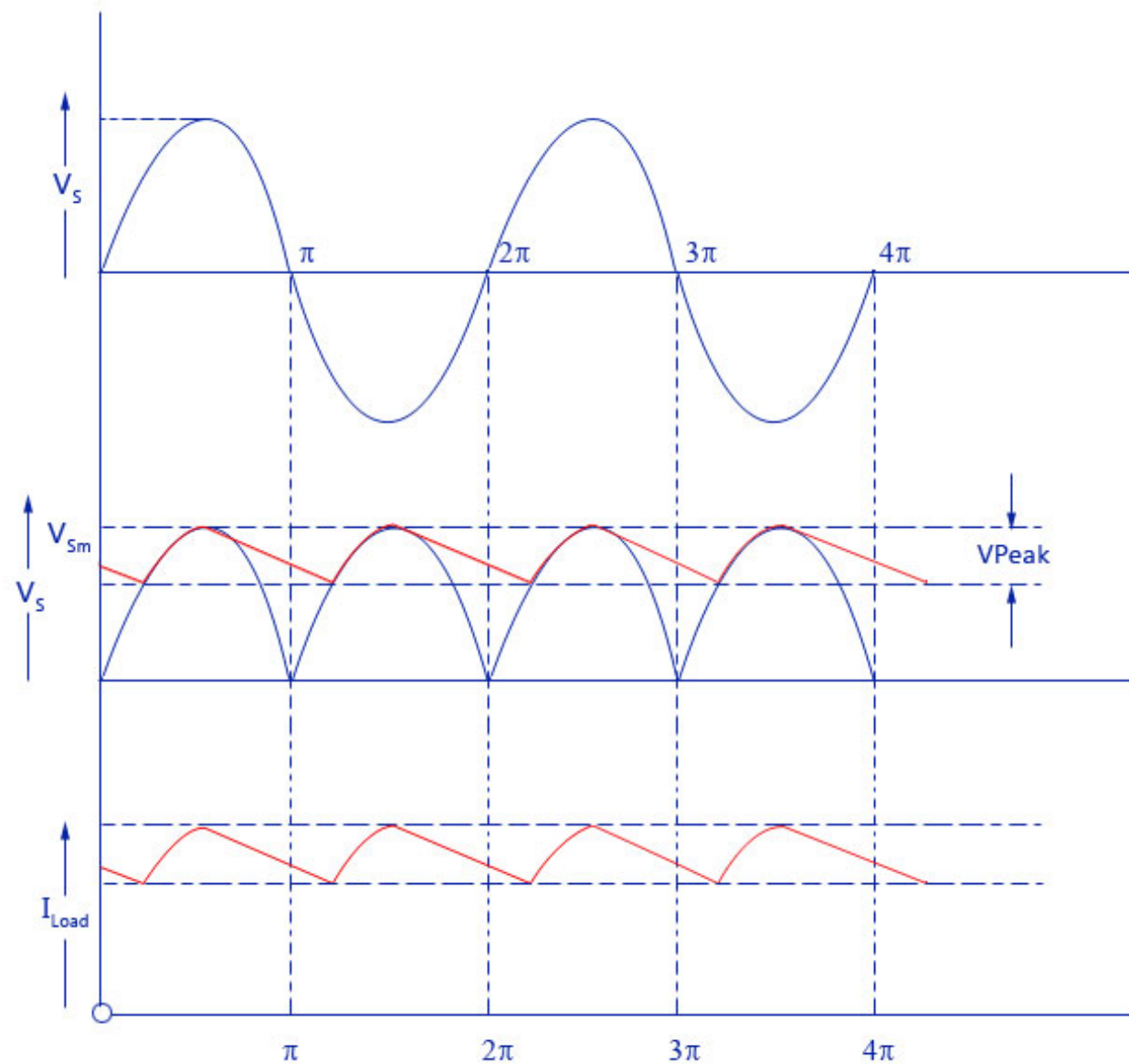

Here the discharge time is  $T/2$ .

$$\tau = R_L C \gg T$$

$$\begin{aligned} V_r &= \frac{\Delta q}{C} \approx \frac{I_{dc} T}{2C} \\ &= \frac{I_{dc}}{2fC} = \frac{V_{dc}}{2fR_L C} \end{aligned}$$