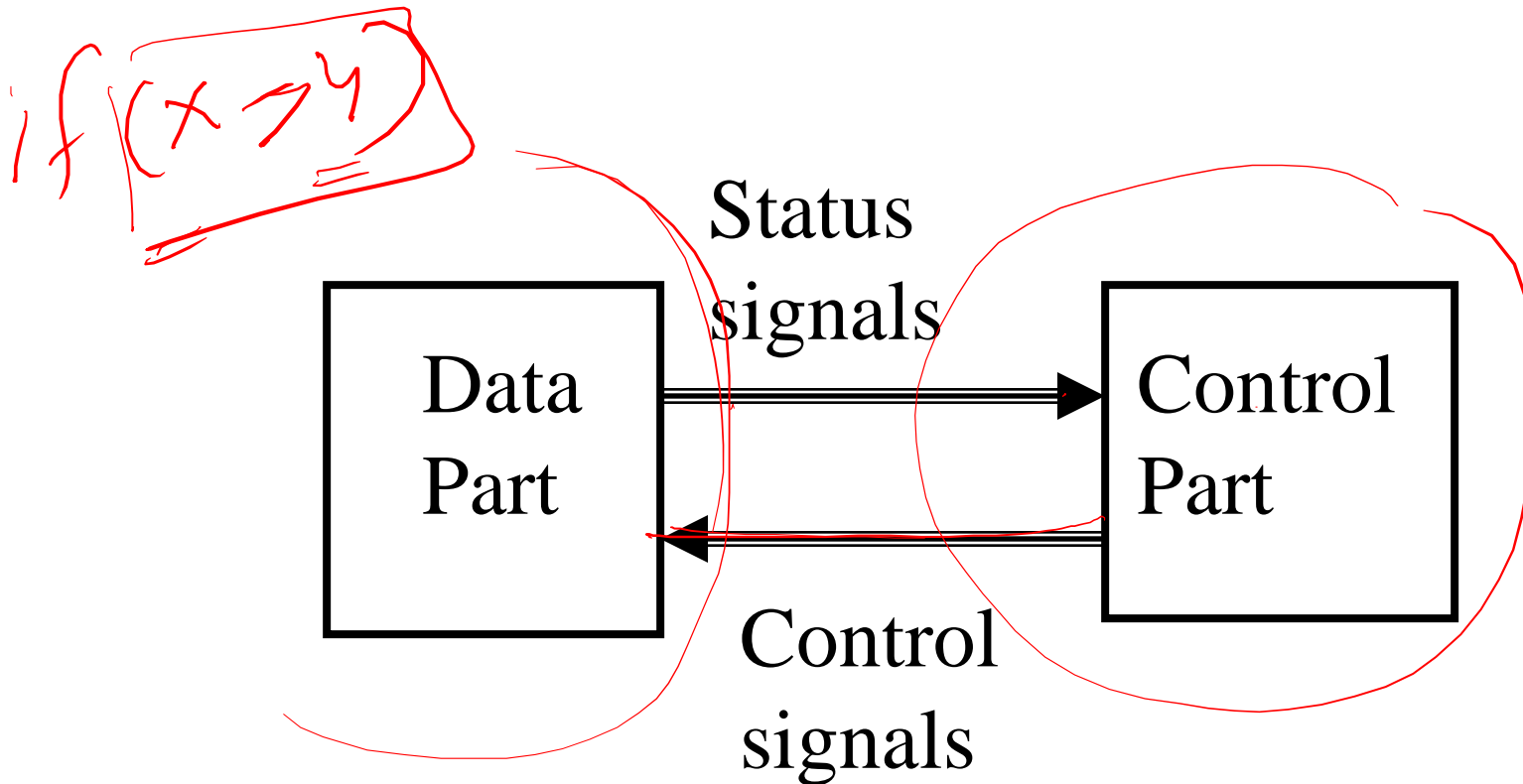


Lecture 24

System Design Case Studies


M. Balakrishnan
Dept. of Comp. Sci. & Engg.
I.I.T. Delhi


Data-Control Partition



Controller for Air-Conditioner

To maintain temperature at 22° C

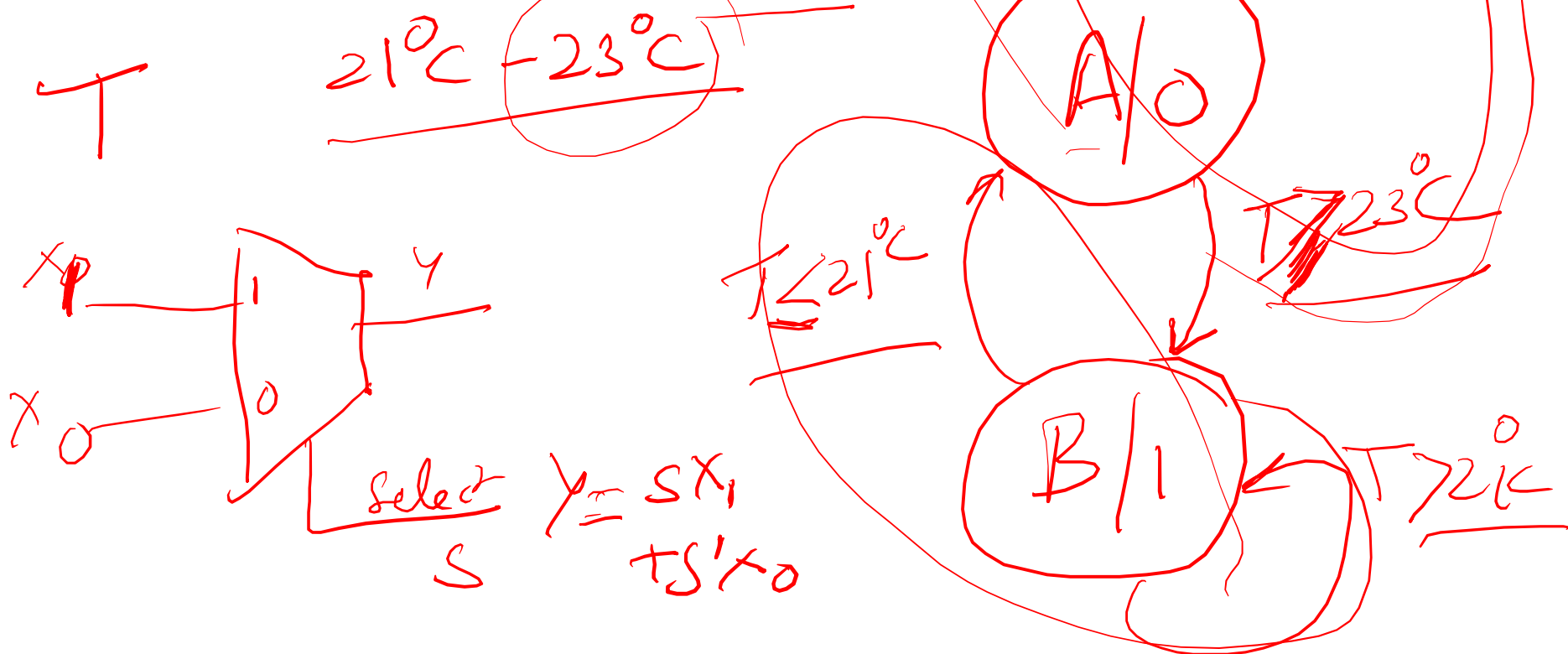

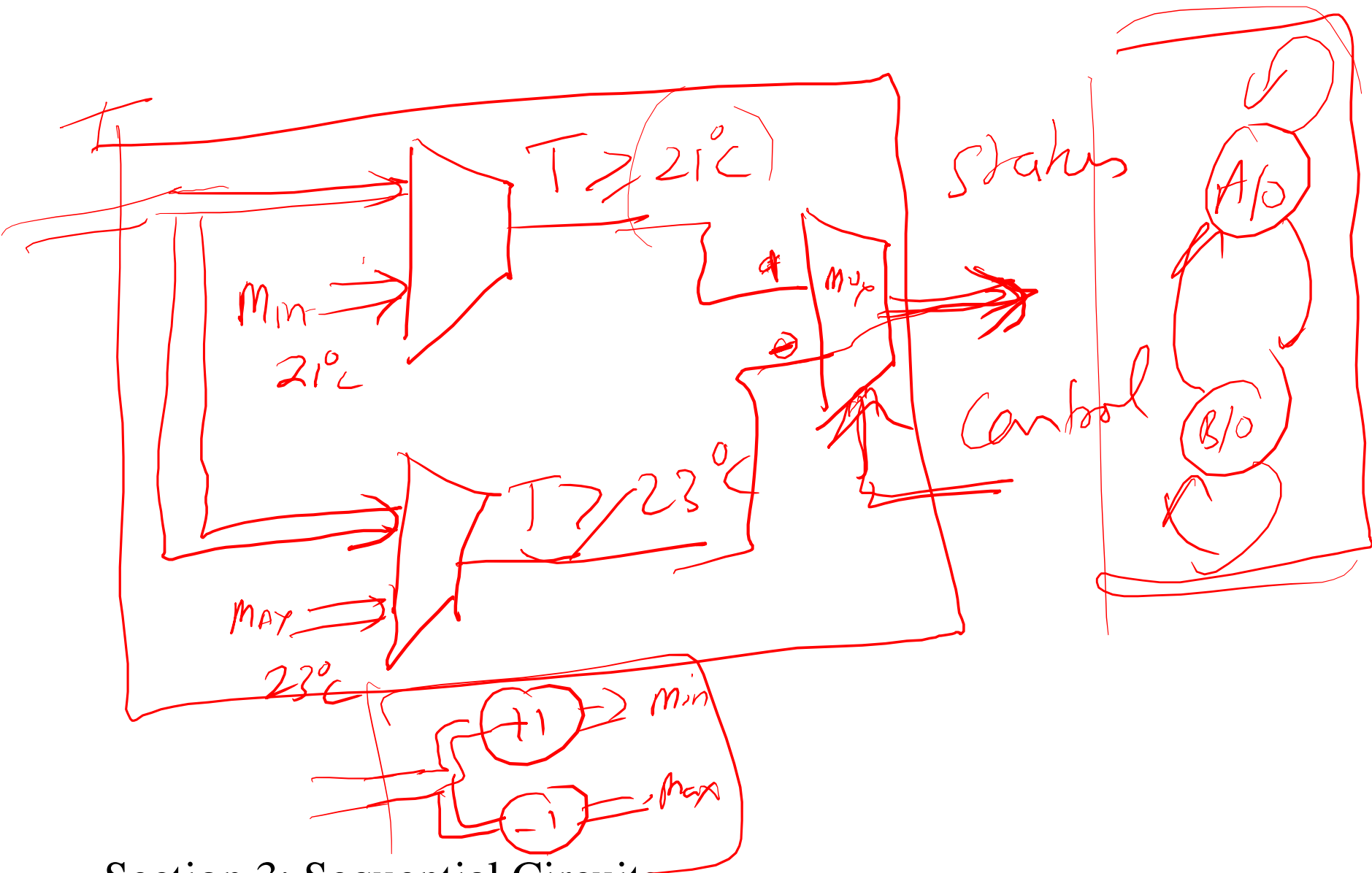

Section 3: Sequential Circuits




Section 3: Sequential Circuits

Steps in System Design

- Choose an algorithm \leftarrow DP + CP
- Identify the data modules (operators & storage)
- Identify the control signals \leftarrow Status signals
- Extract the state machine for control
- Implement the state machine to complete the design

Case Study1: GCD Computer

$$z = \text{gcd}(x, y)$$

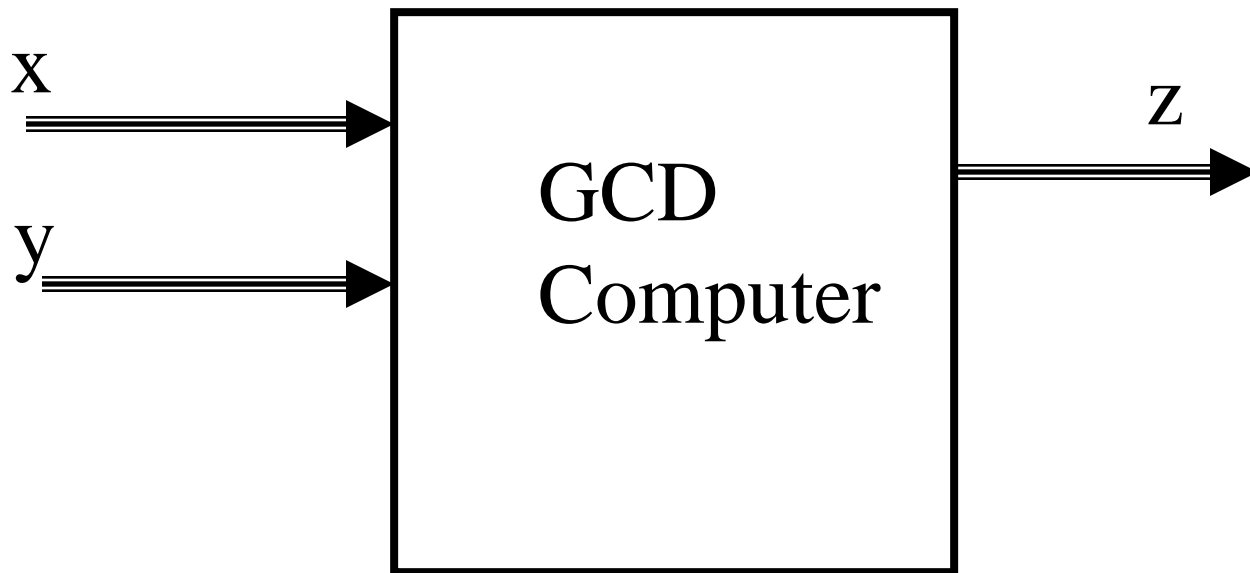

GCD Algorithm

Input x, y;

while ($x \neq y$) do

if ($x > y$) then $x := x - y$

else $y := y - x$

endif;

endwhile;

$z := x$;

end.

Reg  Catch 

Modified GCD Algorithm (RTL)

S0: R1 := x, R2 := y;

S1: while (R1 \neq R2) do

S2: if (R1 > R2)


S3: then R1 := R1 - R2

S4: else R2 := R2 - R1

endif;

endwhile;

S5: R3 := R1;

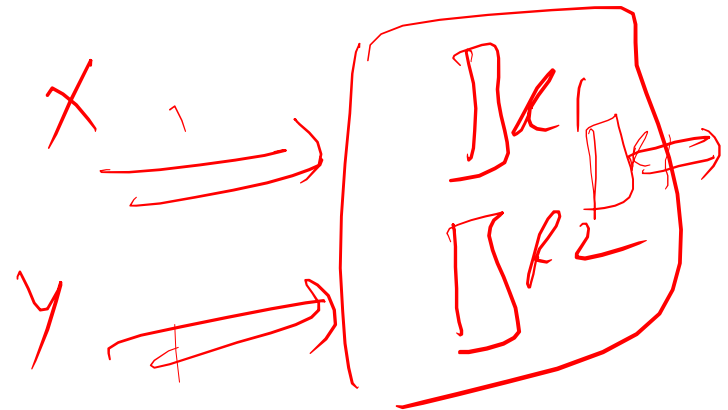

GCD Computer: Data Part

