

# ELL100: INTRODUCTION TO ELECTRICAL ENGG.

## Boolean Logic

Instructor for this part: Debanjan Bhowmik, Assistant Professor,  
Department of Electrical Engineering, IIT Delhi


Contact : [debanjan@ee.iitd.ac.in](mailto:debanjan@ee.iitd.ac.in)

Textbook: Moris Mano's 'Digital Design':

Chapter 2 (Boolean Algebra and Logic Gates)
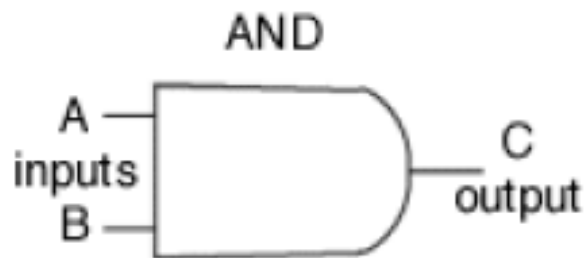
# Boolean Algebra

- Branch of algebra in which variable values are: True (1) or False (0)
- Basic set of TRUE/FALSE operations and rules
- Formulated by George Boole in 19<sup>th</sup> century
  - Two **binary** operators:
    - **AND (conjunction)**: Output is TRUE 'only if' E




$$C = A \cdot B$$

A	B	C
0	0	0
1	0	0
0	1	0
1	1	1

JE
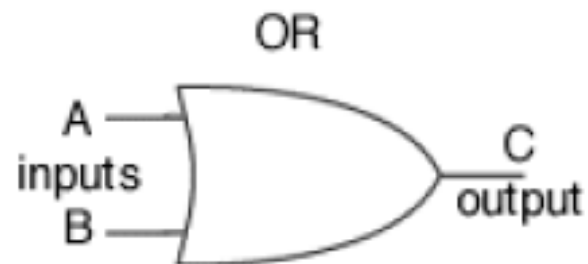
# Boolean Algebra

- Two **binary** operators:
  - AND (conjunction): Output is TRUE 'only if' BOTH inputs are TRUE
  - OR (disjunction): Output is TRUE 'if' ANY input is TRUE




$$C = A + B$$

A	B	C
0	0	0
1	0	1
0	1	1
1	1	1
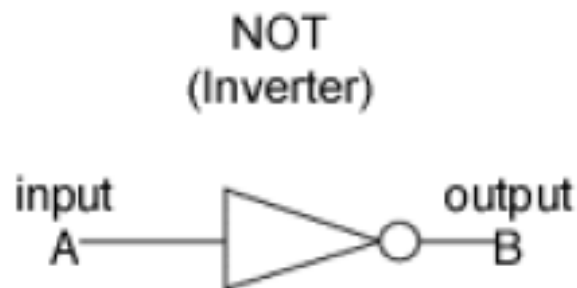
# Boolean Algebra

- Two binary operators: AND (conjunction), OR (disjunction)
- One **unary** operator: **NOT** (Negation)



$$B = \bar{A}$$

$$B = A'$$

A	B
0	1
1	0

# Boolean Algebra: Basic Properties

- Both the binary operations satisfy: If A,B are 1/0
  - Closure (If A, B are 1/0  $\rightarrow$   $A+B$ ,  $A.B$  are also 1/0)
  - Commutativity
    - $A + B = B + A$ ,  $A . B = B . A$
  - Associativity
    - $(A + B) + C = A + (B + C)$ ,  $A . (B . C) = (A . B) . C$
  - Distributivity
    - $A . (B + C) = A . B + A . C$   $A + (B . C) = (A + B) . (A + C)$
  - Idempotence
    - $A + A = A$   $A . A = A$
  - Identity
    - $A + 1 = 1$   $A . 0 = 0$

# Boolean Algebra: Basic Properties

- Both the binary operations satisfy: If A,B are 1/0

- Closure

- Commutativity

- Associativity

- Distributivity

- Idempotence

- Absorption (  $A + A.B = A. (A + B) = A$  )

- Involution (  $\bar{\bar{A}} = A \rightarrow \text{NOT}(\text{NOT}(A))=A$  )

- Complement (  $A + \bar{A} = 1, A.\bar{A} = 0$  )

$$\begin{aligned} A + A.B &= (A.1) + (A.B) \\ &= A.(B + 1) = A \end{aligned}$$

$$\begin{aligned} A.(A + B) &= (A + 0).(A + B) \\ &= A + (B.0) = A \end{aligned}$$

# Boolean Algebra : Basic Properties

- Both the binary operations satisfy: If A,B are 1/0
  - Closure
  - Commutativity
  - Associativity
  - Distributivity
  - Idempotence
  - Absorption
  - Involution
  - Complement

De Morgan's Laws:

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$


# Universal Gates

- **Universal Gates:** Logic Gates that can implement any Boolean function, without the use of any other type of gates.
- They are more easier to fabricate and are the *actual* 'basic' gates in digital electronics




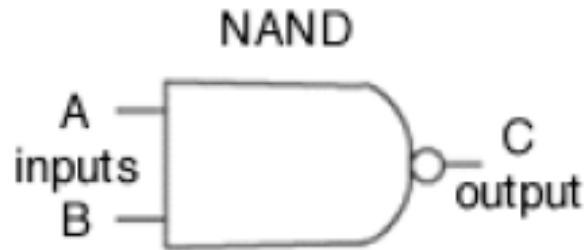
# Universal Gates

- **Universal Gates:** Logic Gates that can implement any Boolean function, without the use of any other type of gates.
- **NAND Gate:**  $\overline{AB}$  (NOT-AND)




A	B	C
0	0	1
1	0	1
0	1	1
1	1	0

# NAND Implementation of NOT/AND/OR

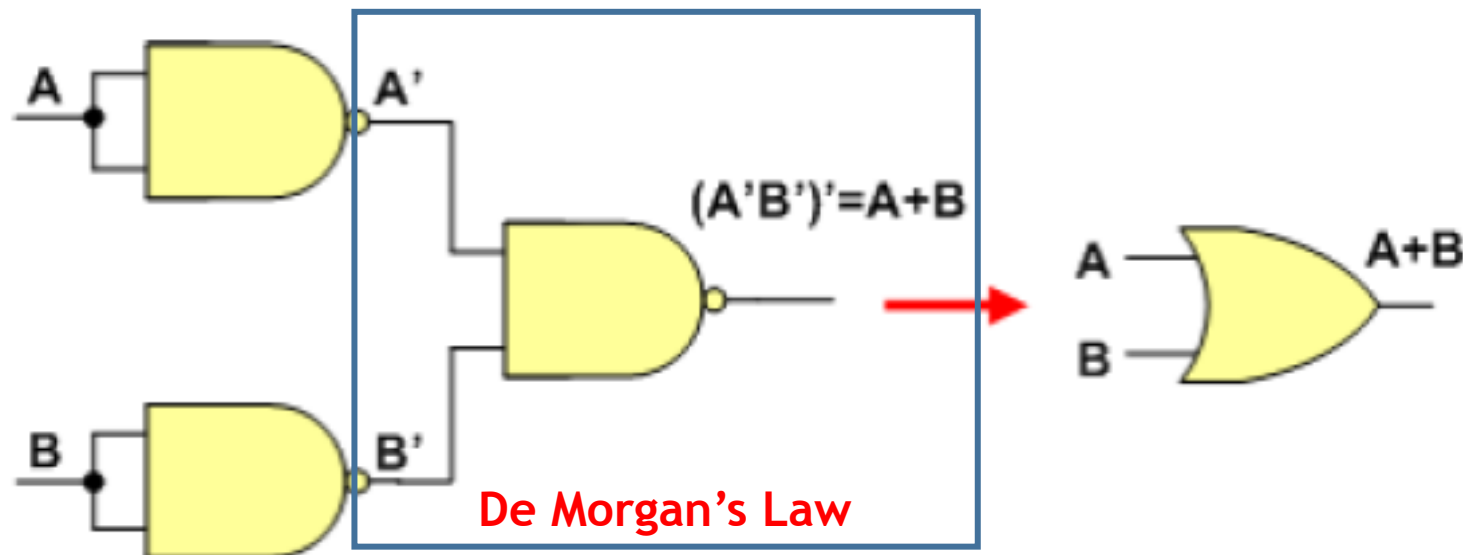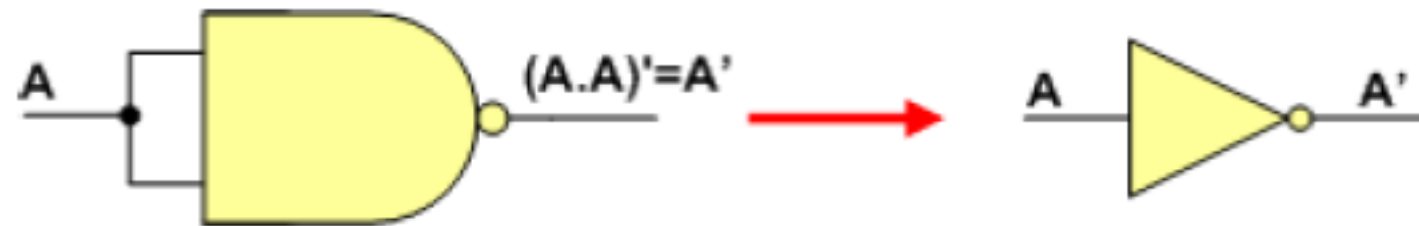

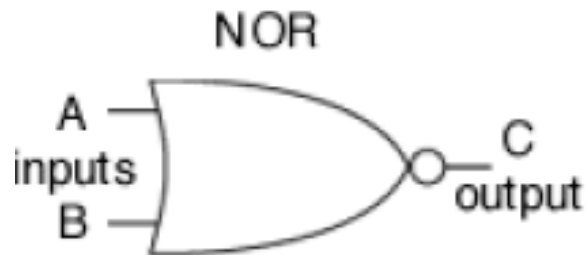
# Universal Gates

- **Universal Gates:** Logic Gates that can implement any Boolean function, without the use of any other type of gates.
- **NOR Gate :**  $\overline{A + B}$  (NOT-OR)




A	B	C
0	0	1
1	0	0
0	1	0
1	1	0

# NOR Implementation of NOT/OR/AND

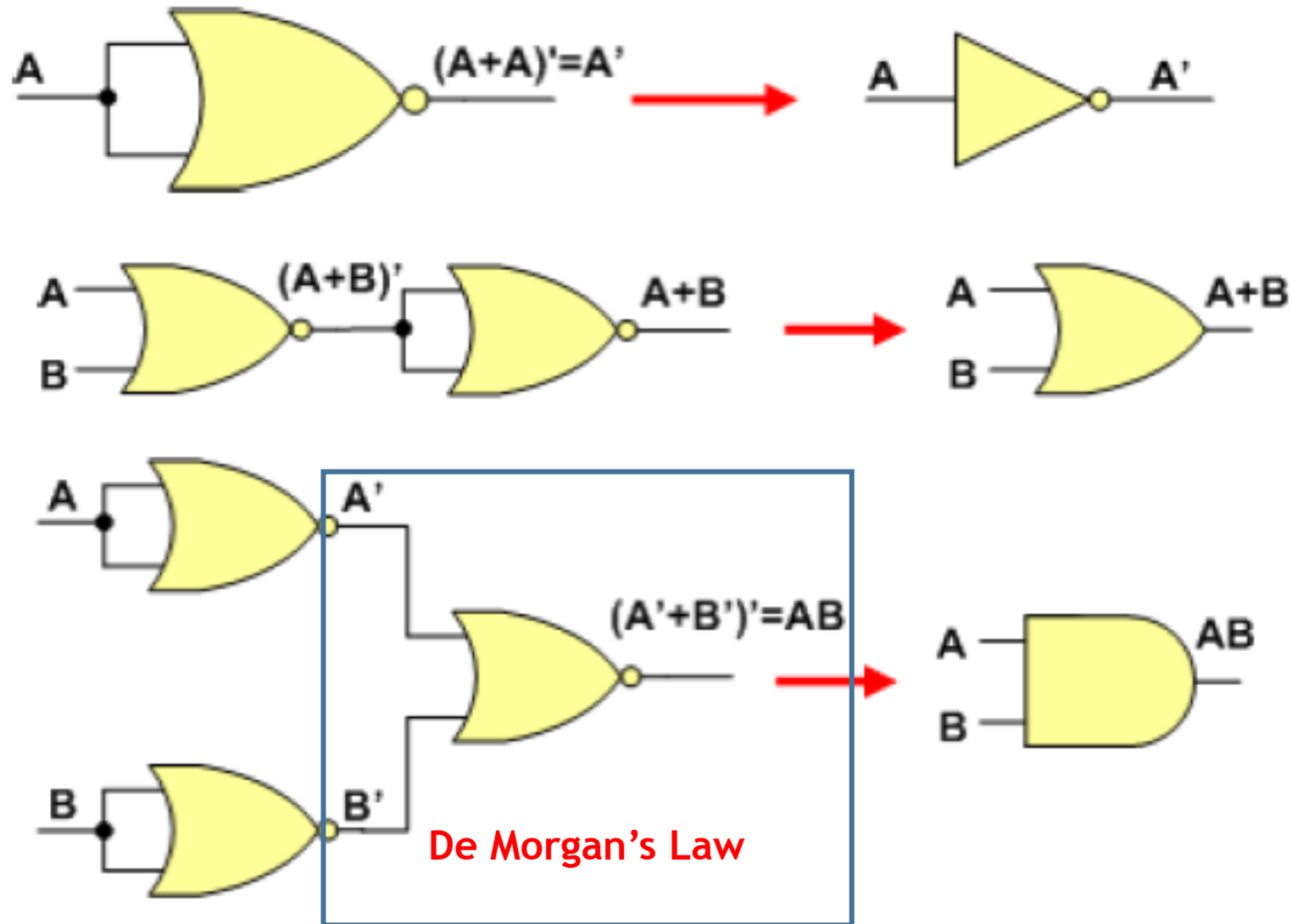
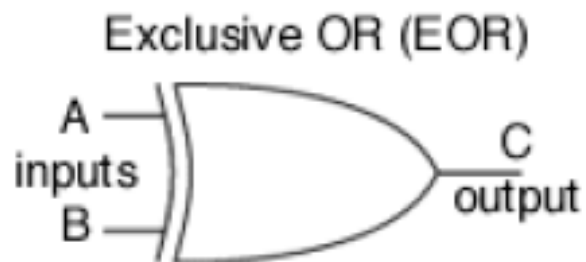
# Other Commonly Used Gates


- **Exclusive OR (XOR):**  $A \oplus B = \bar{A}B + A\bar{B}$
- Also called **Exclusive Disjunction**
- Output is TRUE if **odd** number of inputs are TRUE
- Becomes “one and only one” in case of 2 inputs



A	B	C
0	0	0
1	0	1
0	1	1
1	1	0
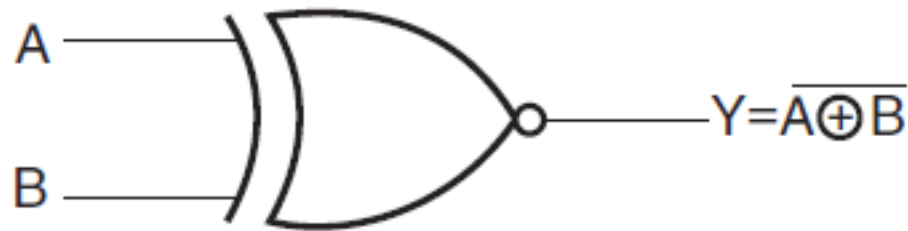
# Other Commonly Used Gates

- **Exclusive NOR (XNOR)** :  $A \odot B = \bar{A}\bar{B} + AB = \overline{A \oplus B}$
- Output is TRUE if **even** number of inputs are TRUE
- Becomes '**Equivalence**' in case of two inputs



$$Y = \overline{(A \oplus B)} = (A.B + \bar{A}.\bar{B})$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1