



# ELL100: INTRODUCTION TO ELECTRICAL ENGG.

## Impedance Concepts

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik,  
Harshan Jagadeesh

Department of Electrical Engineering, IITD

# Impedance

- Impedance ( $Z$ ): measure of opposition that a circuit presents to current when a voltage is applied.
- Impedance ( $Z$ ) extends the concept of resistance to inductance and capacitance.

# Impedance

- Impedance ( $Z$ ): measure of opposition that a circuit presents to current when a voltage is applied.
- Impedance ( $Z$ ) extends the concept of resistance to inductance and capacitance.
- Impedance ( $Z$ ) is a complex number; units same as resistance (Ohms). Thus, has both magnitude and phase.

# Impedance

- Impedance (Z): measure of opposition that a circuit presents to current when a voltage is applied.
- Impedance (Z) extends the concept of resistance to inductance and capacitance.
- Impedance (Z) is a complex number; units same as resistance (Ohms). Thus, has both magnitude and phase.

$$Z = (R + jX) \Omega$$

$R$  = Resistance

$X$  = Reactance

# Impedance

- Impedance ( $Z$ ): measure of opposition that a circuit presents to current when a voltage is applied.
- Impedance ( $Z$ ) extends the concept of resistance to inductance and capacitance.
- Impedance ( $Z$ ) is a complex number; units same as resistance (Ohms). Thus, has both magnitude and phase.
- For exponential/sinusoidal functions  $Z$  is defined as: ratio of complex representation of the voltage to complex representation of current.

# Impedance

- In the previous analysis, we have assumed the 'exponential' template for voltage and current.

# Impedance

- In the previous analysis, we have assumed the ‘exponential’ template for voltage and current.

$$\begin{aligned} i(t) = I_0 e^{st} &\implies \frac{di}{dt} = sI_0 e^{st} = si(t) \\ v(t) = V_0 e^{st} &\implies \frac{dv}{dt} = sV_0 e^{st} = sv(t) \end{aligned}$$

# Impedance

- In the previous analysis, we have assumed the ‘exponential’ template for voltage and current.

$$\begin{aligned} i(t) = I_0 e^{st} &\implies \frac{di}{dt} = sI_0 e^{st} = si(t) \\ v(t) = V_0 e^{st} &\implies \frac{dv}{dt} = sV_0 e^{st} = sv(t) \end{aligned}$$

- For Resistor  $Z_R = \frac{v}{i} = \frac{iR}{i} = R \Omega$



# Impedance

- In the previous analysis, we have assumed the ‘exponential’ template for voltage and current.

$$\begin{aligned} i(t) &= I_0 e^{st} \implies \frac{di}{dt} = sI_0 e^{st} = si(t) \\ v(t) &= V_0 e^{st} \implies \frac{dv}{dt} = sV_0 e^{st} = sv(t) \end{aligned}$$

- For Resistor  $Z_R = \frac{v}{i} = \frac{iR}{i} = R \Omega$
- For Inductor  $Z_L = \frac{v}{i} = \frac{L \frac{di}{dt}}{i} = \frac{Lsi}{i} = sL \Omega$

# Impedance

- In the previous analysis, we have assumed the ‘exponential’ template for voltage and current.

$$\begin{aligned} i(t) &= I_0 e^{st} \implies \frac{di}{dt} = sI_0 e^{st} = si(t) \\ v(t) &= V_0 e^{st} \implies \frac{dv}{dt} = sV_0 e^{st} = sv(t) \end{aligned}$$

- For Resistor  $Z_R = \frac{v}{i} = \frac{iR}{i} = R \Omega$
- For Inductor  $Z_L = \frac{v}{i} = \frac{L \frac{di}{dt}}{i} = \frac{Lsi}{i} = sL \Omega$
- For Capacitor  $Z_C = \frac{v}{i} = \frac{v}{C \frac{dv}{dt}} = \frac{v}{Cs v} = \frac{1}{sC} \Omega$

# Impedance - Scope

- Impedance is defined only when the waveforms involved are DC, exponential or those which can be represented as combination of exponentials (eg : sinusoidal waveform)

# Impedance - Scope

- Impedance is defined only when the waveforms involved are DC, exponential or those which can be represented as combination of exponentials (eg : sinusoidal waveform)
- DC case:  $s = 0$

$$Z_R(0) = R$$

$$Z_L(0) = Ls|_{s=0} = 0$$

$$Z_C(0) = \frac{1}{Cs}|_{s=0} = \infty$$

# Impedance - Scope

- Impedance is defined only when the waveforms involved are DC, exponential or those which can be represented as combination of exponentials (eg : sinusoidal waveform)
- DC case :  $s = 0$



$$Z_R(0) = R$$

$$Z_L(0) = Ls|_{s=0} = 0 \quad (\text{Inductance is short circuit to DC current})$$

$$Z_C(0) = \frac{1}{Cs}|_{s=0} = \infty \quad (\text{Capacitance is open circuit to DC voltage})$$

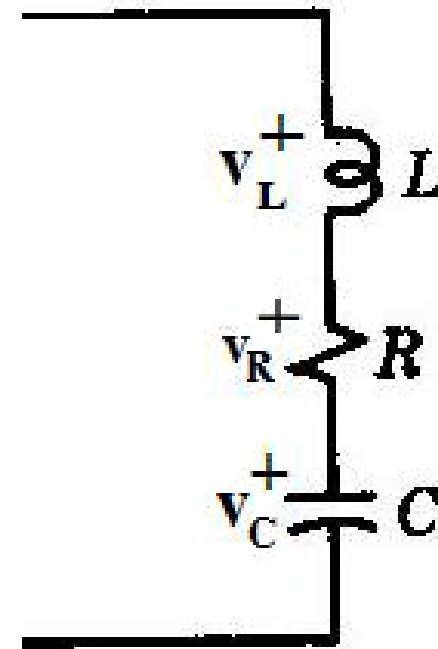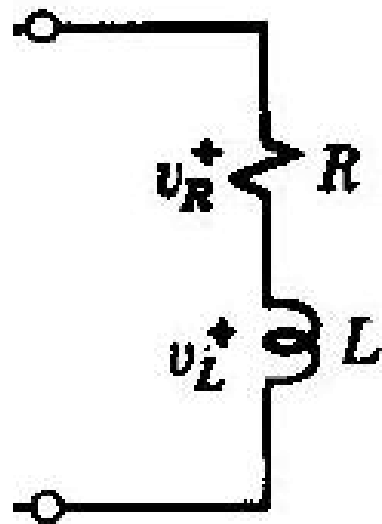
# Equivalent Impedance

- Impedance can be combined in series or parallel, just like resistances



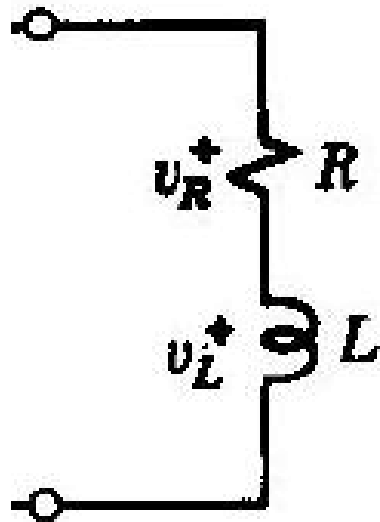
# Equivalent Impedance

- Impedance can be combined in series or parallel, just like resistances




$$Z(s) = R + sL$$

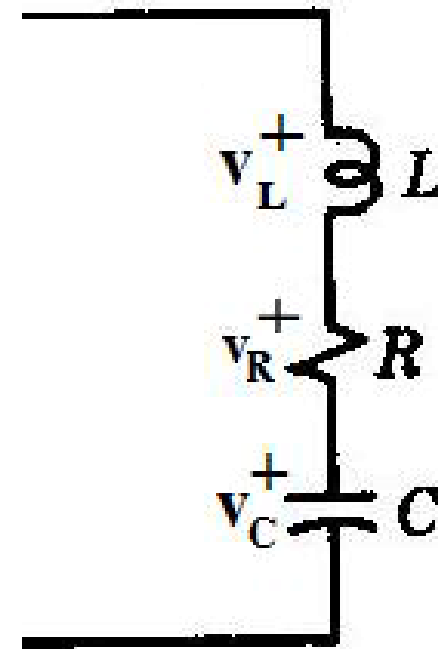

$$Z(s) = R + sL + \frac{1}{sC}$$
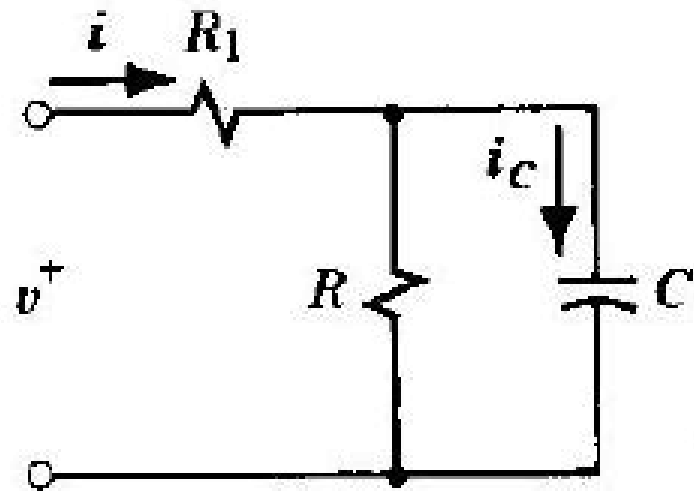
# Example

$R_1 = 2\Omega$  ,  $C = 0.25F$  and  
 $R = 4\Omega$ . Using impedance  
concept, find the current  $i$  and  $i_c$   
for  $v = 6 e^{-2 t} V$






# Example

$R_1 = 2\Omega$  ,  $C = 0.25F$  and  
 $R = 4\Omega$ . Using impedance  
concept, find the current  $i$  and  $i_c$   
for  $v = 6 e^{-2 t} V$


$$Z = Z_1 + \frac{Z_R Z_C}{Z_R + Z_C}$$

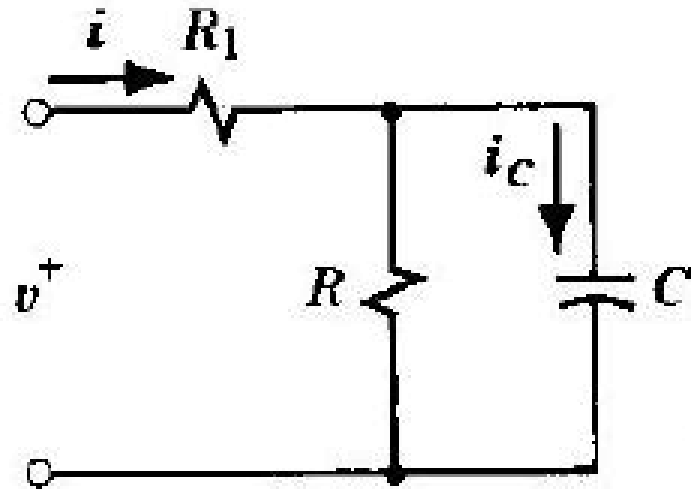
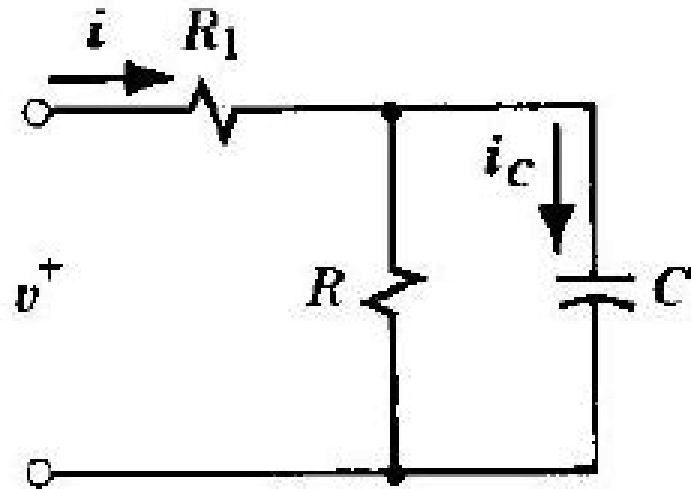
# Example


$R_1 = 2\Omega$  ,  $C = 0.25F$  and  
 $R = 4\Omega$ . Using impedance  
concept, find the current  $i$  and  $i_c$   
for  $v = 6 e^{-2 t} V$

$$\begin{aligned} Z &= Z_1 + \frac{Z_R Z_C}{Z_R + Z_C} \\ &= R_1 + \frac{R(1/sC)}{R + (1/sC)} \end{aligned}$$


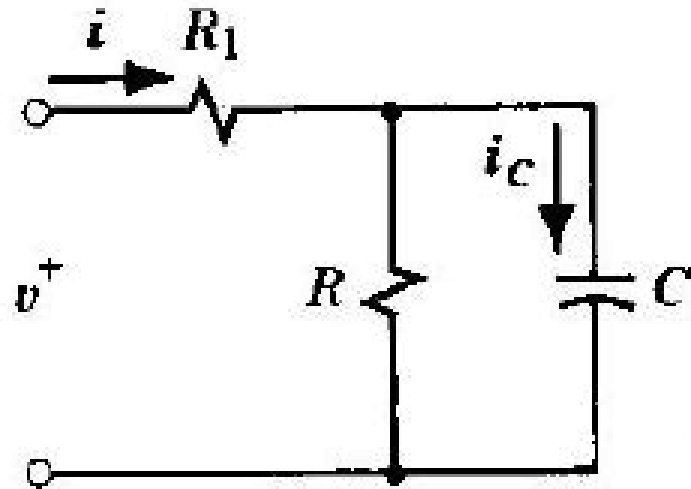
# Example


$R_1 = 2\Omega$  ,  $C = 0.25F$  and  $R = 4\Omega$ . Using impedance concept, find the current  $i$  and  $i_c$  for  $v = 6 e^{-2 t} V$



$$\begin{aligned} Z &= Z_1 + \frac{Z_R Z_C}{Z_R + Z_C} \\ &= R_1 + \frac{R(1/sC)}{R + (1/sC)} \\ &= 2 + \frac{4/(-2 \times 0.25)}{4 + 1/(-2 \times 0.25)} \\ &= 2 + \frac{-8}{2} = -2\Omega \end{aligned}$$
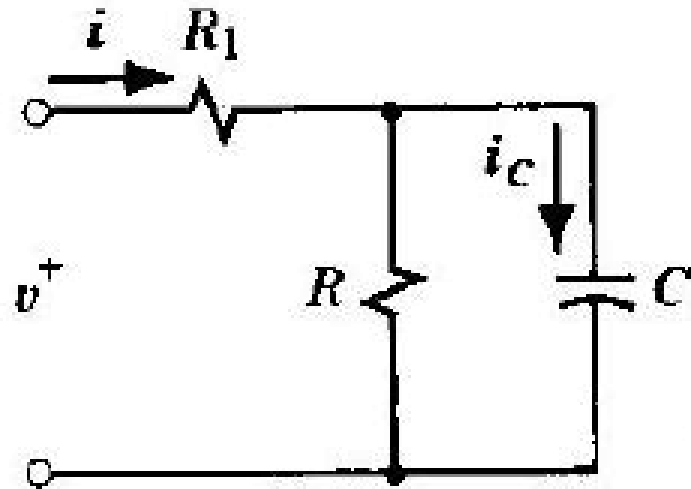
# Example

$R_1 = 2\Omega$  ,  $C = 0.25F$  and  $R = 4\Omega$ . Using impedance concept, find the current  $i$  and  $i_c$  for  $v = 6 e^{-2 t} V$




$$\begin{aligned} Z &= Z_1 + \frac{Z_R Z_C}{Z_R + Z_C} \\ &= R_1 + \frac{R(1/sC)}{R + (1/sC)} \\ &= 2 + \frac{4/(-2 \times 0.25)}{4 + 1/(-2 \times 0.25)} \\ &= 2 + \frac{-8}{2} = -2\Omega \end{aligned}$$

Then,

$$i = \frac{v}{Z} = \frac{6 e^{-2t}}{-2} = -3 e^{-2t} A$$
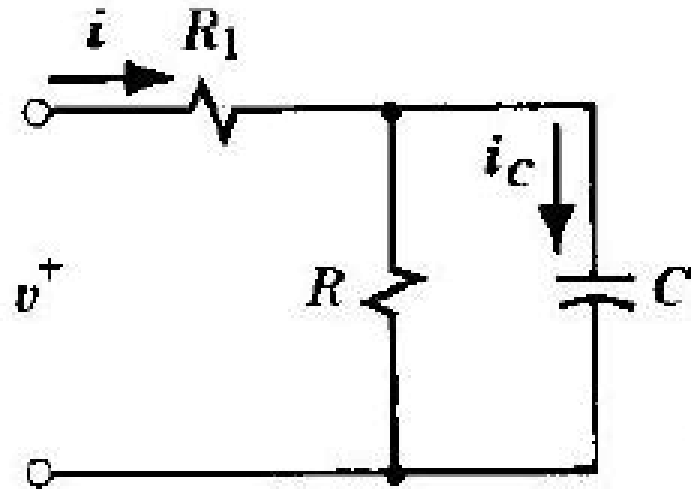
# Example

$R_1 = 2\Omega$  ,  $C = 0.25F$  and  $R = 4\Omega$ . Using impedance concept, find the current  $i$  and  $i_c$  for  $v = 6 e^{-2 t} V$



$$\begin{aligned} Z &= Z_1 + \frac{Z_R Z_C}{Z_R + Z_C} \\ &= R_1 + \frac{R(1/sC)}{R + (1/sC)} \\ &= 2 + \frac{4/(-2 \times 0.25)}{4 + 1/(-2 \times 0.25)} \\ &= 2 + \frac{-8}{2} = -2\Omega \end{aligned}$$

Then,


$$i = \frac{v}{Z} = \frac{6 e^{-2t}}{-2} = -3 e^{-2t} A$$

Using current divider and impedance concepts,

$$i_C = \frac{Z_R \cdot i}{Z_R + Z_C} = \frac{4 \cdot i}{4 - 2} = -6 e^{-2t} A$$

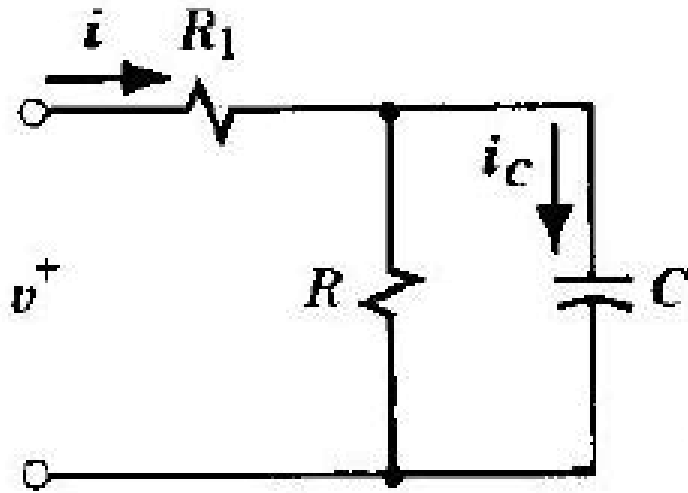
# General Impedance or Impulse Function

- Typical impedance functions are of type


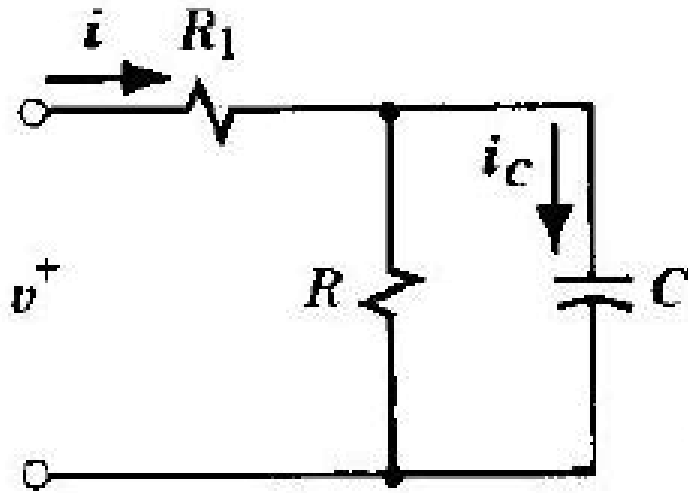
# General Impedance Function



- Typical impedance functions are of type



$$\begin{aligned} Z(s) &= R_1 + \frac{R(1/sC)}{R + (1/sC)} \\ &= \frac{s(R_1 RC) + (R_1 + R)}{sRC + 1} \end{aligned}$$
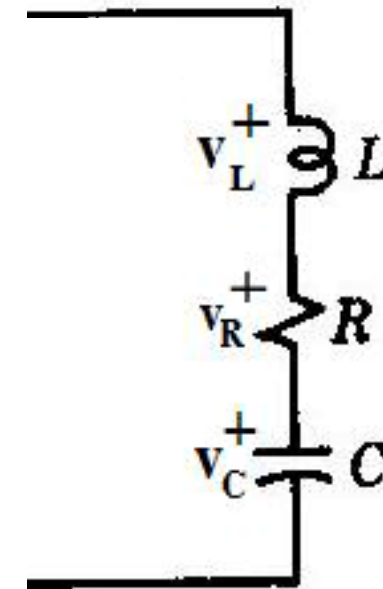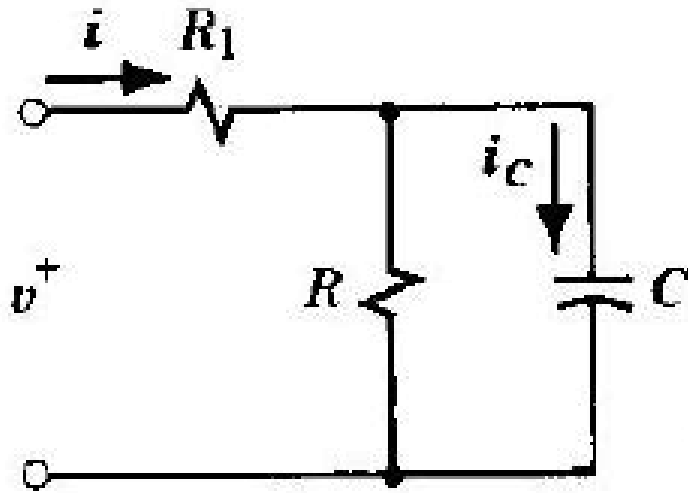
# General Impedance Function

- Typical impedance functions are of type




$$\begin{aligned} Z(s) &= R_1 + \frac{R(1/sC)}{R + (1/sC)} \\ &= \frac{s(R_1RC) + (R_1 + R)}{sRC + 1} \end{aligned}$$



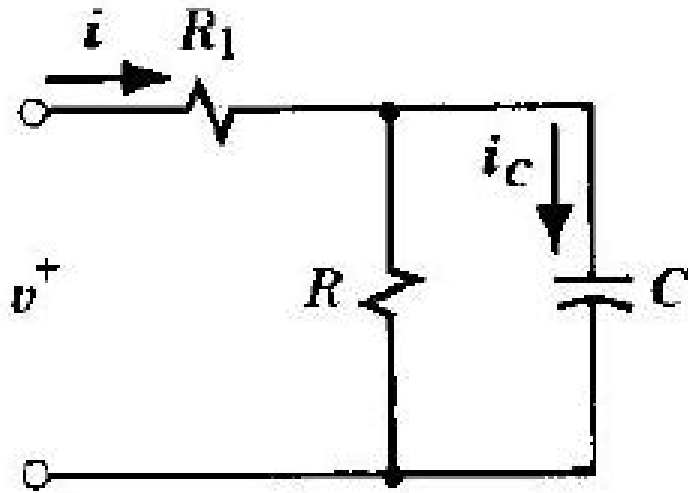
# General Impedance Function

- Typical impedance functions are of type


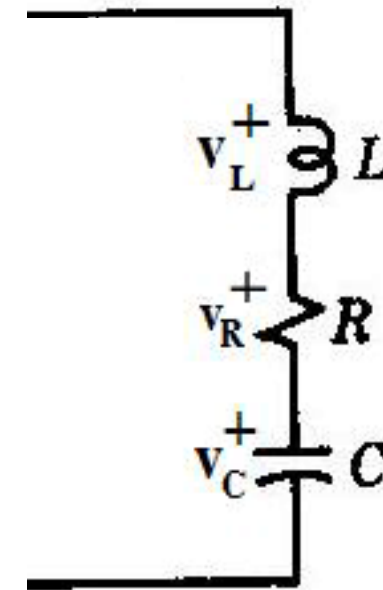
$$\begin{aligned} Z(s) &= R_1 + \frac{R(1/sC)}{R + (1/sC)} \\ &= \frac{s(R_1RC) + (R_1 + R)}{sRC + 1} \end{aligned}$$



$$\begin{aligned} Z(s) &= sL + R + \frac{1}{sC} \\ &= \frac{s^2LC + sRC + 1}{sC} \end{aligned}$$

# General Impedance Function

- In all cases, the impedance can be expressed as a **rational function**

# General Impedance Function

- In all cases, the impedance can be expressed as a **rational function** i.e., a function which is a ratio of two polynomials

$$Z(s) = K \frac{s^m + \dots + b_2 s^2 + b_1 s + b_0}{s^n + \dots + a_2 s^2 + a_1 s + a_0}$$

# General Impedance Function

- In all cases, the impedance can be expressed as a **rational function** i.e., a function which is a ratio of two polynomials

$$Z(s) = K \frac{s^m + \dots + b_2 s^2 + b_1 s + b_0}{s^n + \dots + a_2 s^2 + a_1 s + a_0}$$

- If the numerator and denominators are factored then

$$Z(s) = K \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

# General Impulse Function

- In all cases, the impedance can be expressed as a **rational function** i.e., a function which is a ratio of two polynomials

$$Z(s) = K \frac{s^m + \dots + b_2 s^2 + b_1 s + b_0}{s^n + \dots + a_2 s^2 + a_1 s + a_0}$$

- If the numerator and denominators are factored then

$$Z(s) = K \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

- Here, the  $z_i$ 's are called zeros as  $Z(z_i) = 0$ ,
- The  $p_i$ 's are called poles.

# General Impulse Function


- The impulse function can also be used in conjunction with voltage division/current division rules.
- Obtain relationship between any voltages/currents in the circuit.

# General Impulse Function

- The impulse function can also be used in conjunction with voltage division/current division rules.
- Obtain relationship between any voltages/currents in the circuit.

Eg : The R-L-C circuit is connected across

$$V_S(t) = V_0 e^{st}$$

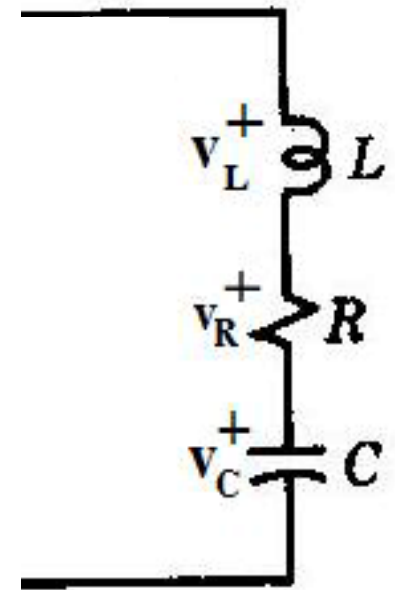


# General Impulse Function

- The impulse function can also be used in conjunction with voltage division/current division rules.
- Obtain relationship between any voltages/currents in the circuit.

Eg : The R-L-C circuit is connected across
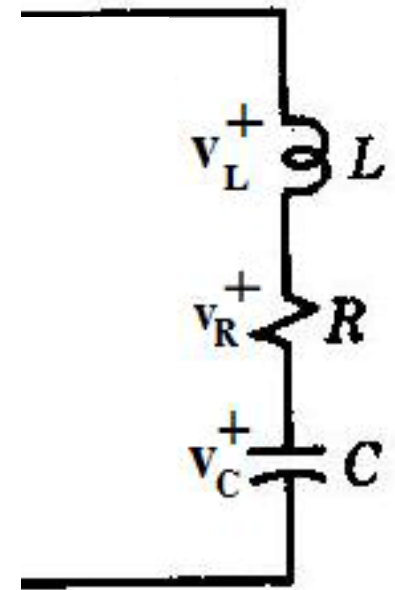
$$V_S(t) = V_0 e^{st}$$
$$i(t) = \frac{V_S(t)}{Z(s)} = V_S(t) \frac{Cs}{Ls^2 + Rs + 1}$$






# General Impulse Function

- The impulse function can also be used in conjunction with voltage division/current division rules.
- Obtain relationship between any voltages/currents in the circuit.

Eg : The R-L-C circuit is connected across
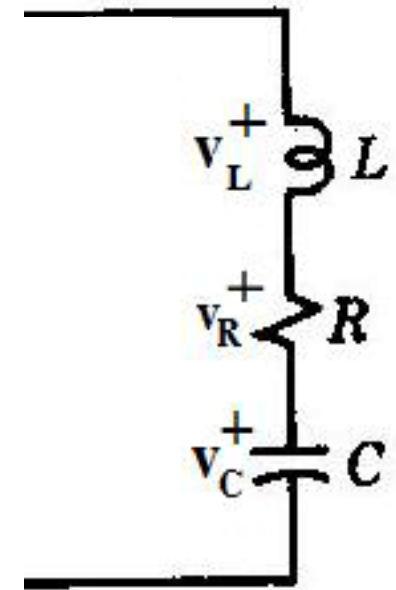
$$\begin{aligned}V_S(t) &= V_0 e^{st} \\ i(t) &= \frac{V_S(t)}{Z(s)} = V_S(t) \frac{Cs}{Ls^2 + Rs + 1} \\ v_c(t) &= \frac{1}{C} \int i dt = \frac{1}{Cs} i(t) \\ v_c(t) &= \frac{1}{Ls^2 + Rs + 1} V_S(t)\end{aligned}$$



# Zero/Infinite Impedance

- It is known that
  - Inductor gives zero impedance to DC
  - Capacitor gives infinite impedance to DC

# Zero/Infinite Impedance

- It is known that
  - Inductor gives zero impedance to DC
  - Capacitor gives infinite impedance to DC
- Is it possible that a circuit (with R-L-C elements) has zero impedance to time varying input (not DC)?
  - The circuit gives no “opposition” despite the presence of a resistor!

# Zero/Infinite Impedance

- It is known that
  - Inductor gives zero impedance to DC
  - Capacitor gives infinite impedance to DC
- Is it possible that a circuit (with R-L-C elements) has zero impedance to time varying input (not DC)?
  - The circuit gives no “opposition” despite the presence of a resistor!
  - The circuit ‘responds’ without an input.. Natural response.

# Zero/Infinite Impedance

- It is known that
  - Inductor gives zero impedance to DC
  - Capacitor gives infinite impedance to DC
- Is it possible that a circuit (with R-L-C elements) has zero impedance to time varying input (not DC)?
  - The circuit gives no “opposition” despite the presence of a resistor!
  - The circuit ‘responds’ without an input.. Natural response.

$$Z(s) = K \frac{(s-z_1)(s-z_2)\cdots(s-z_m)}{(s-p_1)(s-p_2)\cdots(s-p_n)}$$