

ELL101: INTRODUCTION TO ELECTRICAL ENG.



Network Theorems (Thevenin's and Norton's Theorems)

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik, Harshan Jagadeesh

Department of Electrical Engineering, IITD

1

1

Introduction

- ❑ One of the main uses of Thevenin's and Norton's theorems is the replacement of a large part of a circuit, often a complicated and uninteresting part, with a very simple equivalent
- ❑ The new, simpler circuit enables us to make rapid calculations of the voltage, current, and power which the original circuit is able to deliver to a load

2

2

Introduction(contd.)

- ❑ It also helps us to choose the best value of this load resistance
- ❑ In a transistor power amplifier, for example, the Thévenin or Norton equivalent enables us to determine the maximum power that can be taken from the amplifier and delivered to the speakers

3

3

Thevenin's Theorem

- ❑ Thevenin's theorem tells us that it is possible to replace everything except the load resistor(R_L) with an independent voltage source(V_{TH}) in series with a resistor(R_{TH})

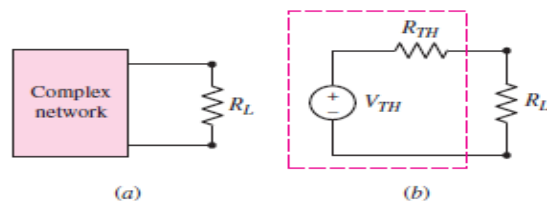


Fig. 1 (a) A complex network including a load resistor R_L . (b) A Thevenin equivalent network connected to the load resistor R_L .

4

4

Procedure To Determine Thevenin's Equivalent Circuit


- ❑ Make the Load resistor R_L as open circuit
- ❑ Now, define a voltage V_{TH} or V_{oc} (Thevenin's voltage) across the open circuited terminals of R_L and determine V_{TH} or V_{oc}
- ❑ V_{oc} is the voltage that could be measured by a voltmeter at the output
- ❑ To determine R_{TH} (Thevenin's resistance or the equivalent resistance seen from the open circuited terminals of R_L), we proceed as follows:
- ❑ Deactivate all the independent sources, i.e., short circuit the voltage source and open circuit the current source

5

5

Contd.

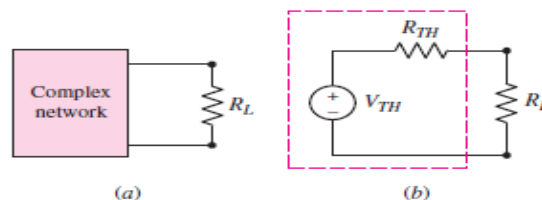- ❑ Measure the resistance at across the open circuited terminals of R_L
- ❑ Finally, we can obtain the Thevenin's equivalent circuit as shown in Fig. 1(b)



6

6

Problem 1(Independent source)

- Find V_X by first finding V_{TH} and R_{TH} to the left of A-B

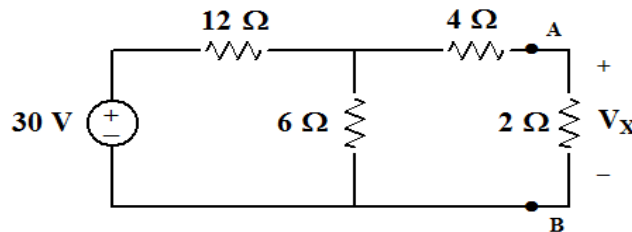



Fig. 2: Circuit for Problem 1

7

7

Solution

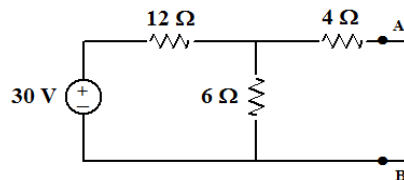- We first open circuit the terminals of A-B to obtain V_{TH} as shown below:



- Using voltage division rule, we get:


$$V_{AB} = V_{TH} = \frac{(30)(6)}{6+12} = 10V$$

8

8

Solution(contd.)

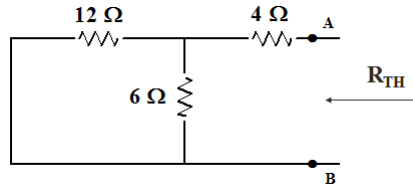- To get R_{TH} , we deactivate all the independent sources as described in the procedure as follows:




$$R_{TH} = 12 || 6 + 4 = 8\ \Omega$$

9

9

Solution(contd.)

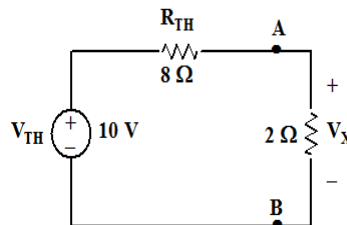- Now, the Thevenin's equivalent circuit can be obtained as:



Using voltage division rule, we get:

$$\therefore V_X = \frac{(10)(2)}{8 + 2} = 2\text{ V}$$

10

10

Problem 2(Scenario of Dependent Source)

- ❑ Determine the Thevenin equivalent of the circuit shown below:

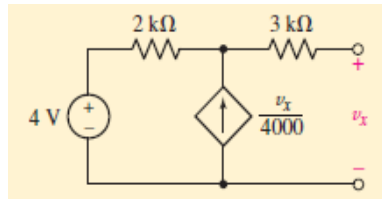


Fig.3: A given network whose Thevenin equivalent is desired

11

11

Solution


- ❑ To find V_{TH} , we note that $v_x = V_{TH}$ and that the dependent source current must pass through the $2k\Omega$ resistor, since no current can flow through the $3k\Omega$ resistor.

- ❑ Using KVL around the outer loop:

$$4 + 2 \times 10^3 \left(\frac{v_x}{4000} \right) = v_x$$

and

$$V_{TH} = v_x = 8V$$


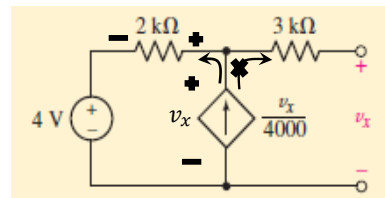


12

12

Solution(contd.)

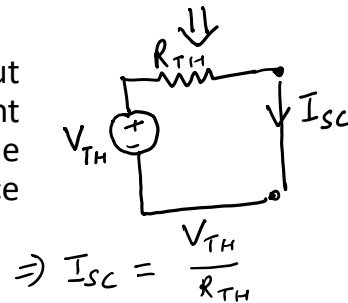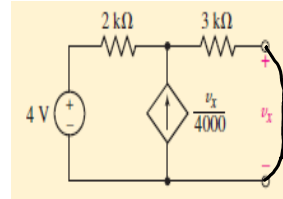- ❑ The dependent source prevents us from determining directly R_{TH}
- ❑ Therefore, we short circuit the output terminals of the given circuit and determine the short-circuited current (I_{SC})
- ❑ Upon short-circuiting the output terminals in figure, it is apparent that $v_x = 0$ and therefore the dependent current source becomes inactive




13

13

Solution(contd.)

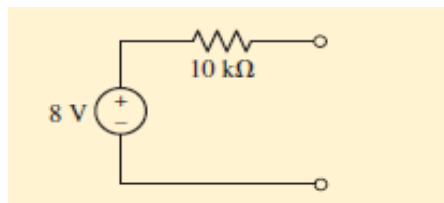- ❑ Hence, $I_{SC} = \frac{4}{5 \times 10^3} = 0.8 \text{mA}$
- ❑ Thus, $R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{8}{0.8 \times 10^{-3}} = 10 \text{k}\Omega$
- ❑ Therefore, the thevenin's equivalent circuit is as shown below:



14

14

Norton's Theorem

- ❑ Using Norton's theorem, we obtain an equivalent composed of an independent current source (I_N) in parallel with a resistor (R_N)

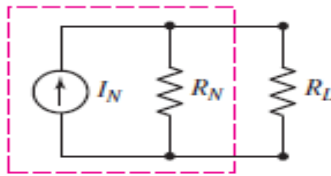


Fig.4: A Norton equivalent network connected to the load resistor R_L

15

15

Procedure To Determine Norton's Equivalent Circuit

- ❑ Make the Load resistor R_L as short circuit
- ❑ Now, define a current I_N or I_{sc} (Norton's current) across the short-circuited terminals of R_L and determine I_N or I_{sc}
- ❑ The procedure for determining R_N (Norton's equivalent resistance) is same as that of R_{TH}
- ❑ Finally, we can obtain the Norton's equivalent circuit as shown in Fig. 4

16

16

Problem 3 (Independent source)

- Find the Norton's equivalent circuit for the network faced by the $1k\Omega$ load resistor

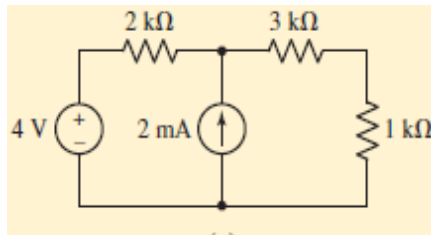


Fig. 5: Circuit for Problem 3

17

17


Solution

- We first define the node voltage (V_a) at the upper terminal of 2mA current source
- Now, we short circuit the $1k\Omega$ load resistor and determine the short-circuited current I_N or I_{sc} using nodal analysis as follows:

$$\frac{V_a - 4}{2k\Omega} - 2\text{mA} + \frac{V_a - 0}{3k\Omega} = 0$$

$$\Rightarrow V_a = 4.8\text{V}$$
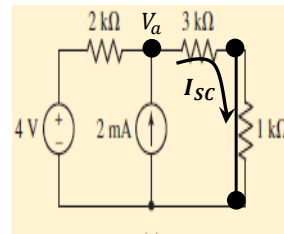
$$\therefore I_N = \frac{V_a}{3k} = 1.6\text{mA}$$





18

18

Solution(contd.)

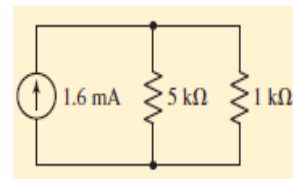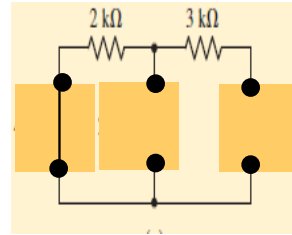- ❑ Now, to determine R_N , the $1\text{ k}\Omega$ load resistor is open circuited
- ❑ Moreover, we deactivate all the independent sources, i.e., voltage source is short-circuited and current source is open-circuited
- ❑ We get: $R_N = 2\text{ k}\Omega + 3\text{ k}\Omega = 5\text{ k}\Omega$ and the Norton's equivalent circuit is as shown below:



19

19

Problem 4(Scenario of Dependent Source)

- ❑ For the circuit shown below, find the Norton's equivalent circuit to the left of terminals A-B

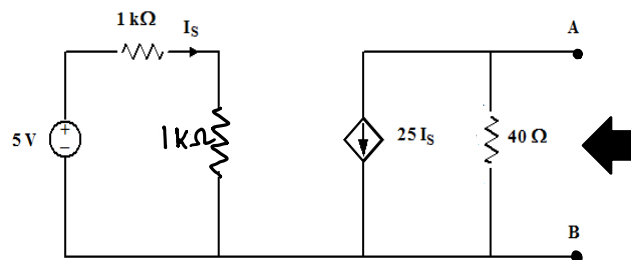


Fig. 6 Circuit for Problem 4

20

20

Solution


- In case of a dependent source, R_N is obtained as:

$$R_N = \frac{V_{OC}}{I_{SC}} = \frac{V_{AB}}{I_{SC}}$$

- Where $V_{OC} = V_{AB}$ is the open-circuited voltage across the load resistor

- We first find V_{AB} :
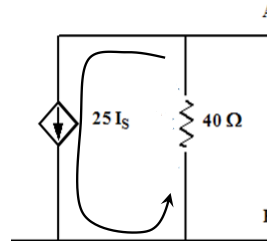
$$\begin{aligned} V_{AB} &= (-25I_S)(40) \\ &= -1000I_S \end{aligned}$$




21

21

Solution(contd.)

- To find I_{SC} , the output terminals are short-circuited and due to this the entire current of $25I_S$ flows through the short-circuited arm

- Therefore, $I_{SC} = -25 I_S$

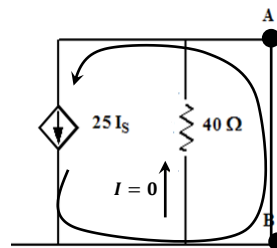

- Hence, $R_N = \frac{V_{AB}}{I_{SC}} = \frac{-1000I_S}{-25 I_S} = 40\Omega$

22

22

Solution(contd.)


□ Note that we have obtained V_{AB} in terms of I_S , i.e., $V_{AB} = -1000I_S$

□ Now, I_S can be obtained using mesh analysis as follows:

$$-5 + 1000I_S + 1000I_S = 0$$

$$\Rightarrow I_S = 2.5\text{mA}$$

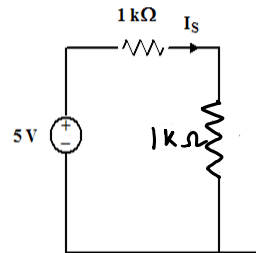□ Thus $I_{SC} = -25I_S = -62.5\text{mA}$




23

23

Solution(contd.)

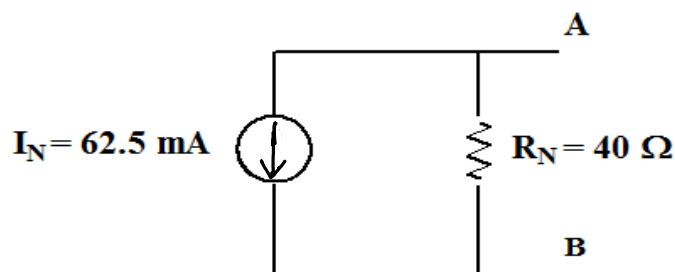□ The Norton's equivalent circuit is as shown below:



24

24

Problem 5 (Another Scenario of Dependent Source)

□ For the circuit shown below, find the Norton's equivalent circuit

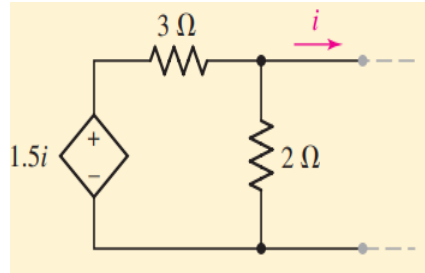



Fig. 7 Circuit for Problem 5

25

25

Solution

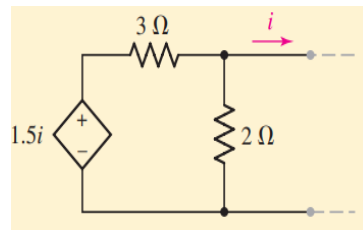- Dependent voltage source depends upon the current i
- $i=0$ for short circuit or open circuit
- So the dependent voltage source of $1.5i$ value is inactive
- It is not possible to determine the value of I_{SC} and V_{OC}




26

26


Solution(contd.)

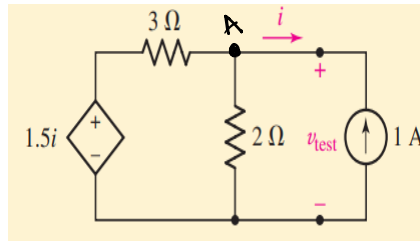- Let us apply a 1A current source at the O/P nodes
- Then $R_N = \frac{v_{test}}{1}$
- As $i = -1$ A
- Apply nodal analysis at A



$$\frac{v_{test} - 1.5(-1)}{3} + \frac{v_{test}}{2} = 1$$

- $v_{test} = 0.6$ V
- $R_N = 0.6$ ohm

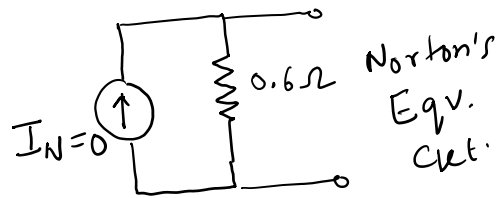

27

27