



ELL100: INTRODUCTION TO ELECTRICAL ENGG.

Forced Response and Phasor Analysis

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik,
Harshan Jagadeesh

Department of Electrical Engineering, IITD

Forced Response

- Natural response was response due to **initial state** without external input.
- Complementary to natural response, forced response is **solely** due to external input.

Forced Response


- Natural response was response due to **initial state** without external input.
- Complementary to natural response, forced response is **solely** due to external input.
- Types of input worth exploring.
 - Decaying exponential signal ($s = \text{negative real}$)
 - DC ($s=0$)
 - AC ($s=\text{imaginary}$)

Impedance (Recap)

- For Resistor $Z_R = \frac{v}{i} = \frac{iR}{i} = R \ \Omega$
- For Inductor $Z_L = \frac{v}{i} = \frac{L \frac{di}{dt}}{i} = \frac{Lsi}{i} = sL \ \Omega$
- For Capacitor $Z_C = \frac{v}{i} = \frac{v}{C \frac{dv}{dt}} = \frac{v}{Csv} = \frac{1}{sC} \ \Omega$


Important Pointers

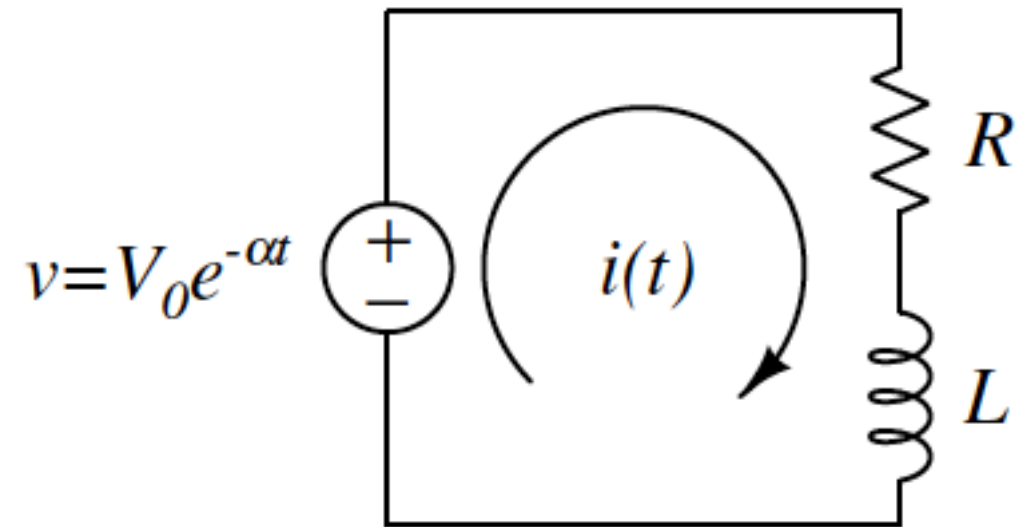- The differential equation reads $Ri + L\frac{di}{dt} = V_0e^{-\alpha t}$
- Equation is no longer homogenous




Important Pointers

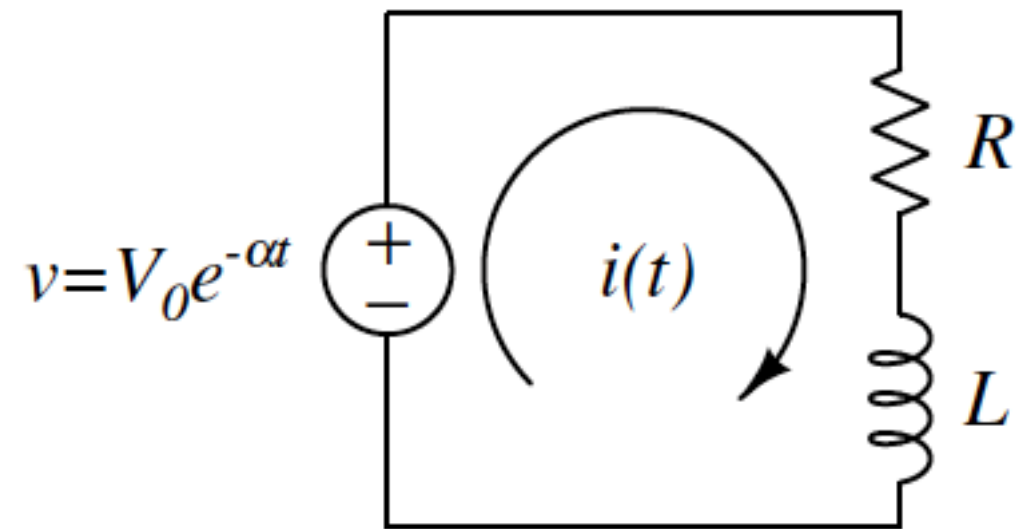- The differential equation reads $Ri + L\frac{di}{dt} = V_0e^{-\alpha t}$
- Equation is no longer homogenous
- For forced response calculation initial conditions are **assumed** as zero.




Important Pointers

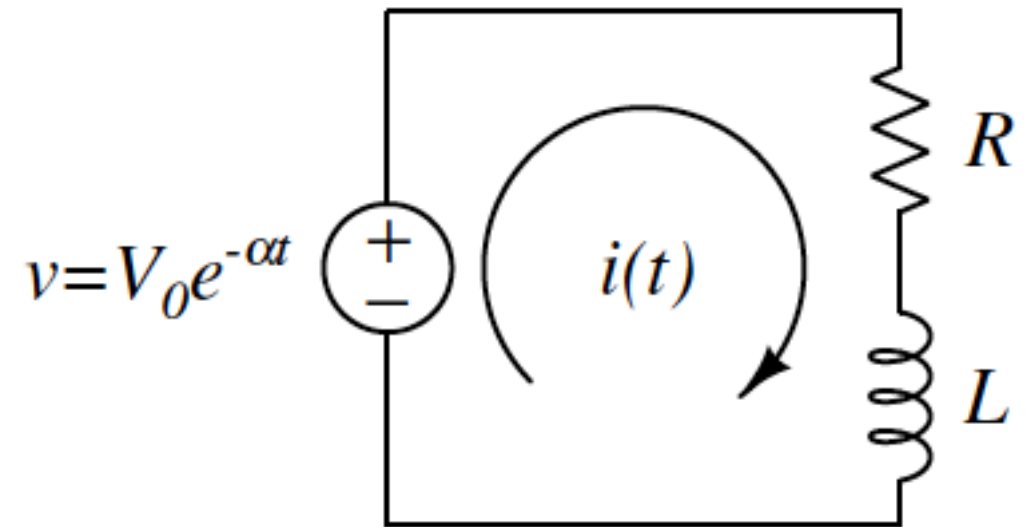- The differential equation reads $Ri + L\frac{di}{dt} = V_0e^{-\alpha t}$
- Equation is no longer homogenous
- For forced response calculation initial conditions are **assumed** as zero.
- The forced response would be composed only of components present in the input ($e^{-\alpha t}$ here)



Forced Response - Exponentials

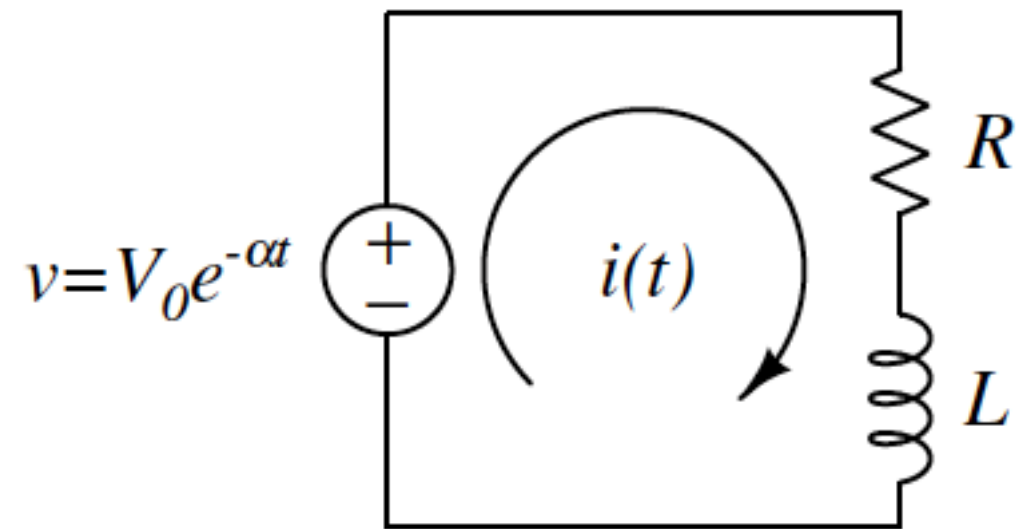- Using the template solution $i(t) = Ae^{-\alpha t}$




$$Ri + L \frac{di}{dt} = V_0 e^{-\alpha t}$$

Forced Response - Exponentials

- Using the template solution $i(t) = Ae^{-\alpha t}$
- We have
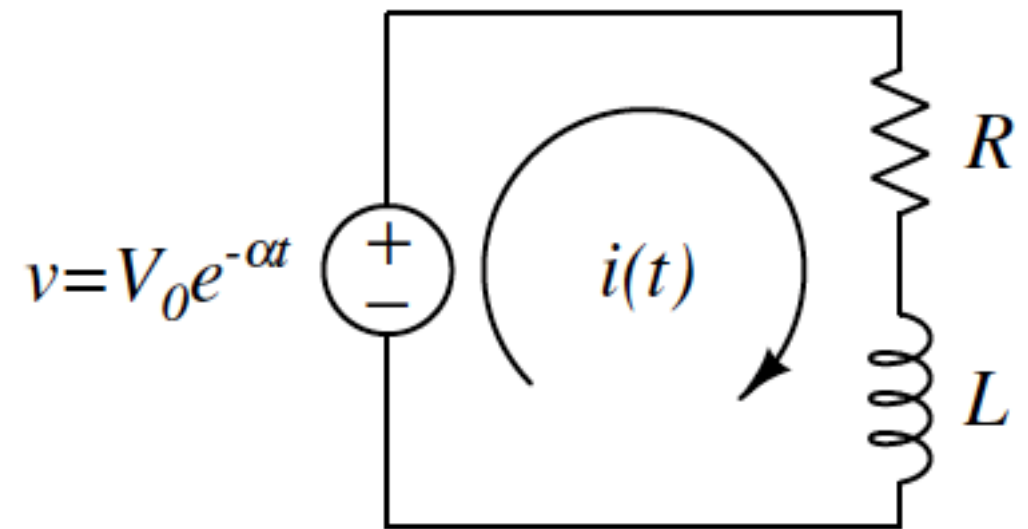
$$-L\alpha Ae^{-\alpha t} + RAe^{-\alpha t} = V_0e^{-\alpha t}$$
$$A = \frac{V_0}{R - \alpha L}$$



$$Ri + L \frac{di}{dt} = V_0 e^{-\alpha t}$$

Forced Response - Exponentials


- Using the template solution $i(t) = Ae^{-\alpha t}$
- We have

$$-L\alpha Ae^{-\alpha t} + RAe^{-\alpha t} = V_0e^{-\alpha t}$$
$$A = \frac{V_0}{R - \alpha L}$$

$$i(t) = \frac{V_0}{R - \alpha L} e^{-\alpha t}$$

$$v_R(t) = \frac{RV_0}{R - \alpha L} e^{-\alpha t}$$

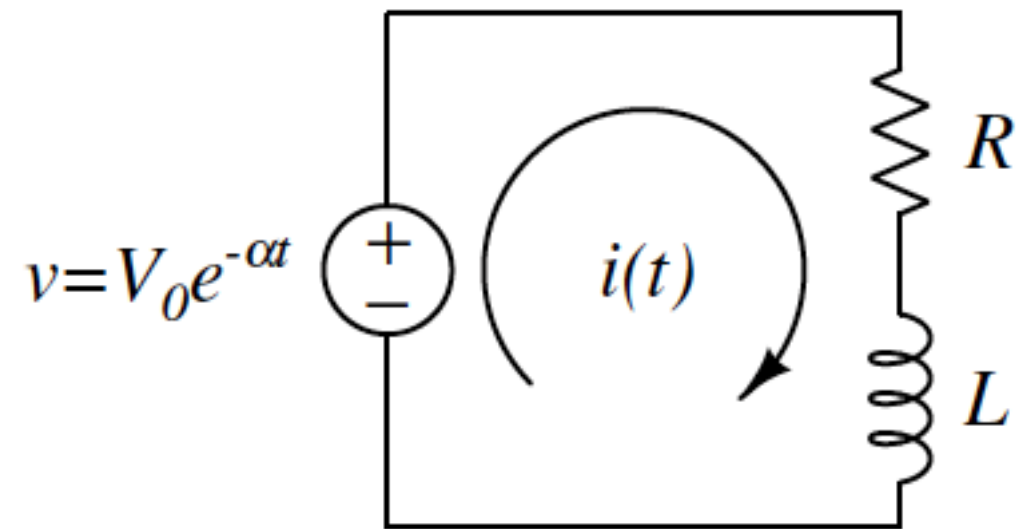
$$v_L(t) = -\frac{\alpha LV_0}{R - \alpha L} e^{-\alpha t}$$



$$Ri + L \frac{di}{dt} = V_0 e^{-\alpha t}$$

Example 2


- An R-L-C circuit is powered by a source $V_s(t) = 5e^{-2t}$
With $R = 4 \Omega$, $L = 1 \text{ H}$, $C = 1/3 \text{ F}$
- None of the components are energized till $t=0$.

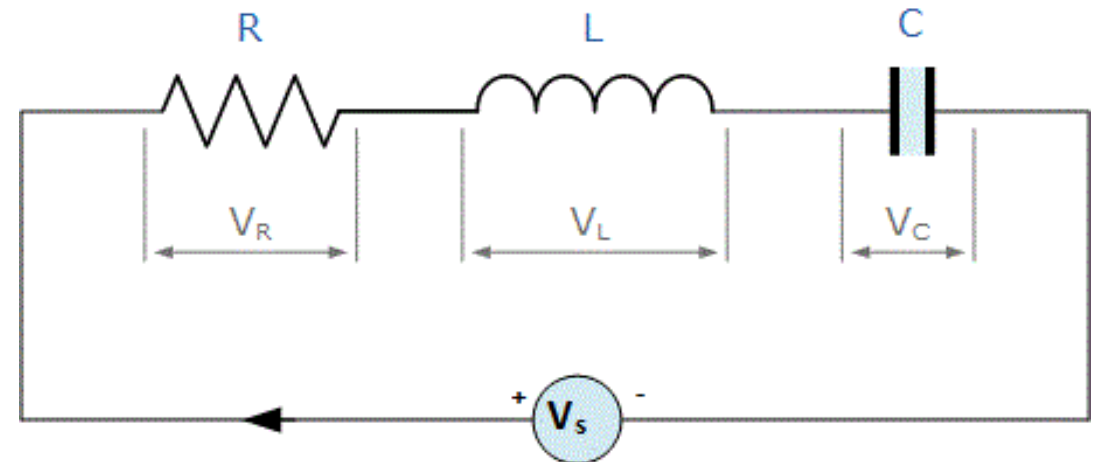

Example 2

- An R-L-C circuit is powered by a source $V_s(t) = 5e^{-2t}$
With $R = 4 \Omega$, $L = 1 \text{ H}$, $C = 1/3 \text{ F}$
- None of the components are energized till $t=0$.
- What is (i) the current in the circuit, (ii) voltages across the three components?
- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C}$$
$$\alpha = -2$$

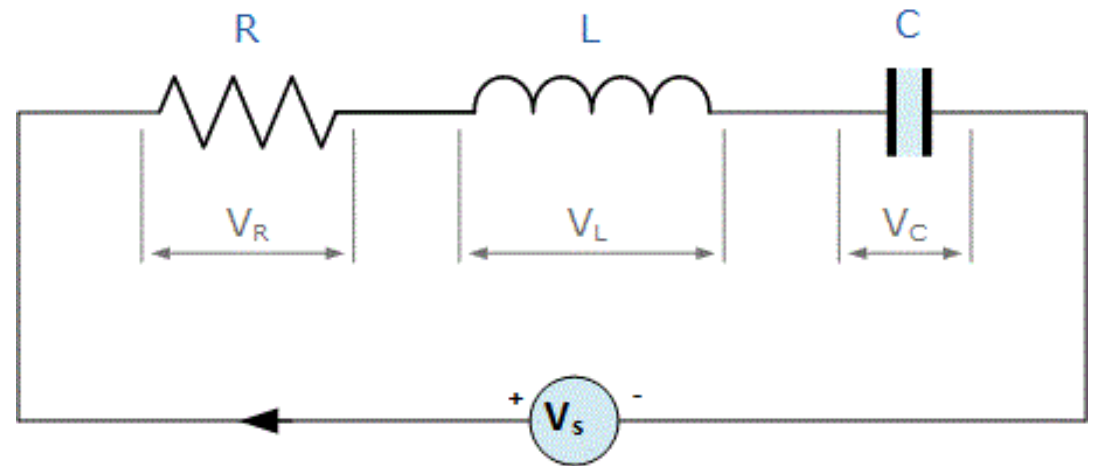

Example 2


- An R-L-C circuit is powered by a source $V_s(t) = 5e^{-2t}$

With $R = 4 \Omega$, $L = 1 \text{ H}$, $C = 1/3 \text{ F}$

- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C} = \frac{\alpha^2 + 4\alpha + 3}{\alpha}$$

$$\alpha = -2$$

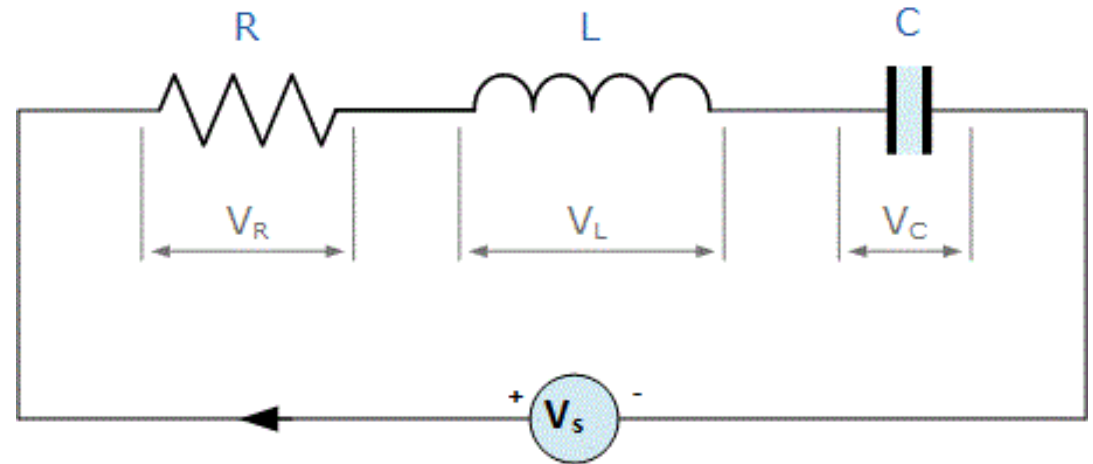

Example 2

- An R-L-C circuit is powered by a source $V_s(t) = 5e^{-2t}$

With $R = 4 \Omega$, $L = 1 \text{ H}$, $C = 1/3 \text{ F}$


- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C} = \frac{\alpha^2 + 4\alpha + 3}{\alpha}$$

$$\alpha = -2$$

$$Z(-2) = 0.5$$

$$i(t) = \frac{V}{Z} = \frac{5e^{-2t}}{0.5}$$

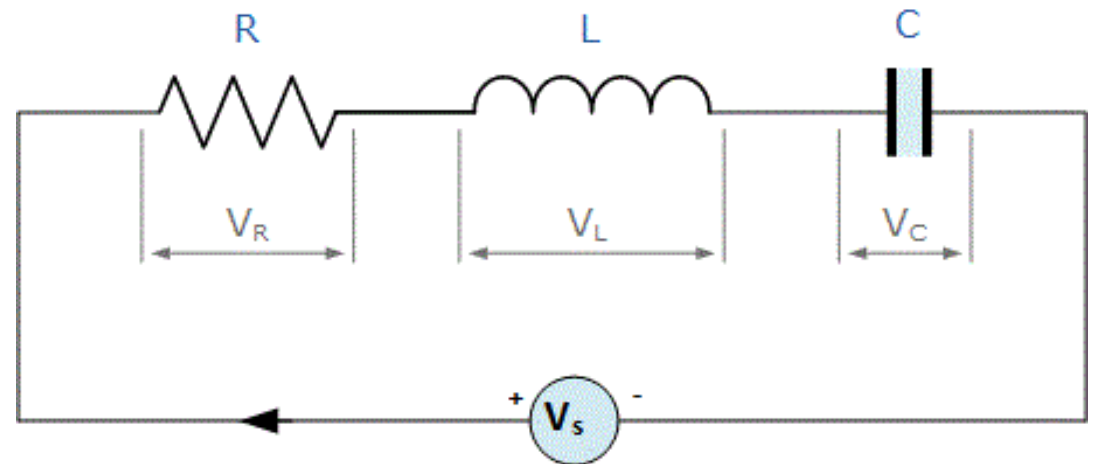

Example 2

- An R-L-C circuit is powered by a source $V_s(t) = 5e^{-2t}$

With $R = 4 \Omega$, $L = 1 \text{ H}$, $C = 1/3 \text{ F}$


- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C} = \frac{\alpha^2 + 4\alpha + 3}{\alpha}$$

$$\alpha = -1$$

$$Z(-2) = 0.5$$

$$i(t) = \frac{V}{Z} = \frac{5e^{-2t}}{0.5} = 10e^{-2t}$$

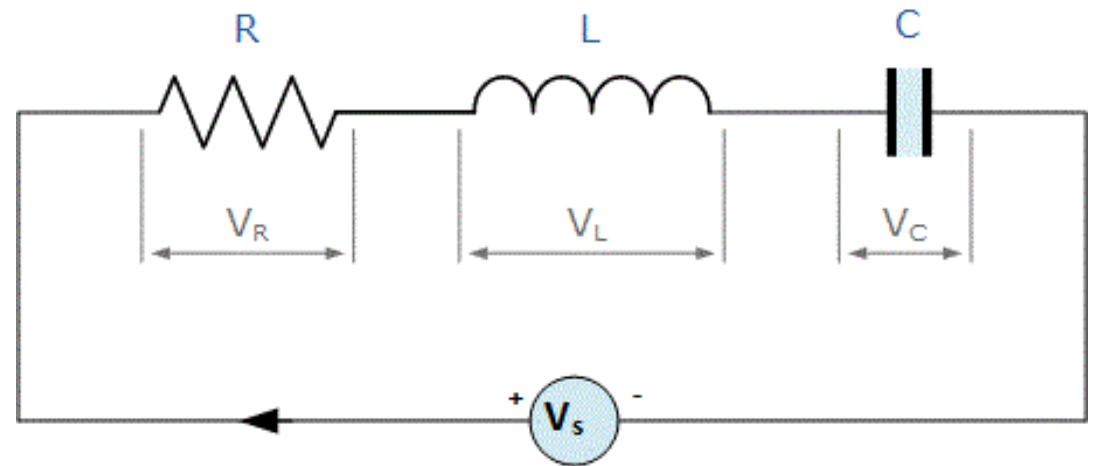

Example 2

- An R-L-C circuit is powered by a source $V_s(t) = 5e^{-2t}$

With $R = 4 \Omega$, $L = 1 \text{ H}$, $C = 1/3 \text{ F}$

- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C} = \frac{\alpha^2 + 4\alpha + 3}{\alpha}$$


$$\alpha = -1$$

$$i(t) = \frac{V}{Z} = \frac{5e^{-2t}}{0.5} = 10e^{-2t}$$

$$V_R = iR = 40e^{-2t}$$


$$V_L = \alpha Li = -20e^{-2t}$$
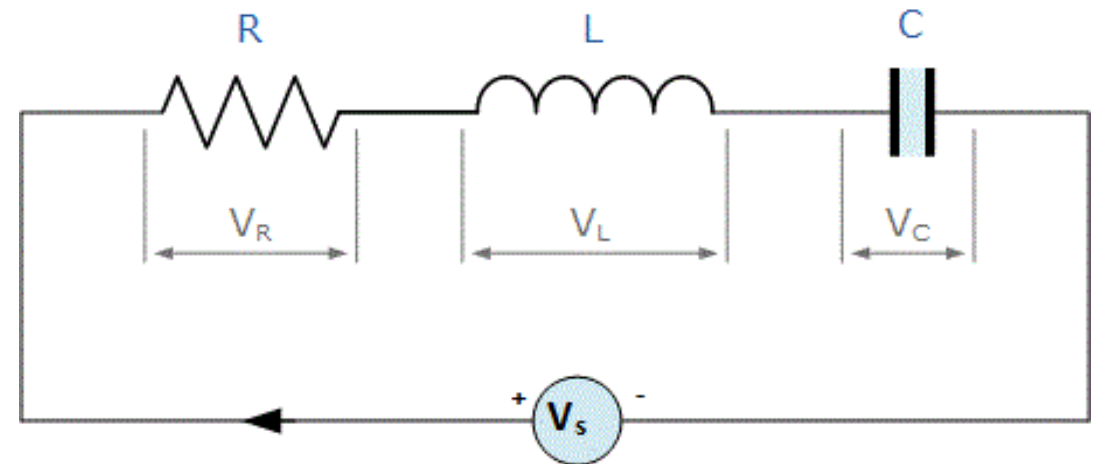
$$V_C = \frac{i}{\alpha C} = -15e^{-2t}$$



Phasors – Representation

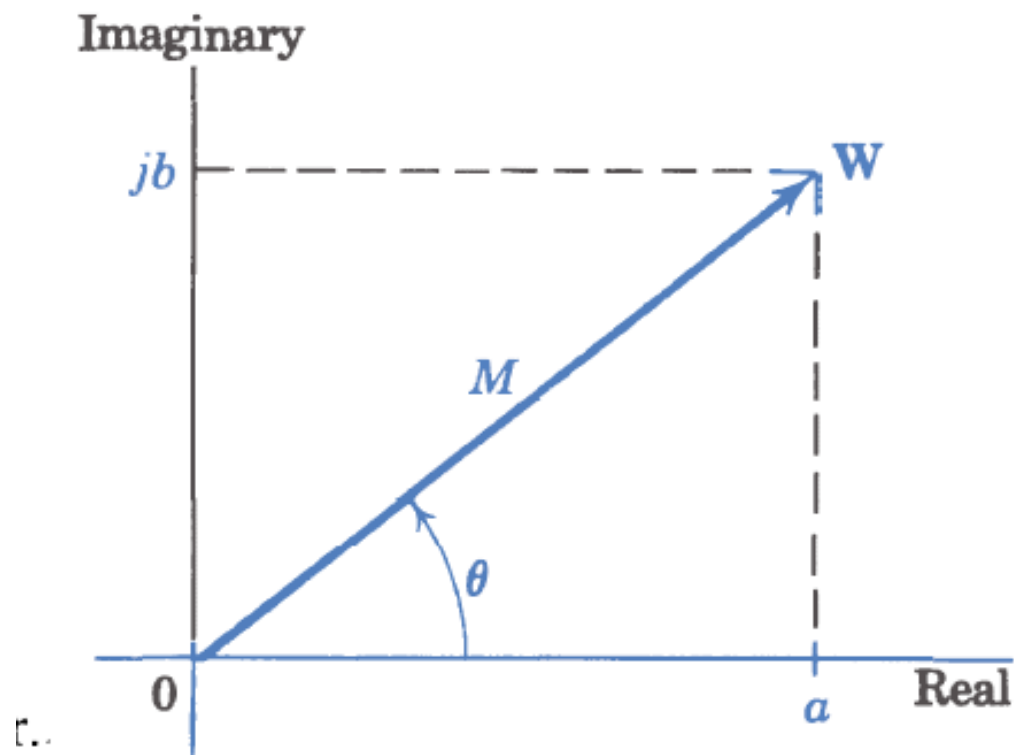- Sine/Cosine value can be visualized as imaginary/real part of a complex number (vector).




$$a = M \cos(\theta)$$

$$b = M \sin(\theta)$$

$$W = M e^{j\theta} = M \angle \theta$$

Phasors – Representation

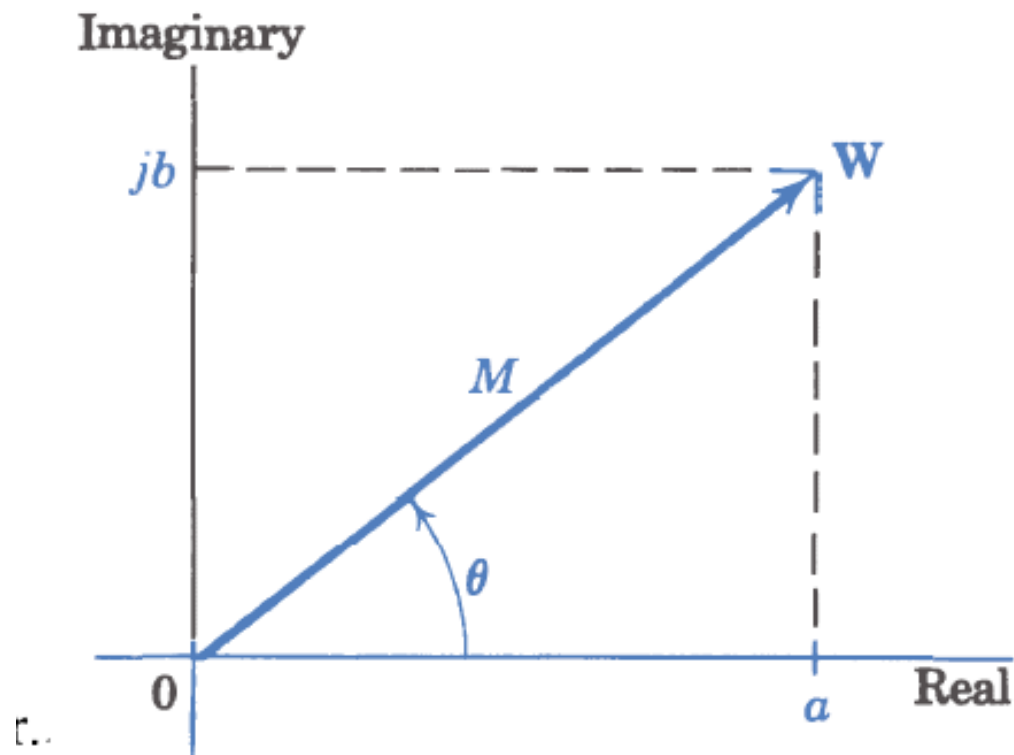- Sine/Cosine value can be visualized as imaginary/real part of a complex number (vector).



$$a = M \cos(\theta)$$

$$b = M \sin(\theta)$$


$$W = M e^{j\theta} = M \angle \theta$$

$$M = \sqrt{a^2 + b^2}$$

$$\theta = \arctan\left(\frac{b}{a}\right)$$

Phasors – Representation

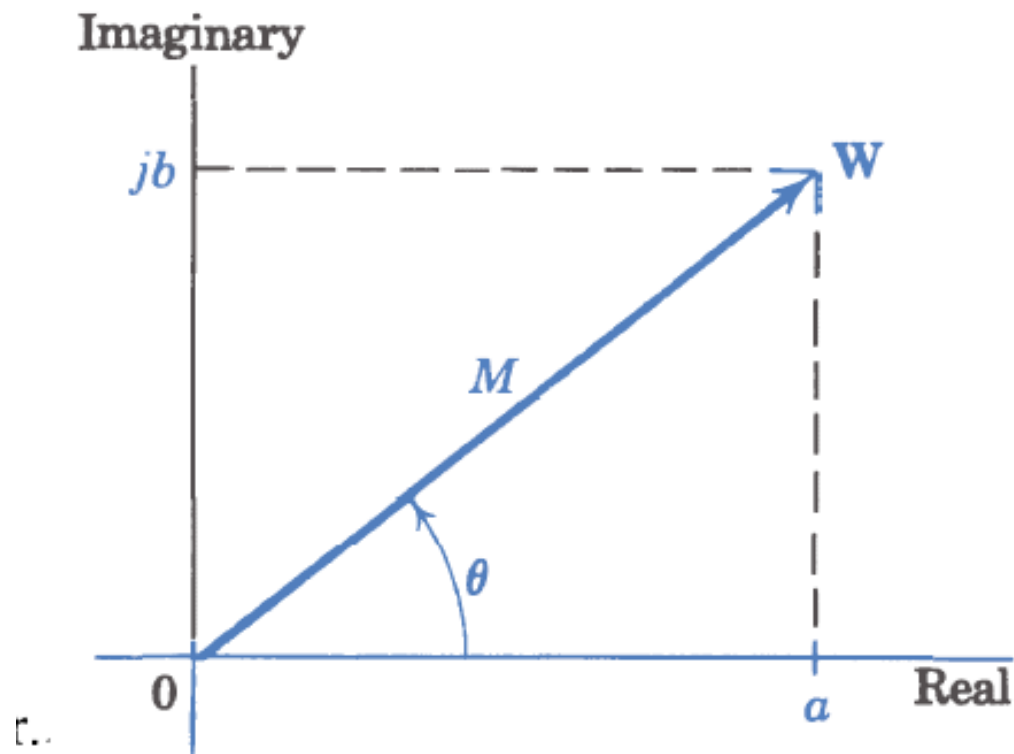- Sine/Cosine value can be visualized as imaginary/real part of a complex number (vector).



$$\begin{aligned} a &= M \cos(\theta) & M &= \sqrt{a^2 + b^2} \\ b &= M \sin(\theta) & \theta &= \arctan\left(\frac{b}{a}\right) \\ W &= M e^{j\theta} = M \angle \theta \end{aligned}$$


- This representation is called as a **phasor**
- A convention of either the real or imaginary part can be adopted.
- Here, we use real part.

Phasors – Computations

- Certain arithmetic operations involving phasors :
- Addition/Subtraction : $z_1 \pm z_2 = (x_1 \pm x_2) + j(y_1 \pm y_2)$
- Multiplication : $z_1 z_2 = r_1 r_2 \angle(\phi_1 + \phi_2)$
- Division : $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle(\phi_1 - \phi_2)$ Reciprocal : $\frac{1}{z_2} = \frac{1}{r_2} \angle(-\phi_2)$
- Square root : $\sqrt{z} = \sqrt{r} \angle(\phi/2)$


Phasor Diagrams

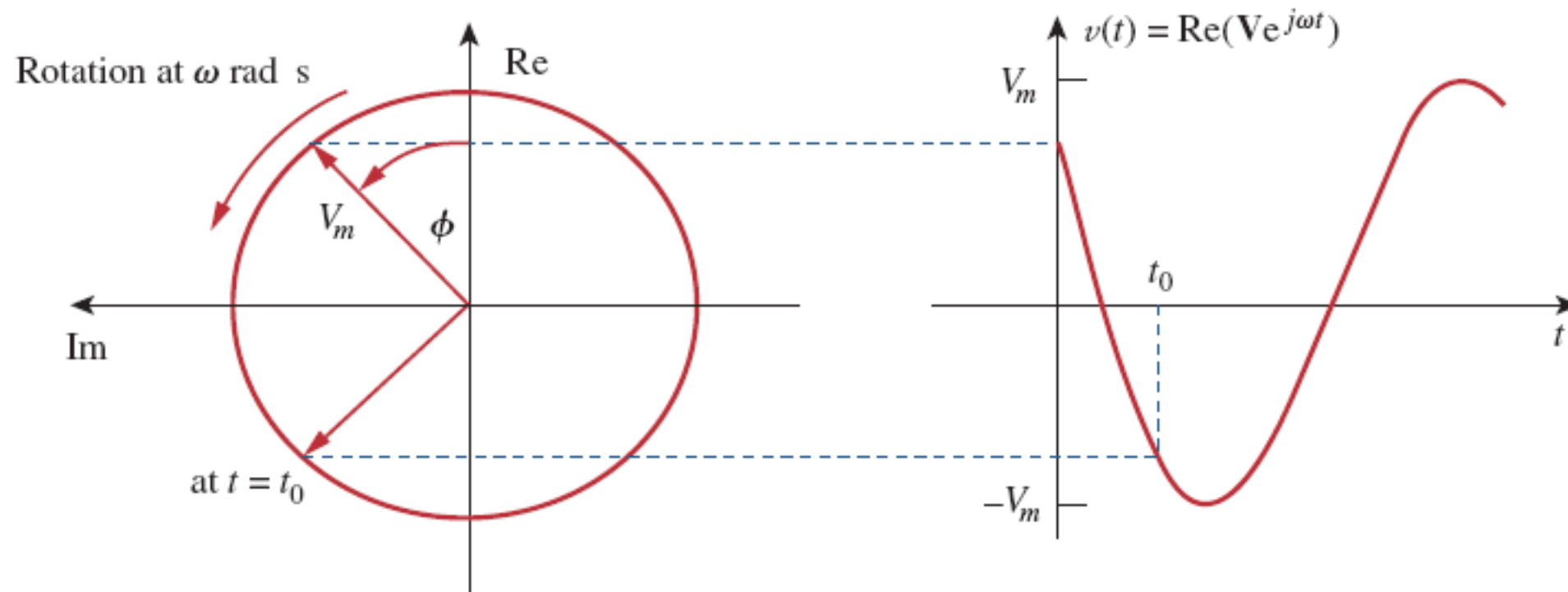- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference




Phasor Diagrams

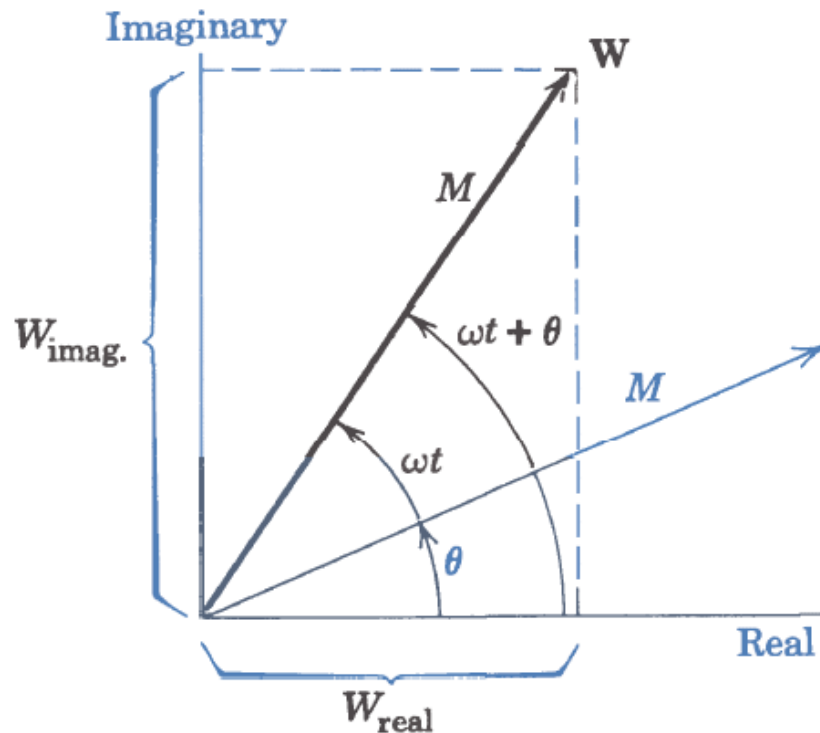- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference.



Phasor Diagrams

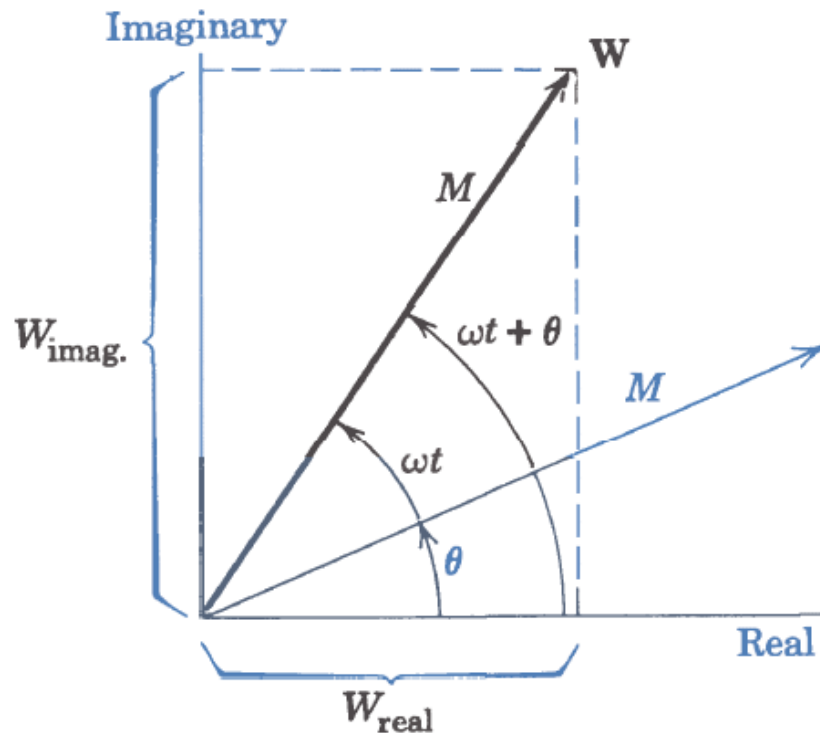
- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference.



So, all the phasors can be represented wrt a common reference in a phasor diagram

Phasor Diagrams

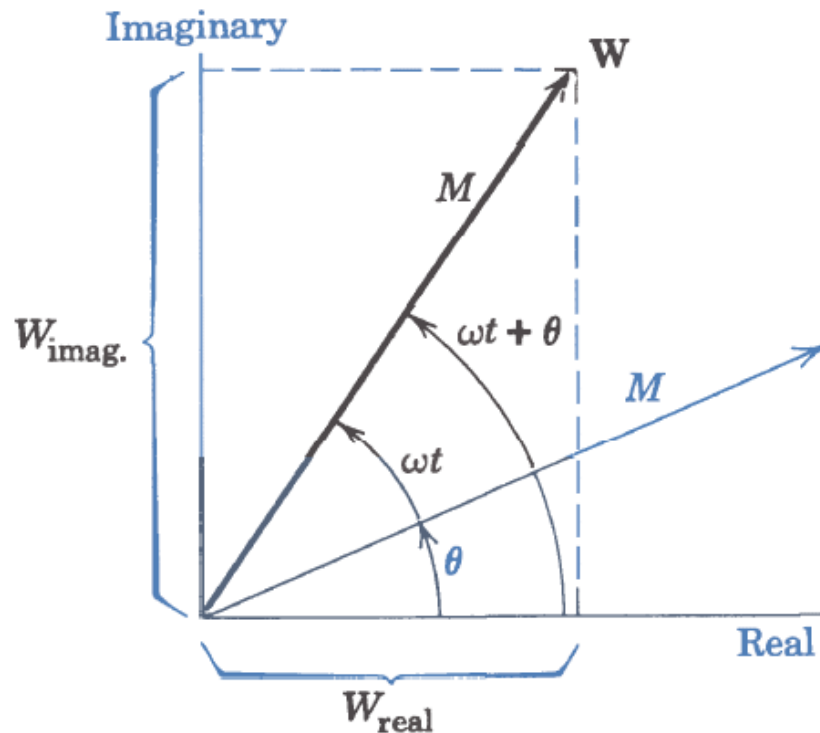- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference.




So, all the phasors can be represented wrt a common reference in a phasor diagram

$$v(t) = V_m \cos(\omega t + \theta)$$

Phasor Diagrams

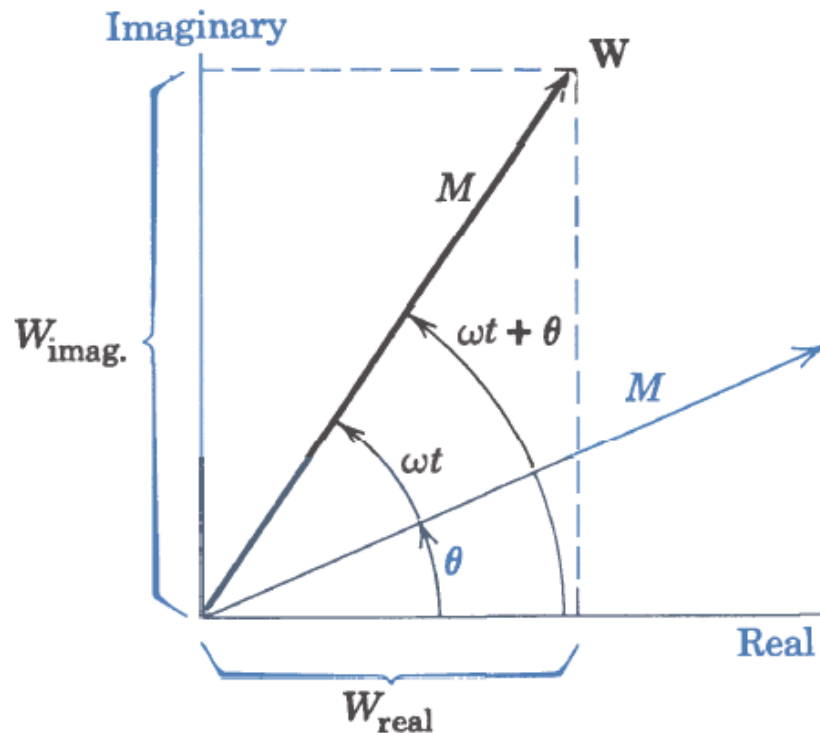- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference.




So, all the phasors can be represented wrt a common reference in a phasor diagram

$$\begin{aligned} v(t) &= V_m \cos(\omega t + \theta) \\ &= \sqrt{2}V \cos(\omega t + \theta) \quad \text{RMS Value} \end{aligned}$$

Phasor Diagrams

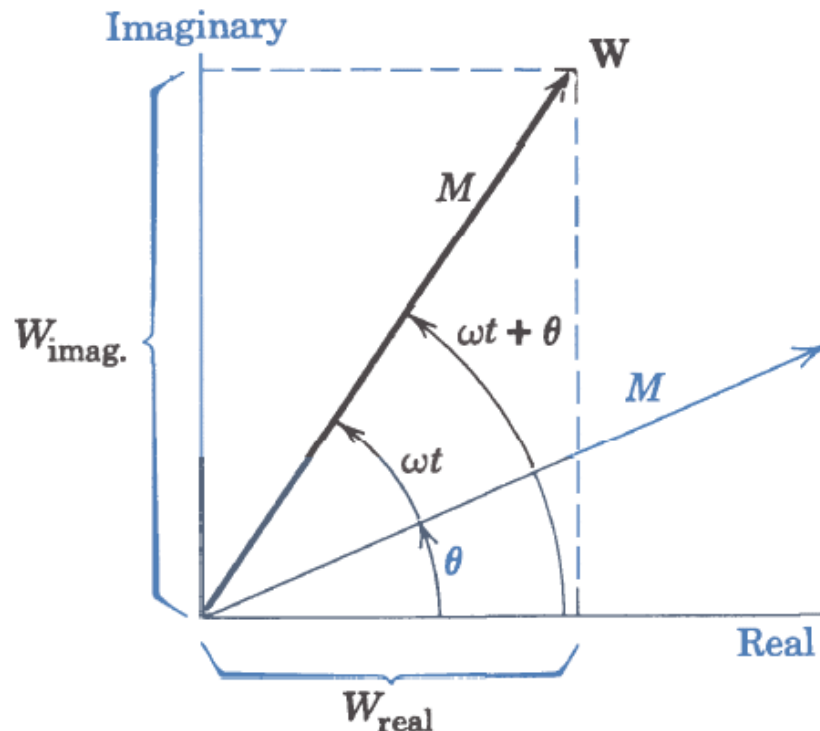- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference.




So, all the phasors can be represented wrt a common reference in a phasor diagram

$$\begin{aligned} v(t) &= V_m \cos(\omega t + \theta) \\ &= \sqrt{2}V \cos(\omega t + \theta) \end{aligned}$$

$$v(t) = \text{Re} \{ V_m e^{j(\omega t + \theta)} \} = \text{Re} \{ (V e^{j\theta}) (\sqrt{2} e^{j\omega t}) \}$$

Phasor Diagrams

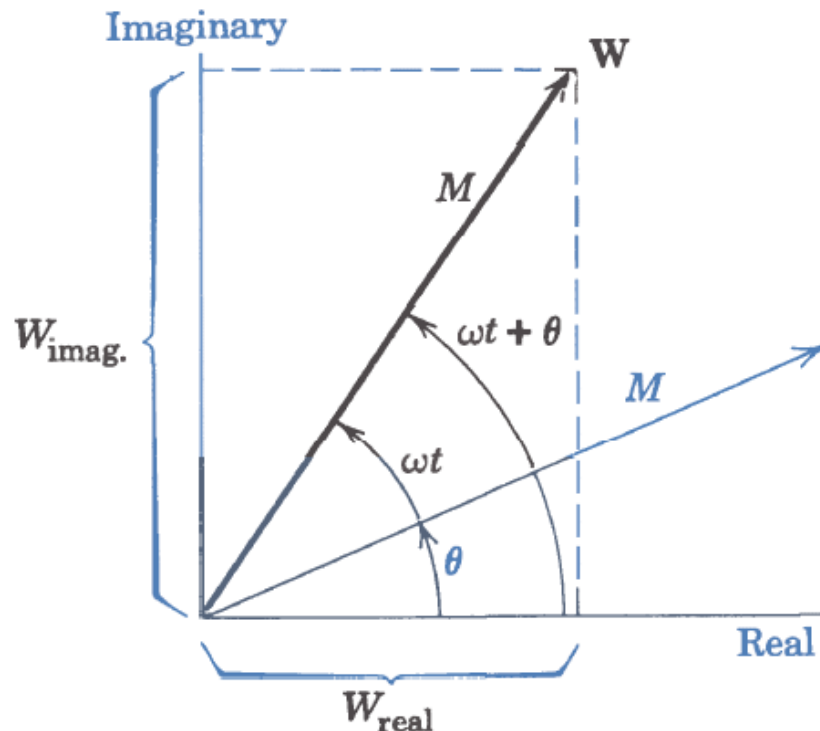- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference.




So, all the phasors can be represented wrt a common reference in a phasor diagram

$$\begin{aligned}v(t) &= V_m \cos(\omega t + \theta) \\ &= \sqrt{2}V \cos(\omega t + \theta)\end{aligned}$$

$$\begin{aligned}v(t) &= \text{Re} \{ V_m e^{j(\omega t + \theta)} \} = \text{Re} \{ (V e^{j\theta}) (\sqrt{2} e^{j\omega t}) \} \\ \mathbf{V} &= V e^{j\theta} = V \angle \theta\end{aligned}$$

Phasor Diagrams

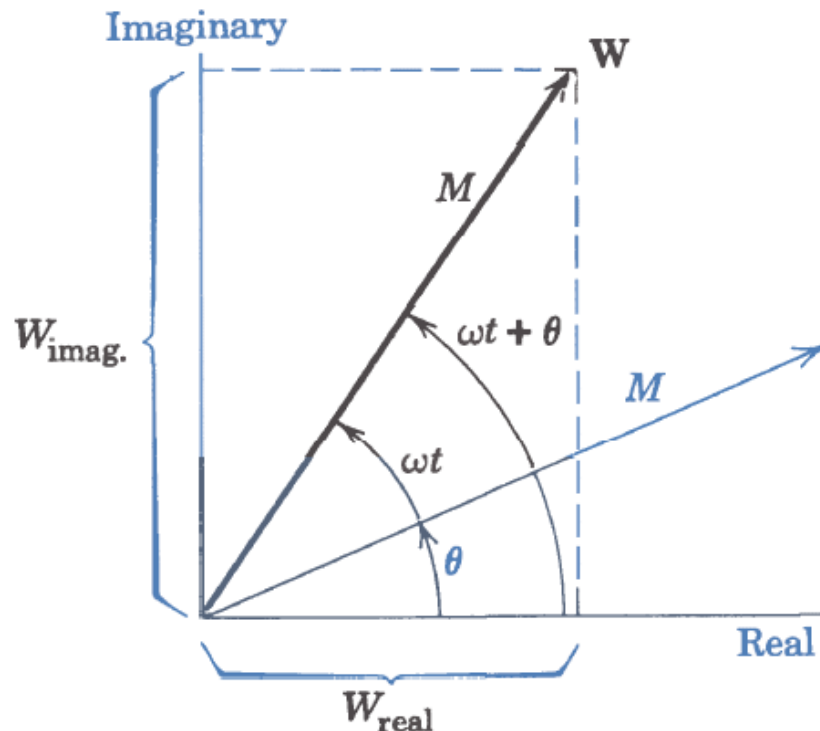- When a linear circuit is excited by a sinusoidal source of frequency ω (a rotating phasor)
- Voltages/currents in the circuit are also sinusoids of frequency ω , but with some phase difference.



So, all the phasors can be represented wrt a common reference in a phasor diagram


$$\begin{aligned}v(t) &= V_m \cos(\omega t + \theta) \\ &= \sqrt{2}V \cos(\omega t + \theta)\end{aligned}$$

$$\begin{aligned}v(t) &= \text{Re} \{ V_m e^{j(\omega t + \theta)} \} = \text{Re} \{ (V e^{j\theta}) (\sqrt{2} e^{j\omega t}) \} \\ \mathbf{V} &= V e^{j\theta} = V \angle \theta\end{aligned}$$

All essential information of magnitude and phase difference is retained. The common 'rotation' is ignored.

Phasor Diagram Example

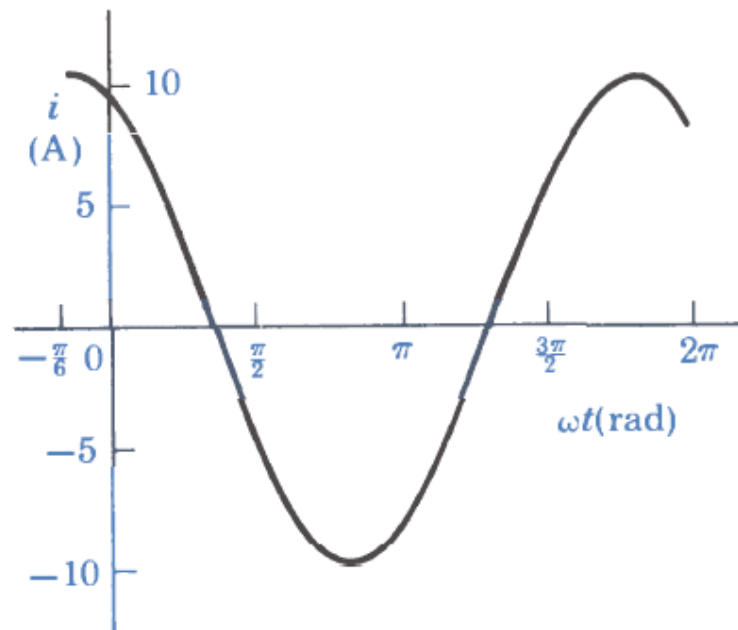
Write the eq. of the current shown in fig. as a function of time and represent the current by a phasor.



Phasor Diagram Example


Write the eq. of the current shown in fig. as a function of time and represent the current by a phasor.

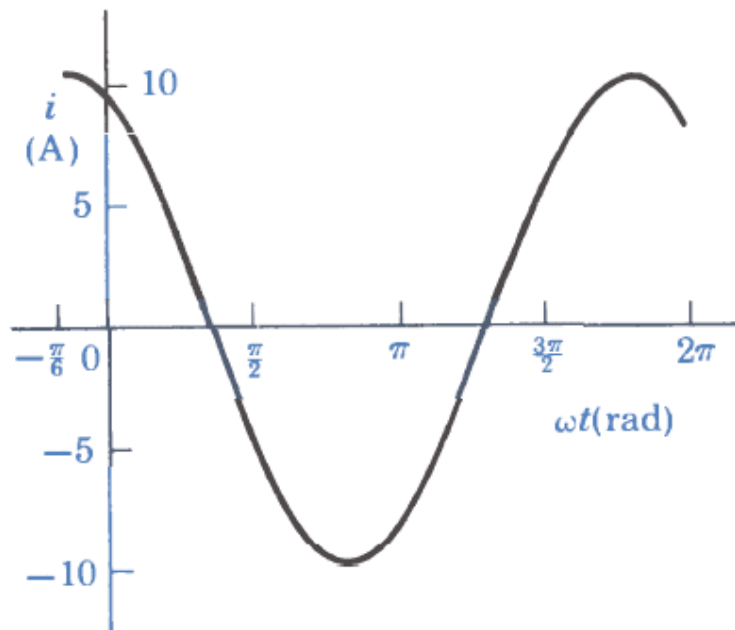The current reaches a positive maximum of 10 A at $\pi/6$ rad or 30° before $\omega t = 0$; therefore ,
 $i = 10 \cos(\omega t + \pi/6) \text{ A}$



Phasor Diagram Example

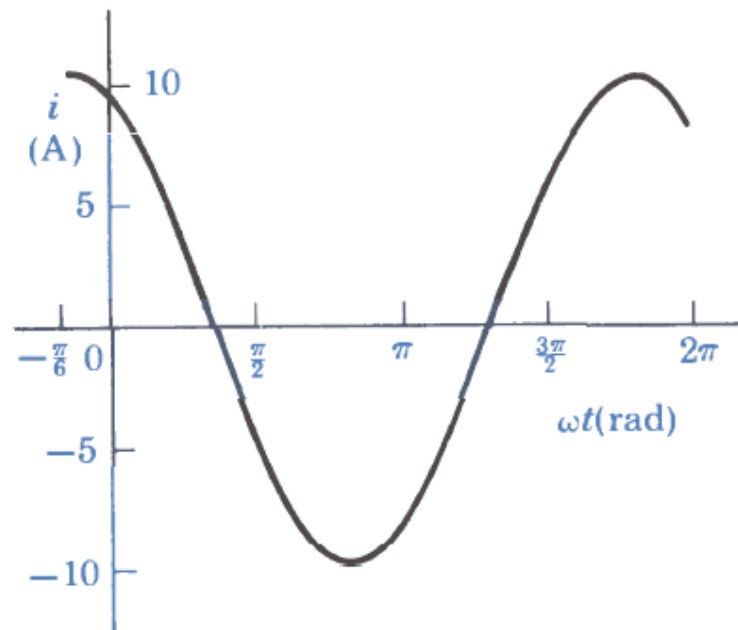Write the eq. of the current shown in fig. as a function of time and represent the current by a phasor.




The current reaches a positive maximum of 10 A at $\pi/6$ rad or 30° before $\omega t = 0$; therefore ,
 $i = 10 \cos(\omega t + \pi/6) \text{ A}$

or

$$\begin{aligned} i(t) &= \text{Re}\{10 e^{j(\omega t + \pi/6)}\} \\ &= \text{Re}\{7.07 e^{j(\pi/6)} \sqrt{2} e^{j\omega t}\} \text{ A} \end{aligned}$$

Phasor Diagram Example

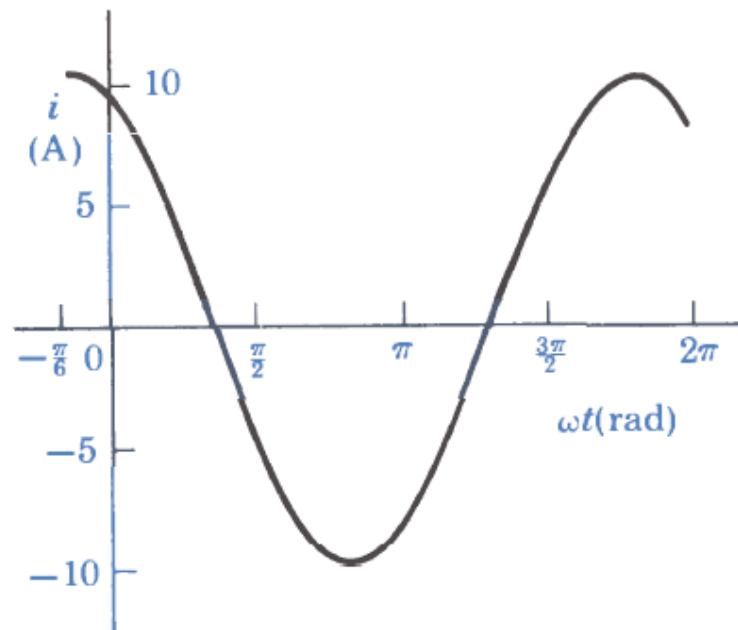Write the eq. of the current shown in fig. as a function of time and represent the current by a phasor.



The current reaches a positive maximum of 10 A at $\pi/6$ rad or 30° before $\omega t = 0$; therefore ,
 $i = 10 \cos(\omega t + \pi/6) \text{ A}$

or


$$i(t) = \text{Re}\{10 e^{j(\omega t + \pi/6)}\}$$
$$= \text{Re}\{7.07 e^{j(\pi/6)} \sqrt{2} e^{j\omega t}\} \text{ A}$$

Current phasor

$$I = 7.07 e^{j\pi/6} \text{ A}$$

Phasor Diagram Example

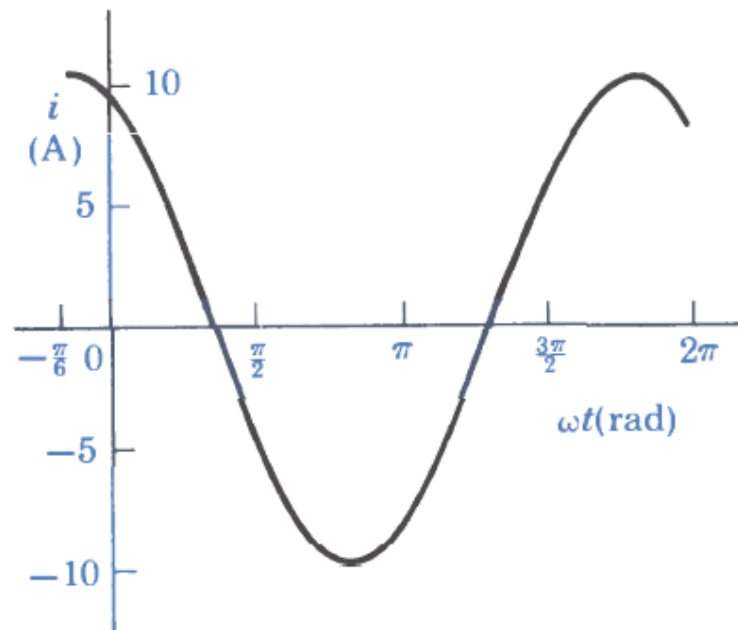Write the eq. of the current shown in fig. as a function of time and represent the current by a phasor.



The current reaches a positive maximum of 10 A at $\pi/6$ rad or 30° before $\omega t = 0$; therefore ,
 $i = 10 \cos(\omega t + \pi/6) \text{ A}$

or

$$i(t) = \text{Re}\{10 e^{j(\omega t + \pi/6)}\}$$
$$= \text{Re}\{7.07 e^{j(\pi/6)} \sqrt{2} e^{j\omega t}\} \text{ A}$$

Current phasor

$$I = 7.07 e^{j\pi/6} \text{ A}$$

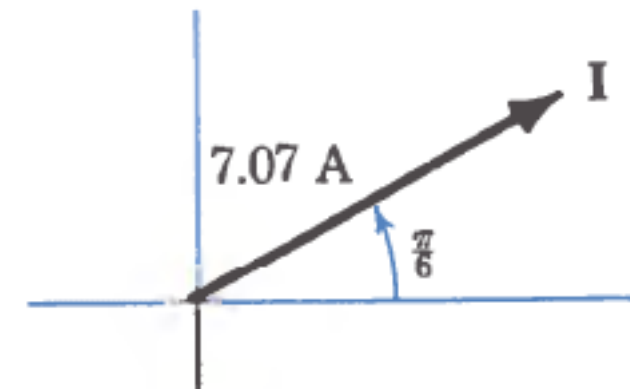


Figure: Phasor


Phasor Diagram Example 2

Given

$$v_1 = 150\sqrt{2} \cos(377t - \pi/6) \text{ V}$$

and $V_2 = 200 \angle +60^\circ \text{ V}$, find

$$V = V_1 + V_2$$

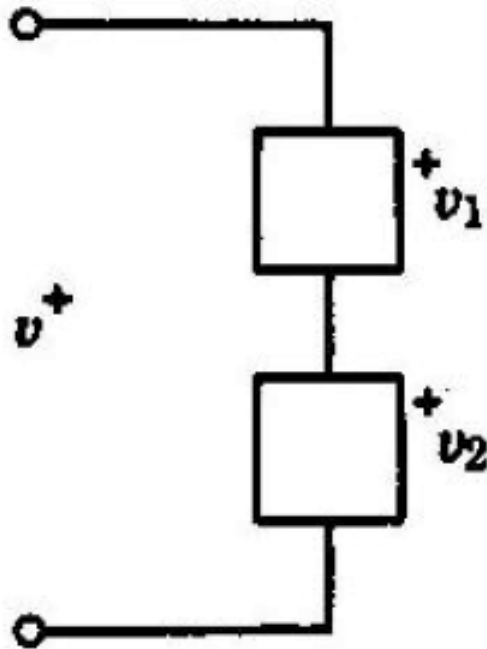


Phasor Diagram Example 2

Given

$$v_1 = 150\sqrt{2} \cos(377t - \pi/6) \text{ V}$$


and $V_2 = 200 \angle +60^\circ \text{ V}$, find

$$V = V_1 + V_2$$

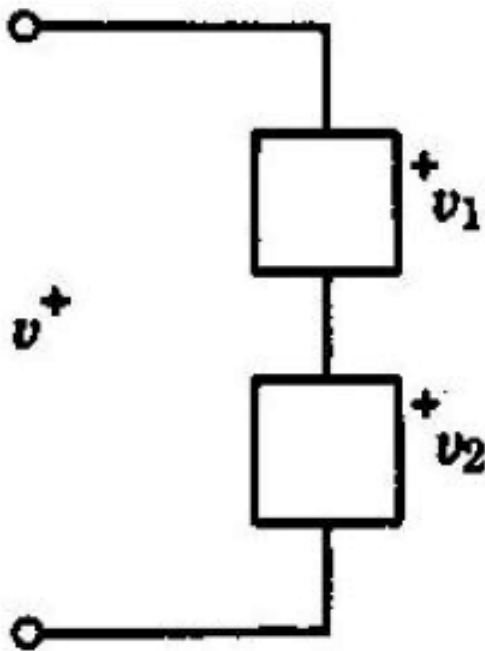


Phasor notation:

$$V_1 = 150 \angle -30^\circ \text{ V}$$

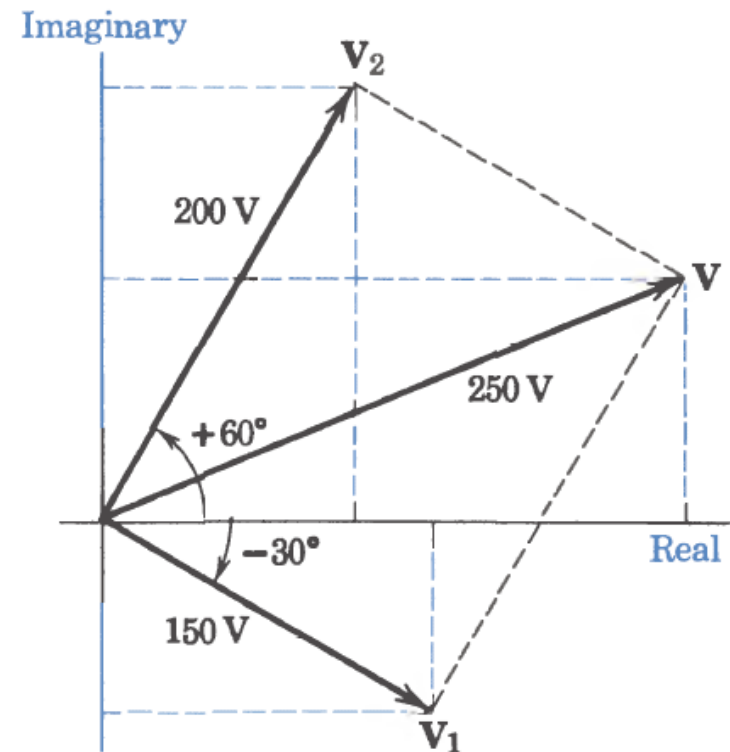

Phasor Diagram Example 2

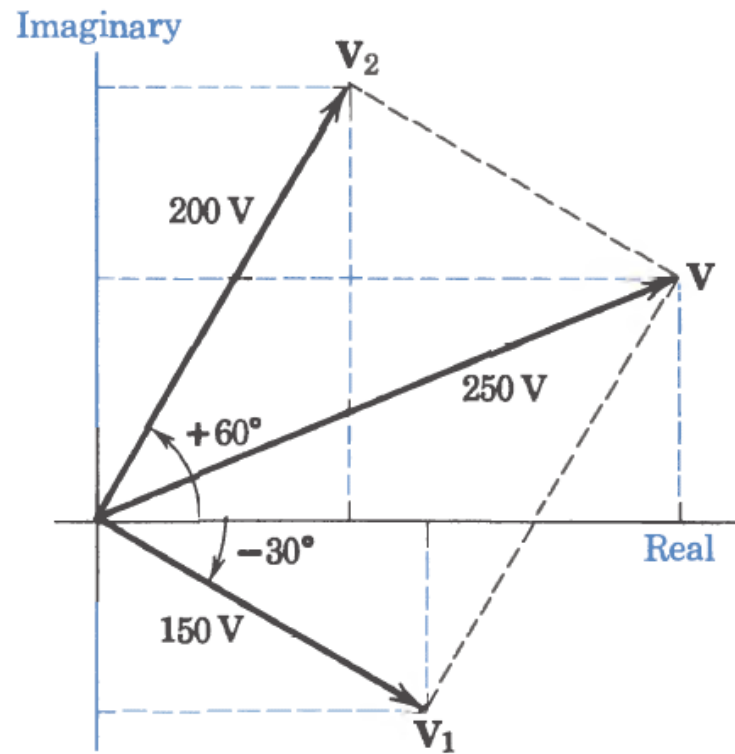


$$V_1 = 150 \cos(-30^\circ) + j150 \sin(-30^\circ) \\ = 130 - j75 \text{ V}$$

$$V_2 = 200 \cos 60^\circ + j200 \sin 60^\circ \\ = 100 + j173 \text{ V}$$

$$V = V_1 + V_2 = 230 + j98 \\ = 250 \angle 23.1^\circ \text{ V}$$

Phasor Diagram Example 2

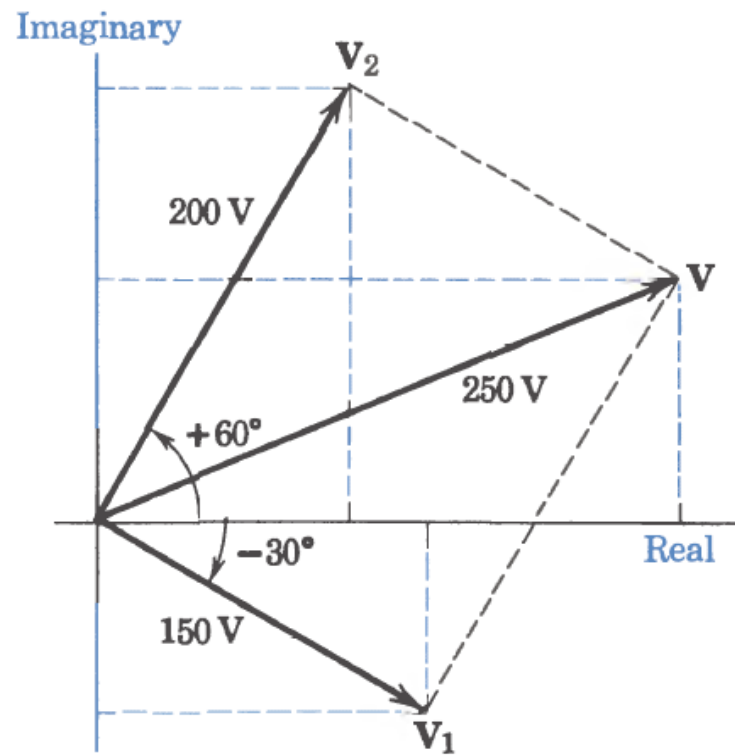

$$V_1 = 150 \cos(-30^\circ) + j150 \sin(-30^\circ) \\ = 130 - j75 \text{ V}$$

$$V_2 = 200 \cos 60^\circ + j200 \sin 60^\circ \\ = 100 + j173 \text{ V}$$

$$V = V_1 + V_2 = 230 + j98 \\ = 250 \angle 23.1^\circ \text{ V}$$


After inverse transformation on V ,

$$v = v_1 + v_2 =$$

$$250\sqrt{2} \cos(377t + 23.1^\circ) \text{ V}$$


Phasor Diagram : Leading/Lagging

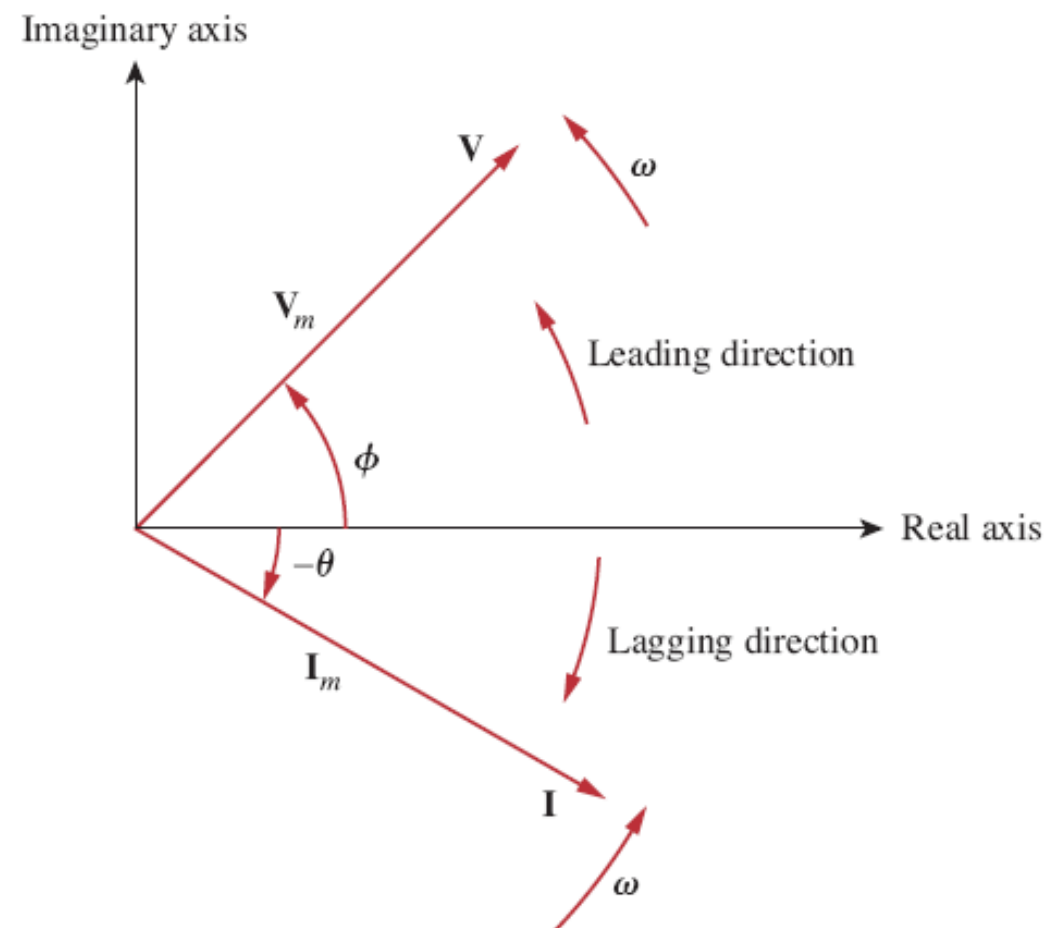- Phasors may have positive/negative phase difference with the reference signal.



Phasor Diagram : Leading/Lagging

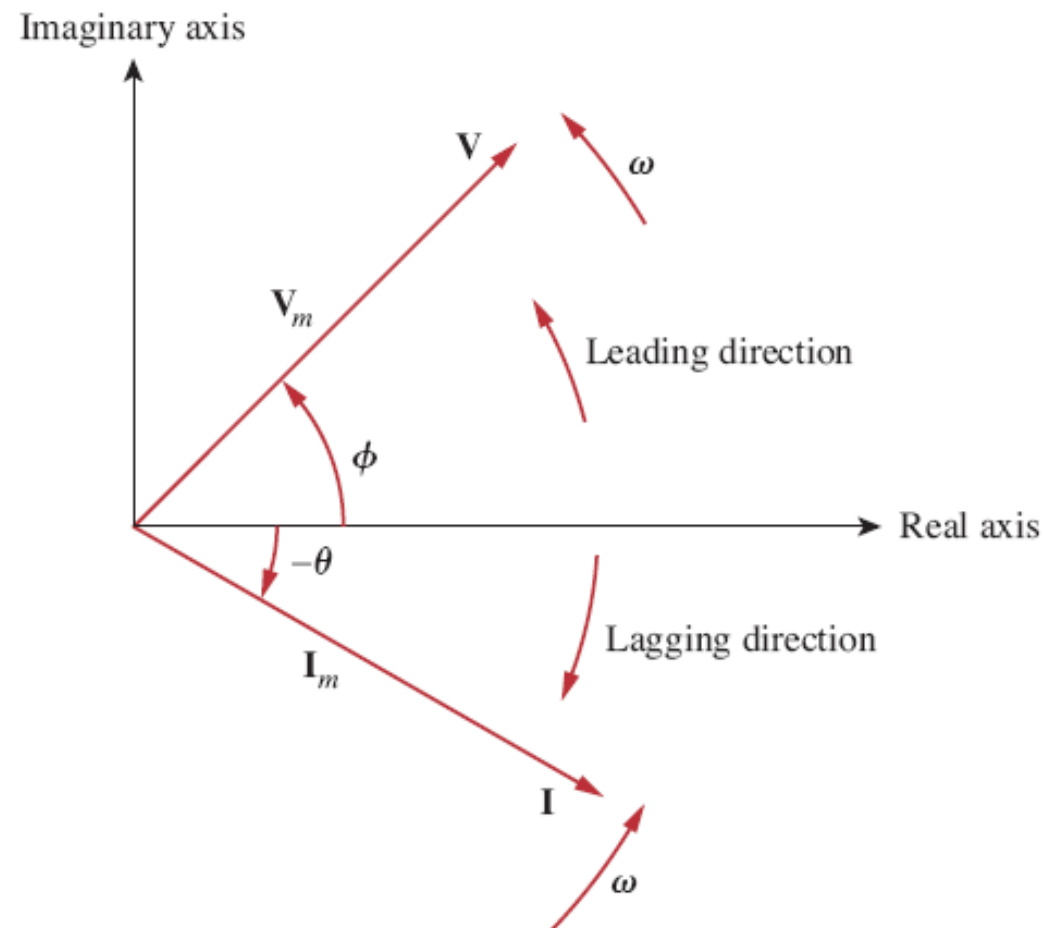
- Phasors may have positive/negative phase difference with the reference signal.



- Positive phase difference wrt reference is termed as **leading**
- Negative phase difference wrt reference is termed as **lagging**

Phasor Diagram : Leading/Lagging

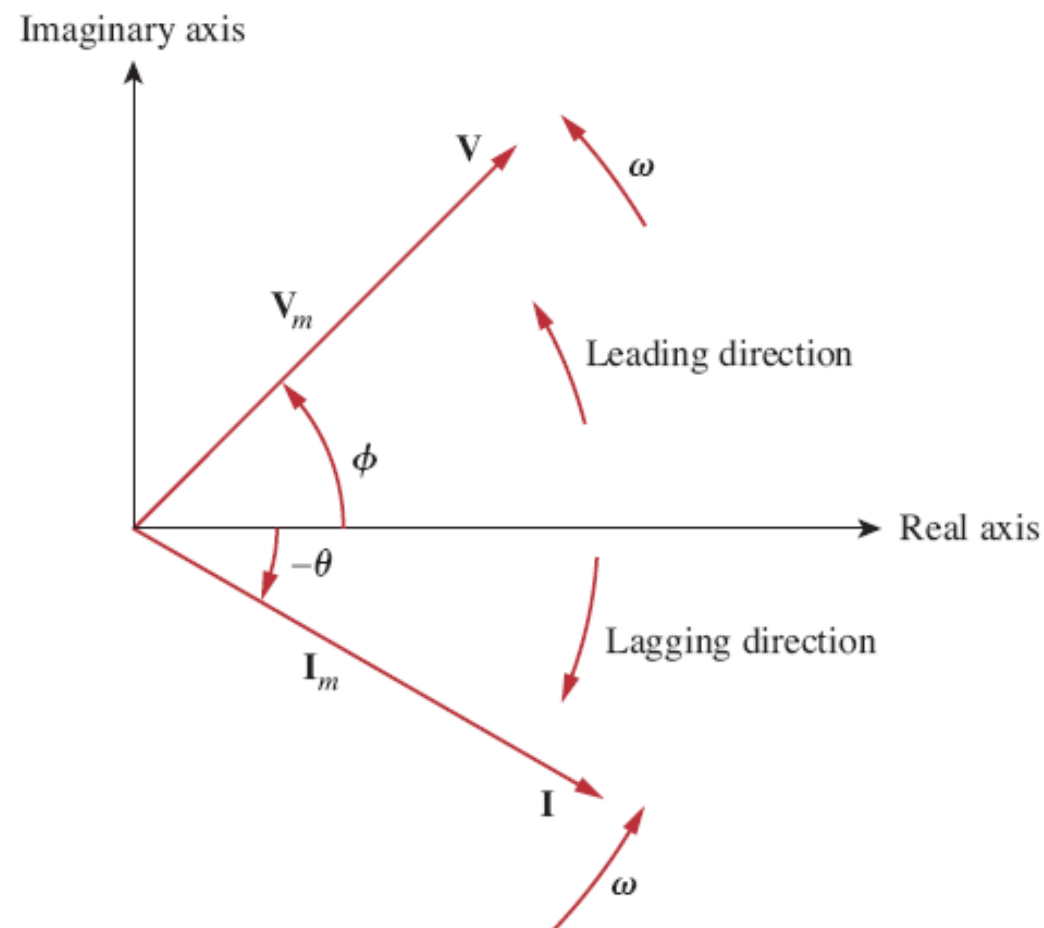- Phasors may have positive/negative phase difference with the reference signal.



- Positive phase difference wrt reference is termed as **leading**
- Negative phase difference wrt reference is termed as **lagging**

Reference Signal : Signal common to various circuit parts.

- Current in series-connected circuits
- Voltage in parallel connected circuit (power supply)

Impedance and Phasors

- Sinusoidal signals are basically composed of exponentials with 'imaginary' decay rates i.e. of type $\text{Re}\{Ae^{j\omega t}\}$

Impedance and Phasors

- Sinusoidal signals are basically composed of exponentials with 'imaginary' decay rates i.e. of type $\text{Re}\{Ae^{j\omega t}\}$
- So, we have $s=j\omega$

Impedance and Phasors

- Sinusoidal signals are basically composed of exponentials with 'imaginary' decay rates i.e. of type $\text{Re}\{Ae^{j\omega t}\}$
- So, we have $s=j\omega$
- Recall
 - For Resistance $Z_R(j\omega) = R \quad \Omega = R\angle 0^\circ$


Impedance and Phasors

- Sinusoidal signals are basically composed of exponentials with 'imaginary' decay rates i.e. of type $\text{Re}\{Ae^{j\omega t}\}$
- So, we have $s=j\omega$
- Recall
 - For Resistance $Z_R(j\omega) = R \quad \Omega = R \angle 0^\circ$
 - For Inductance $Z_L(j\omega) = j\omega L \quad \Omega = \omega L \angle 90^\circ$

Impedance and Phasors

- Sinusoidal signals are basically composed of exponentials with 'imaginary' decay rates i.e. of type $\text{Re}\{Ae^{j\omega t}\}$
- So, we have $s=j\omega$
- Recall
 - For Resistance $Z_R(j\omega) = R \quad \Omega = R \angle 0^\circ$
 - For Inductance $Z_L(j\omega) = j\omega L \quad \Omega = \omega L \angle 90^\circ$
 - For Capacitance $Z_C(j\omega) = \frac{1}{j\omega C} \quad \Omega = \frac{1}{\omega C} \angle -90^\circ$


Impedance and Phasors

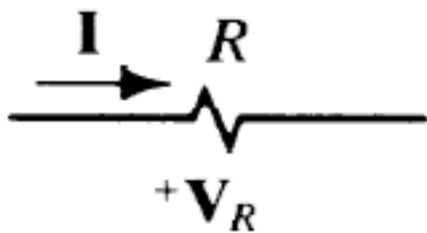

$$\mathbf{V}_R = R\mathbf{I}$$

$$\mathbf{I}_R = \frac{1}{R} \mathbf{V}_R$$


V in phase with I

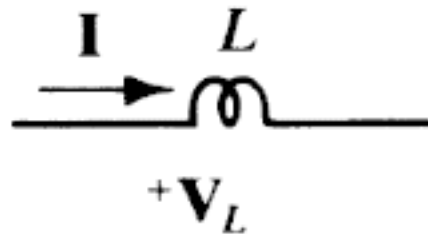

$$\mathbf{V}_L = j\omega L\mathbf{I}$$

$$\mathbf{I}_L = \frac{1}{j\omega L} \mathbf{V}_L$$

V leads I by 90 deg

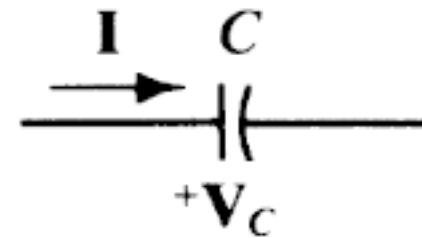

$$\mathbf{V}_C = \frac{1}{j\omega C} \mathbf{I}$$

$$\mathbf{I}_C = j\omega C \mathbf{V}_C$$

V lags I by 90 deg

Admittance

The reciprocal of impedance is admittance, SI unit: siemens or mho

$$Y = \frac{I}{V} = \frac{1}{Z} \text{ Siemens}$$


$$Y_R = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ$$

$$Y_L = \frac{1}{j\omega L} = \frac{1}{\omega L} \angle -90^\circ$$

$$Y_C = j\omega C = \omega C \angle 90^\circ$$

Phasors for R-L-C elements

The typical phasors for R-L-C elements

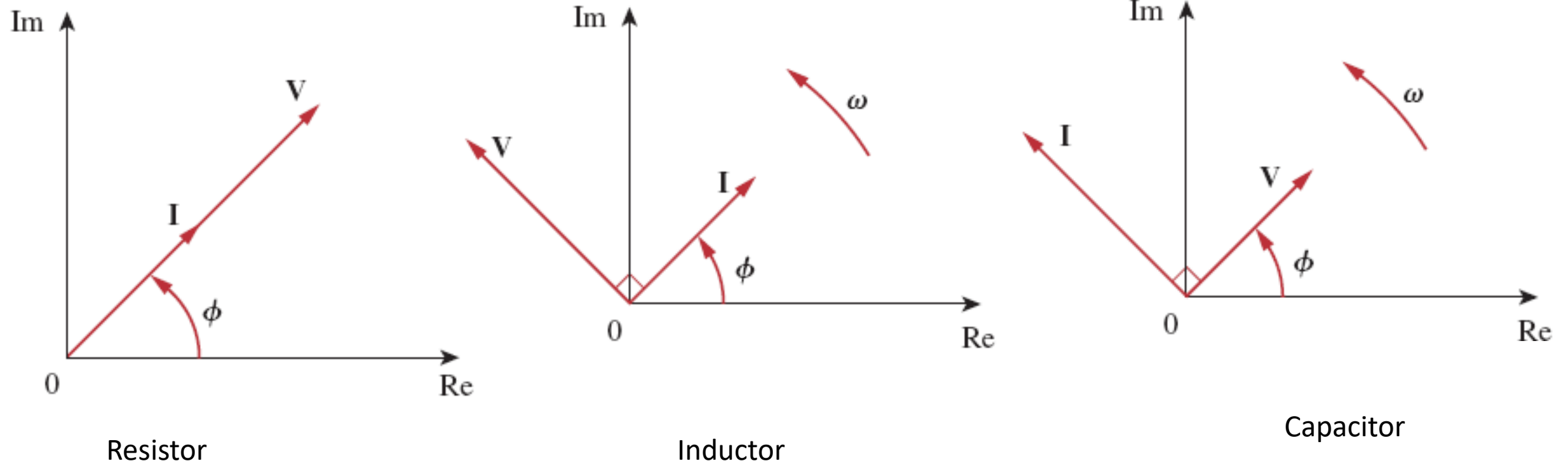

Example


Voltage

$$v = 120\sqrt{2}\cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

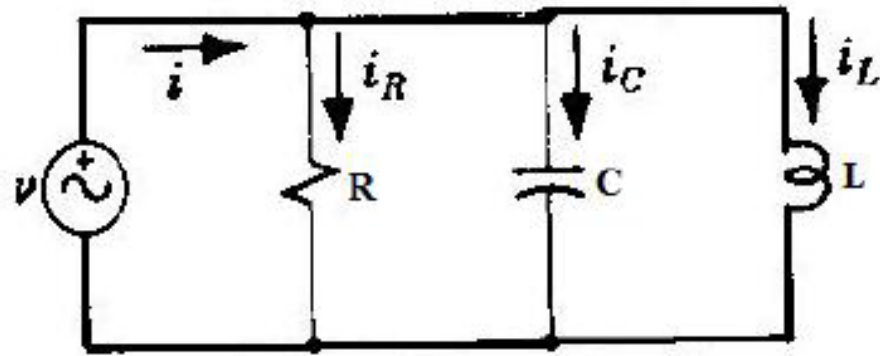

Example

Voltage

$$v = 120\sqrt{2}\cos(1000t + 90^\circ) \text{ V}$$


is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

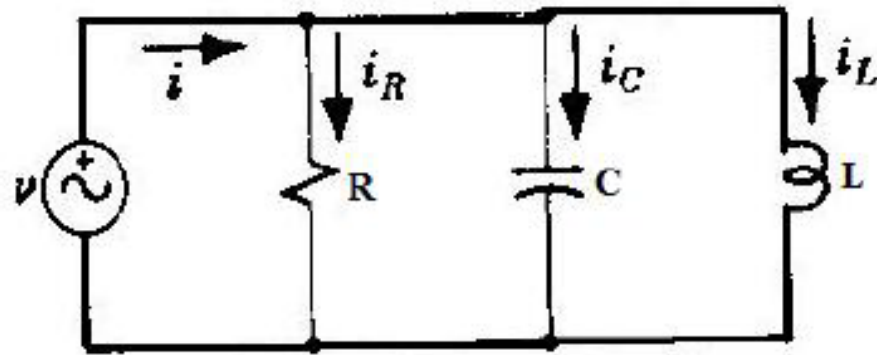

Example

Voltage

$$v = 120\sqrt{2}\cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where


$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

Solution:

$$V = 120\angle 90^\circ \text{ V}$$
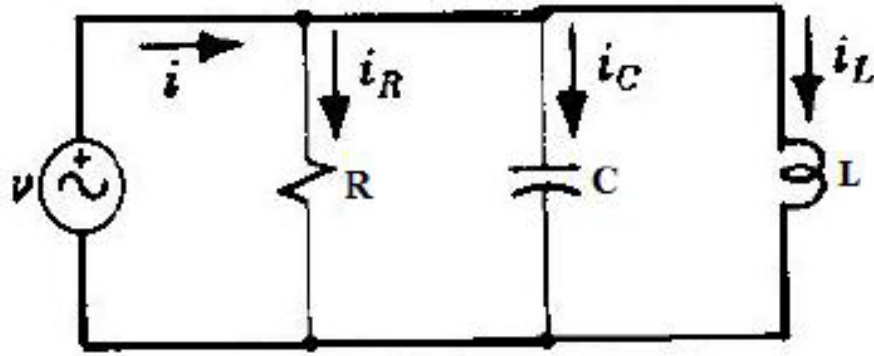
$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$



Example


Voltage

$$v = 120\sqrt{2} \cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

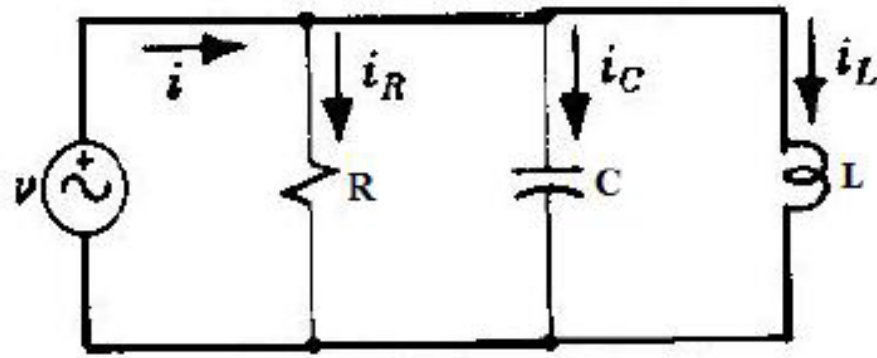

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ)$$

Example


Voltage

$$v = 120\sqrt{2}\cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

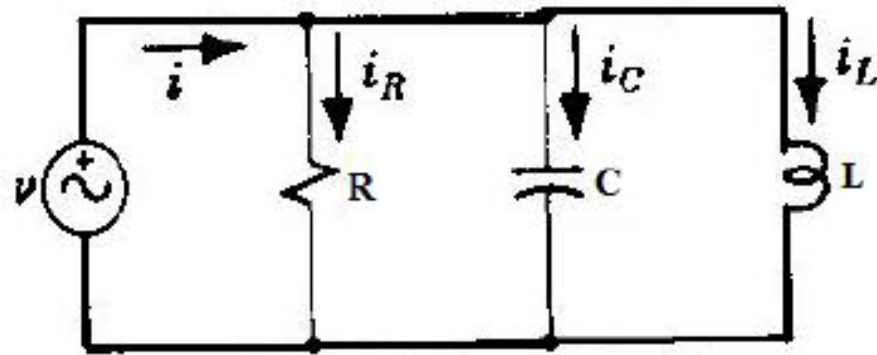

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ)$$

$$\mathbb{C} = M_1 * M_2\angle\phi_1 + \phi_2$$

Example


Voltage

$$v = 120\sqrt{2} \cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

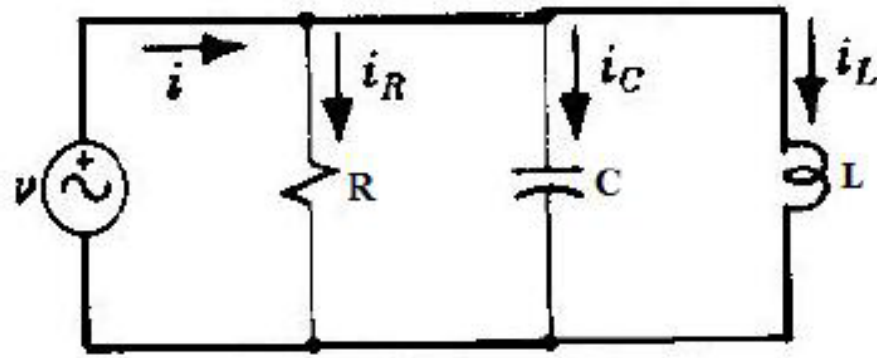

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ) \\ = 10\angle 180^\circ = -10 + j0 \text{ A}$$

$$\mathbb{C} = M_1 * M_2 \angle \phi_1 + \phi_2$$

Example


Voltage

$$v = 120\sqrt{2}\cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

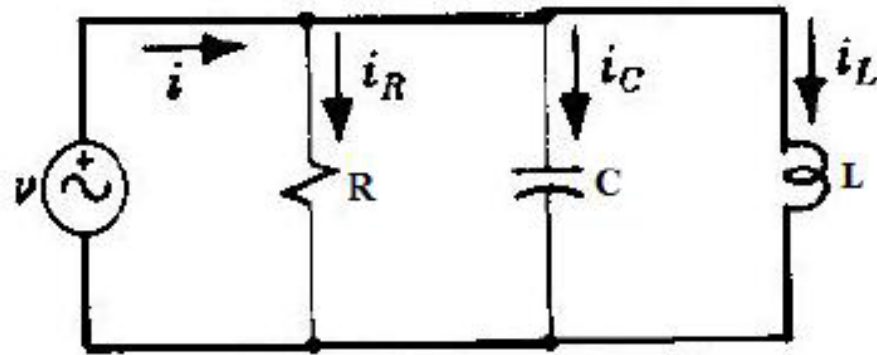

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ) \\ = 10\angle 180^\circ = -10 + j0 \text{ A}$$

$$I_L = \frac{1}{j\omega L} V = \frac{120\angle 90^\circ}{30\angle 90^\circ}$$

$$\mathbb{C} = M_1 * M_2 \angle \phi_1 + \phi_2$$

Example


Voltage

$$v = 120\sqrt{2} \cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

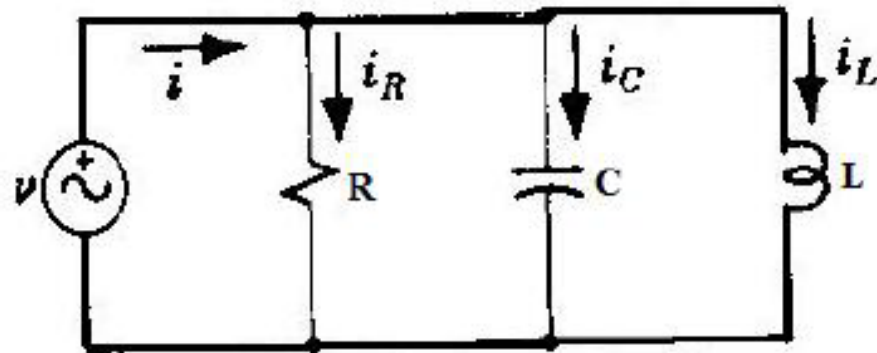

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ) \\ = 10\angle 180^\circ = -10 + j0 \text{ A}$$

$$I_L = \frac{1}{j\omega L} V = \frac{120\angle 90^\circ}{30\angle 90^\circ}$$

$$\mathbb{C} = M_1 * M_2 \angle \phi_1 + \phi_2$$

$$\mathbb{C} = \frac{M_1}{M_2} \angle \phi_1 - \phi_2$$

Example


Voltage

$$v = 120\sqrt{2} \cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

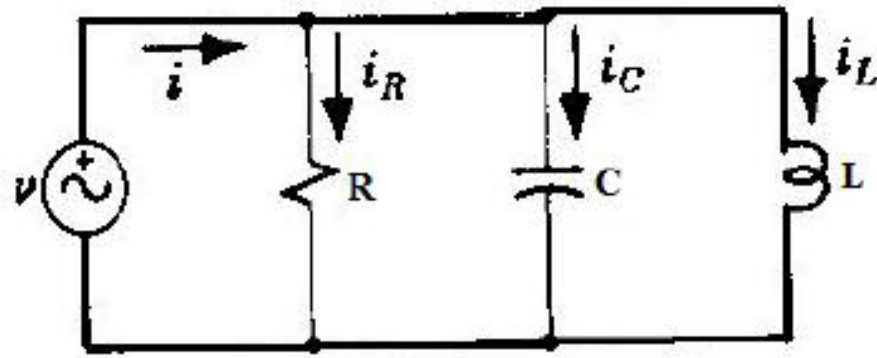

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ) \\ = 10\angle 180^\circ = -10 + j0 \text{ A}$$

$$I_L = \frac{1}{j\omega L} V = \frac{120\angle 90^\circ}{30\angle 90^\circ} \\ = 4\angle 0^\circ = 4 + j0 \text{ A}$$

$$\mathbb{C} = M_1 * M_2 \angle \phi_1 + \phi_2$$

$$\mathbb{C} = \frac{M_1}{M_2} \angle \phi_1 - \phi_2$$

Example


Voltage

$$v = 120\sqrt{2} \cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

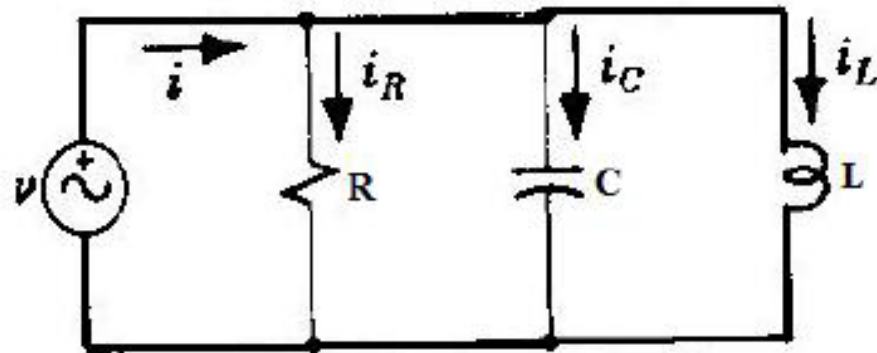

$$C = M_1 * M_2 \angle \phi_1 + \phi_2$$

$$C = \frac{M_1}{M_2} \angle \phi_1 - \phi_2$$

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ) \\ = 10\angle 180^\circ = -10 + j0 \text{ A}$$

$$I_L = \frac{1}{j\omega L} V = \frac{120\angle 90^\circ}{30\angle 90^\circ} \\ = 4\angle 0^\circ = 4 + j0 \text{ A}$$

By Kirchhoff's current law, $\sum I = 0$
or

$$I = I_R + I_C + I_L = (0 - 10 + 4) + j(8 + 0 + 0) \\ = -6 + j8 = 10\angle 127^\circ \text{ A}$$

$$i(t) = 10\sqrt{2} \cos(1000t + 127^\circ) \text{ A}$$

Example


Voltage

$$v = 120\sqrt{2} \cos(1000t + 90^\circ) \text{ V}$$

is applied to the circuit where

$$R = 15\Omega, C = 83.3\mu\text{F}, \text{ and}$$

$$L = 30\text{mH}. \text{ Find } i(t)$$

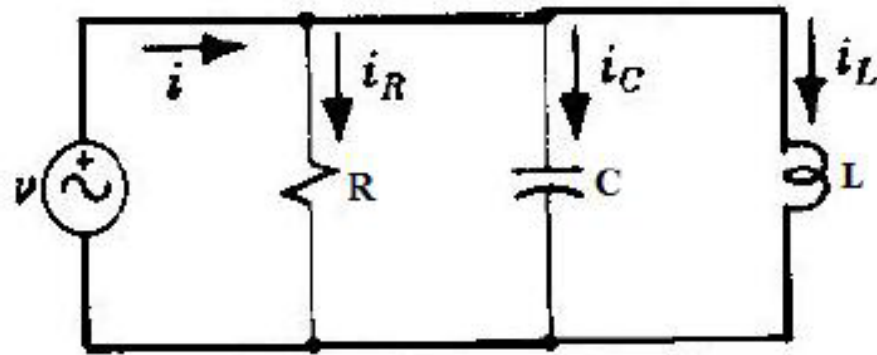

$$\mathbb{C} = M_1 * M_2 \angle \phi_1 + \phi_2$$

$$\mathbb{C} = \frac{M_1}{M_2} \angle \phi_1 - \phi_2$$

Solution:

$$V = 120\angle 90^\circ \text{ V}$$

$$I_R = \frac{1}{R} V = \frac{1}{15} 120\angle 90^\circ = 8\angle 90^\circ \\ = 0 + j8 \text{ A} \quad \text{In Phase}$$

$$I_C = j\omega C V \\ = (0.0833\angle 90^\circ)(120\angle 90^\circ) \\ = 10\angle 180^\circ = -10 + j0 \text{ A} \quad \text{Leading}$$

$$I_L = \frac{1}{j\omega L} V = \frac{120\angle 90^\circ}{30\angle 90^\circ} \\ = 4\angle 0^\circ = 4 + j0 \text{ A} \quad \text{Lagging}$$

By Kirchhoff's current law, $\sum I = 0$
or

$$I = I_R + I_C + I_L = (0 - 10 + 4) + j(8 + 0 + 0) \\ = -6 + j8 = 10\angle 127^\circ \text{ A}$$

$$i(t) = 10\sqrt{2} \cos(1000t + 127^\circ) \text{ A} \quad \text{Leading}$$

Example – Impedance as Complex No.

Voltage $v = 12\sqrt{2} \cos 5000t$ V
is applied to the circuit. Find the
individual and combined
impedances and the current $i(t)$


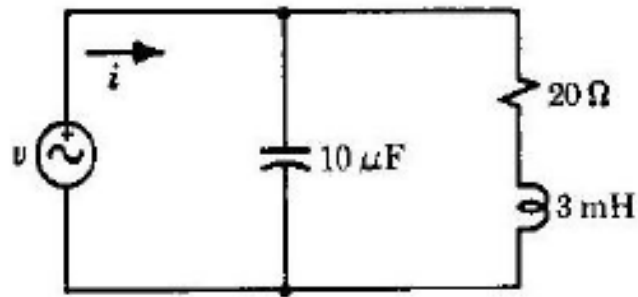


Figure: Circuit Elements

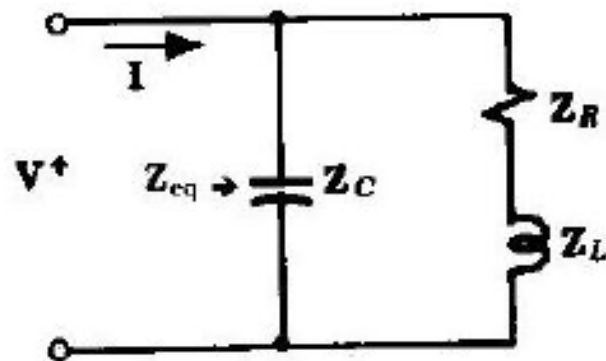

Example – Impedance as Complex No.

Voltage $v = 12\sqrt{2} \cos 5000t$ V is applied to the circuit. Find the individual and combined impedances and the current $i(t)$

Solution:

$$Z_R = R = 20 = 20 + j0 = 20\angle 0^\circ \Omega$$


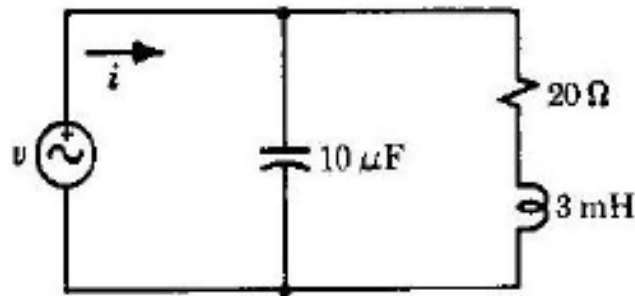


Figure: Circuit Elements

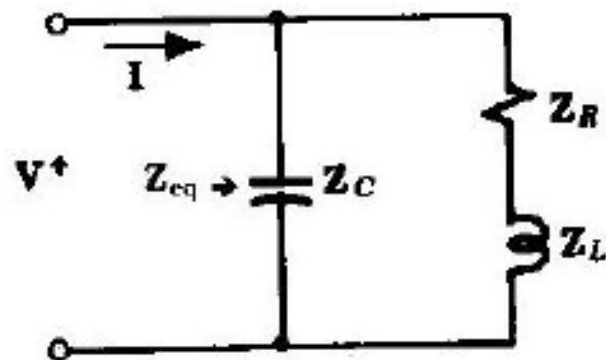

Example – Impedance as Complex No.

Voltage $v = 12\sqrt{2} \cos 5000t$ V is applied to the circuit. Find the individual and combined impedances and the current $i(t)$

Solution:

$$Z_R = R = 20 = 20 + j0 = 20\angle 0^\circ \Omega$$

$$Z_L = j\omega L = j5000 \times 0.003 = j15 \Omega \\ = 15\angle 90^\circ \Omega$$


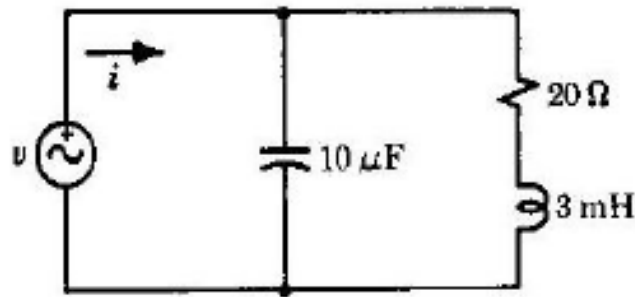


Figure: Circuit Elements

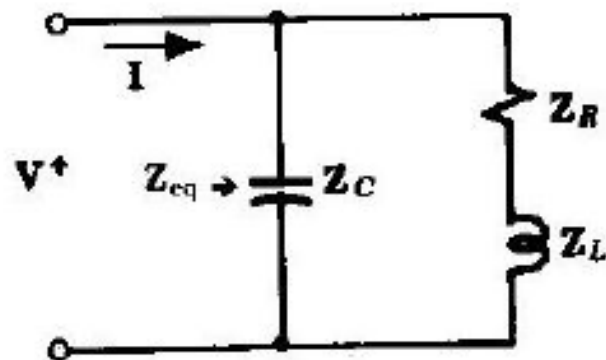

Example – Impedance as Complex No.

Voltage $v = 12\sqrt{2} \cos 5000t$ V is applied to the circuit. Find the individual and combined impedances and the current $i(t)$


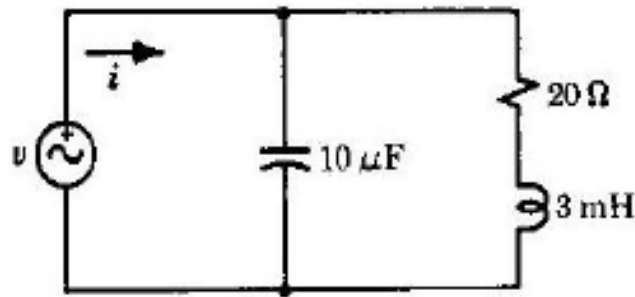


Figure: Circuit Elements

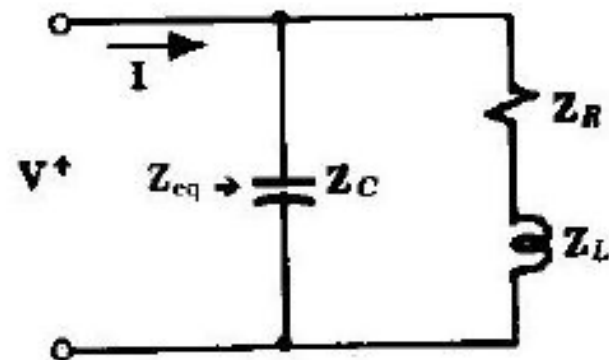

Solution:

$$Z_R = R = 20 = 20 + j0 = 20 \angle 0^\circ \Omega$$

$$Z_L = j\omega L = j5000 \times 0.003 = j15 \Omega \\ = 15 \angle 90^\circ \Omega$$

$$Z_C = -j \frac{1}{\omega C} = \frac{-j}{5000 \times 10^{-5}} \\ = -j20 = 20 \angle -90^\circ \Omega$$

Example – Impedance as Complex No.

Voltage $v = 12\sqrt{2} \cos 5000t$ V is applied to the circuit. Find the individual and combined impedances and the current $i(t)$


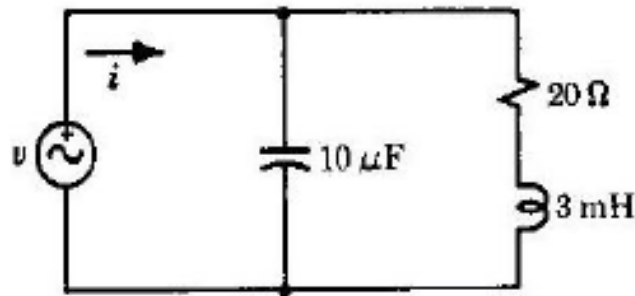


Figure: Circuit Elements

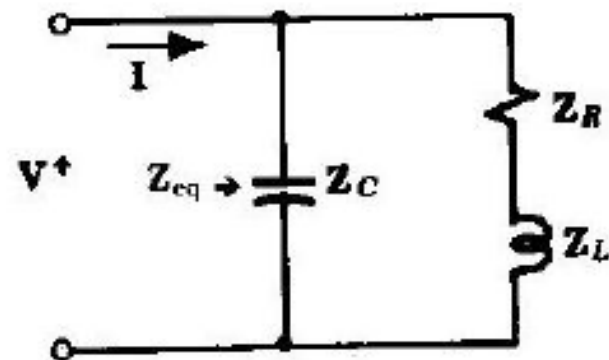

Solution:

$$Z_R = R = 20 = 20 + j0 = 20 \angle 0^\circ \Omega$$

$$Z_L = j\omega L = j5000 \times 0.003 = j15 \Omega \\ = 15 \angle 90^\circ \Omega$$

$$Z_C = -j \frac{1}{\omega C} = \frac{-j}{5000 \times 10^{-5}} \\ = -j20 = 20 \angle -90^\circ \Omega$$

$$Z_{RL} = Z_R + Z_L = 20 + j15 = 25 \angle 37^\circ \Omega$$

Example – Impedance as Complex No.

Voltage $v = 12\sqrt{2} \cos 5000t$ V is applied to the circuit. Find the individual and combined impedances and the current $i(t)$


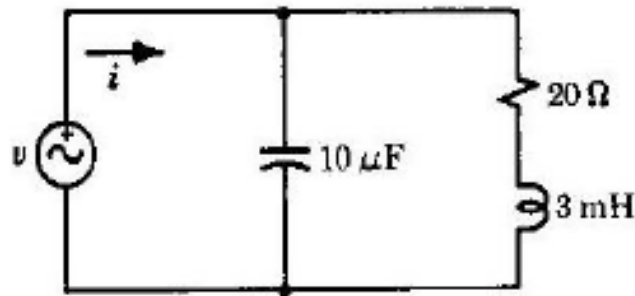


Figure: Circuit Elements

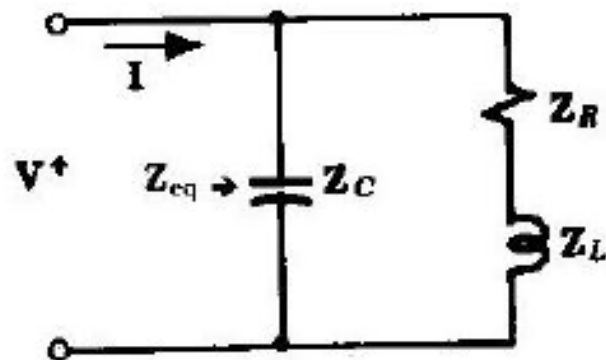

Solution:

$$Z_R = R = 20 = 20 + j0 = 20 \angle 0^\circ \Omega$$

$$Z_L = j\omega L = j5000 \times 0.003 = j15 \Omega = 15 \angle 90^\circ \Omega$$

$$Z_C = -j \frac{1}{\omega C} = \frac{-j}{5000 \times 10^{-5}} = -j20 = 20 \angle -90^\circ \Omega$$

$$Z_{RL} = Z_R + Z_L = 20 + j15 = 25 \angle 37^\circ \Omega$$

$$\begin{aligned} Z_{eq} &= \frac{Z_{RL} \cdot Z_C}{Z_{RL} + Z_C} = \frac{25 \angle 37^\circ \cdot 20 \angle -90^\circ}{20 + j15 - j20} \\ &= \frac{500 \angle -53^\circ}{20 - j5} = 24.3 \angle -39^\circ \\ &= 18.9 - j15.3 \Omega \end{aligned}$$

Example – Impedance as Complex No.

Voltage $v = 12\sqrt{2} \cos 5000t$ V is applied to the circuit. Find the individual and combined impedances and the current $i(t)$


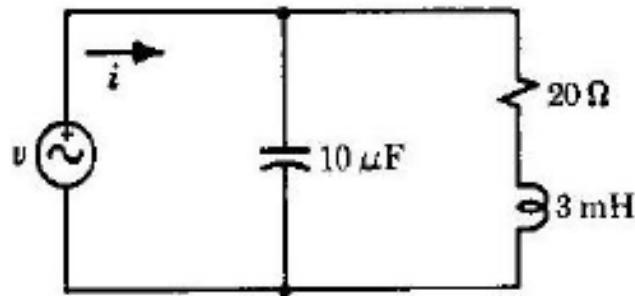


Figure: Circuit Elements

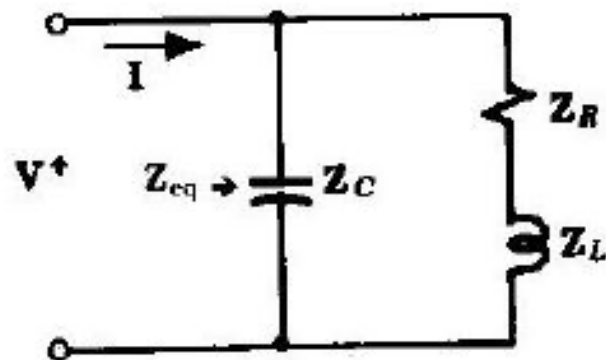

Solution:

$$Z_R = R = 20 = 20 + j0 = 20 \angle 0^\circ \Omega$$

$$Z_L = j\omega L = j5000 \times 0.003 = j15 \Omega = 15 \angle 90^\circ \Omega$$

$$Z_C = -j \frac{1}{\omega C} = \frac{-j}{5000 \times 10^{-5}} = -j20 = 20 \angle -90^\circ \Omega$$

$$Z_{RL} = Z_R + Z_L = 20 + j15 = 25 \angle 37^\circ \Omega$$

$$\begin{aligned} Z_{eq} &= \frac{Z_{RL} \cdot Z_C}{Z_{RL} + Z_C} = \frac{25 \angle 37^\circ \cdot 20 \angle -90^\circ}{20 + j15 - j20} \\ &= \frac{500 \angle -53^\circ}{20 - j5} = 24.3 \angle -39^\circ \\ &= 18.9 - j15.3 \Omega \end{aligned}$$

$$I = \frac{V}{Z} = \frac{12 \angle 0^\circ}{24.3 \angle -39^\circ} = 0.49 \angle 39^\circ \text{ A}$$

$$i(t) = 0.49\sqrt{2} \cos(5000t + 39^\circ) \text{ A}$$

General Procedure

- Transform the time functions into phasors and element values into impedances/admittances.
- Combine impedances/admittances to simplify circuit.
- Draw the phasor diagram of the phasors of interest
- Compute the desired result in phasor form and transform to time function (if required)