

• Name-plate on transformer

Rating of the transformer

50 KVA, 2400/240 V, 50 Hz (1- ϕ transfm)

↑
 Power output

↓
 voltages of primary & secondary

↑
 operating frequency




Depends on the purpose

For Step-down purpose $\left\{ \begin{array}{l} \text{Primary } 2400 \text{ V (supply)} \\ \text{Secondary } 240 \text{ (out/for load)} \end{array} \right.$


step-up purpose $\left\{ \begin{array}{l} \text{Primary } 240 \text{ V} \\ \text{Secondary } 2400 \text{ V} \end{array} \right.$

The rated primary current $= \frac{50000}{2400} = 20.83 \text{ A}$

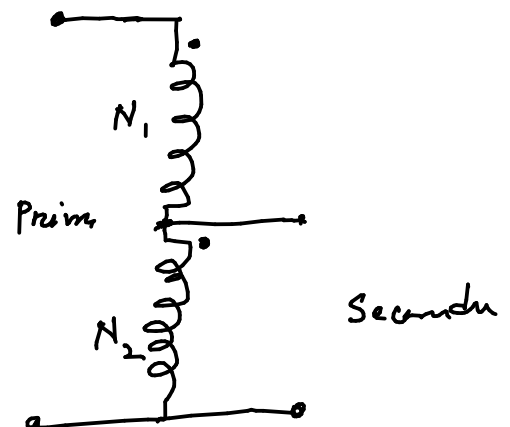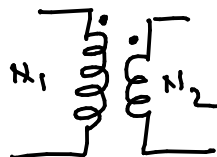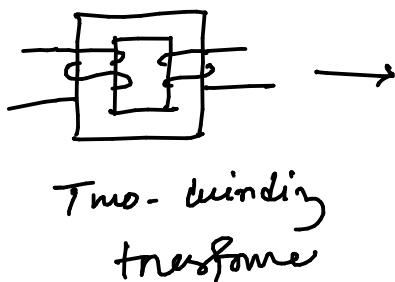Secondary current $= \frac{50000}{240} = 208.3 \text{ A}$



Autotransformer

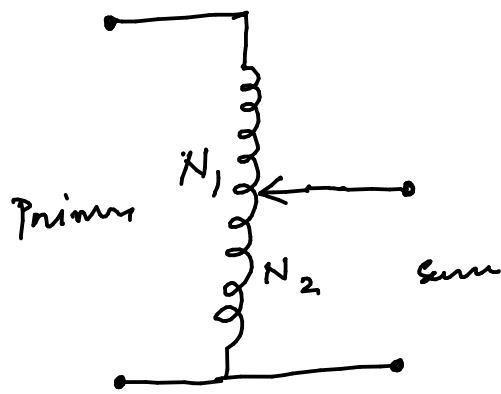


auto-transformer
or (variac)

- Regulate output voltage
- The difference between two-winding transformer & auto-transformer is that


the windings in an auto-transformer are not electrically isolated.

- Some portion of the winding in auto-transformer is common to both primary & secondary.

Transformer tests

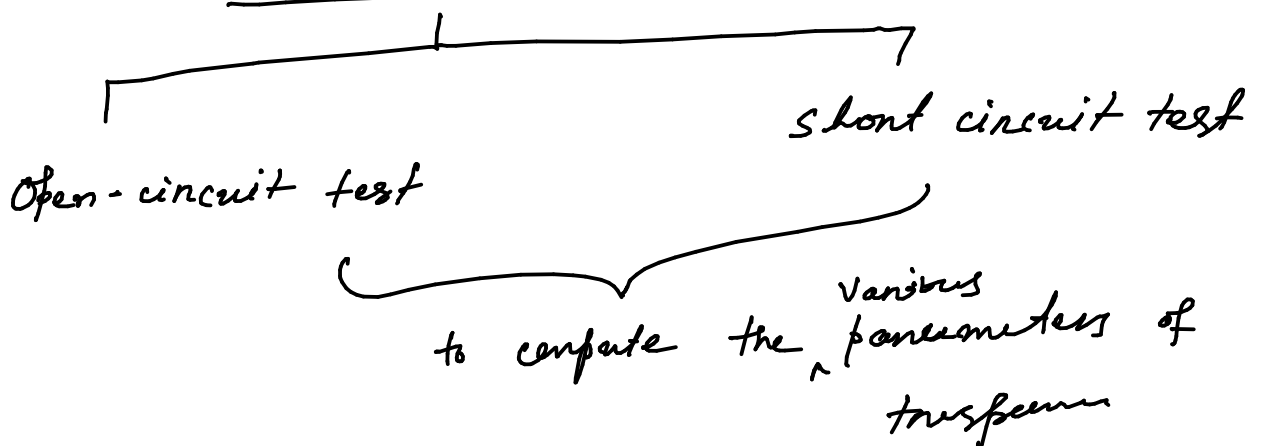


→ Core-loss

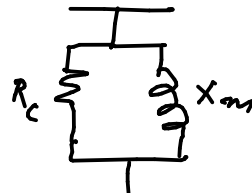

→ All these parameters can be computed.

- Open Circuit test (No-load test)

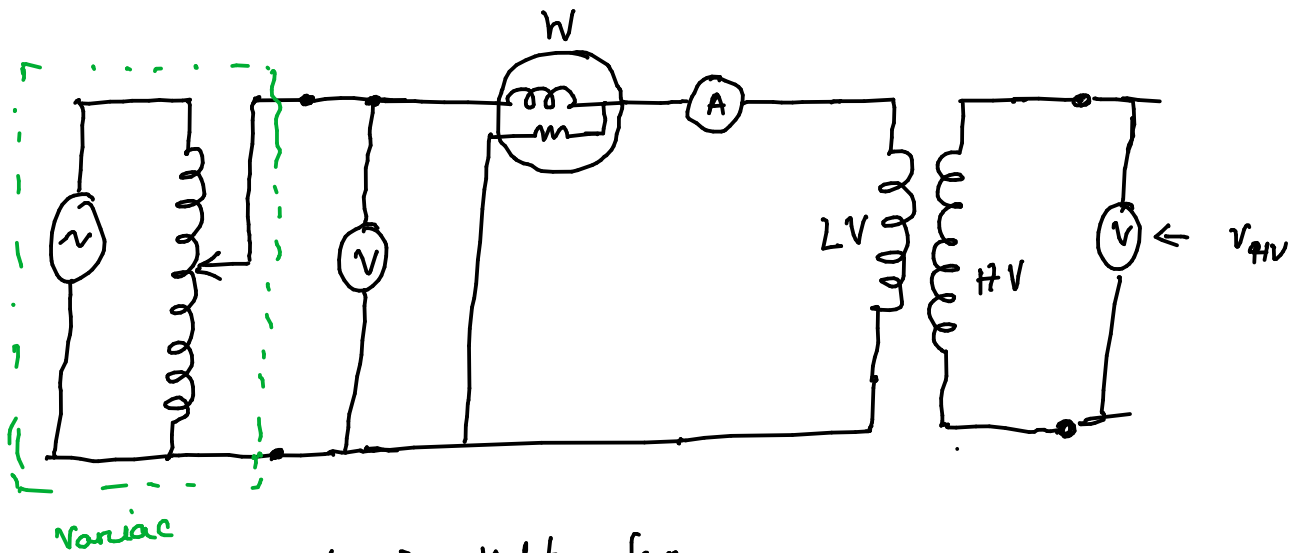


V \rightarrow Voltmeter

A \rightarrow Ammeter

W \rightarrow Wattmeter

\rightarrow low voltage

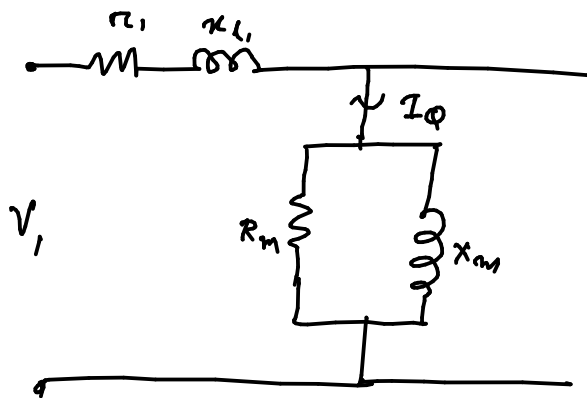- Apply rated voltage to the LV side of transformer.



Only a small amount of current will flow in primary side just to establish flux in the core.


Since the current is very low

Neglect the drop in leakage impedance

\Downarrow

$$V_1 = E_1$$

The equivalent circuit

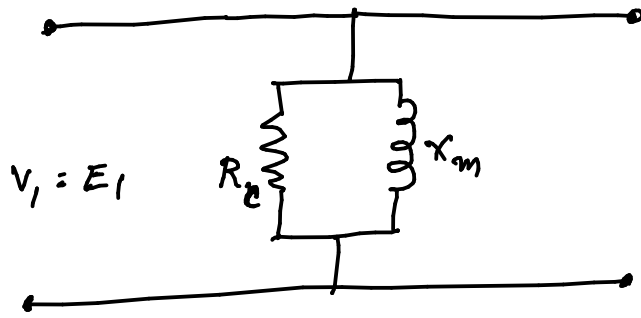

The measured quantities

- V_{oc} (voltage meter reads)
- I_{oc} (ammeter reads)
- P_{oc} (Watt meter reads)

$$Z_{oc} \approx \frac{R_c (jX_m)}{R_c + jX_m}$$

$$R_c = \frac{V_{oc}^2}{P_{oc}}$$

$$|Z_{oc}| = \frac{V_{oc}}{I_{oc}}$$

$$|Z_{oc}| = \frac{|jR_cX_m|}{|R + jX_m|}$$

$$= \frac{R_c X_m}{\sqrt{R^2 + X_m^2}}$$

$$\Rightarrow \frac{1}{|Z_{oc}|^2} = \frac{R_c^2}{R_c^2 X_m^2} + \frac{X_m^2}{R_c^2 X_m^2} = \frac{1}{X_m^2} + \frac{1}{R_c^2}$$

$$\Rightarrow \frac{1}{X_m^2} = \frac{1}{|Z_{oc}|^2} - \frac{1}{R_c^2}$$

$$\Rightarrow X_m = \frac{1}{\sqrt{\frac{1}{|Z_{oc}|^2} - \frac{1}{R_c^2}}}$$

$$V_1 = E_1 \quad E_2 = V_2$$

From open circuit test

→ Core loss in transformer (by wattmeter reading)

→ The short branch parameters


(X_m & R_c in equivalent ckt)

$$\rightarrow \frac{E_1}{E_2} = \frac{\text{Voltmeter reading at LV side}}{\text{Voltmeter reading at HV side}} = \frac{N_1}{N_2}$$

• Short circuit test

50KVA

220/220

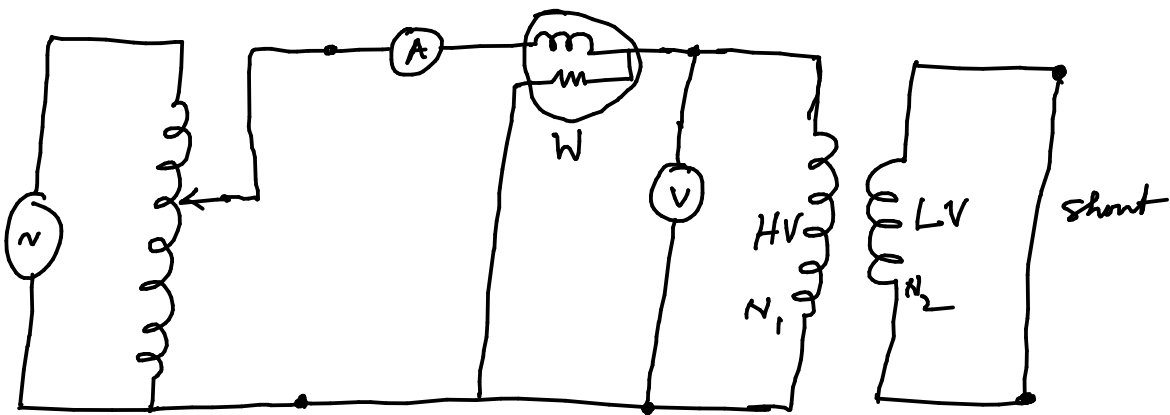

- Apply a regulated voltage through the variac s.t. the rated current in HV will flow.


↓

The mmf needs to be balanced.

$$I_1' N_1 = I_2 N_2$$

↓

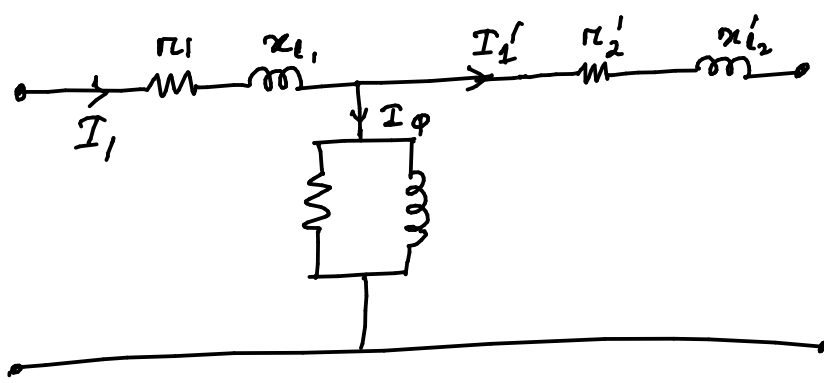
The rated current will also flow in LV side.



- Since the secondary is short, the load component of primary current I_1' is very high in comparison to the magnetizing component of current $I_φ$

↓

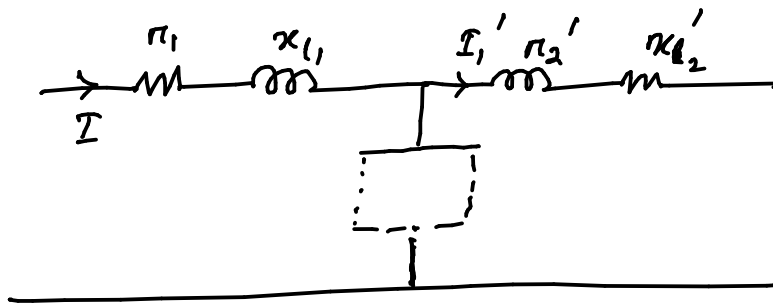Hence $I_φ$ can be neglected from the equivalent circuit $\rightarrow I_1 \approx I_1'$



$$Z_{sc} \approx \underbrace{r_1 + r_2'}_{R_{eq}} + j \underbrace{(x_{l1} + x_{l2}')}_{X_{eq}}$$

$$Z_{sc} = R_{eq} + j X_{eq}$$

Measured quantities :

- I_{sc} (Ammeter reading)
- V_{sc} (Voltmeter reading)
- P_{sc} (Wattmeter reading)

$$|Z_{sc}| = \frac{V_{sc}}{I_{sc}}$$

$$R_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$X_{eq} = \sqrt{|Z_{sc}|^2 - |R_{sc}|^2}$$

$$(\text{Sim } Z_{sc} = R_{eq} + jX_{eq})$$

- For short-circuit tests

$$\begin{aligned} \rightarrow R_{eq} &= R_1 + R_2' \\ X_{eq} &= X_1 + X_2' \end{aligned} \quad \left. \vphantom{\begin{aligned} R_{eq} &= R_1 + R_2' \\ X_{eq} &= X_1 + X_2' \end{aligned}} \right\}$$

$$\rightarrow I^2 R \text{ loss (Ohmic loss)}$$

The reading of wattmeter gives
Ohmic loss

- The open ckt test \rightarrow Core-loss (in core)
- The short ckt test \rightarrow Ohmic-loss (in the winding)

- The efficiency of transformer (in terms of per cent)

$$\eta = \left(\frac{P_{out}}{P_{input}} \right) \times 100$$

$$= \left(\frac{P_{input} - P_{losses}}{P_{input}} \right) \times 100$$