



# ELL100: INTRODUCTION TO ELECTRICAL ENGG.

## **Complete Response - II**

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik, Harshan  
Jagadeesh

Department of Electrical Engineering, IITD


# Complete Response

- If source (excitation) is exponential/sinusoidal :
  - Forced response – composed of exponentials present in source signal
  - Natural response – composed of exponentials depending on circuit components.
- EXCEPT when there are common modes
- For other excitations, ONLY

Complete Response = Natural Response + Forced Response
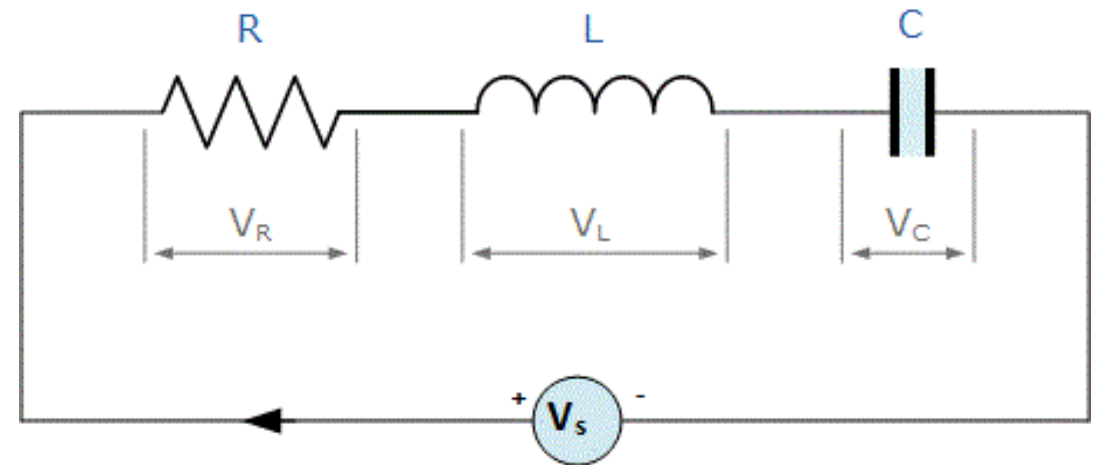
# Example

$V_s(t) = 5e^{-t}$  with  $R = 4 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1/3 \text{ F}$ ,  $i(0)=1 \text{ A}$ ,  $di/dt(0) = 3 \text{ A/s}$ . What is  $i(t)$  for  $t \geq 0$ ?



# Example


$V_s(t) = 5e^{-t}$  with  $R = 4 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1/3 \text{ F}$ ,  $i(0)=1 \text{ A}$ ,  $di/dt(0) = 3 \text{ A/s}$ . What is  $i(t)$  for  $t \geq 0$ ?

- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C} = \frac{\alpha^2 + 4\alpha + 3}{\alpha}$$

$$\alpha = -1$$

$$Z(\alpha) = 0$$

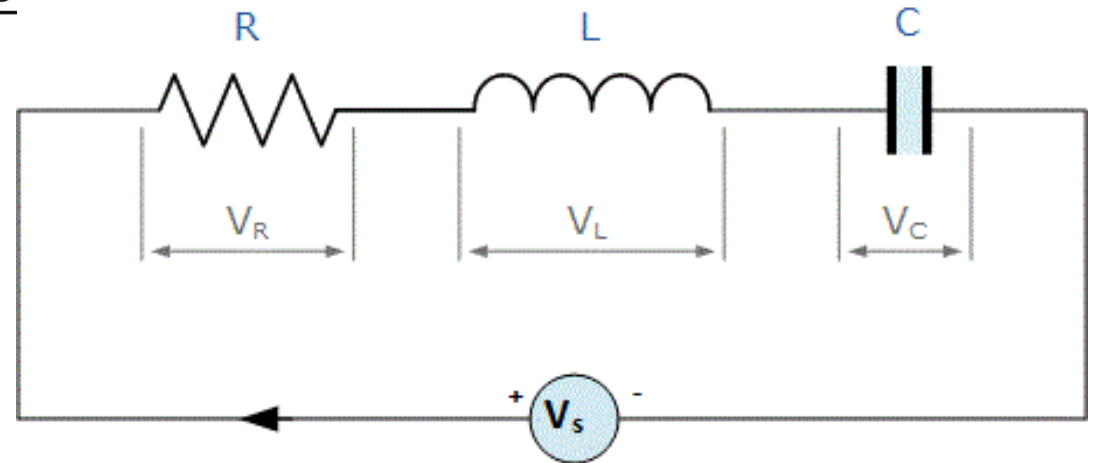

# Example

$V_s(t) = 5e^{-t}$  with  $R = 4 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1/3 \text{ F}$ ,  $i(0)=1 \text{ A}$ ,  $di/dt(0) = 3 \text{ A/s}$ . What is  $i(t)$  for  $t \geq 0$ ?


- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C} = \frac{\alpha^2 + 4\alpha + 3}{\alpha}$$

$$\alpha = -1$$

$$Z(\alpha) = 0$$

$$i(t) = \frac{V_s(t)}{Z(\alpha)} = ??$$

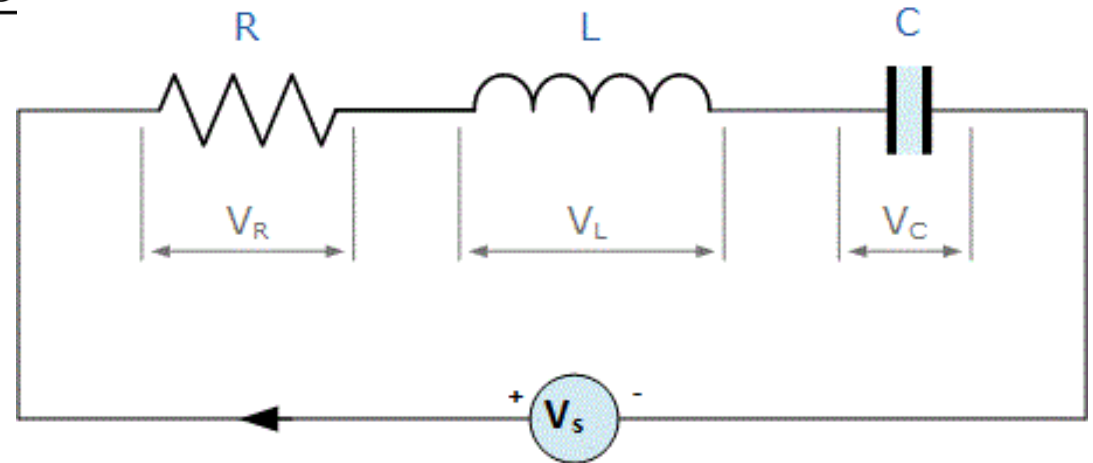

# Example

$V_s(t) = 5e^{-t}$  with  $R = 4 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1/3 \text{ F}$ ,  $i(0)=1 \text{ A}$ ,  $di/dt(0) = 3 \text{ A/s}$ . What is  $i(t)$  for  $t \geq 0$ ?


- The impedance function is

$$Z(\alpha) = \frac{\alpha^2 LC + \alpha RC + 1}{\alpha C} = \frac{\alpha^2 + 4\alpha + 3}{\alpha}$$

$$\alpha = -1$$

$$Z(\alpha) = 0$$

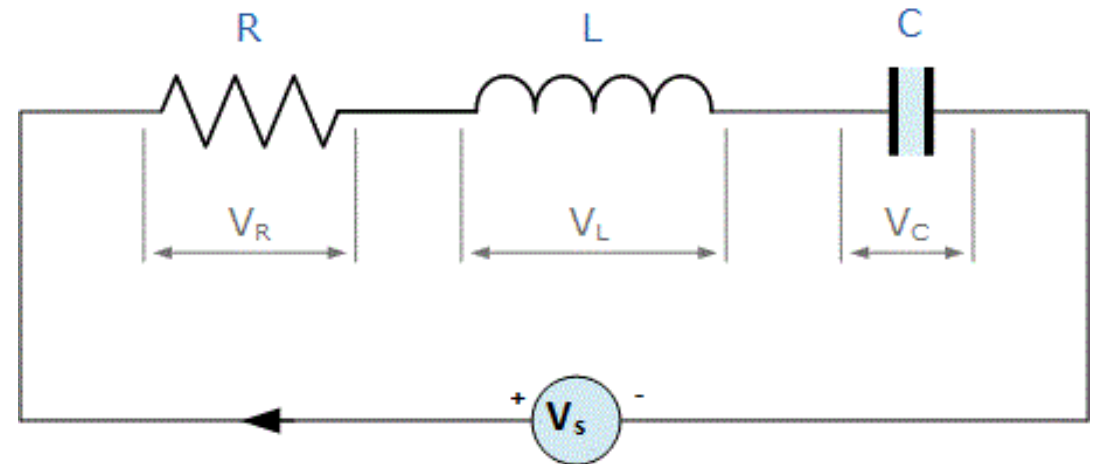- We cannot determine  $i(t)$  using Impedance function.



# What is the problem?

The problem is because the inherent 'exponentials' in the natural response get excited by the source. In the current example, both natural response and source have  $e^{-t}$  component.

# What is the problem?

The problem is because the inherent 'exponentials' in the natural response get excited by the source. In the current example, both natural response and source have  $e^{-t}$  component. In such a case, the actual response of the circuit would have  $e^{-t}$  and  $te^{-t}$ . How is this ?



# Solution to our example

The complete response will be  $(A_1 + A_2 t)e^{-t} + A_3 e^{-3t}$

# Particular Solution and Initial Conditions

- $V_s(t) = 5e^{-t}$  with  $R = 4 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1/3 \text{ F}$ ,  $i(0)=1 \text{ A}$ ,  $di/dt(0) = 3 \text{ A/s}$ .

- $$i(t) = (A_1 + A_2 t)e^{-t} + A_3 e^{-3t}$$
$$\frac{di}{dt} = (-A_1 + A_2 - A_2 t)e^{-t} - 3A_3 e^{-3t}$$
$$\frac{d^2 i}{dt^2} = (A_1 - 2A_2 + A_2 t)e^{-t} + 9A_3 e^{-3t}$$

$$i(0) = A_1 + A_3 = 1$$
$$\frac{di}{dt}(0) = -A_1 + A_2 - 3A_3 = 3$$

# Particular Solution and Initial Conditions

- $V_s(t) = 5e^{-t}$  with  $R = 4 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1/3 \text{ F}$ ,  $i(0)=1 \text{ A}$ ,  $di/dt(0) = 3 \text{ A/s}$ .

- $$i(t) = (A_1 + A_2 t)e^{-t} + A_3 e^{-3t}$$
$$\frac{di}{dt} = (-A_1 + A_2 - A_2 t)e^{-t} - 3A_3 e^{-3t}$$
$$\frac{d^2 i}{dt^2} = (A_1 - 2A_2 + A_2 t)e^{-t} + 9A_3 e^{-3t}$$

$$i(0) = A_1 + A_3 = 1$$
$$\frac{di}{dt}(0) = -A_1 + A_2 - 3A_3 = 3$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = \frac{d}{dt} V_s$$
$$-5e^{-t} = ((A_1 + A_2 t)e^{-t} + A_3 e^{-3t})$$
$$+ 4((-A_1 + A_2 - A_2 t)e^{-t} - 3A_3 e^{-3t})$$
$$+ 3((A_1 - 2A_2 + A_2 t)e^{-t} + 9A_3 e^{-3t})$$
$$= -2A_2 e^{-t} \implies A_2 = 2.5$$

$$A_1 = 1.75, A_2 = 2.5, A_3 = -0.75$$
$$i(t) = (1.75 + 2.5t)e^{-t} - 0.75e^{-3t}$$

# General Procedure

1. Express the source signal as a combination of exponential signals (complex exponents allowed).

# General Procedure

1. Express the source signal as a combination of exponential signals (complex exponents allowed). Let the set of exponents be  $\{a_1, a_2, \dots, a_k\}$ .

# General Procedure

1. Express the source signal as a combination of exponential signals (complex exponents allowed). Let the set of exponents be  $\{a_1, a_2, \dots, a_k\}$ . In our example, we had the input signal as  $5e^{-t}$ , therefore the set is  $\{a_1 = -1\}$ .

# General Procedure

1. Express the source signal as a combination of exponential signals (complex exponents allowed). Let the set of exponents be  $\{a_1, a_2, \dots, a_k\}$ . For our example,  $\{a_1 = -1\}$ .  
Note: Repeated entries will not appear here. However, a signal of type  $t^n e^{at}$  may appear.

# General Procedure

1. Express the source signal as a combination of exponential signals (complex exponents allowed). Let the **set of exponents** be  $\{a_1, a_2, \dots, a_k\}$ . For our example,  $\{a_1 = -1\}$ . Note: Repeated entries will not appear here. However, a signal of type  $t^n e^{at}$  may appear.

For each  $e^{at}$ , find the maximum 'n' such that  $t^n e^{at}$  appears.

Make (n+1) copies of the exponent in the **set of exponents for source**.

Eg:  $(3t^2 + 2)e^{-t} + te^{-2t} + 2e^{-4t} \implies \{-1, -1, -1, -2, -2, -4\}$



# General Procedure

2. Determine the differential equation governing the circuit behavior. Solve for the roots associated polynomial. Let the set be  $\{b_1, b_2, \dots, b_n\}$

# General Procedure

2. Determine the differential equation governing the circuit behavior. Solve for the roots associated polynomial. Let the set be  $\{b_1, b_2, \dots, b_n\}$ . Remember repeated roots deserve repeated mention.

In our example problem, the polynomial is

$$s^2 + 4s + 3 = 0 \quad \implies \quad e^{-t}, e^{-3t}$$

Thus, set corresponding to natural response is  $\{-1, -3\}$

# General Procedure

2. Determine the differential equation governing the circuit behavior. Solve for the roots associated polynomial. Let the set be  $\{b_1, b_2, \dots, b_n\}$  **Remember repeated roots deserve repeated mention.** [In our example this set is  $\{-1, -3\}$ ]
3. Combine both the sets, and count the number of time any entry is repeated.

# General Procedure

2. Determine the differential equation governing the circuit behavior. Solve for the roots associated polynomial. Let the set be  $\{b_1, b_2, \dots, b_n\}$  **Remember repeated roots deserve repeated mention.** [In our example this set was  $\{-1, -3\}$ ]
3. Combine both the sets, and count the number of time any entry is repeated.

$$\{-1\} + \{-1, -3\} \rightarrow \{-1, -1, -3\}$$

# General Procedure

2. Determine the differential equation governing the circuit behavior. Solve for the roots associated polynomial. Let the set be  $\{b_1, b_2, \dots, b_n\}$  **Remember repeated roots deserve repeated mention.** [ In our example this set was  $\{-1, -3\}$  ]
3. Combine both the sets, and count the number of time an entry is repeated. [ $\{-1, -1, -3\}$  in our example]
4. For each entry  $\alpha$  repeated  $k$  times, the response will have

$$(A_{\alpha_1} + A_{\alpha_2}t + \dots + A_{\alpha_k}t^{k-1}) e^{\alpha t}$$

# General Procedure

2. Determine the differential equation governing the circuit behavior. Solve for the roots associated polynomial. Let the set be  $\{b_1, b_2, \dots, b_n\}$  **Remember repeated roots deserve repeated mention.** [ In our example this set is  $\{-1, -3\}$ ]

3. Combine both the sets, and count the number of time an entry is repeated. [ $\{-1, -1, -3\}$  in our example]

4. For each entry  $\alpha$  repeated  $k$  times, the response will have

$$(A_{\alpha_1} + A_{\alpha_2}t + \dots + A_{\alpha_k}t^{k-1}) e^{\alpha t}$$

For our example, complete response was  $(A_1 + A_2t)e^{-t} + A_3e^{-3t}$