

# ELL100: INTRODUCTION TO ELECTRICAL ENGG.



## **Minimization through Karnaugh maps**

**Instructor: Debanjan Bhowmik**

**Textbook: Moris Mano's 'Digital Design'**

**Chapter 3 (Gate-Level Minimization)**
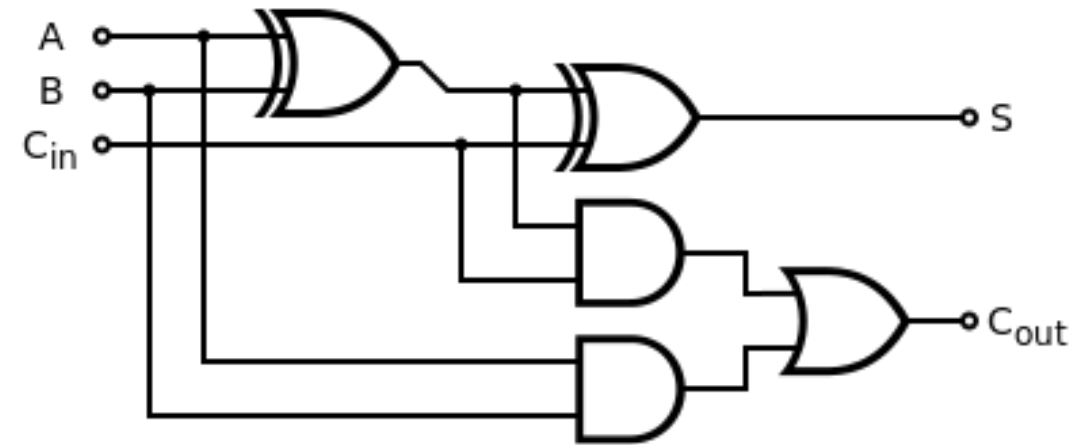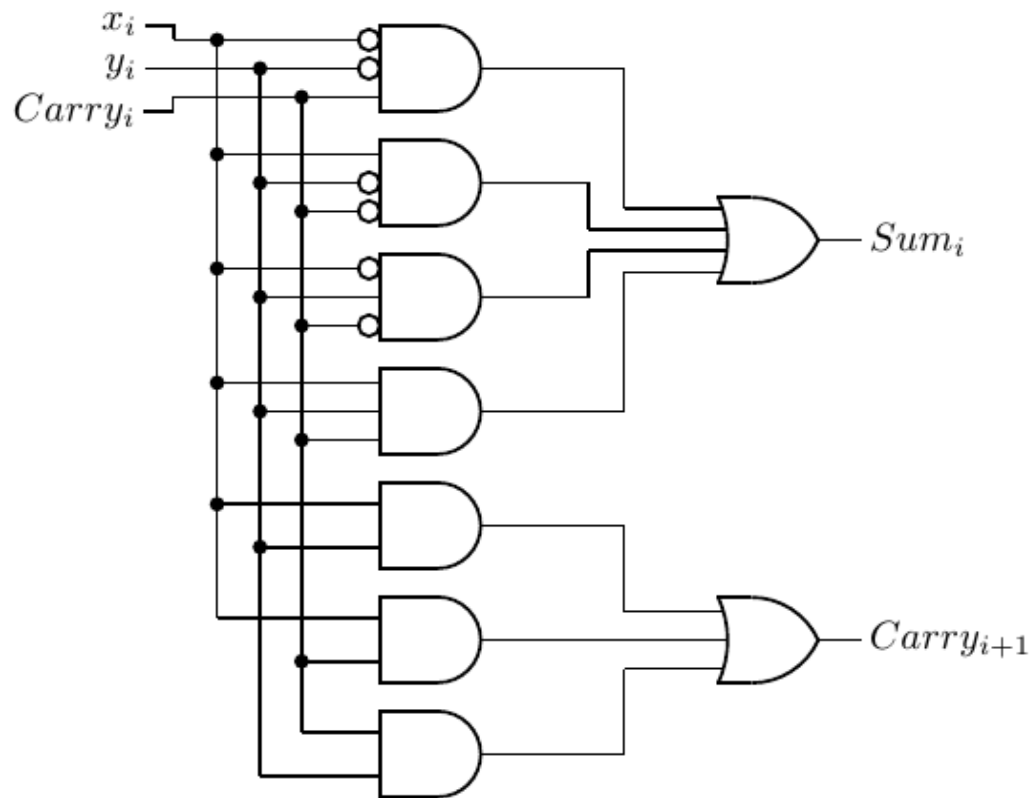
# Multiple Expressions for One Truth Table




It is useful if the same logic can be implemented using lesser number of logic gates and logic levels.

Note: There is more than one way to implement the same logic
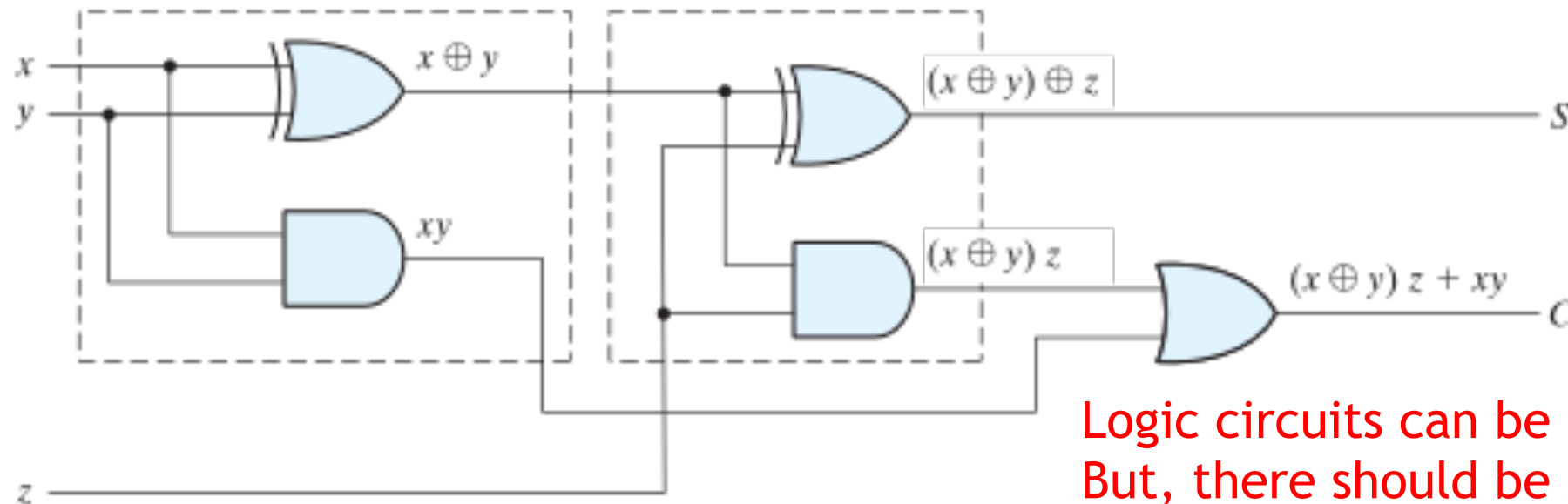
# Simplification is not Simple

$$S = (x \oplus y) \oplus z$$

$$\begin{aligned} C &= xy + yz + xz = xy + (x + y)z \\ &= xy + (x(y + y') + (x + x')y)z = xy + (xy + x \oplus y)z \\ &= xy + xyz + (x \oplus y)z = xy + (x \oplus y)z \end{aligned}$$



Logic circuits can be simplified.  
But, there should be some  
systematic approach.

# Karnaugh Map

- **Karnaugh Map:** A graphical and systematic way to obtain simplest expression for a truth table

# Definitions

Some definitions:

$$\begin{aligned} C(x, y, z) &= \boxed{\begin{aligned} &x'yz + xy'z \\ &+xyz' + xyz \end{aligned}} \\ &= \boxed{xy + yz + xz} \end{aligned}$$

Sum of Products (SOP)  
representation  
Derived from entries where the  
Output is 1 (TRUE)

$$\begin{aligned} C(x, y, z) &= \boxed{\begin{aligned} &(x' + y + z)(x + y' + z) \dots \\ &(x + y + z')(x + y + z) \end{aligned}} \\ &= \boxed{(x + y)(y + z)(x + z)} \end{aligned}$$

Product of Sums (POS)  
representation  
Derived from entries where the  
Output is 0 (FALSE)

# Definitions

Some definitions:

$$\begin{aligned} C(x, y, z) &= \boxed{\begin{aligned} &x'yz + xy'z \\ &+xyz' + xyz \end{aligned}} \\ &= xy + yz + xz \end{aligned}$$

Canonical Sum of Products (SOP)  
representation. All inputs present  
in all terms

$$\begin{aligned} C(x, y, z) &= \boxed{\begin{aligned} &(x' + y + z)(x + y' + z) \dots \\ &(x + y + z')(x + y + z) \end{aligned}} \\ &= (x + y)(y + z)(x + z) \end{aligned}$$

Canonical Product of Sums (POS)  
representation. All inputs present  
in all terms

# Definitions

Some definitions:

$$\begin{aligned} C(x, y, z) &= x'yz + xy'z \\ &\quad +xyz' + xyz \\ &= \boxed{xy + yz + xz} \end{aligned}$$

Minimal Sum of Products (SOP) representation. Cannot have a shorter SOP form.

$$\begin{aligned} C(x, y, z) &= (x' + y + z)(x + y' + z) \dots \\ &\quad (x + y + z')(x + y + z) \\ &= \boxed{(x + y)(y + z)(x + z)} \end{aligned}$$

Minimal Product of Sums (POS) representation. Cannot have a shorter POS form.

# Definitions

Some definitions:

$$\begin{aligned} C(x, y, z) &= \boxed{x'yz} + \boxed{xy'z} \\ &\quad + \boxed{xyz'} + \boxed{xyz} \\ &= xy + yz + xz \end{aligned}$$

Minterm: Each of the terms in a canonical SOP form

$$\begin{aligned} C(x, y, z) &= \boxed{(x' + y + z)} \boxed{(x + y' + z)} \dots \\ &\quad \boxed{(x + y + z')} \boxed{(x + y + z)} \\ &= (x + y)(y + z)(x + z) \end{aligned}$$

Maxterm: Each of the terms in a canonical POS form



# Definitions

Some definitions:

$$\begin{aligned}C(x, y, z) &= x'yz + xy'z \\ &\quad +xyz' + xyz \\ &= xy + yz + xz \\ &= m_3 + m_5 + m_6 + m_7\end{aligned}$$

If the inputs are ordered, then minterms can be indexed.

$$\begin{aligned}xy'z &\rightarrow m_{101_2} \rightarrow m_5 \\ (x = 1, y = 0, z = 1) &\implies (C = 1)\end{aligned}$$

$$\begin{aligned}C(x, y, z) &= (x' + y + z)(x + y' + z) \dots \\ &\quad (x + y + z')(x + y + z) \\ &= (x + y)(y + z)(x + z) \\ &= M_4M_2M_1M_0\end{aligned}$$

If inputs are ordered, then maxterms can be indexed.

$$\begin{aligned}(x + y' + z) &\rightarrow M_{010_2} \rightarrow M_2 \\ (x = 0, y = 1, z = 0) &\implies (C = 0)\end{aligned}$$

# Definitions

Some definitions:

$$\begin{aligned}C(x, y, z) &= x'yz + xy'z \\ &\quad + xyz' + xyz \\ &= xy + yz + xz \\ &= m_3 + m_5 + m_6 + m_7\end{aligned}$$

If the inputs are ordered, then minterms can be indexed.

$$C(x, y, z) = \sum m(3, 5, 6, 7)$$

$$\begin{aligned}C(x, y, z) &= (x' + y + z)(x + y' + z) \dots \\ &\quad (x + y + z')(x + y + z) \\ &= (x + y)(y + z)(x + z) \\ &= M_4 M_2 M_1 M_0\end{aligned}$$

If inputs are ordered, then maxterms can be indexed.

$$C(x, y, z) = \prod M(0, 1, 2, 4)$$

# Karnaugh Map

- **Karnaugh Map:** A graphical and systematic way to obtain simplest expression for a truth table (K-Map)
- The map is made up of squares, with **each square** representing **one minterm** of the function
- This produces a circuit diagram with a minimum number of gates and the minimum number of inputs to the gate
- It is sometimes possible to find two or more expressions that satisfy the minimization criteria

# Two Variable Map

- Two-variable has four minterms, and consists of four squares.
- $m_1 + m_2 + m_3 = x'y + xy' + xy = x + y$
- $\uparrow$

$m_0$	$m_1$
$m_2$	$m_3$

		$y$	
		0	1
$x$	0	$x'y'$	$x'y$
	1	$xy'$	$xy$

ffe

		$y$	
		0	1
$x$	0		
	1		1

(a)  $xy$

		$y$	
		0	1
$x$	0		1
	1	1	1

(b)  $x + y$

# Three Variable Map

- Note that the **minterms** are not **arranged** in a binary sequence.
- For simplifying Boolean functions, we must recognize the basic property possessed by **adjacent squares**.
- $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

cancel

		$y \quad z$				
			00	01	11	10
$x$	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$	
$x$	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$	
		$y \quad z$				


The diagram illustrates the simplification of the Boolean expression  $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$ . The Karnaugh map shows the minterms  $m_5$  and  $m_7$  (represented by the terms  $xy'z$  and  $xyz$ ) are adjacent in the map. These two terms are grouped together, and the common factor  $xz$  is identified. The variable  $y$  is shown to be canceled out because it appears in both terms with opposite phases ( $y'$  and  $y$ ), resulting in the simplified expression  $xz$ .

# Simplification

- A larger number of adjacent squares are combined, we obtain a product term with fewer literals.
  - 1 square = 1 term with three literals
  - 2 adjacent squares = 1 term with two literals
  - 4 adjacent squares = 1 term with one literal
  - 8 adjacent squares encompass the entire map and produce a function that is always equal to 1
- The number of adjacent squares is combined in a power of two such as 1, 2, 4, and 8.

# Example 1

$$F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$$

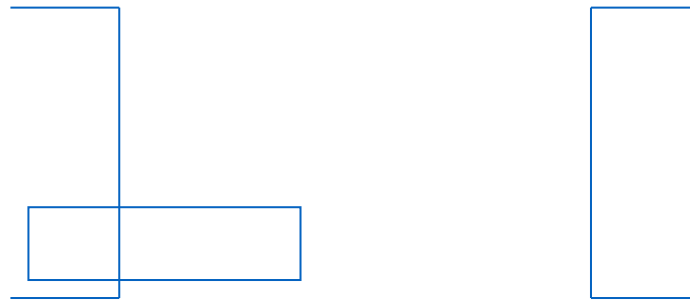

## Example 2

Design the minimal product-of-sums expression for the function

$$f(x_1, x_2, x_3) = \Sigma m(0, 2, 4, 5, 6, 7)$$



# Minterms and Maxterms

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

# Minterms and Maxterms

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

**The function is  
1 for these rows**

# Minterms and Maxterms

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7) = \prod M(1, 3)$$

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

**The function is  
1 for these rows**

**The function is  
0 for these rows**

# Minterms and Maxterms

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7) = \prod M(1, 3)$$

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

$$f(x_1, x_2, x_3) = \prod M(1, 3) = (x_1 + x_2 + \bar{x}_3) \cdot (x_1 + \bar{x}_2 + \bar{x}_3)$$

# The K-Map

$x_3 \backslash x_1 x_2$		00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$	
1	$m_1$	$m_3$	$m_7$	$m_5$	

# The K-Map

$x_3 \backslash x_1 x_2$					
		00	01	11	10
0	1	1	1	1	1
1	0	0	1	1	

# The K-Map - Solution

$x_1x_2$ $x_3$		00	01	11	10
0	1	1	1	1	1
1	0	0	1	1	1

$F = 0$  when  $x_1=0$  AND  $x_3=1$

$F = 1$  when  $x_1=1$  OR  $x_3=0$   
(De Morgan's theorems)

$(x_1 + \bar{x}_3)$

# 4 Variable Map

1 square = 1 term with 4 literals

2 adjacent squares = 1 term with 3 literals

4 adjacent squares = 1 term with 2 literals

8 adjacent squares = 1 term with 1 literal

16 adjacent squares = 1

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

		$yz$		$y$	
		0 0	0 1	1 1	1 0
$w$	$wx$	0 0	0 1	1 1	1 0
	0 0	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	0 1	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	1 1	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	1 0	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		$z$			

$x$




# 4 Variable Map Example

$$F = \sum m(0, 1, 2, 6, 8, 9, 10)$$

		<i>CD</i>		<i>C</i>	
<i>AB</i>		00	01	11	10
<i>A</i>	00	1	1		1
	01				1
	11				
	10	1	1		1
		<i>D</i>		<i>B</i>	

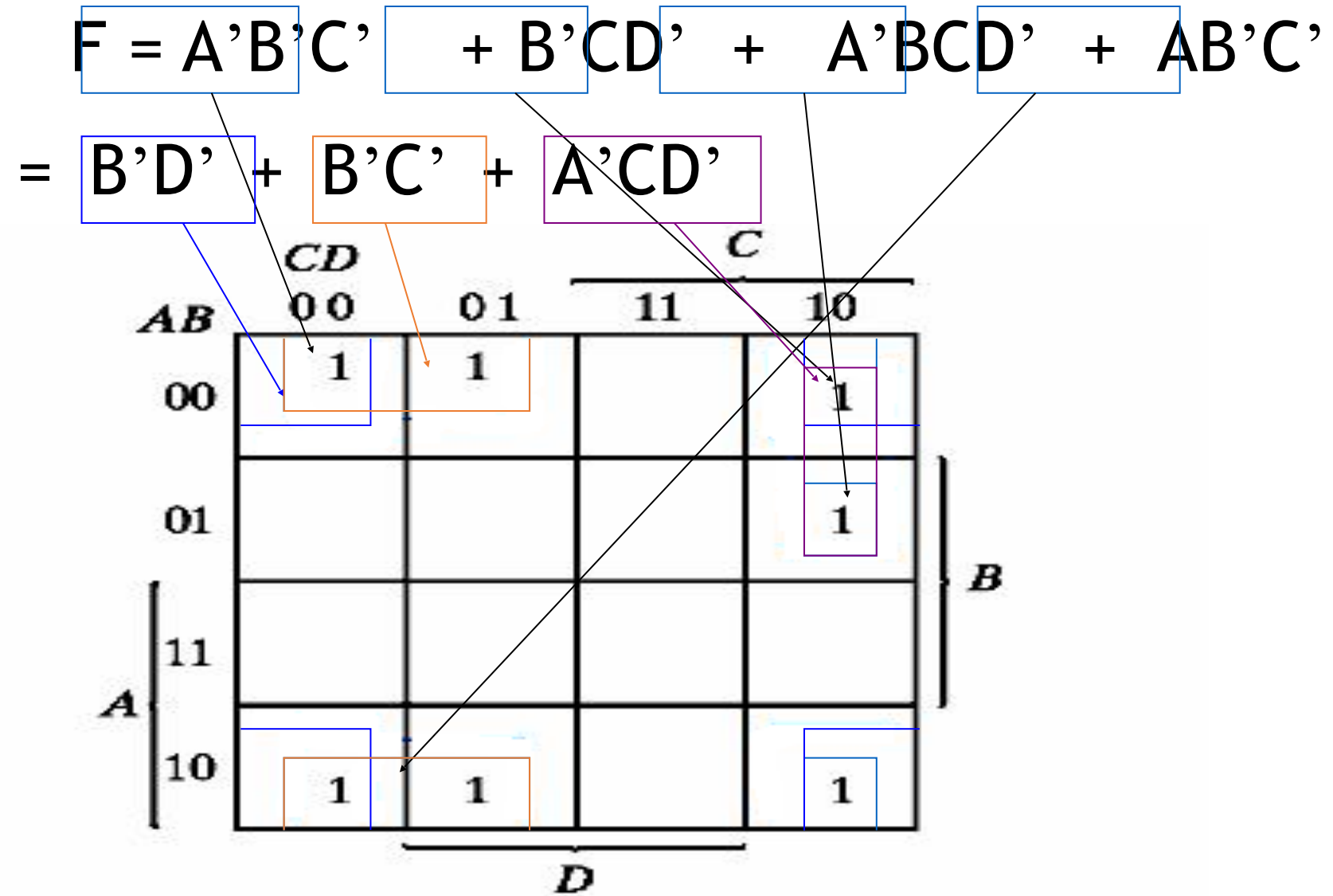
# 4 Variable Map Example $F = \sum m(0, 1, 2, 6, 8, 9, 10)$


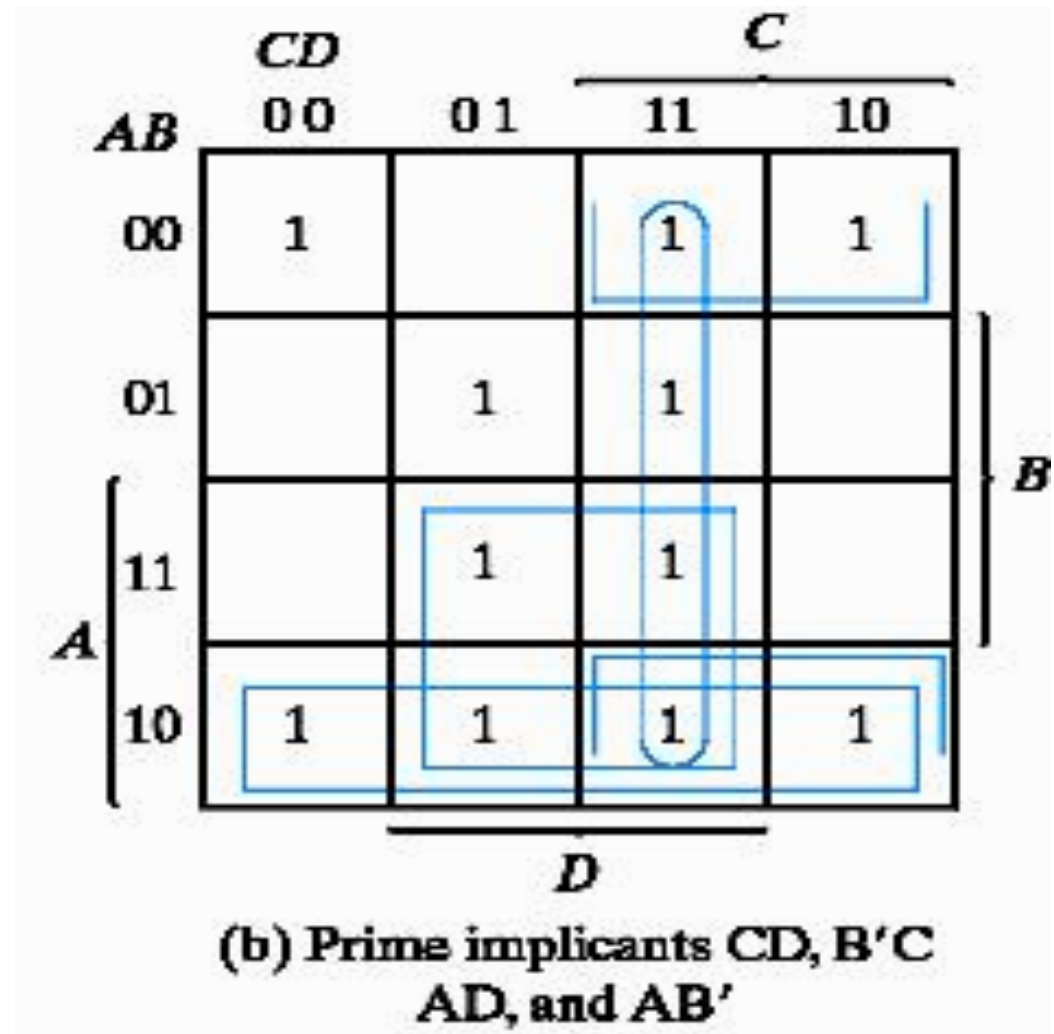
# Prime Implicant

- A **prime implicant** is a product term obtained by combining the maximum possible number of adjacent squares in the map.
- This shows all possible ways that the three minterms ( $m_3, m_9, m_{11}$ ) can be **covered with prime implicants**.

$$\begin{aligned}
 F &= BD + B'D' + \textcolor{red}{CD} + \textcolor{red}{AD} \\
 &= BD + B'D' + \textcolor{red}{CD} + \textcolor{red}{AB}' \\
 &= BD + B'D' + \textcolor{red}{B}'\textcolor{red}{C} + \textcolor{red}{AD} \\
 &= BD + B'D' + \textcolor{red}{B}'\textcolor{red}{C} + \textcolor{red}{AB}'
 \end{aligned}$$



Note: A Prime implicant is never completely covered by another prime implicant.

# Essential Prime Implicant

- If a minterm in a square is covered by only one prime implicant, then the prime implicant is said to be essential.
- $F = BD + B'D'$

