



ELL100: INTRODUCTION TO ELECTRICAL ENGG.

Adder and Subtractor Circuits

Instructor for this part: Debanjan Bhowmik, Assistant Professor,
Department of Electrical Engineering, IIT Delhi

Contact : debanjan@ee.iitd.ac.in

Textbook: Moris Mano's 'Digital Design':

Chapter 4.5 Binary Adder - Subtractor

Logic Circuits: Half Adder

- **Half Adder:** Sums two binary digits. Gives out sum (S) and carry (C) bits.

Half Adder

<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy'$$


$$C = xy$$

Logic Circuits: Half Adder

- **Half Adder:** Sums two binary digits. Gives out sum (S) and carry (C) bits.

Half Adder

<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


(a) $S = xy' + x'y$
 $C = xy$

Logic Circuits: Half Adder


- **Half Adder:** Sums two binary digits. Gives out sum (S) and carry (C) bits.

Half Adder


<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

(b) $S = x \oplus y$
 $C = xy$

 


Logic Circuits: Full Adder

 

- **Half Adder** can only accept 2 input bits
- If two n-bit binary numbers are to be added, there can be carry-in bit also
- **Full Adder** makes provision for carry in bit


Logic Circuits: Full Adder

 

Full Adder

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Logic Circuits: Full Adder

 


Full Adder

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x'y'z + x'yz' + xy'z' + xyz$$

Output is 1 when an odd number of inputs are 1

Logic Circuits: Full Adder

 

Full Adder


x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$S = x'(y'z + yz') + x(y'z' + yz) = x'(y \oplus z) + x(y \oplus z)' = x \oplus y \oplus z$$

Distributive

Logic Circuits: Full Adder

 


Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C = x'yz + xy'z + xyz' + xyz$$

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

Logic Circuits: Full Adder

 


Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 C &= x'y z + x y' z + x y z' + x y z \\
 &= x'y z + x y z + x y' z + x y z + x y z' + x y z \quad \text{Idempotence}
 \end{aligned}$$

$$S = x'y'z + x'y z' + x y' z' + x y z = x \oplus y \oplus z$$

Logic Circuits: Full Adder

 

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




$$\begin{aligned}
 C &= x'yz + xy'z + xyz' + xyz \\
 &= (x' + x)yz + x(y' + y)z + xy(z' + z) \\
 &= xy + yz + xz
 \end{aligned}$$

Distributive

Complement


$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

Full Adder: Logic Gates

   


It is useful if the same logic can be implemented using lesser number of logic gates and logic levels.

Full Adder using Half Adder

 

$$S = (x \oplus y) \oplus z$$


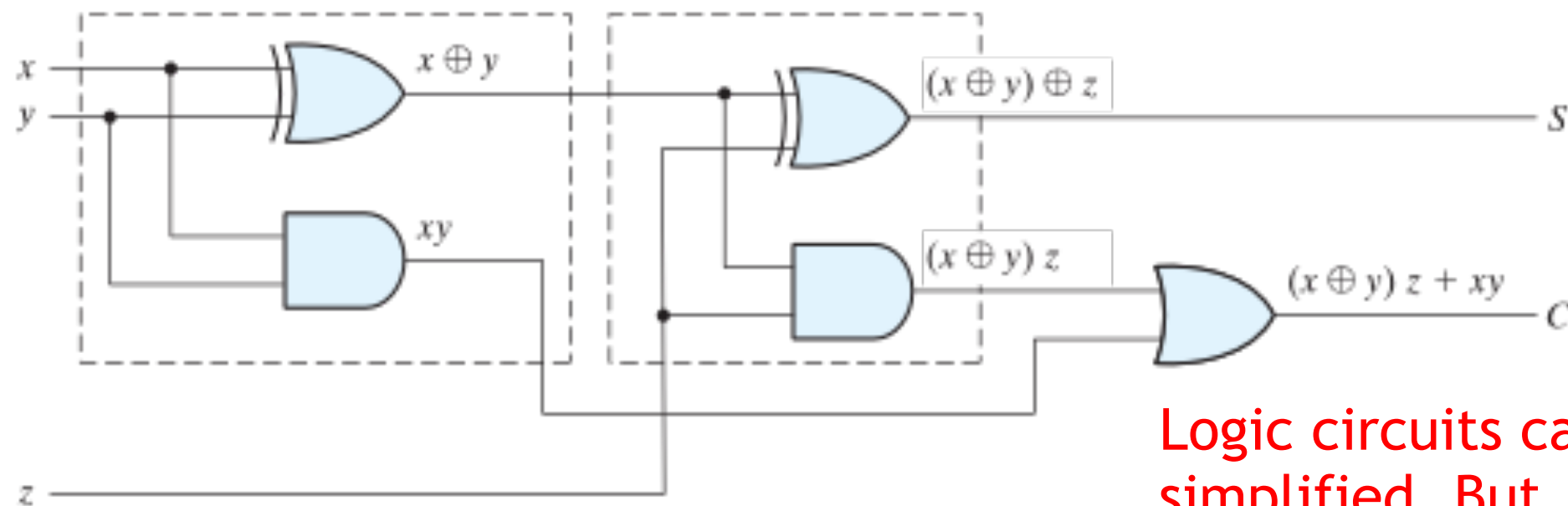
$$\begin{aligned} C &= xy + yz + xz = xy + (x + y)z \\ &= xy + (x(y + y') + (x + x')y)z = xy + (xy + x \oplus y)z \\ &= xy + xyz + (x \oplus y)z = xy + (x \oplus y)z \end{aligned}$$



Logic circuits can be simplified. But, there should be some systematic approach.

4 Bit Binary Adder
  
$$\begin{array}{r}
 A_3A_2A_1A_0 \leftarrow C_0 \\
 + \quad B_3B_2B_1B_0 \\
 \hline
 \\
 \hline
 C_4S_3S_2S_1S_0
 \end{array}$$



4 Bit Binary Adder+Subtractor

$$\begin{array}{r} A_3A_2A_1A_0 \leftarrow C_0 \\ +/\ - \ B_3B_2B_1B_0 \\ \hline \end{array}$$

$$\begin{array}{r} C_4S_3S_2S_1S_0 \\ \hline \end{array}$$

1. Need a selection bit to select between the 2 operations - ADD or SUB
2. If SUB, then first Flip all the bits of B, and find B'
3. Add B' to A (like the normal ADDER)
4. Add 1 to the Sum

