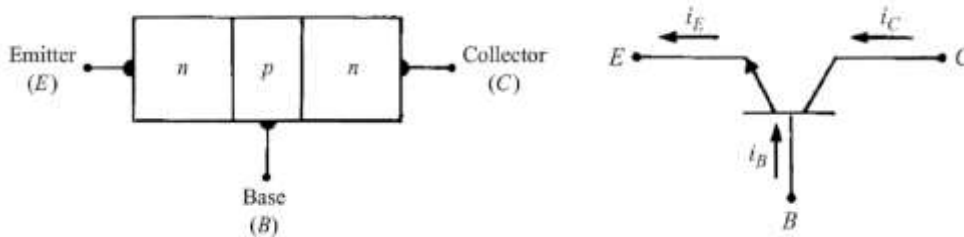


1. In a npn transistor, 10^8 holes/ μ s move from the base to the emitter region while 10^{10} electrons/ μ s move from the emitter to the base region. An ammeter reads the base current as $I_B = 16\mu A$.

- a) Determine the emitter current I_E and the collector current I_C .



The emitter current is found out as the net rate of flow of positive charge into the emitter region:

$$\begin{aligned} I_E &= (1.602 \times 10^{-19} \text{ C / hole})(10^8 \text{ holes / } \mu\text{s}) - (-1.602 \times 10^{-19} \text{ C / electron})(10^{10} \text{ holes / } \mu\text{s}) \\ &= (1.602 \times 10^{-19} \text{ C / hole})(10^{14} \text{ holes / s}) - (-1.602 \times 10^{-19} \text{ C / electron})(10^{16} \text{ holes / s}) \\ &= 1.602 \times 10^{-5} + 1.602 \times 10^{-3} \end{aligned}$$

$$I_E = 1.61802 \text{ mA}$$

Further, by KCL,

$$I_C = I_E - I_B = 1.618 \times 10^{-3} - 16 \times 10^{-6} = 1.602 \text{ mA}$$

Therefore, emitter current, $I_E = 1.618 \text{ mA}$ and collector current, $I_C = 1.602 \text{ mA}$

- b) For the previous example, find the α and β , if the leakage currents are considered negligible, and the described charge flow is constant.

Given data: npn transistor, $I_B = 16\mu A$, $I_E = 1.618 \text{ mA}$, $I_C = 1.602 \text{ mA}$

If we assume $I_{CBO} = I_{CEO} = 0$, then

$$\alpha = \frac{I_C}{I_E} = \frac{I_E - I_B}{I_E} = \frac{1.618 - 0.016}{1.618} = 0.9901$$

$$\beta = \frac{I_C}{I_B} = \frac{I_E - I_B}{I_B} = \frac{1.618 - 0.016}{0.016} = 100.125$$

$$\beta = \frac{\alpha}{1 - \alpha} \text{ gives the same result.}$$

Therefore, gains, $\alpha = 0.9901$ and $\beta = 100.125$

2. A BJT has $\alpha=0.99$, Base current, $I_B=25\mu A$, Leakage current, $I_{CBO} = 200nA$

Find the following parameters:

- DC collector Current
- DC emitter Current
- % Error in the emitter current when the leakage current is neglected.

a) With $\alpha = 0.99$,

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = 99$$

$$I_C = \beta I_B + (\beta + 1)I_{CBO} = 99(25 \times 10^{-6}) + (99 + 1)(200 \times 10^{-9}) = 2.495mA$$

b) The dc emitter current (I_E) is

$$I_E = \frac{I_C - I_{CBO}}{\alpha} = \frac{2.495 \times 10^{-3} - 200 \times 10^{-9}}{0.99} = 2.52mA$$

c) Neglecting the leakage current, we have


$$I_C = \beta I_B = 99(25 \times 10^{-6}) = 2.475mA$$

$$I_E = \frac{I_C}{\alpha} = \frac{2.475}{0.99} = 2.5mA$$

giving an emitter current error of

$$\frac{2.52 - 2.5}{2.5} \times 100\% = 0.793\%$$

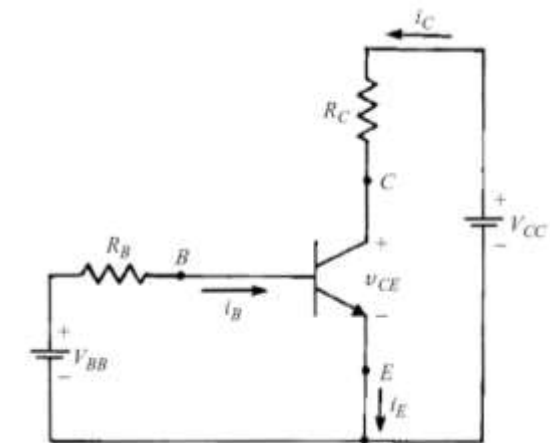3. In the circuit of Figure, $\beta = 100$; $I_{BQ} = 20\mu A$, $V_{CC}=15V$ and $R_C = 3k$. If $I_{CBO} = 0$, find (a) I_{EQ} b) V_{CEQ} . (c) Find V_{CEQ} if R_C is changed to $6k\Omega$ and all else remains the same.



a) From $\alpha = \frac{\beta}{1+\beta} = 0.9901$

Now, with $I_{CBO}=I_{CEO}=0$, we get

$$I_{CQ} = \beta I_{BQ} = 2mA$$

$$I_{EQ} = \frac{I_{CQ}}{\alpha} = \frac{2mA}{0.9901} = 2.02mA$$


b) From an application of KVL around the collector circuit,

$$V_{CEQ} = V_{CC} - I_{CQ}R_C = 15 - (2mA \times 3k) = 9V$$

c) If I_{BQ} is unchanged, then I_{CQ} is unchanged.

$$V_{CEQ} = V_{CC} - I_{CQ}R_C = 15 - (2mA \times 6k) = 3V$$

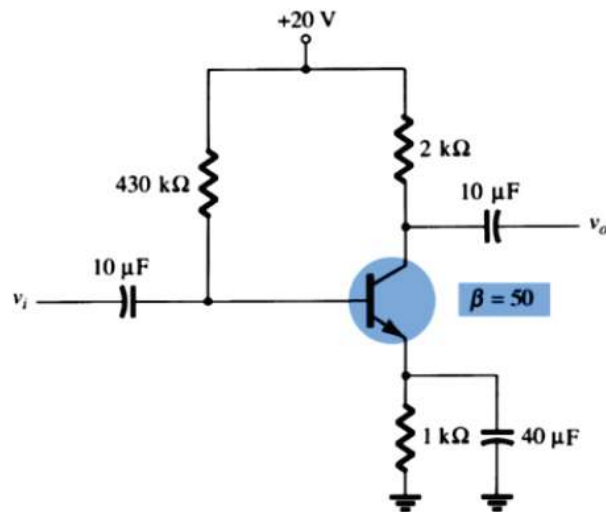4. For the emitter bias circuit shown below, determine collector current I_C (in mA). Assume $V_{BE} = 0.7$ V



Consider the unit of I_C , I_B in mA

$$V_E = I_E \times (1 \text{ k}\Omega) = (I_C + I_B) \times 1 \text{ k}\Omega = I_C + I_B = (1 + \beta) I_B = 51 I_B$$


$$V_B = 20 - 430 I_B$$

$$V_B - V_E = 0.7 \text{ V}$$

$$\Rightarrow 20 - 430 I_B - 51 I_B = 0.7$$

$$\Rightarrow I_C = 50 I_B = 2.006$$

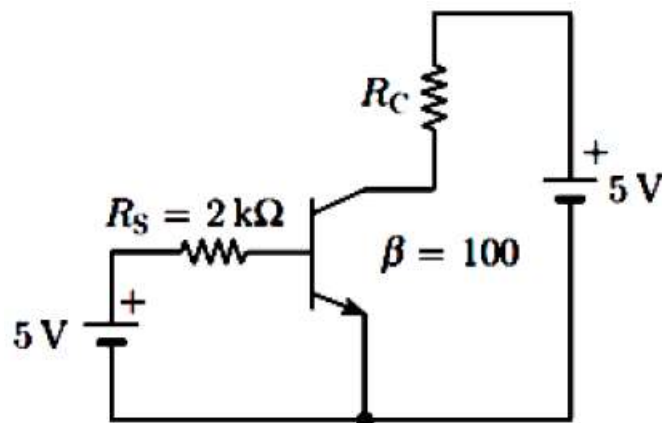5. The transistor in the given circuit should always be in the active region. Take $V_{CE(\text{Sat})} = 0.2$ V, $V_{BE} = 0.7$ V. What is the maximum value of R_C in Ω which can be used?




$$5 - R_S I_B = V_{BE} = 0.7$$

$$\Rightarrow I_C = 100 I_B = (100 \times 4.3 / 2) \text{ mA} = 0.215 \text{ A}$$

$$5 - R_C I_C = V_{CE} > 0.2$$

$$\Rightarrow R_C < 4.8 / I_C = 22.32 \text{ }\Omega$$

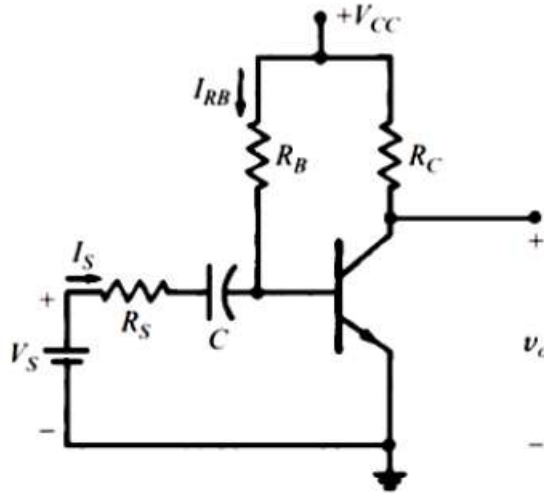6. In the circuit of given figure $V_{CC} = 12\text{ V}$, $V_S = 2\text{ V}$, $R_C = 4\text{ k}\Omega$, and $R = 100\text{ k}\Omega$. The Ge transistor is characterized by $\beta = 50$; $I_{CEO} = 0$, and $V = 0.2\text{ V}$. Find the value of R (in $\text{k}\Omega$) that just results in saturation if the capacitor is replaced with a short circuit. V_{BE} for germanium transistor = 0.3 V



$$V_B = 2 - 100 I_S$$

$$\Rightarrow I_S = 0.017\text{ mA}$$

$$I_C = \beta (I_S + (12 - 0.3)/R_B) = 12 - V_{CE} / 4$$

$$\Rightarrow R_B = 278.57\text{ k}\Omega$$