



# ELL100: INTRODUCTION TO ELECTRICAL ENGG.

## **Complete Response - I**

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik, Harshan  
Jagadeesh


Department of Electrical Engineering, IITD

# Complete Response


- Natural response
  - Energy storage elements
  - The form of natural response is governed by circuit itself
- Forced response
  - External sources, e.g., batteries or generators
  - The amplitude of forced response is determined by the magnitude of the forcing function and impedance
- Complete response = Natural response + Forced response

# Step response of RL circuit

Find  $i$  for  $t \geq 0$

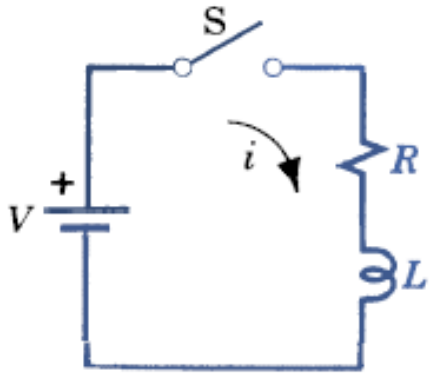


(a) Circuit

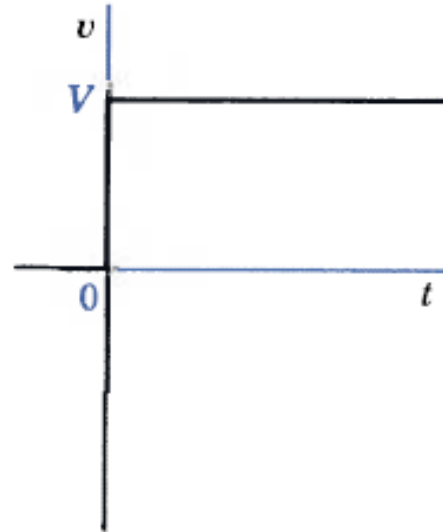


(b) Applied voltage

# Step response of RL circuit

Find  $i$  for  $t \geq 0$

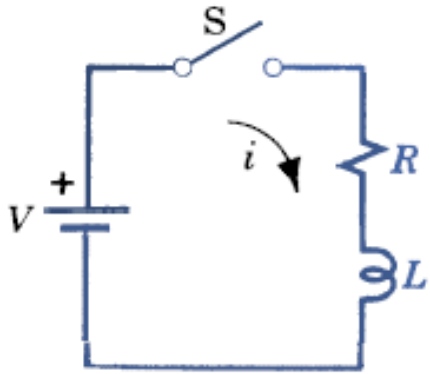

(a) Circuit

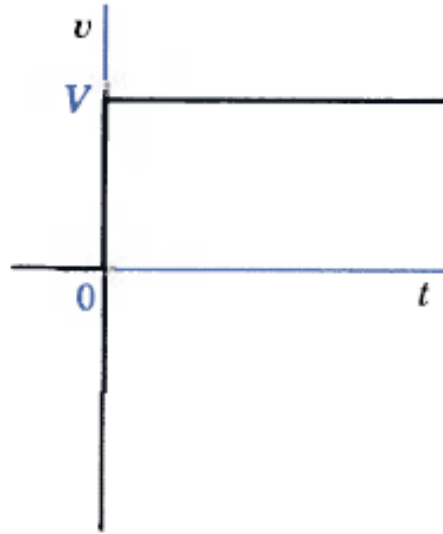


(b) Applied voltage

1. Write the impedance function


$$Z(s) = R + sL$$

# Step response of RL circuit

Find  $i$  for  $t \geq 0$

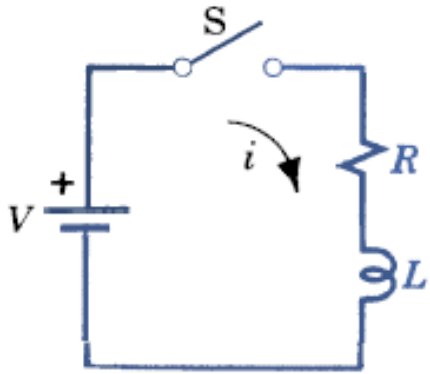

(a) Circuit

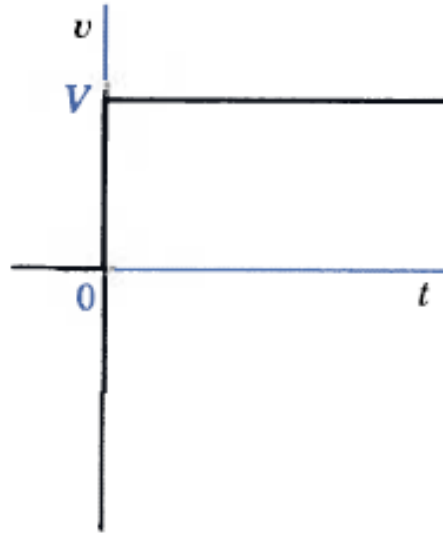

(b) Applied voltage

1. Write the impedance function


$$Z(s) = R + sL$$

2. Determine forced response: DC  $\Rightarrow s = 0$


$$Z(s)|_{s=0} = R, i_f = V/R$$

# Step response of RL circuit

Find  $i$  for  $t \geq 0$

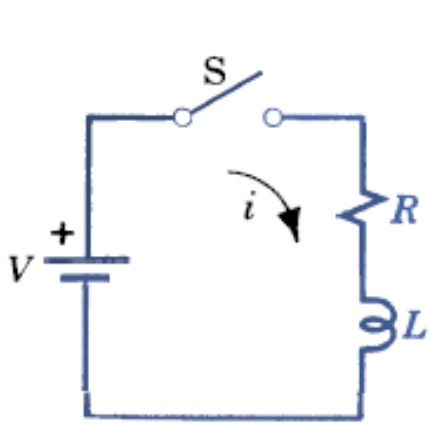

(a) Circuit

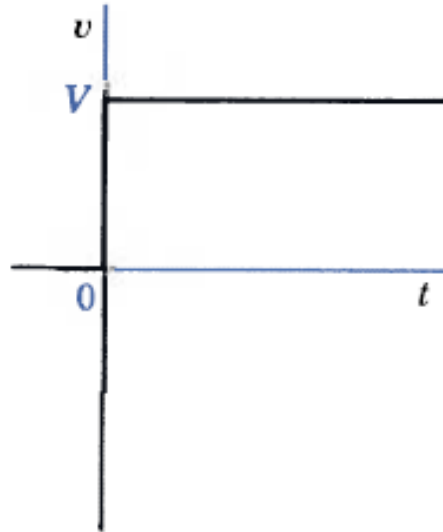

(b) Applied voltage

1. Write the impedance function

$$Z(s) = R + sL$$

2. Determine forced response: DC  $\Rightarrow s = 0$


$$Z(s)|_{s=0} = R, i_f = V/R$$

3. Identify natural component: short circuited,  $Z(s) = 0 \Rightarrow s = -\frac{R}{L}$


$$i_n = Ae^{-\frac{R}{L}t}$$

# Step response of RL circuit

Find  $i$  for  $t \geq 0$

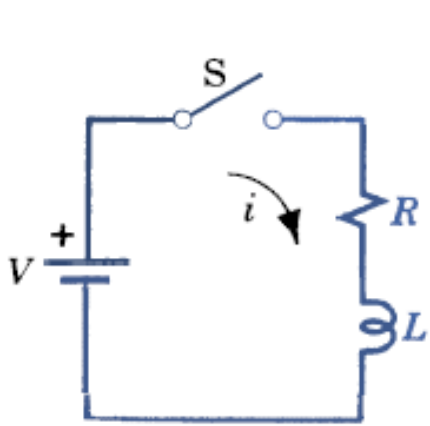

(a) Circuit

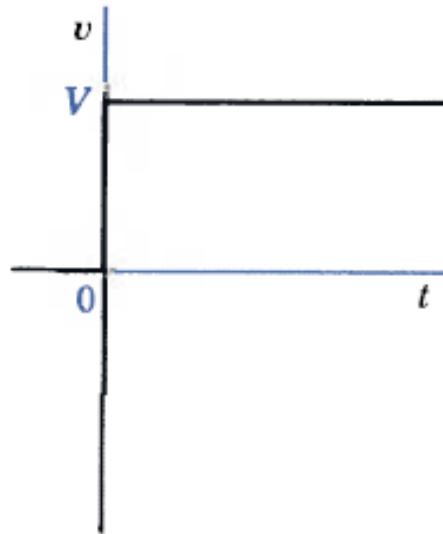

(b) Applied voltage

1. Write the impedance function

$$Z(s) = R + sL$$

2. Determine forced response: DC  $\Rightarrow s = 0$

$$Z(s)|_{s=0} = R, i_f = V/R$$

3. Identify natural component: short circuited,  $Z(s) = 0 \Rightarrow s = -\frac{R}{L}$

$$i_n = Ae^{-\frac{R}{L}t}$$


4. Evaluate the undetermined constants

$$i = i_f + i_n = \frac{V}{R} + Ae^{-\frac{R}{L}t} \Rightarrow$$


$$i = 0 \text{ @ } t = 0: A = -\frac{V}{R}$$

# Step response of RL circuit

Find  $i$  for  $t \geq 0$

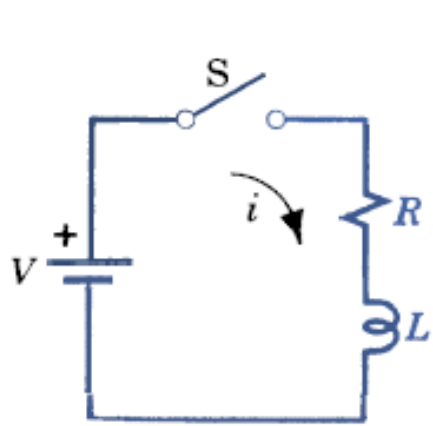

(a) Circuit

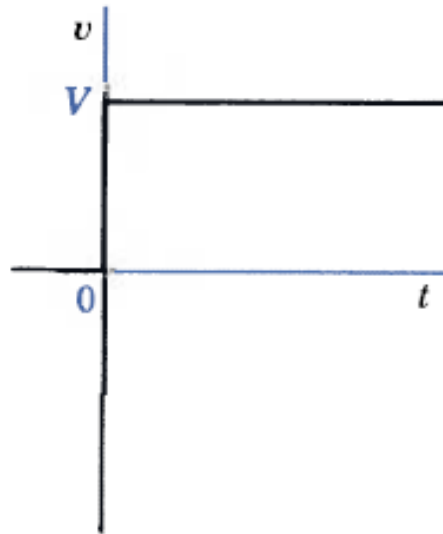

(b) Applied voltage

1. Write the impedance function

$$Z(s) = R + sL$$

2. Determine forced response: DC  $\Rightarrow s = 0$

$$Z(s)|_{s=0} = R, i_f = V/R$$


3. Identify natural component: short circuited,  $Z(s) = 0 \Rightarrow s = -\frac{R}{L}$

$$i_n = Ae^{-\frac{R}{L}t}$$

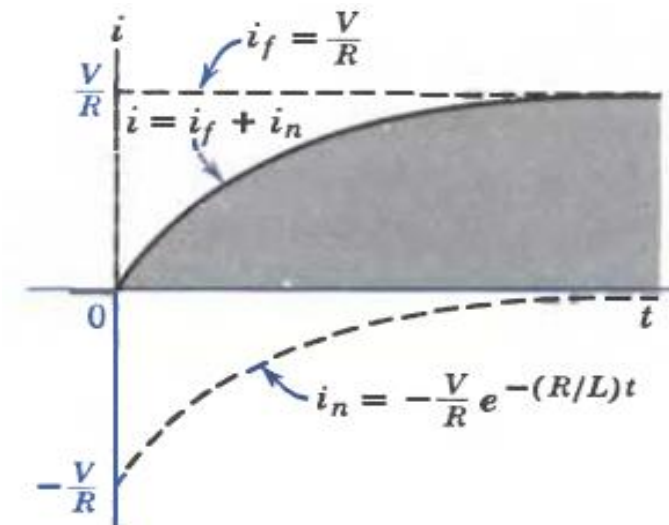4. Evaluate the undetermined constants

$$i = i_f + i_n = \frac{V}{R} + Ae^{-\frac{R}{L}t} \Rightarrow$$

$$i = 0 \text{ @ } t = 0: A = -\frac{V}{R}$$






# Complete Response

- Write the impedance function (or admittance)
- Determine the forced response from the forcing function
- Identify the natural response from poles and zeros with undetermined constants
- Add the forced and natural responses and evaluate the undetermined constants
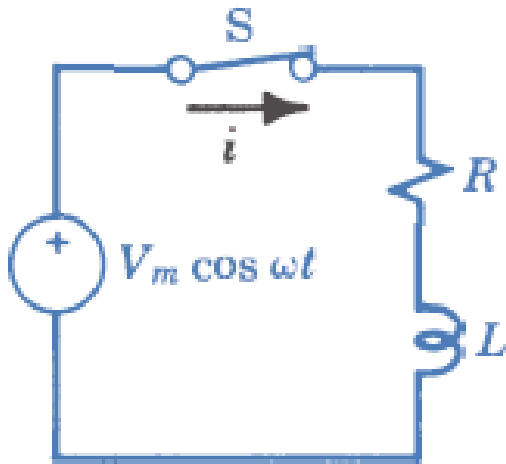
# Complete Response

Suppose that the switch is closed at  $t = 0$



# Complete Response

Suppose that the switch is closed at  $t = 0$

For  $t \geq 0$  (forced response)

$$L \frac{di}{dt} + Ri = V_m \cos \omega t$$


$$i_f = I_m \cos(\omega t + \phi)$$

For  $t \leq 0$  (natural response)


$$L \frac{di}{dt} + Ri = 0$$

$$i_n = I_n e^{-(R/L)t}$$
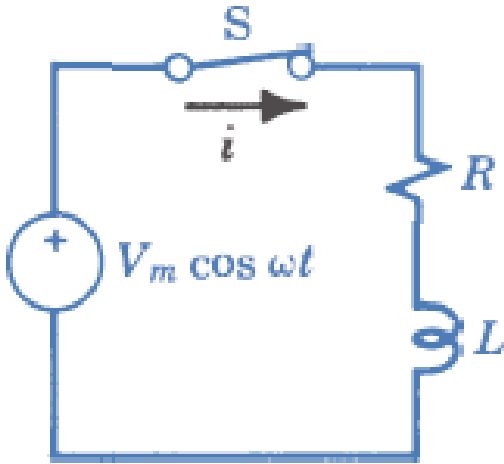
$$i = i_n + i_f = I_m \cos(\omega t + \phi) + I_n e^{-(R/L)t}$$




# Example

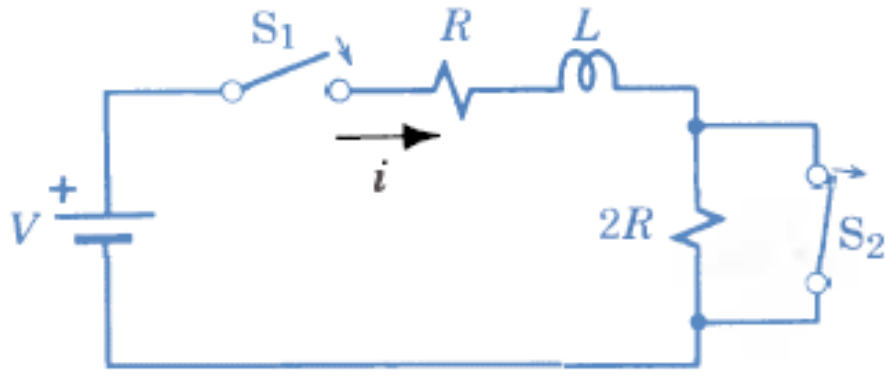

- For  $t < 0$ ,  $S_1$  open and  $S_2$  closed
- For  $0 \leq t < t'$ ,  $S_1$  closed and  $S_2$  closed
- For  $t' \leq t$ ,  $S_1$  closed and  $S_2$  open

# Example

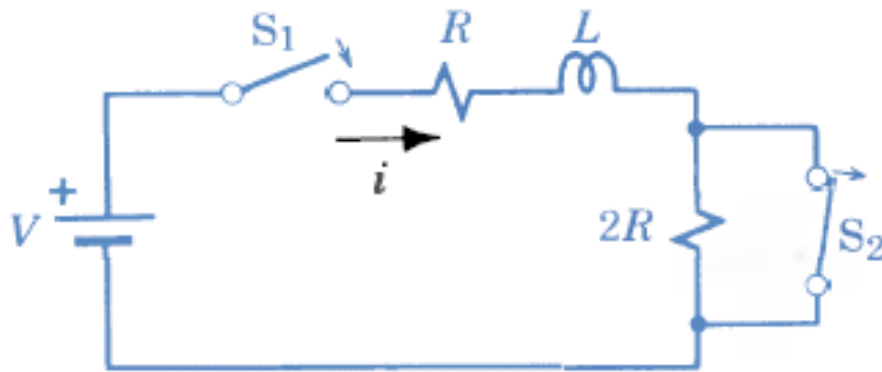

- For  $t < 0$ ,  $S_1$  open and  $S_2$  closed
- For  $0 \leq t < t'$ ,  $S_1$  closed and  $S_2$  closed
- For  $t' \leq t$ ,  $S_1$  closed and  $S_2$  open

1. Determine the impedance function for  $0 \leq t \leq t'$ :

$$Z(s) = R + sL$$


2. Forced response:  $i_f = \frac{V}{R}$

3. Natural response:  $i_n = Ae^{-\frac{R}{L}t}$

4. Complete response:  $i = i_n + i_f = \frac{V}{R} + Ae^{-\frac{R}{L}t}$


$$i = 0 \text{ @ } t = 0: A = -\frac{V}{R} \qquad i = \frac{V}{R} \left(1 - e^{-\frac{R}{L}t}\right)$$

# Example

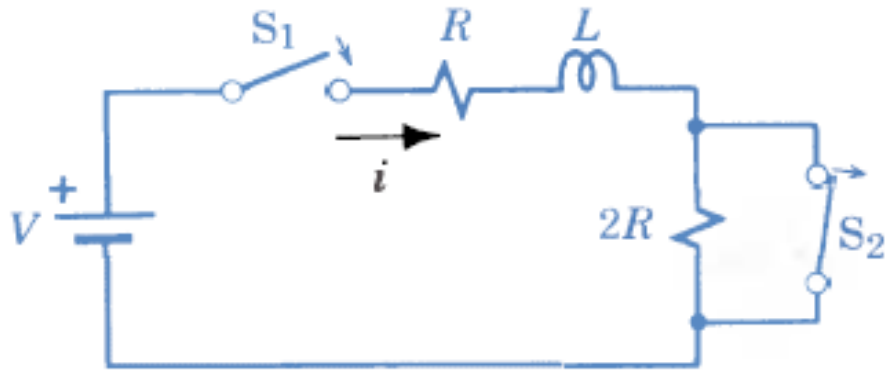

- For  $t < 0$ ,  $S_1$  open and  $S_2$  closed
- For  $0 \leq t < t'$ ,  $S_1$  closed and  $S_2$  closed
- For  $t' \leq t$ ,  $S_1$  closed and  $S_2$  open

# Example

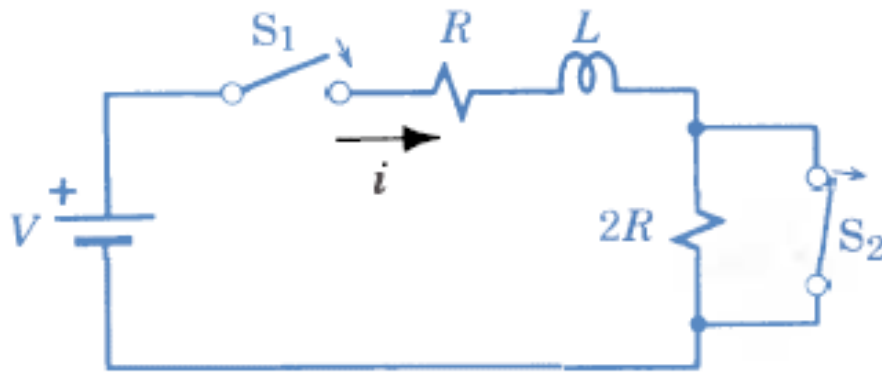

- For  $t < 0$ ,  $S_1$  open and  $S_2$  closed
- For  $0 \leq t < t'$ ,  $S_1$  closed and  $S_2$  closed
- For  $t' \leq t$ ,  $S_1$  closed and  $S_2$  open

1. Determine the impedance function for  $t' \leq t$ :

$$Z(s) = R + sL + 2R = 3R + sL$$


2. Forced response:  $i_f = \frac{V}{3R}$

3. Natural response:  $i_n = A'e^{-\frac{3R}{L}(t-t')}$


4. Complete response:  $i = i_n + i_f = \frac{V}{3R} + A'e^{-\frac{3R}{L}(t-t')}\bigg|_{t=t'} = \frac{V}{R} \left(1 - e^{-\frac{R}{L}t}\right)$   
Previous solution

$\therefore A'$  is determined by  $\frac{V}{3R} + A' = \frac{V}{R}(1 - e^{-\frac{R}{L}t'})$

# Example

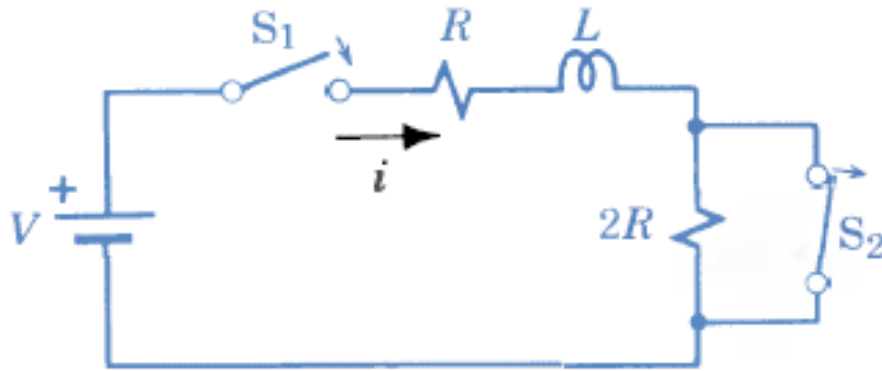


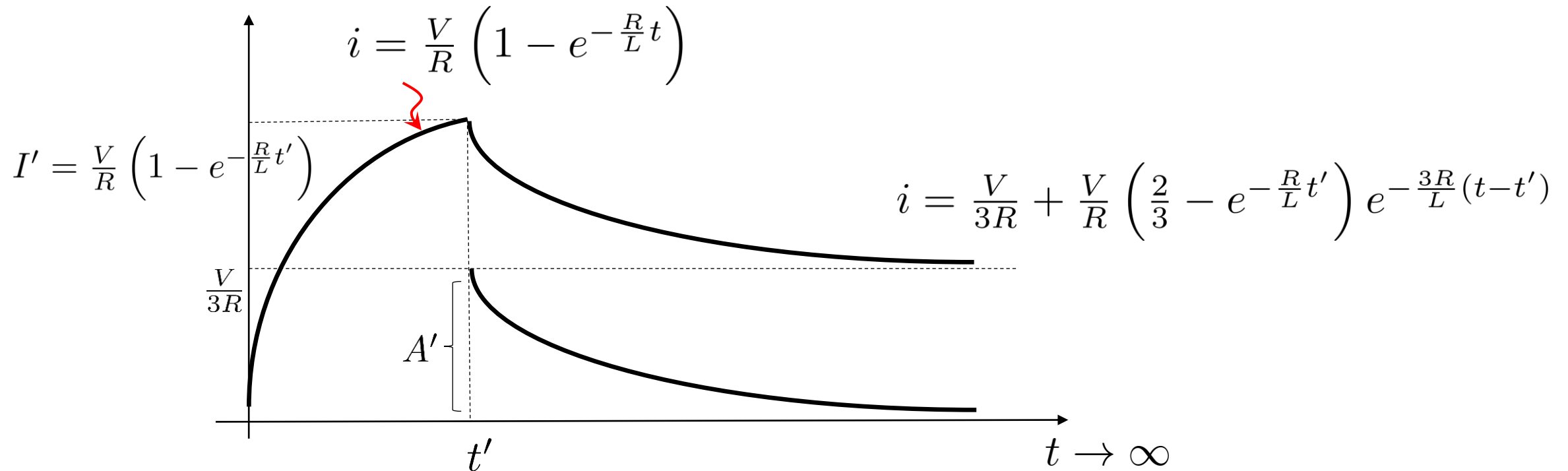- For  $t < 0$ ,  $S_1$  open and  $S_2$  closed
- For  $0 \leq t < t'$ ,  $S_1$  closed and  $S_2$  closed
- For  $t' \leq t$ ,  $S_1$  closed and  $S_2$  open





# Step response of RLC circuit

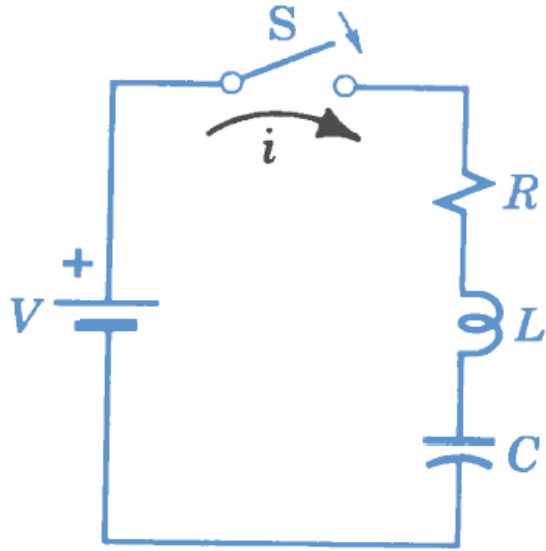

- $C$  is initially uncharged
- $L$  carries no current
- Voltage is applied for  $t \geq 0$


The impedance for this circuit

$$Z(s) = R + sL + \frac{1}{sC}$$

The forced response at DC, i.e.,  $s = 0$ :

$$i_f = \frac{V}{Z(s)} \Big|_{s=0} = \frac{V}{\infty} = 0$$

# Step response of RLC circuit

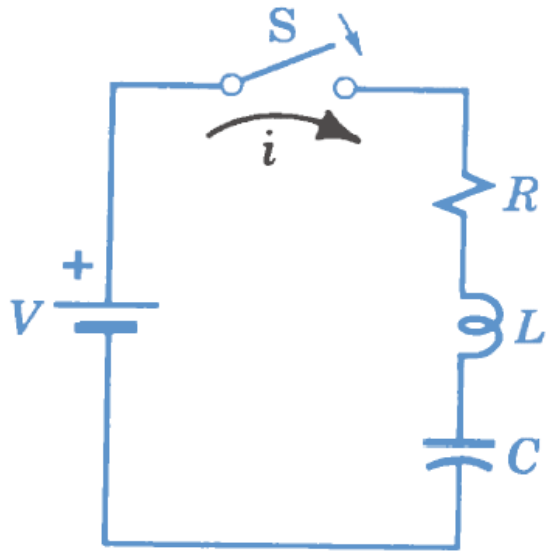

- $C$  is initially uncharged
- $L$  carries no current
- Voltage is applied for  $t \geq 0$


The impedance for this circuit

$$Z(s) = R + sL + \frac{1}{sC} \Rightarrow \frac{s^2 L + sR + \frac{1}{C}}{s}$$

The natural component for  $i$  at  $Z(s) = 0$ :


$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} = -\alpha \pm j\omega$$

# Step response of RLC circuit

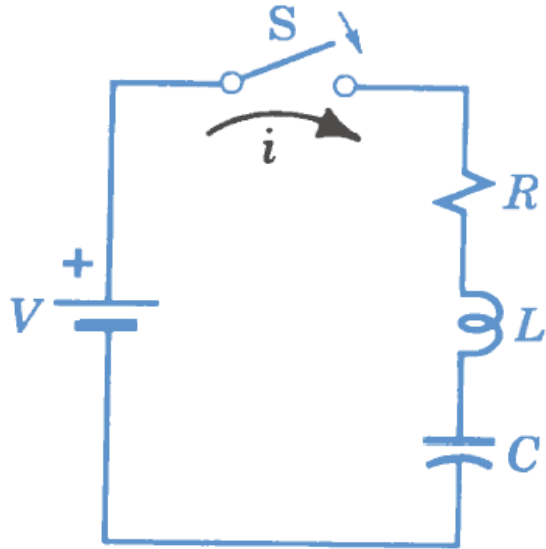

- real and distinct roots:  $i_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
- real and equal roots:  $i_n = A_1 e^{st} + A_2 t e^{st}$
- complex roots:  
$$i_n = e^{-\alpha t} (B_1 \cos \omega t + B_2 \sin \omega t)$$
$$= A e^{-\alpha t} \sin(\omega t + \theta)$$

# Step response of RLC circuit

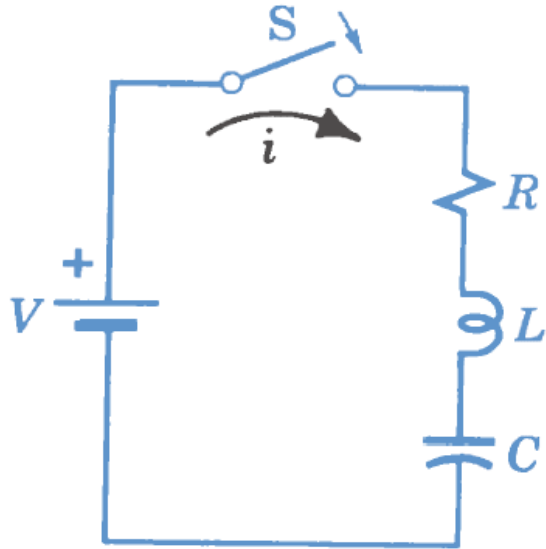

- real and distinct roots:  $i_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
- real and equal roots:  $i_n = A_1 e^{st} + A_2 t e^{st}$
- complex roots:  $i_n = e^{-\alpha t} (B_1 \cos \omega t + B_2 \sin \omega t)$   
 $= A e^{-\alpha t} \sin(\omega t + \theta)$


Assuming  $i_L = 0$  at  $t = 0$ :

$$i(0^+) = i_f + i_n = 0$$

Assuming  $v_C = 0$  and  $v_R = Ri = 0$  at  $t = 0$  due to  $i = 0$  at  $t = 0$

$$v_L(0^+) = L \frac{di}{dt} = V$$

# Step response of RLC circuit

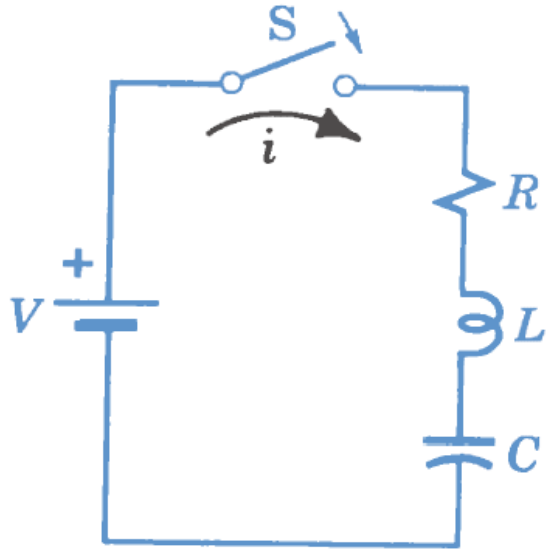

Let us assume 'real and distinct roots':

$$i_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

The condition  $v_L(0^+) = L \frac{di}{dt} = V$  gives

$$v_L(0^+) = L \frac{di}{dt} = L(s_1 A e^{s_1 t} + s_2 A e^{s_2 t}) \Big|_{t=0}$$


$$\Rightarrow s_1 A_1 + s_2 A_2 = \frac{V}{L}$$

Assuming  $i_L = 0$  at  $t = 0$ :

$$i_n = A_1 + A_2 = 0$$
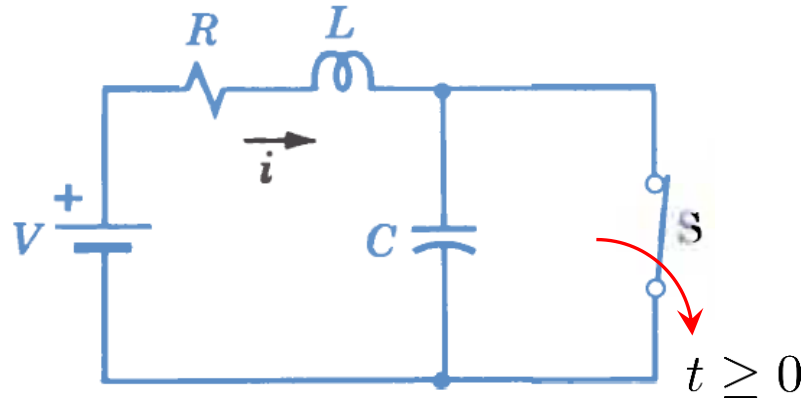
# Example – 1

$$V = 20(V), R = 4(\Omega), L = 2(H), C = 0.01(F),$$




The impedance for this circuit

$$Z(s) = R + sL + \frac{1}{sC} = 4 + 2s + \frac{100}{s}$$
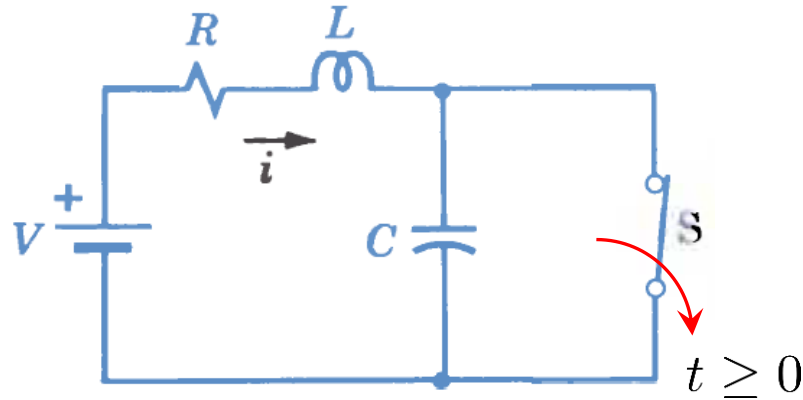
# Example – 1

$$V = 20(V), R = 4(\Omega), L = 2(H), C = 0.01(F),$$



The impedance for this circuit

$$Z(s) = R + sL + \frac{1}{sC} = 4 + 2s + \frac{100}{s}$$

The forced response at DC, i.e.,  $s = 0$ :

$$i_f = \frac{V}{Z(s)} \Big|_{s=0} = \frac{V}{\infty} = 0$$


The natural component for  $i$  at  $Z(s) = 0$ :

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} = -1 \pm 7j$$

$$i_n = Ae^{-t} \sin(7t + \theta) \Rightarrow i = i_n + i_f = i_n$$
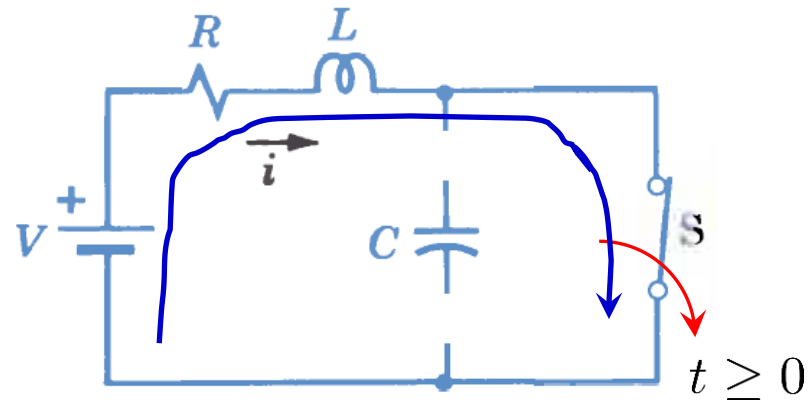
# Example – 1

$$V = 20(V), R = 4(\Omega), L = 2(H), C = 0.01(F),$$




$$\text{At } t = 0^+, i = i_L(0^-) = V/R = 20/4 = 5$$


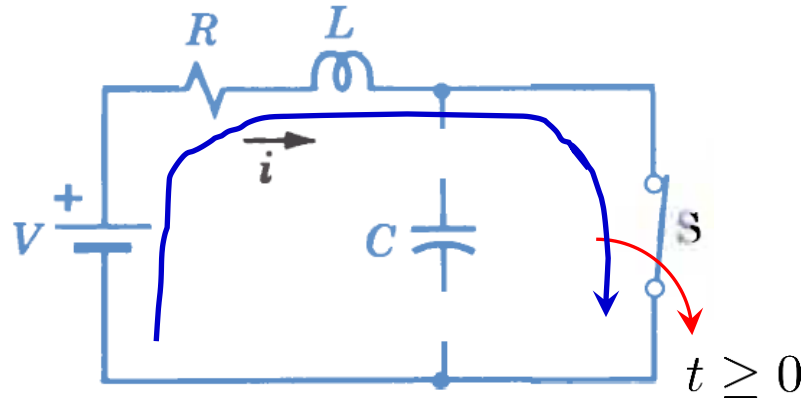
# Example – 1

$$V = 20(V), R = 4(\Omega), L = 2(H), C = 0.01(F),$$




$$\text{At } t = 0^+, i = i_L(0^-) = V/R = 20/4 = 5$$

$$i_n = Ae^{-t} \sin(7t + \theta) \Big|_{t=0} = 5$$

$$\Rightarrow A \sin \theta = 5$$
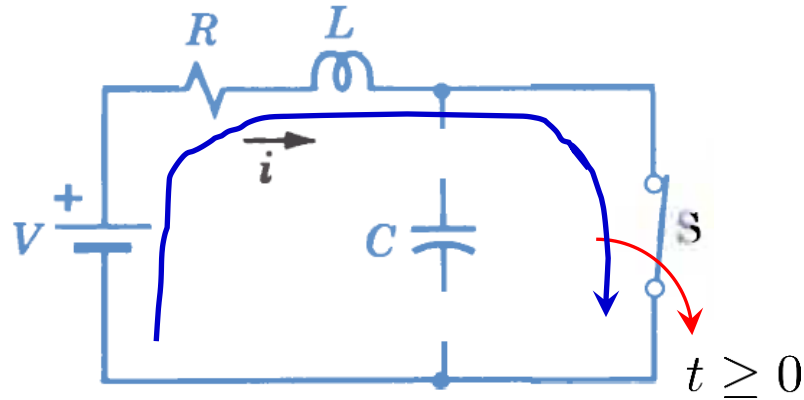
# Example – 1

$$V = 20(V), R = 4(\Omega), L = 2(H), C = 0.01(F),$$



$$\text{At } t = 0^+, i = i_L(0^-) = V/R = 20/4 = 5$$


$$i_n = Ae^{-t} \sin(7t + \theta)|_{t=0} = 5$$

$$\Rightarrow A \sin \theta = 5$$

$$\text{Another initial condition: } v_C = 0, v_R = V, v_L = L \frac{di}{dt} \Big|_{t=0} = 0$$
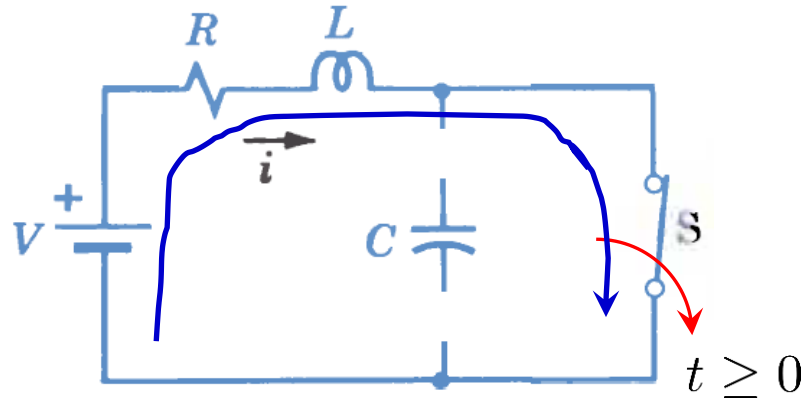
# Example – 1

$$V = 20(V), R = 4(\Omega), L = 2(H), C = 0.01(F),$$



$$\text{At } t = 0^+, i = i_L(0^-) = V/R = 20/4 = 5$$

$$i_n = Ae^{-t} \sin(7t + \theta)|_{t=0} = 5$$

$$\Rightarrow A \sin \theta = 5$$

$$\text{Another initial condition: } v_C = 0, v_R = V, v_L = L \frac{di}{dt} \Big|_{t=0} = 0$$

$$\Rightarrow \frac{di_n}{dt} = -Ae^{-t} \sin(7t + \theta) + 7Ae^{-t} \cos(7t + \theta)$$


$$\Rightarrow -A \sin(\theta) + 7A \cos(\theta) = 0$$

$$\Rightarrow \frac{\sin(\theta)}{\cos(\theta)} = 7 = \tan \theta \Rightarrow \arctan(7) = 81.9^\circ$$

$$\Rightarrow A \sin(81.9^\circ) = 5$$
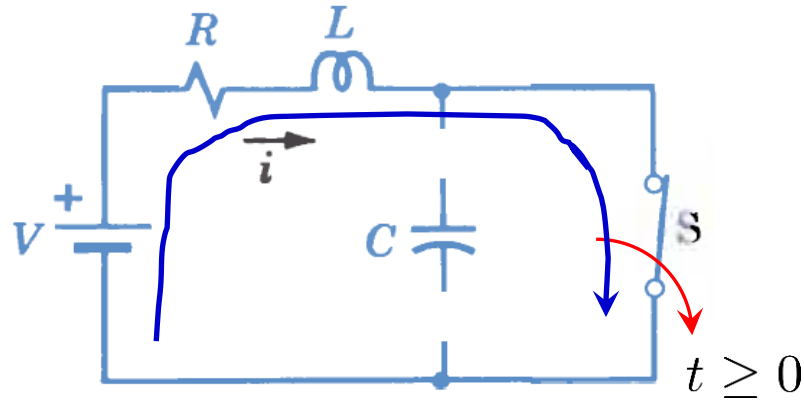
# Example – 1

$$V = 20(V), R = 4(\Omega), L = 2(H), C = 0.01(F),$$




$$\text{At } t = 0^+, i = i_L(0^-) = V/R = 20/4 = 5$$

$$i_n = Ae^{-t} \sin(7t + \theta) \big|_{t=0} = 5$$

$$\Rightarrow A \sin \theta = 5$$

$$\text{Another initial condition: } v_C = 0, v_R = V, v_L = L \frac{di}{dt} \big|_{t=0} = 0$$

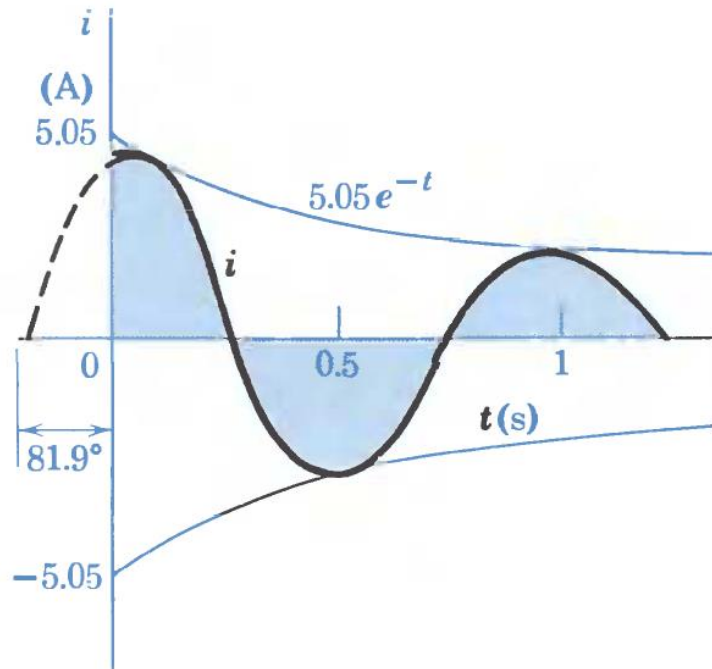

$$\Rightarrow \frac{di_n}{dt} = -Ae^{-t} \sin(7t + \theta) + 7Ae^{-t} \cos(7t + \theta)$$

$$\Rightarrow -A \sin(\theta) + 7A \cos(\theta) = 0$$


$$\Rightarrow \frac{\sin(\theta)}{\cos(\theta)} = 7 = \tan \theta \Rightarrow \arctan(7) = 81.9^\circ$$

$$\Rightarrow A \sin(81.9^\circ) = 5$$

$$\therefore i_n = 5.05e^{-t} \sin(7t + 81.9^\circ)$$
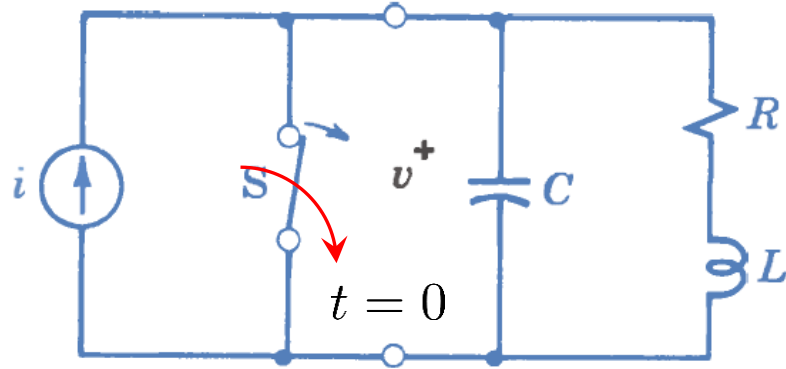
## Example – 2

$$i = 8.5 \cos(4t) \text{ (A)}, R = 2 \text{ } (\Omega), L = 1 \text{ (H)}, C = \frac{1}{17} \text{ (F)},$$




The impedance for this circuit

$$Z(s) = \frac{1}{sC} \parallel (R + sL)$$

$$Y(s) = sC + \frac{1}{R + sL} = \frac{s^2 LC + sRC + 1}{R + sL}$$
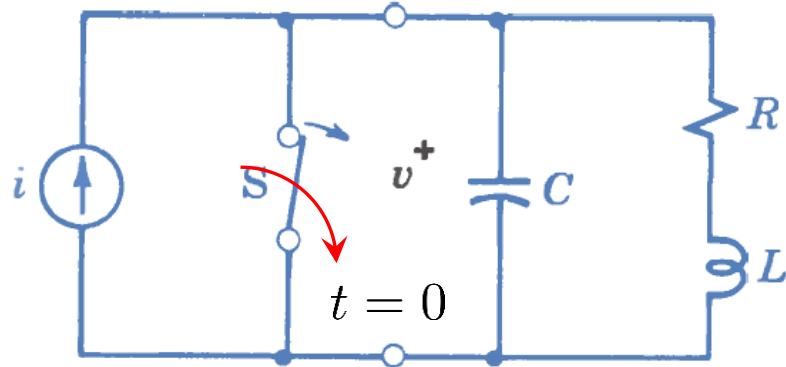
## Example – 2

$$i = 8.5 \cos(4t) \text{ (A)}, R = 2 \text{ } (\Omega), L = 1 \text{ (H)}, C = \frac{1}{17} \text{ (F)},$$



The impedance for this circuit

$$Z(s) = \frac{1}{sC} \parallel (R + sL)$$

$$Y(s) = sC + \frac{1}{R + sL} = \frac{s^2 LC + sRC + 1}{R + sL}$$


$$\Rightarrow \frac{1 - \omega^2 LC + j\omega RC}{R + j\omega L} = \frac{1 - \frac{16}{17} + \frac{8}{17}j}{2 + 4j} = 0.106 \angle 19.5^\circ$$

$$\mathbf{V}_f = \frac{\mathbf{I}}{\mathbf{Y}} = \frac{(8.5/\sqrt{2}) \angle 0^\circ}{0.106 \angle 19.5^\circ} = \frac{80}{\sqrt{2}} \angle -19.5^\circ$$

$$\therefore v_f = 80 \cos(4t - 19.5^\circ)$$
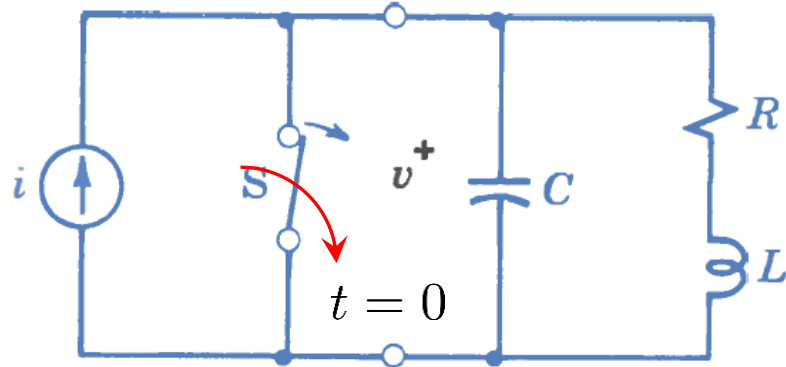
## Example – 2

$$i = 8.5 \cos(4t) \text{ (A)}, R = 2 \text{ } (\Omega), L = 1 \text{ (H)}, C = \frac{1}{17} \text{ (F)},$$



The impedance for this circuit

$$Z(s) = \frac{1}{sC} \parallel (R + sL)$$

$$Y(s) = sC + \frac{1}{R + sL} = \frac{s^2 LC + sRC + 1}{R + sL}$$

To find  $v_n$ , use the poles of the impedance or the zeros of the admittance


$$\begin{aligned} Y(s) = 0 &\Rightarrow s^2 LC + sRC + 1 = 0 \Rightarrow s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \\ &= -1 \pm 4j \end{aligned}$$

$$\therefore v_n = Ae^{-t} \cos(4t + \theta)$$

$$v = v_f + v_n = 80 \cos(4t - 19.5^\circ) + Ae^{-t} \cos(4t + \theta)$$
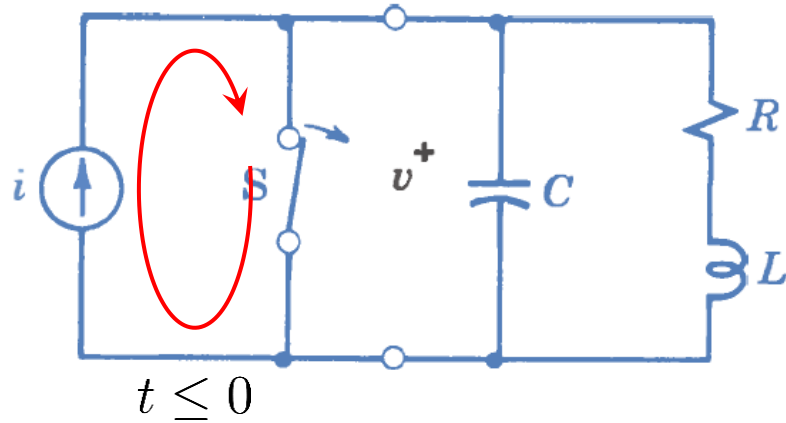
## Example – 2

$$i = 8.5 \cos(4t) \text{ (A)}, R = 2 \text{ } (\Omega), L = 1 \text{ (H)}, C = \frac{1}{17} \text{ (F)},$$



Determine  $A$  and  $\theta$ :

$$v = v_f + v_n = 80 \cos(4t - 19.5^\circ) + Ae^{-t} \cos(4t + \theta)$$


At  $t = 0^+$ ,  $v_C = v = 0$ :

$$80 \cos(-19.5^\circ) + A \cos(\theta) = 0 \quad \therefore A \cos(\theta) = -75.5$$


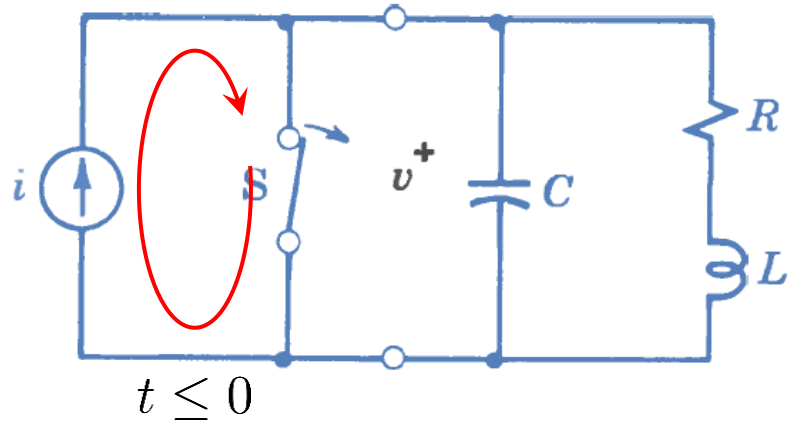
# Example – 2

$$i = 8.5 \cos(4t) \text{ (A)}, R = 2 \text{ } (\Omega), L = 1 \text{ (H)}, C = \frac{1}{17} \text{ (F)},$$



Determine  $A$  and  $\theta$ :

$$v = v_f + v_n = 80 \cos(4t - 19.5^\circ) + Ae^{-t} \cos(4t + \theta)$$

At  $t = 0^+$ ,  $v_C = v = 0$ :

$$80 \cos(-19.5^\circ) + A \cos(\theta) = 0 \quad \therefore A \cos(\theta) = -75.5$$

At  $t = 0^+$ ,  $i_L = 0$ :

$$v_L = L \frac{di_L}{dt} = 0 \quad \Rightarrow v_R = i_L R = 0$$

At  $t = 0^+$ ,  $C \frac{dv_C}{dt} = i_C|_{t=0} = 8.5$ :


$$\frac{dv_C}{dt} = -320 \sin(-19.5^\circ) - A(\cos(\theta) + 4 \sin(\theta)) = 8.5 \times 17 = 144.5$$

$$\Rightarrow -4A \sin(\theta) = 144.5 + 320 \sin(-19.5^\circ) + A \cos(\theta)$$

$$\therefore A \sin(\theta) = 9.4$$
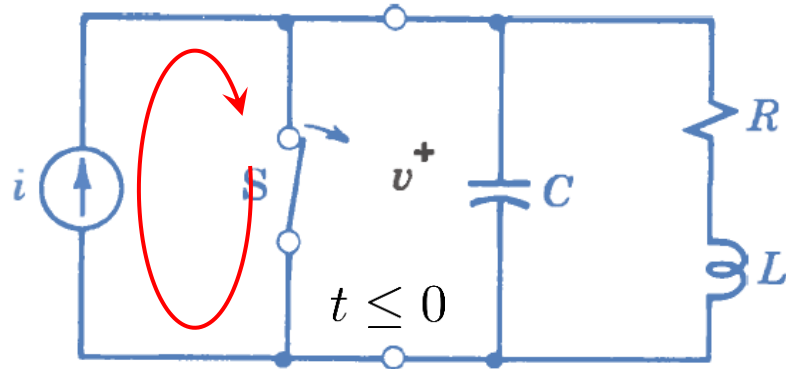
## Example – 2

$$i = 8.5 \cos(4t) \text{ (A)}, R = 2 \text{ } (\Omega), L = 1 \text{ (H)}, C = \frac{1}{17} \text{ (F)},$$



$$v = v_f + v_n = 80 \cos(4t - 19.5^\circ) + Ae^{-t} \cos(4t + \theta)$$

$$\frac{A \sin(\theta)}{A \cos(\theta)} = \tan(\theta) = \frac{9.4}{-75.5} = -0.1245$$

$$\therefore \theta = -7.1^\circ$$


$$\Rightarrow v = 80 \cos(4t - 19.5^\circ) + Ae^{-t} \cos(4t - 7.1^\circ)$$

At  $t = 0^+$ ,  $v_C = v = 0$ :

$$v = 80 \cos(-19.5^\circ) + A \cos(7.1^\circ) = 0 \Rightarrow A = \frac{-80 \cos(-19.5^\circ)}{\cos(-7.1^\circ)} = -75.994$$
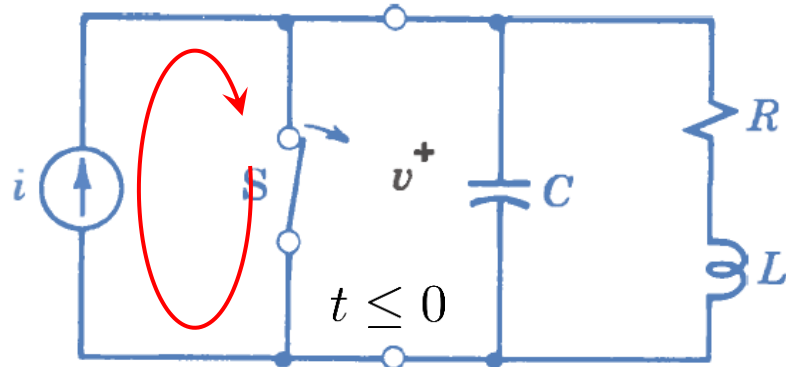
# Example – 2

$$i = 8.5 \cos(4t) \text{ (A)}, R = 2 \text{ } (\Omega), L = 1 \text{ (H)}, C = \frac{1}{17} \text{ (F)},$$



$$v = v_f + v_n = 80 \cos(4t - 19.5^\circ) + Ae^{-t} \cos(4t + \theta)$$


$$\frac{A \sin(\theta)}{A \cos(\theta)} = \tan(\theta) = \frac{9.4}{-75.5} = -0.1245$$

$$\therefore \theta = -7.1^\circ$$

$$\Rightarrow v = 80 \cos(4t - 19.5^\circ) + Ae^{-t} \cos(4t - 7.1^\circ)$$

At  $t = 0^+$ ,  $v_C = v = 0$ :
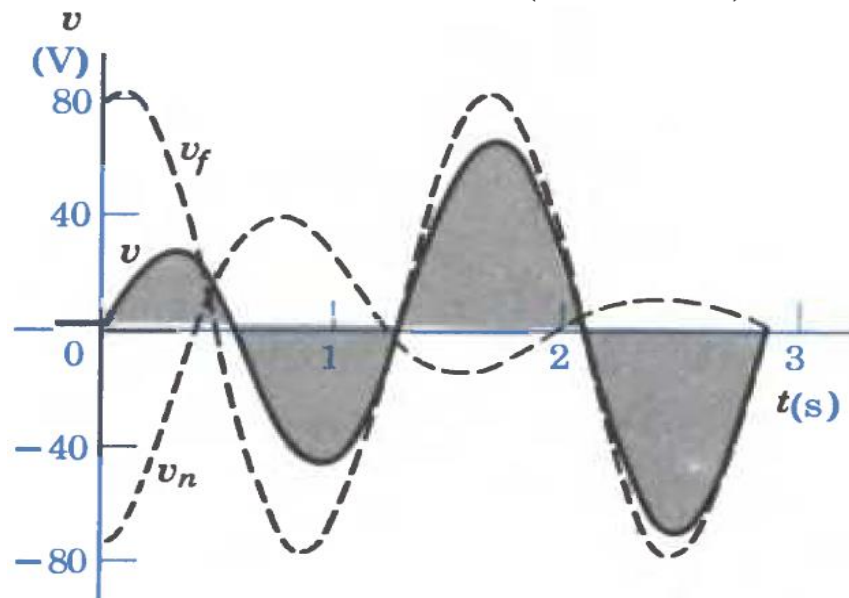
$$v = 80 \cos(-19.5^\circ) + A \cos(7.1^\circ) = 0 \Rightarrow A = \frac{-80 \cos(-19.5^\circ)}{\cos(-7.1^\circ)} = -75.994$$



$$\therefore v = 80 \cos(4t - 19.5^\circ) - 75.994e^{-t} \cos(4t + \theta)$$