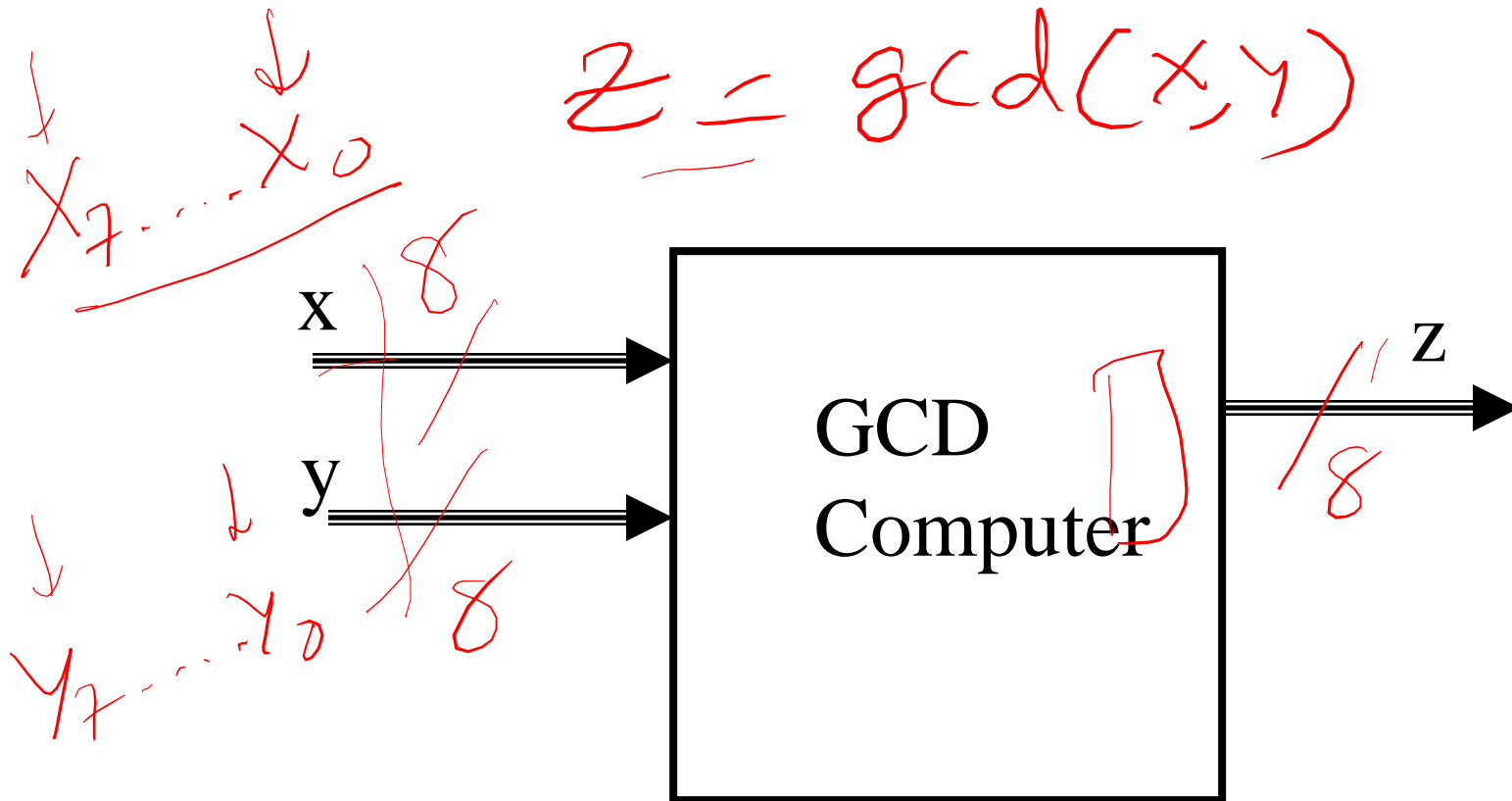


Lecture 25

System Design Case Studies

M. Balakrishnan
Dept. of Comp. Sci. & Engg.
I.I.T. Delhi

Case Study1: GCD Computer



GCD Algorithm

Input x, y;

while ($x \neq y$) do

if ($x > y$) then $x := x - y$

else $y := y - x$

endif;

endwhile;

$z := x$;

end.

leg 5 catch 5

Modified GCD Algorithm (RTL)

S0: $R1 := x, R2 := y;$

S1: while ($R1 \neq R2$) do

S2: if ($R1 > R2$)


S3: then $R1 := R1 - R2$

S4: else $R2 := R2 - R1$

endif;

endwhile;

S5: $R3 := R1;$

 

GCD Computer: Data Part

R1


R2

Comp


R3

SUB

GCD Computer: Data Part

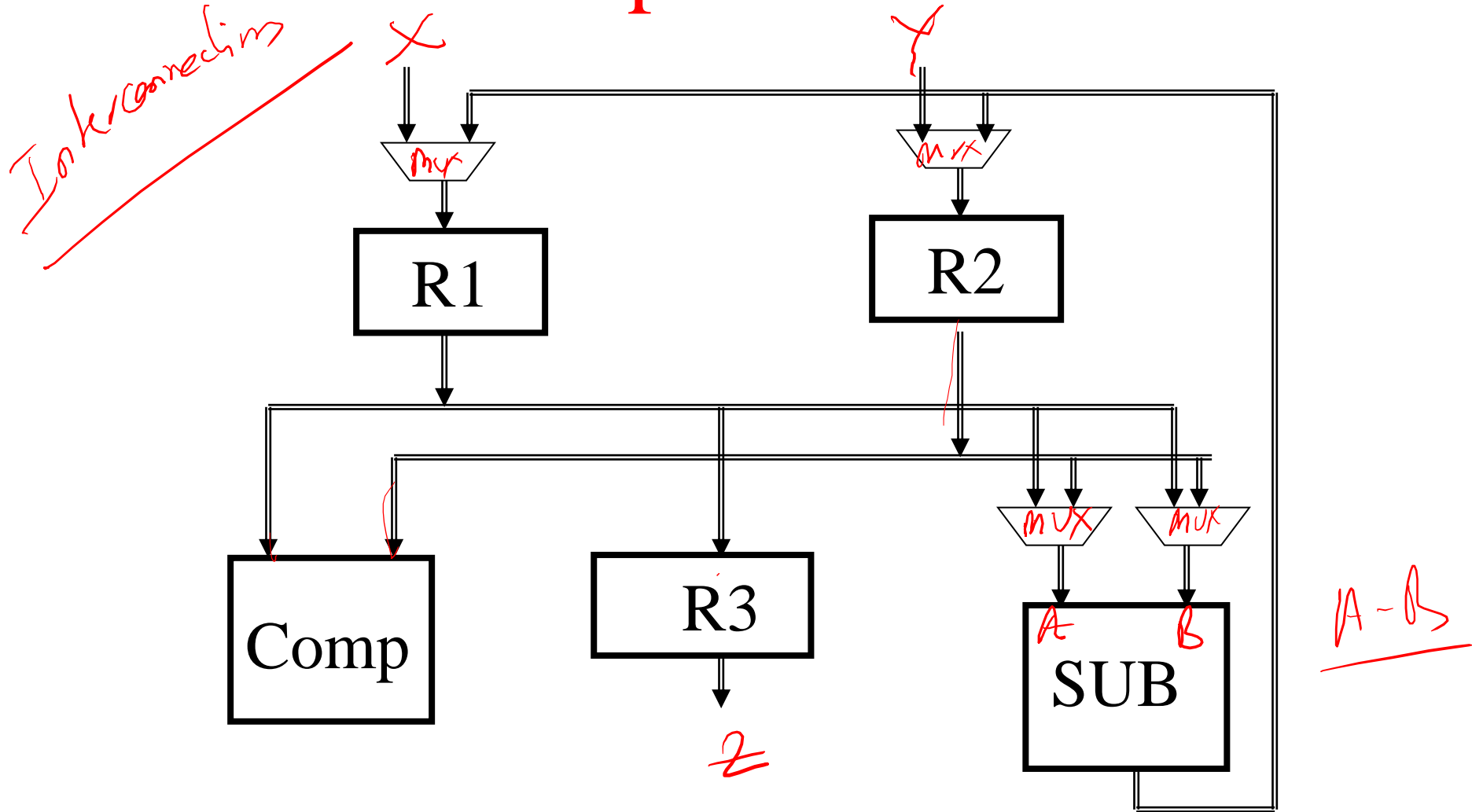

GCD Computer: Data Part

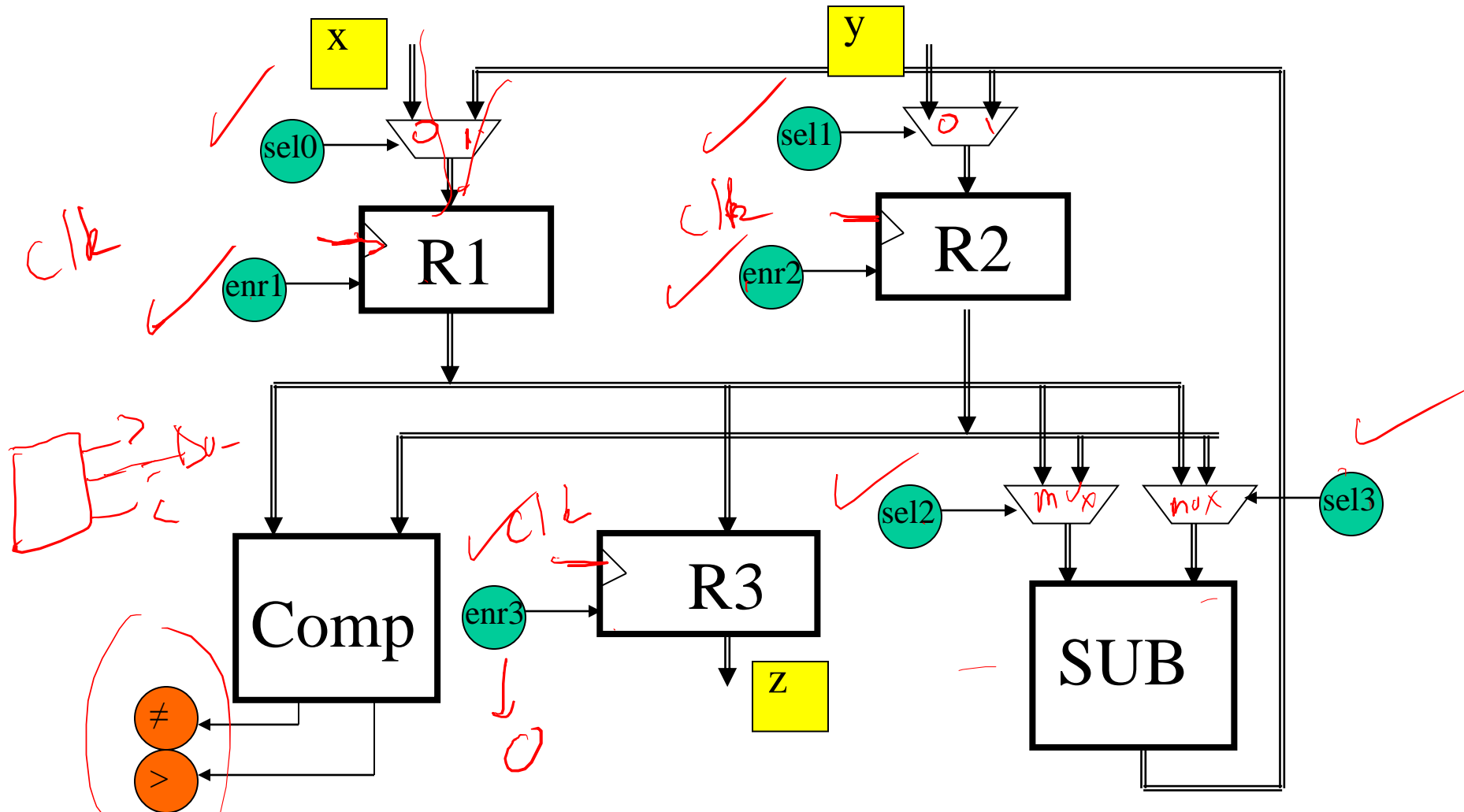

Control Part FSM



S0: R1 := x, R2 := y;

S1: while (R1 \neq R2) do

\neq S2: if (R1 > R2)


$>$ S3: then R1 := R1 - R2

$<$ S4: else R2 := R2 - R1

endif;

endwhile;


S5: R3 := R1;

 


FSM: Control Signals


S0: R1 := x, R2 := y;
S1: while (R1 \neq R2) do
 S2: if (R1 $>$ R2)
 S3: then R1 := R1 - R2
 S4: else R2 := R2 - R1
 endif;
endwhile;
S5: R3 := R1;

Section 3: Sequential Circuits

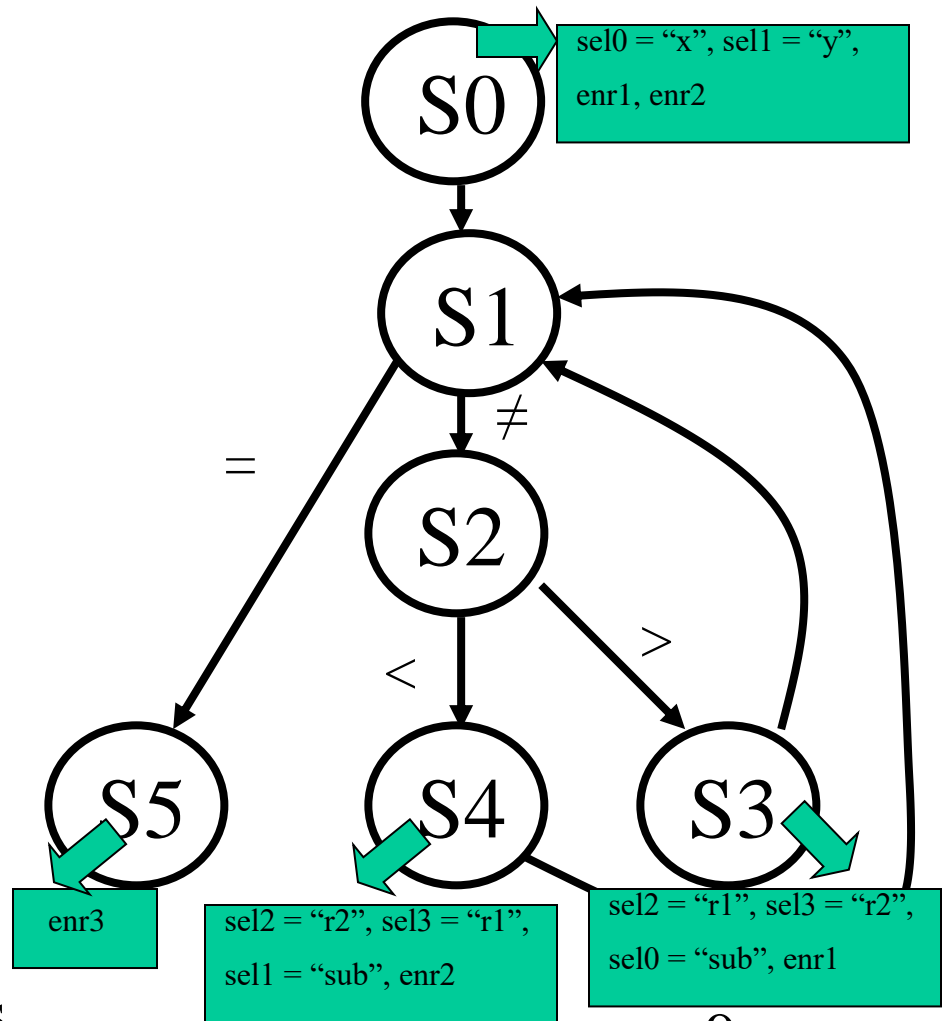

Data-Control Interface

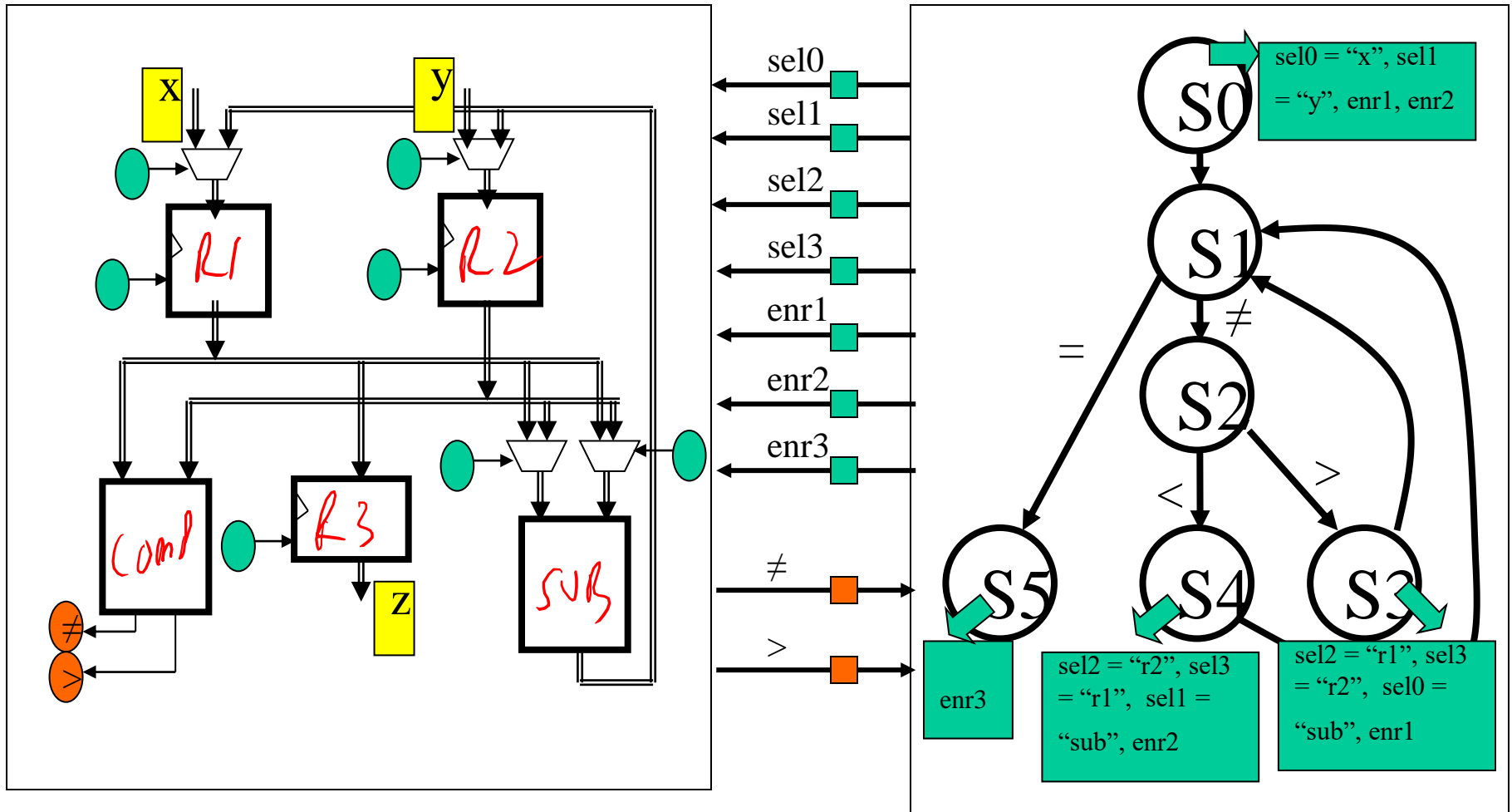

 

Modified RTL + FSM

S0: $R1 := x, R2 := y;$

S1: Case ($R1$ "Compare" $R2$)

S2: ">" $R1 := R1 - R2,$


go to S1;

S3: "<" $R2 := R2 - R1,$


go to S1

S4: "=" $R3 := R1;$

endcase;

 

GCD Computer: Interface

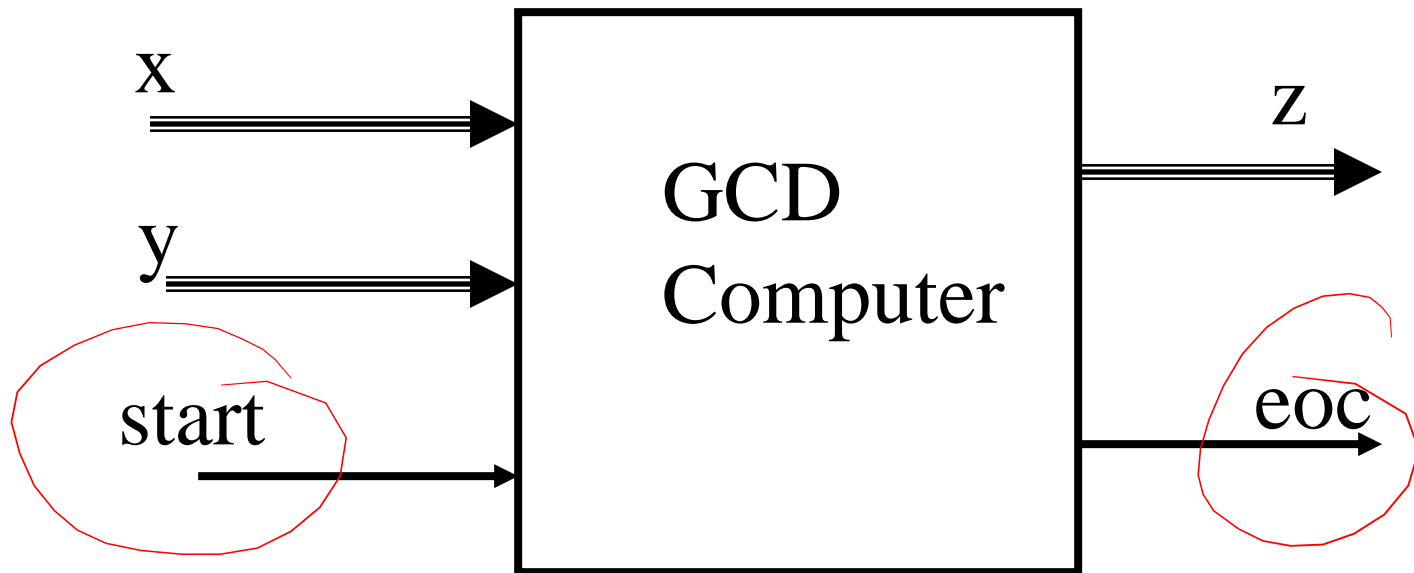

Modified FSM

Si: wait for “start”

S0: R1:= x, R2:= y, eoc := “0”;

S1: while (R1 \neq R2) do

S2: if (R1 > R2)

S3: then R1:= R1 - R2


S4: else R2:= R2 - R1

endif;


endwhile;

S5: R3:= R1, eoc := “1”, goto Si;


jp

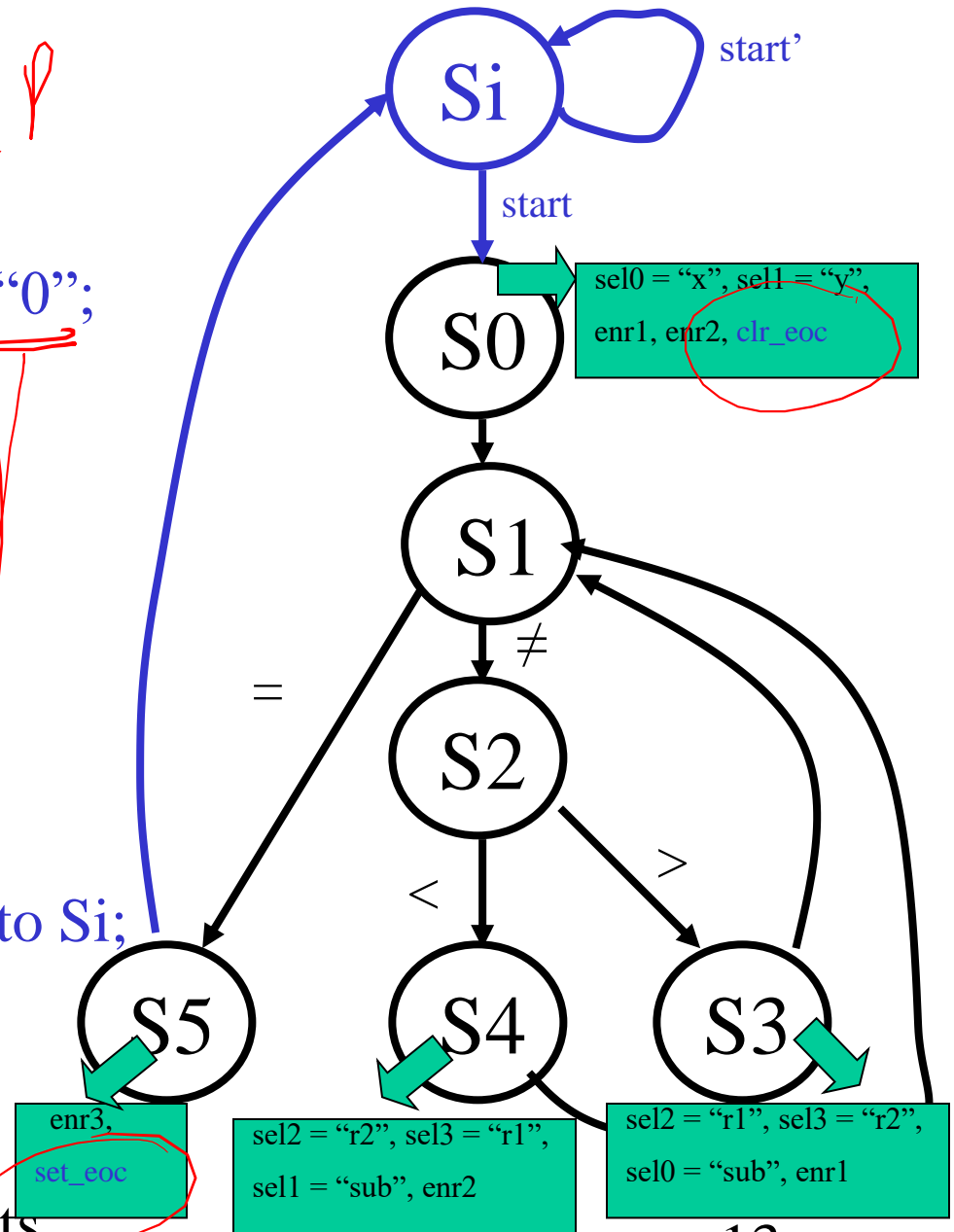


GCD Computer: Data Part

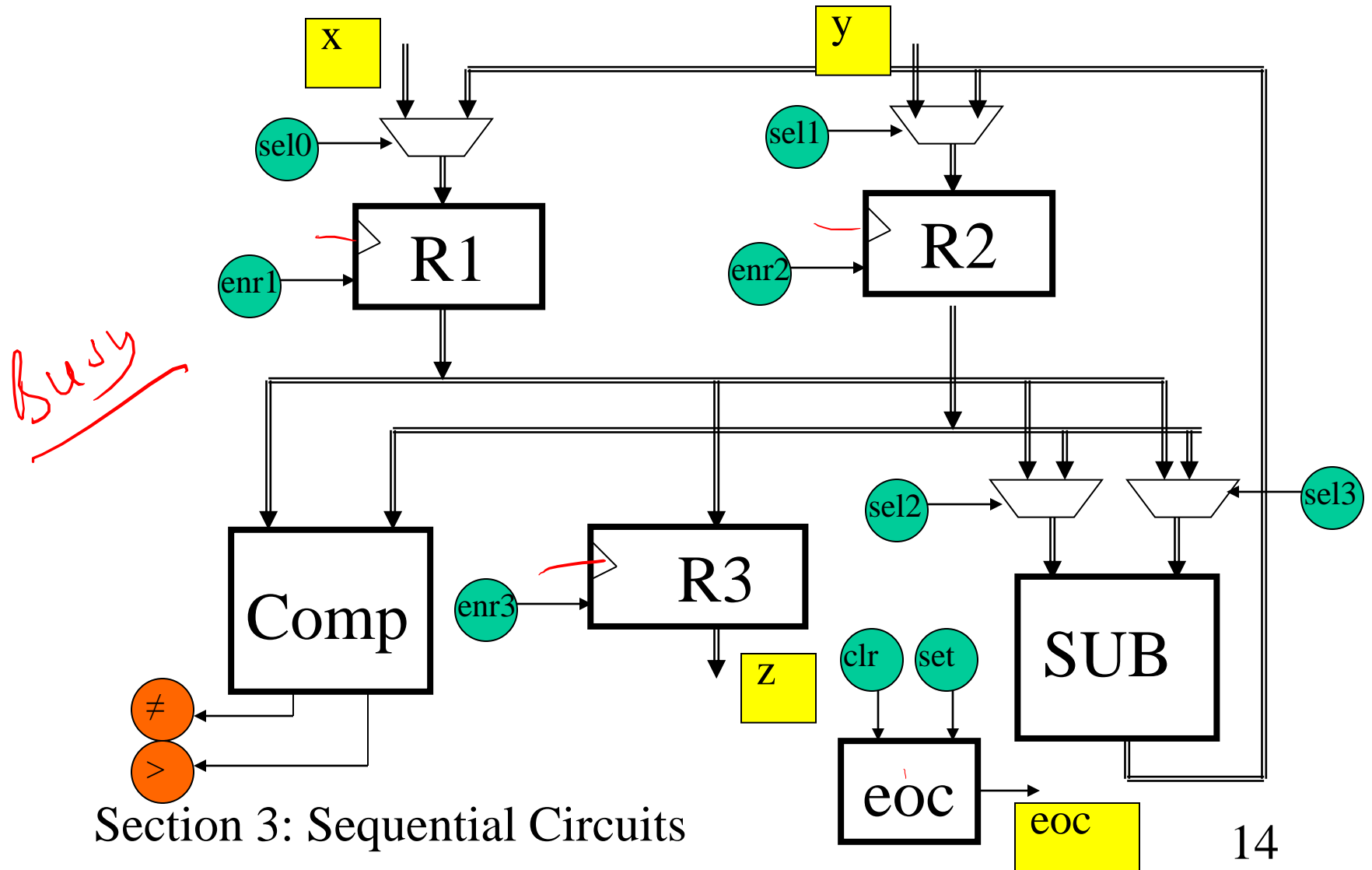

Case Study 2: FIFO

 

FIFO: Data Part

 

FIFO: RTL

Si: head := “0”, tail := “0”, full := “0”, empty := “1”;

S0: If (add and full’) then

S1: mem(head) := data_in;

S2: head := head + 1;

S3:: full := (head == tail); go to S0;

S4: else if (delete and empty’) then

S5: tail := tail + 1;

S6: data_out:= mem(tail);

S7: empty := (head == tail); go to S0;

Design Problem

Design a system which uses GCD module and multiple FIFO modules. An array of numbers are stored in a memory and GCD of these numbers is to be computed and stored back into the memory. FIFO buffers are used to supply the inputs to the GCD module and take the outputs from the GCD module.