

# Synthesis of Digital Systems

COL 719

## Part 7: Field Programmable Gate Arrays

Preeti Ranjan Panda


Department of Computer Science and Engineering

Indian Institute of Technology Delhi

# Field Programmable Gate Array


- “Field Programmable”
  - Customised by designer
  - vs. “Mask Programmable”: customised by foundry
- Customisation process simple/cheap
- FPGA chips produced in bulk
  - independent of functionality

# FPGA architecture

 



# Modern FPGA Architecture

Xilinx  
Zynq 7000  
Series

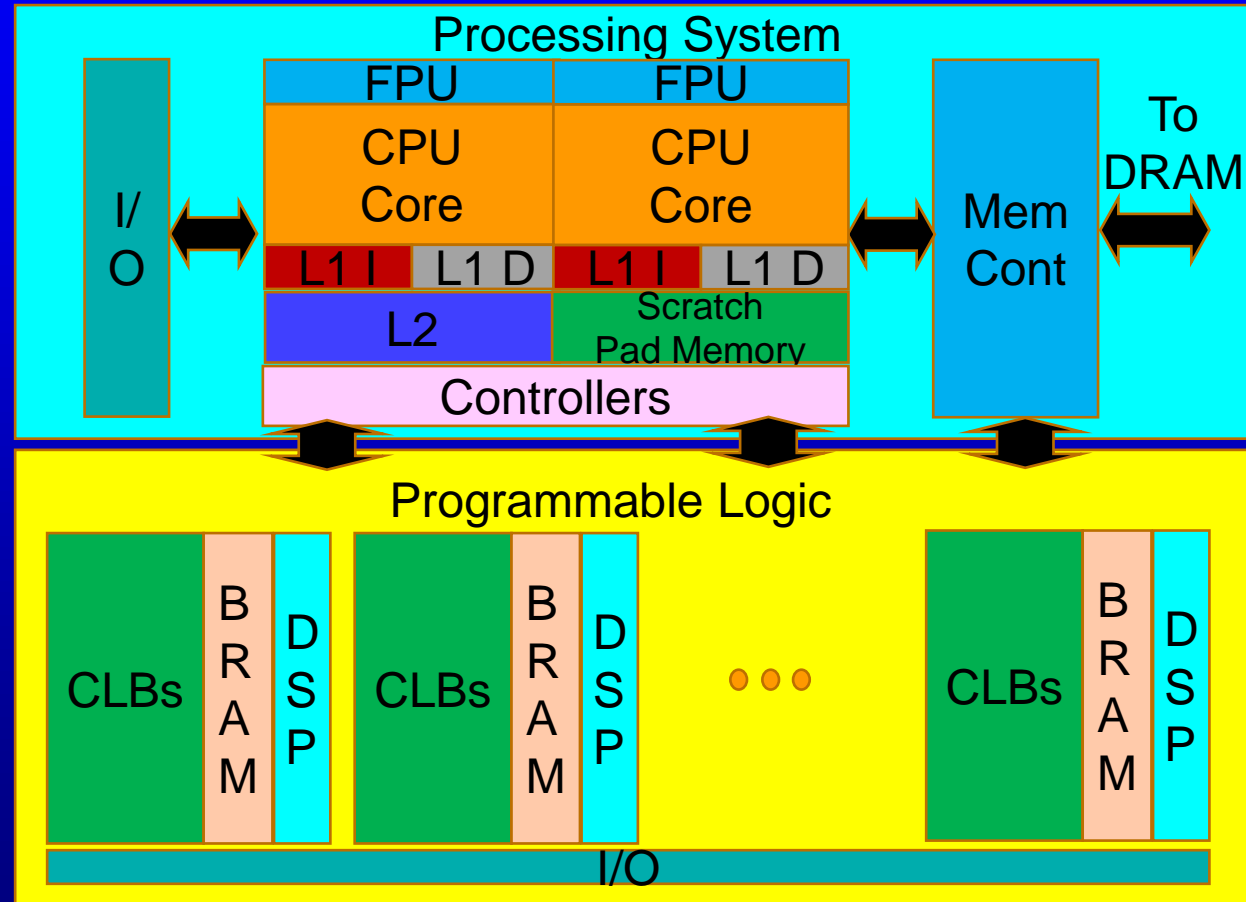
  
# FPGA Programming: SRAM


- Normal SRAM cell
- Programming: writing 0 or 1 into SRAM cell
  - this, in turn, causes selections, connections, etc.



# SRAM-based FPGA


- Each logic block consists of an SRAM
- An SRAM with  $2^n$  bits can implement ANY function of  $n$  inputs
  - Use inputs as address
  - Store value in locations

a	b	y
0	0	1
0	1	0
1	0	1
1	1	1

 
 
# Xilinx 7-Series Architecture


- 64-bit Look-up Tables (LUT)
  - All functions of 6 inputs
- What if we wanted 2 functions of 5 inputs instead?


 
# Xilinx 7-Series Architecture

- 2 Functions of 5 inputs
  - Split into 2 banks
    - 2 functions of 5 inputs

**A6 = 0:** 2 functions **O1** and **O2** of 5 variables (A1-A5)  
**A6 = input variable:** 1 function **O1** of 6 variables (A1-A6)





# Technology Mapping in FPGAs

- More complex “library cells”
- Library cells can be customised
  - cannot enumerate fully

# Matching

- Matching is trivial
  - ANY function can be implemented
  - make sure number of inputs match

# Covering for 4 i/p block

- Treat library cell as
  - Black Box with 4 inputs, 1 output
    - no need to decompose into NAND/INV
- Technology Mapping
  - Cover the network by sub-graphs of 4 inputs, 1 output

