



# ELL100: INTRODUCTION TO ELECTRICAL ENGG.

## **Natural Response: Second Order Circuits**

Course Instructors:

Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik, Harshan  
Jagadeesh


Department of Electrical Engineering, IITD

# Second order Circuits

- The **state** can be represented using a second order differential equation only.

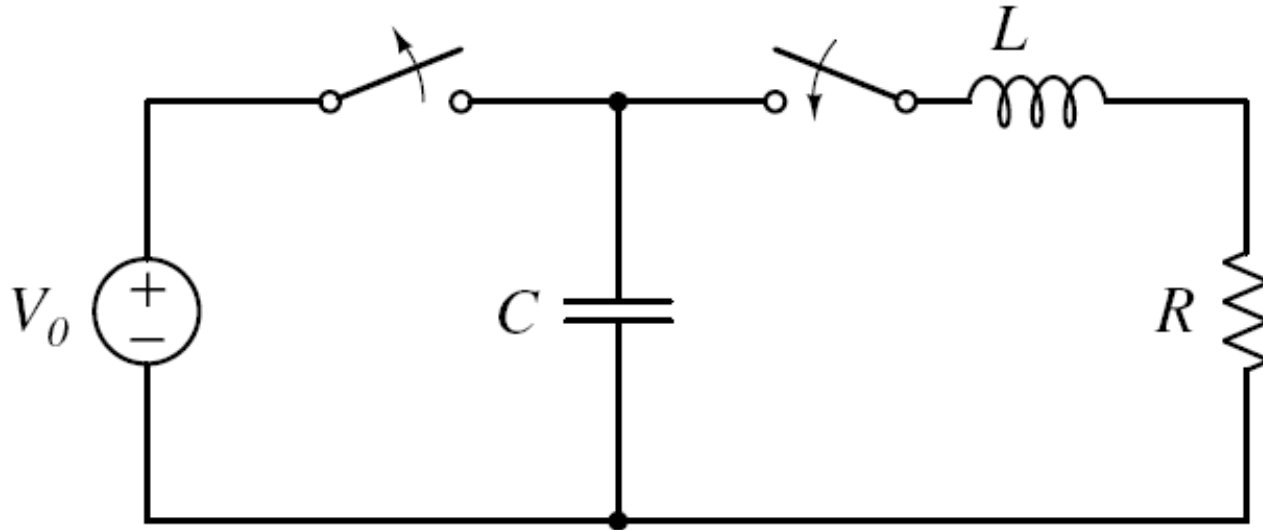
# Second order Circuits

- The **state** can be represented using a second order differential equation only.


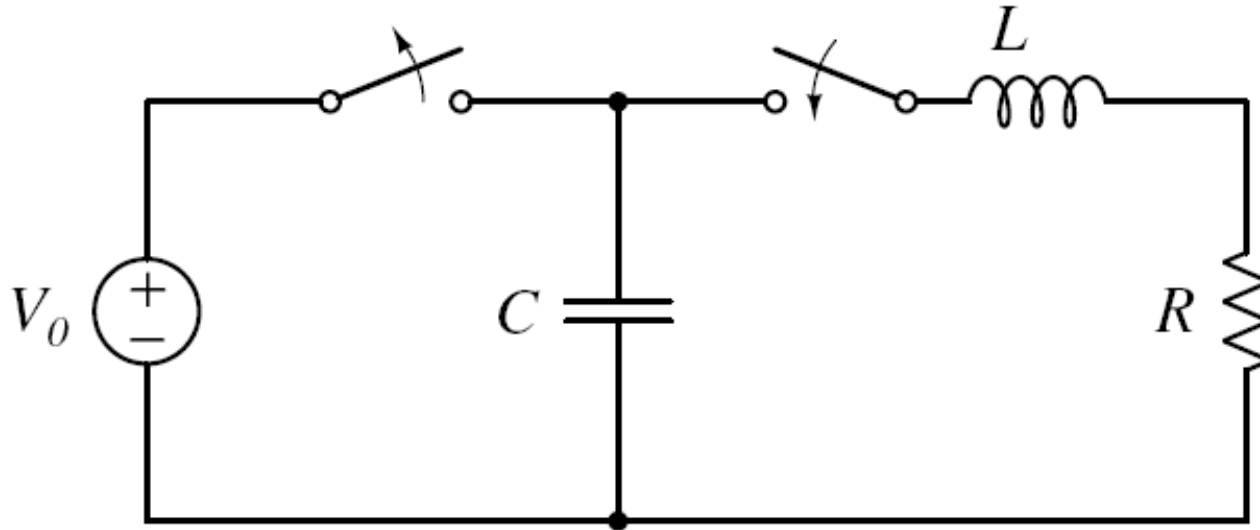
# Second order Circuits

- The **state** can be represented using a second order differential equation only.



After the switch is toggled the loop equation becomes :

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = 0$$

Differentiating this equation gives

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

# Solution

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

- Similar to the first order circuit case, assume the template  $Ae^{st}$

# Solution

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

- Similar to the first order circuit case, assume the template  $Ae^{st}$
- Plugging in the template into the differential equation gives

$$s^2 LAe^{st} + sRAe^{st} + \frac{1}{C}Ae^{st} = 0$$

or  $Js^2 + Rs + \frac{1}{C} = 0$

# Solution(s)

- The quadratic equation in 's' has two solutions

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$
$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

# Solution(s)

- The quadratic equation in 's' has two solutions

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$
$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

- This gives the general solution as

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



# Initial Conditions

- In order to solve for the two parameters  $A_1$  and  $A_2$ , we need two initial conditions.

# Initial Conditions

- In order to solve for the two parameters  $A_1$  and  $A_2$ , we need two initial conditions.
- The current through the inductor at  $t = 0^+$ ,  $i(0^+) = 0$
- The voltage across the capacitor at  $t = 0^+$ ,  $v_c(0^+) = V_0$ 
  - This gives  $L \frac{di}{dt} \big|_{t=0^+} = V_0$
- These two conditions can be used to figure out  $A_1$  and  $A_2$ .

# The Nature of the Roots

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- The two roots  $s_1$  and  $s_2$  can be in one of the following configurations.
- Real Roots
  - Distinct  $L = 1 \text{ H}, C = 1/3 \text{ F}, R = 4 \text{ } \Omega, s^2 + 4s + 3 = 0, s = -3, -1$   
 $\xi = \frac{R}{2} \sqrt{\frac{C}{L}} > 1$

# The Nature of the Roots

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- The two roots  $s_1$  and  $s_2$  can be in one of the following configurations.

- Real Roots

- Distinct

- Repeated  $L = 0.5 \text{ H}, C = 0.5 \text{ F}, R = 2 \text{ } \Omega, s^2 + 4s + 4 = 0, s = -2, -2$

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}} = 1$$

# The Nature of the Roots

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- The two roots  $s_1$  and  $s_2$  can be in one of the following configurations.
- Real Roots
  - Distinct
  - Repeated
- Complex conjugate pairs of roots.

$$L = 1 \text{ H}, C = 1/17 \text{ F}, R = 2 \text{ } \Omega, \quad s^2 + 2s + 17 = 0, \quad s = -1 \pm 4j$$

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}} < 1$$

# Real and Distinct Roots

$$L = 1 \text{ H}, C = 1/3 \text{ F}, R = 4 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 4s + 3 = 0, \quad s = -3, -1$$

- Thus, the solution is  $i(t) = A_1 e^{-t} + A_2 e^{-3t}$


# Real and Distinct Roots

$$L = 1 \text{ H}, C = 1/3 \text{ F}, R = 4 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 4s + 3 = 0, \quad s = -3, -1$$

- Thus, the solution is  $i(t) = A_1 e^{-t} + A_2 e^{-3t}$
- Initial conditions give
  - Initial current  $i(0^+) = 0, \implies A_1 = -A_2$
  - And  $L \frac{di}{dt} \big|_{t=0^+} = V_0, \implies V_0 = -A_1 - 3A_2 = 2A_1$
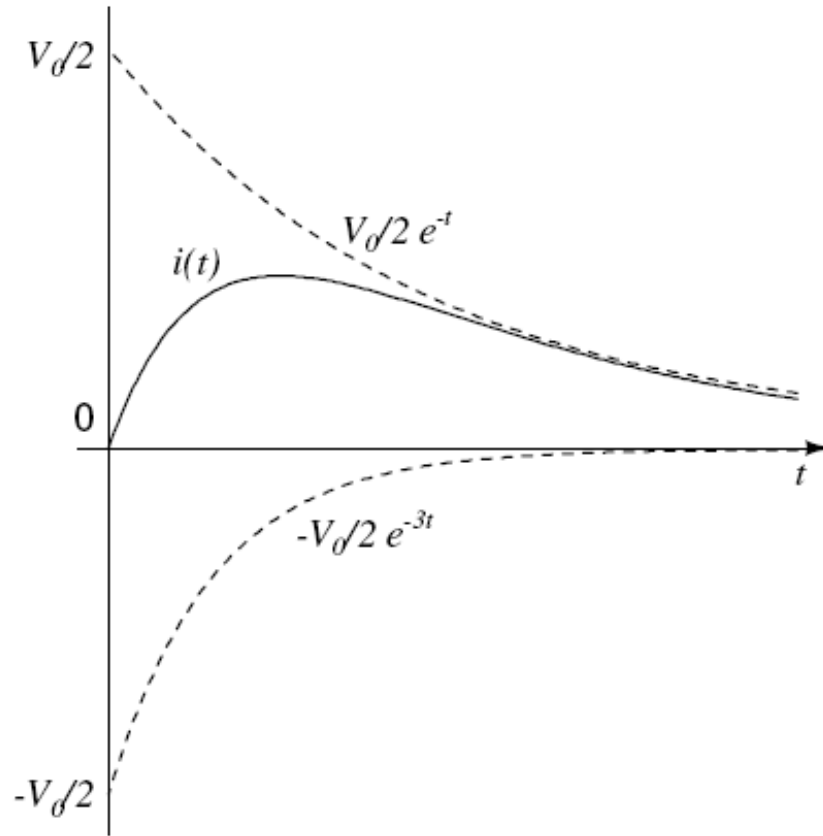
# Real and Distinct Roots: Overdamped Response

- The value of current is thus,  $i(t) = \frac{V_0}{2} (e^{-t} - e^{-3t})$





# Complex Conjugate Roots

$$L = 1 \text{ H}, C = 1/17 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 2s + 17 = 0, \quad s = -1 \pm 4j$$

- When  $s = -\alpha \pm j\omega$ ,  $i(t) = e^{-\alpha t} (A_1 e^{j\omega t} + A_2 e^{-j\omega t})$
- With  $A_1$  and  $A_2$  being complex numbers.

# Complex Conjugate Roots

$$L = 1 \text{ H}, C = 1/17 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 2s + 17 = 0, \quad s = -1 \pm 4j$$

- When  $s = -\alpha \pm j\omega$ ,  $i(t) = e^{-\alpha t} (A_1 e^{j\omega t} + A_2 e^{-j\omega t})$
- With  $A_1$  and  $A_2$  being complex numbers.
- Because the current is a real quantity eventually,

$$i(t) = Ae^{-\alpha t} \cos(\omega t + \theta)$$

with  $A$ ,  $\theta$  to be calculated from the initial conditions.

# For the Example ,

$$L = 1 \text{ H}, C = 1/17 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 2s + 17 = 0, \quad s = -1 \pm 4j$$

$$i(t) = Ae^{-\alpha t} \cos(\omega t + \theta) = Ae^{-t} \cos(4t + \theta)$$

## For the Example ,

$$L = 1 \text{ H}, C = 1/17 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 2s + 17 = 0, \quad s = -1 \pm 4j$$

$$i(t) = Ae^{-\alpha t} \cos(\omega t + \theta) = Ae^{-t} \cos(4t + \theta)$$

- From, the initial condition


$$i(0) = A \cos(\theta) = 0, \implies \theta = -\pi/2, \implies i(t) = Ae^{-t} \sin(4t)$$

- And

$$L \frac{di}{dt} = \frac{di}{dt} \Big|_{t=0^+} = 4A = V_0$$
$$A = \frac{V_0}{4}$$
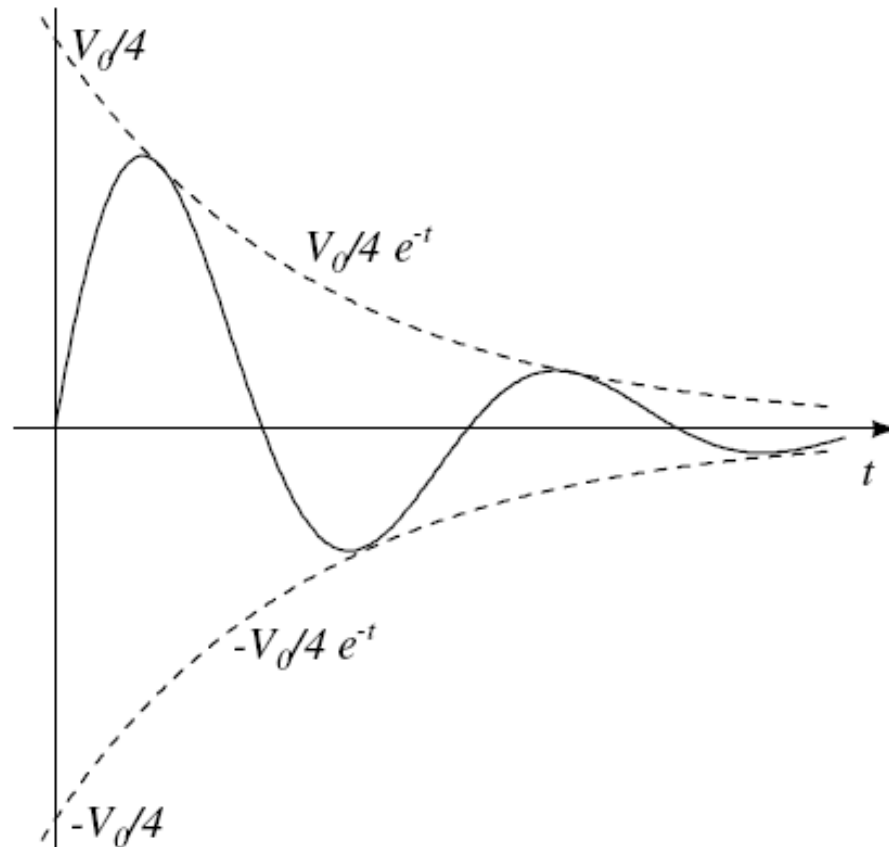
# Complex Roots: Underdamped Response

- The value of current is thus,  $i(t) = \frac{V_0}{4} e^{-t} \sin(4t)$



# Repeated Roots

$$L = 0.5 \text{ H}, C = 0.5 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 4s + 4 = 0, \quad s = -2, -2$$

- In this case the solution is NOT  $i(t) = A_1 e^{st} + A_2 e^{st} = (A_1 + A_2) e^{st}$

# Repeated Roots

$$L = 0.5 \text{ H}, C = 0.5 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 4s + 4 = 0, \quad s = -2, -2$$

- In this case the solution is NOT  $i(t) = A_1 e^{st} + A_2 e^{st} = (A_1 + A_2) e^{st}$
- It is not the most general solution for a second order differential equation
- The solution is of the form

$$i(t) = A_1 e^{st} + A_2 t e^{st}$$

# For the Example ,

$$L = 0.5 \text{ H}, C = 0.5 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 4s + 4 = 0, \quad s = -2, -2$$

$$i(t) = A_1 e^{-2t} + A_2 t e^{-2t}$$



## For the Example ,


$$L = 0.5 \text{ H}, C = 0.5 \text{ F}, R = 2 \text{ } \Omega,$$
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s^2 + 4s + 4 = 0, \quad s = -2, -2$$

$$i(t) = A_1 e^{-2t} + A_2 t e^{-2t}$$

- From the initial condition
- At  $t = 0, i(0) = 0, \implies A_1 = 0$
- Thus,  $i(t) = A_2 t e^{-2t}, \frac{di}{dt} = A_2 e^{-2t} - 2A_2 t e^{-2t}$
- At  $t = 0, \frac{di}{dt} = \frac{V_0}{L} = A_2$
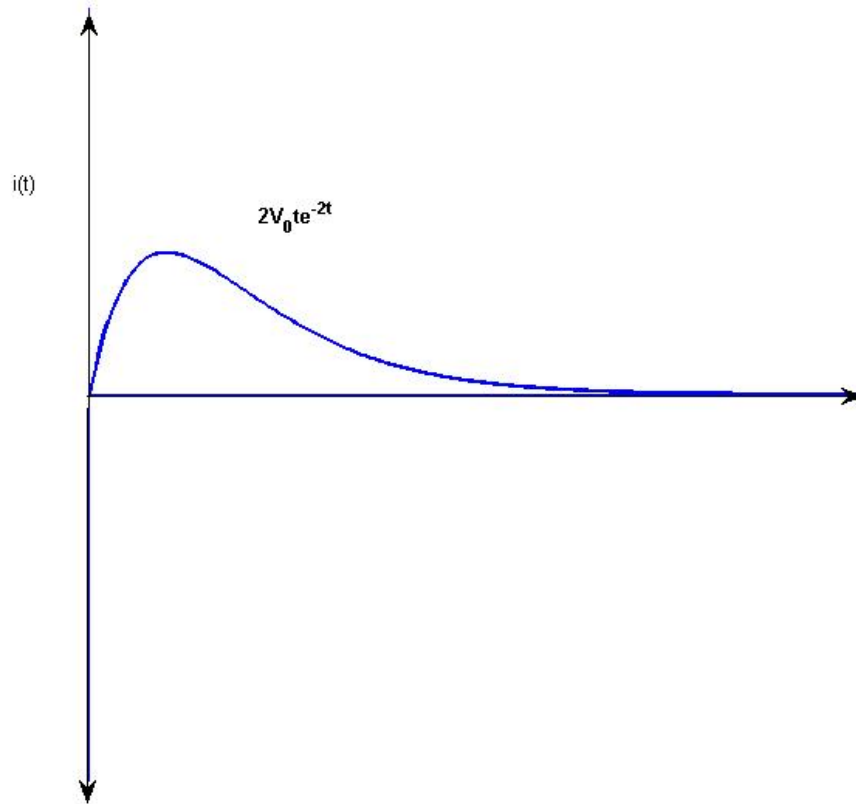
# Repeated Roots: Critically Damped Response

- The value of current is thus,  $i(t) = 2V_0te^{-2t}$




# Root Locus


- The two roots  $s_1$  and  $s_2$  change from being imaginary for  $R=0$  to real and distinct as  $R$  tends to infinity.
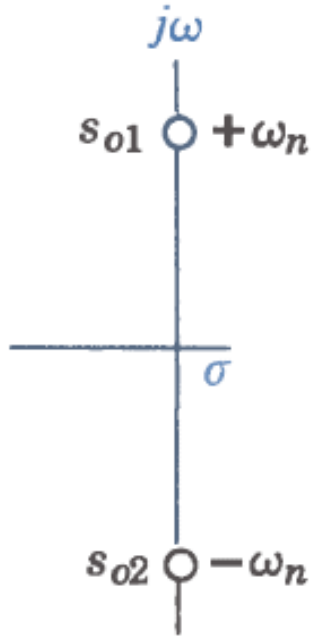
# Root Locus Plot


$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$




$R = 0$   
roots imaginary  
(c)

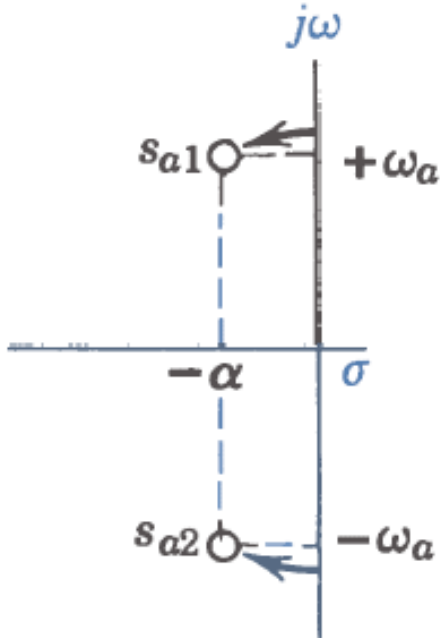


$R = R_a$   
roots complex  
(a)

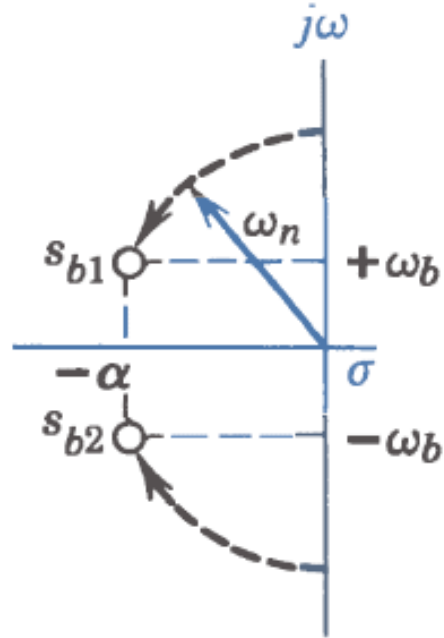

$R = R_b > R_a$   
roots complex  
(b)

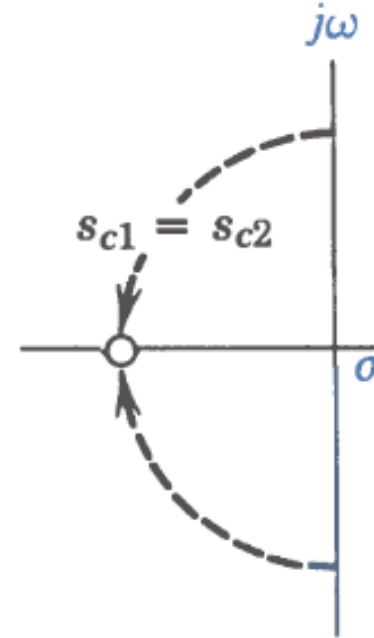

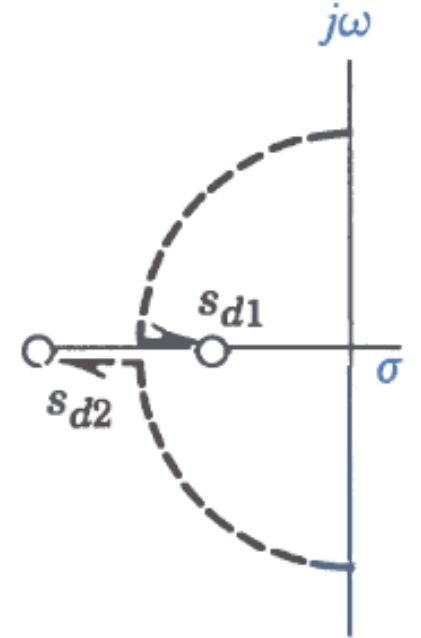$R = R_{\text{critical}}$   
roots identical  
(c)



$R = R_d > R_c$   
roots unequal  
(d)

# Root Locus

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- The two roots  $s_1$  and  $s_2$  change from being imaginary for  $R=0$  to real and distinct as  $R$  tends to infinity.
- $R=0$ , roots are on the  $j\omega$  axis: Sustained Oscillations (Undamped)
- $0 < R < 2\sqrt{\frac{L}{C}}$ , complex roots: Damped Oscillations (Underdamped)
- $R = 2\sqrt{\frac{L}{C}}$ , repeated roots: No Oscillations (Critical Damping)
- $R > 2\sqrt{\frac{L}{C}}$ , real and distinct roots: No Oscillations (Overdamped)