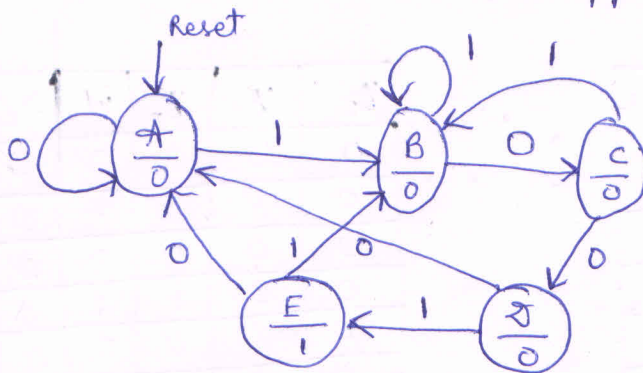



Tutorial - 5 Solutions

① Moore machine - Non-overlapped patterns "1001"




Reset \rightarrow A
 1 \rightarrow B
 10 \rightarrow C
 100 \rightarrow D
 1001 \rightarrow E

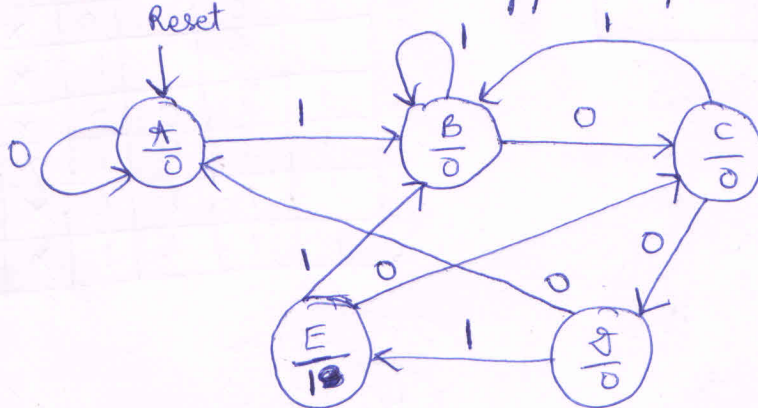② Moore machine - Overlapped pattern "1001"




Reset \rightarrow A
 1 \rightarrow B
 10 \rightarrow C
 100 \rightarrow D
 1001 \rightarrow E

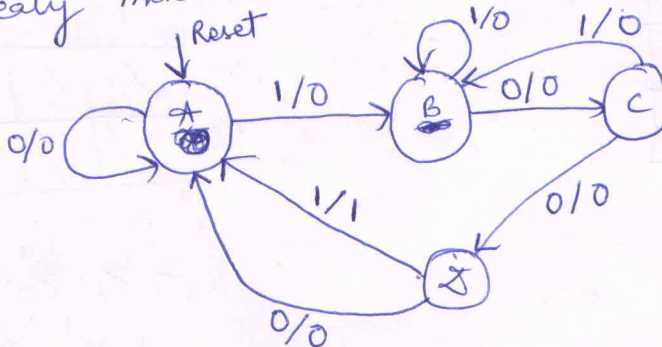③ Mealy machine - Non-overlapped pattern "1001"



Reset \rightarrow A
 1 \rightarrow B
 10 \rightarrow C
 100 \rightarrow D
 1001 \rightarrow A

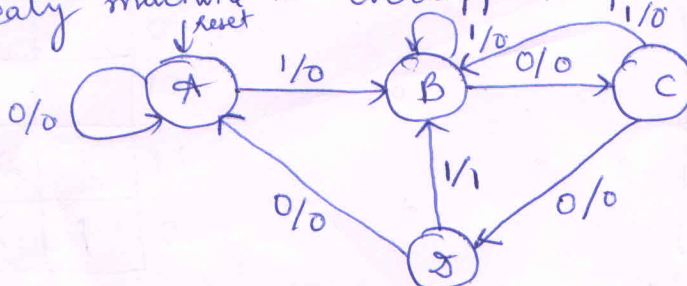
④ Mealy machine - Overlapped pattern "1001"




Reset \rightarrow A
 1 \rightarrow B
 10 \rightarrow C
 100 \rightarrow D
 1001 \rightarrow B

② Problem - 2

Clock

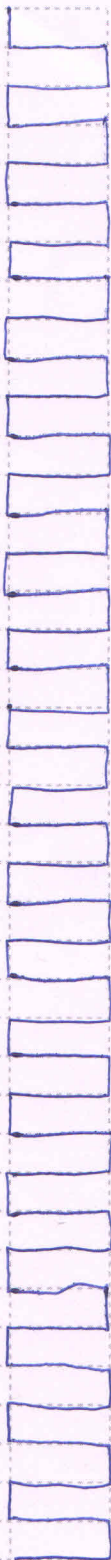


Input

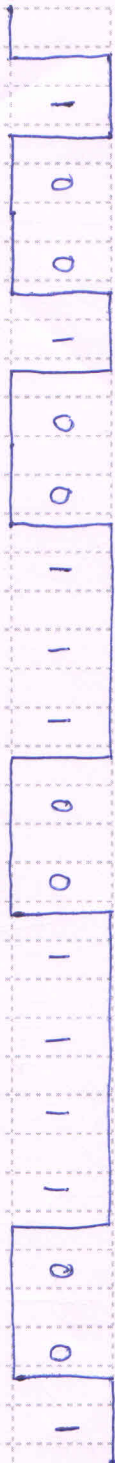

Moore - State
Non-overlapped




Moore - Output
Non-overlapped

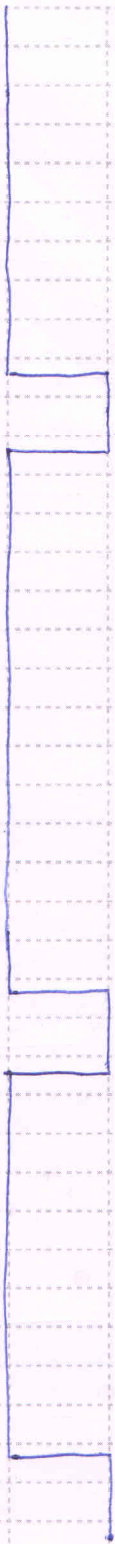

Mealy - State
Non-overlapped



Mealy - Output
Non-overlapped

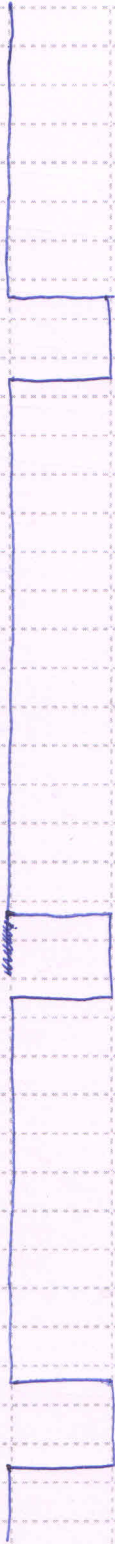

③ (i) Input, w
Output, z

Present state, y_2, y_1, y_0
Next state, Y_2, Y_1, Y_0

	Present State			Next State						Output Z
	y_2	y_1	y_0	w=0			w=1			
	y_2	y_1	y_0	Y_2	Y_1	Y_0	Y_2	Y_1	Y_0	
A →	0	0	0	0	0	0	0	0	1	0
B →	0	0	1	0	1	0	0	0	1	0
C →	0	1	0	0	1	1	0	0	1	0
D →	0	1	1	0	0	0	1	0	0	0
E →	1	0	0	0	1	0	0	0	1	1
	1	0	1	x	x	x	x	x	x	x
	1	1	0	x	x	x	x	x	x	x
	1	1	1	x	x	x	x	x	x	x

State Table

y_2	y_1	y_0	w	Y_2	Y_1	Y_0	z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	0	1	0
0	1	1	0	0	0	0	0
0	1	1	1	1	0	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	0	1	1
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

y_2

$y_2 y_1$ \ $y_0 w$	00	01	10	11
00				
01			1	
11	x	x	x	x
10			x	x

$$Y_2 = y_1 \cdot y_0 \cdot w$$

y_1

$y_2 y_1$ \ $y_0 w$	00	01	11	10
00				1
01	1			
11	x	x	x	x
10	1		x	x

$$Y_1 = y_1 \cdot y_0' \cdot w' + y_2 \cdot w' + y_1' \cdot y_0 \cdot w'$$

y_0

$y_2 y_1$ \ $y_0 w$	00	01	11	10
00		1	1	1
01	1	1		
11	x	x	x	x
10		1	x	x

$$Y_0 = y_1 \cdot y_0' + y_1' \cdot w$$



z

$y_2 y_1$ \ y_0	0	1
00		
01		
11	x	x
10	1	x

$$z = y_2$$

3 i

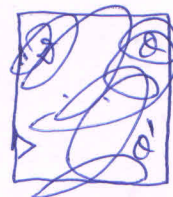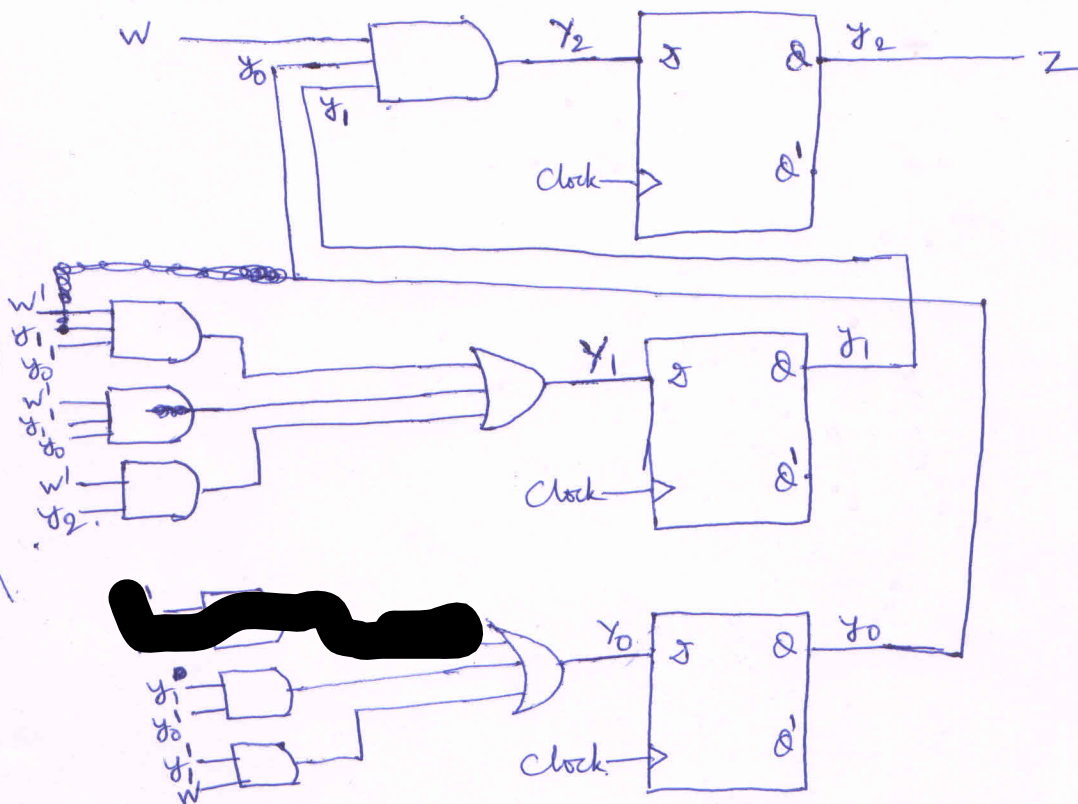The wires can be drawn. For simplicity I have removed them.



2

	Present State					Next State										Output <u>z</u>
						w=0					w=1					
	y ₄	y ₃	y ₂	y ₁	y ₀	y ₄	y ₃	y ₂	y ₁	y ₀	y ₄	y ₃	y ₂	y ₁	y ₀	
A	0	0	0	0	1	0	0	0	0	1	0	0	0	1	0	0
B	0	0	0	1	0	0	0	1	0	0	0	0	0	1	0	0
C	0	0	1	0	0	0	1	0	0	0	0	0	0	1	0	0
D	0	1	0	0	0	0	0	0	0	1	1	0	0	0	0	0
E	1	0	0	0	0	0	0	1	0	0	0	0	0	1	0	1

Since the expressions are simple, we can figure out the expressions for the next state ^{output} by observations.

$$y_4 = w \cdot y_3$$

$$y_3 = w' \cdot y_2$$

$$y_2 = w' \cdot (y_1 + y_4)$$

$$y_1 = w y_3'$$

$$y_0 = w' (y_0 + y_3)$$

$$z = y_4$$

These can be verified as shown in the following sheet.

③ ②

$$y_4 y_3 = 00$$

$$y_4 y_3 = 01$$

$$y_4 y_3 = 11$$

$$y_4 y_3 = 10$$

$y_4 \rightarrow$

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x		
01				x	x
11		x	x	x	x
10				x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00			1	x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x	x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00				x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$$y_4 = y_3 \cdot w$$

$y_3 \rightarrow$

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x		
01				x	x
11		x	x	x	x
10		1		x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00				x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x	x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00				x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$$y_3 = y_2 \cdot w'$$

$y_2 \rightarrow$

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x		
01		1		x	x
11		x	x	x	x
10				x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00				x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x	x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		1		x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$$y_2 = y_1 \cdot w' + y_4 w'$$

$y_1 \rightarrow$

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x	1	
01			1	x	x
11		x	x	x	x
10			1	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00				x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x	x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00			1	x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$$y_1 = y_3' \cdot w$$

$y_0 \rightarrow$

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x		1
01				x	x
11		x	x	x	x
10				x	x


$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		1		x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00		x	x	x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$y_4 y_3$	$y_2 y_1$	00	01	11	10
00				x	x
01		x	x	x	x
11		x	x	x	x
10		x	x	x	x

$$y_0 = y_2 w' + y_0 w'$$

③ ②

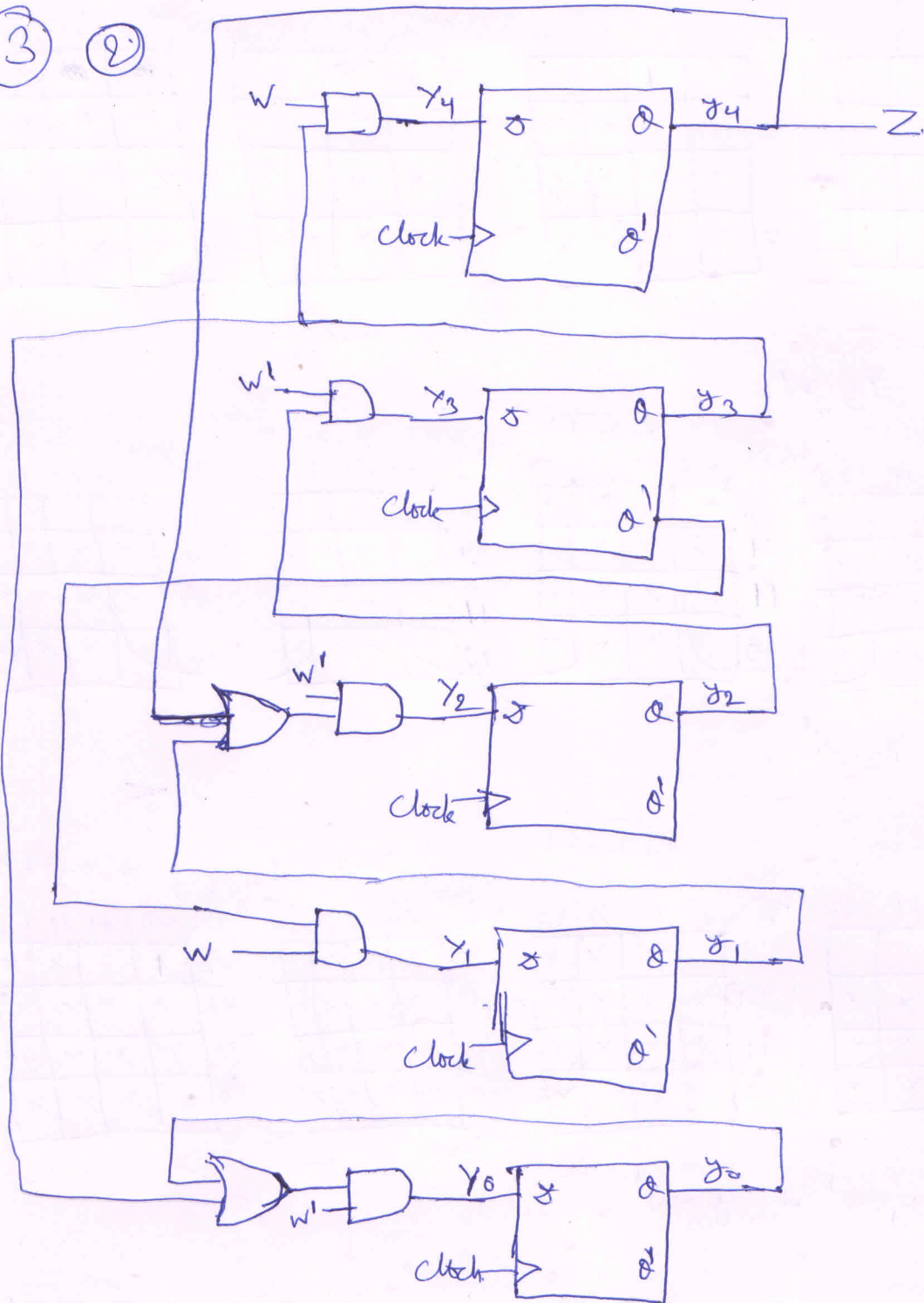

③ ③ The one-hot encoding requires more flip-flops & hence the cost in terms of the number of gates is higher for one-hot encoding when compared with the ~~first~~ ^{minimum} encoding method.

However, the one-hot encoding enables faster circuit because of the simple combinational circuits required to generate the next state as compared to the minimum encoding method.