



ELL100: INTRODUCTION TO ELECTRICAL ENGG.


Signal Waveforms

Course Instructors:


Manav Bhatnagar, Subashish Dutta, Debanjan Bhaumik, Harshan
Jagadeesh

Department of Electrical Engineering, IITD


Signal Waveforms

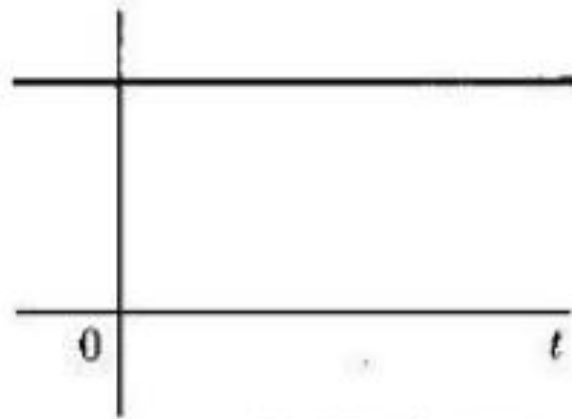

(a) Continuous

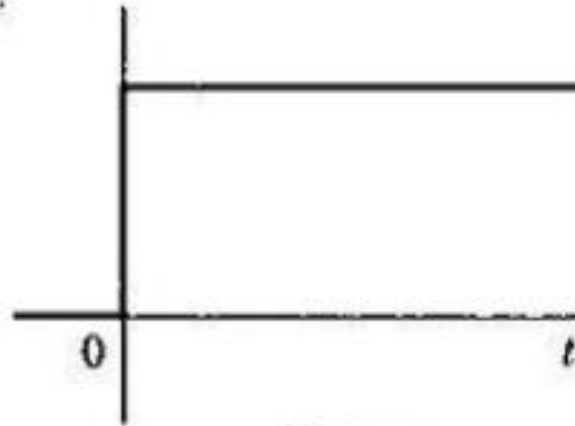


(b) Step

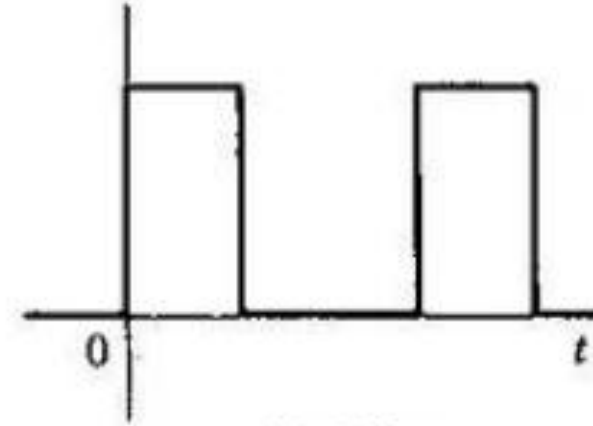


(c) Pulse


Common Signal Waveforms

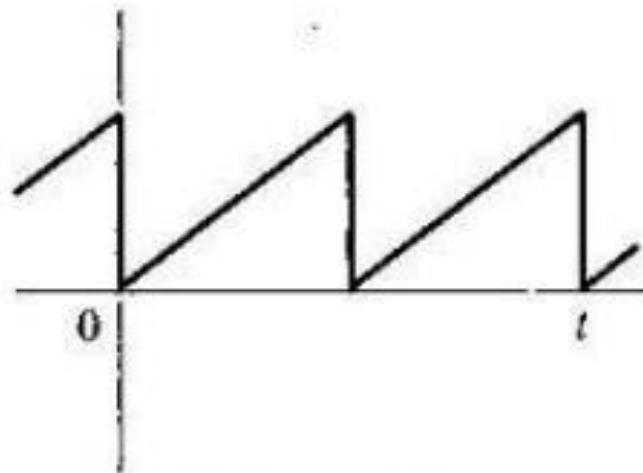

(d) Sawtooth

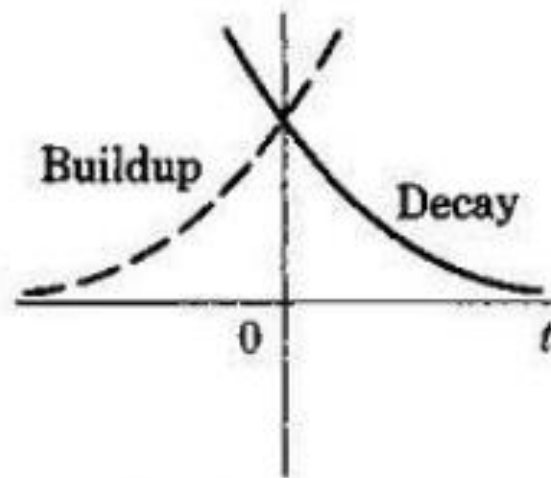


(e) Exponentials

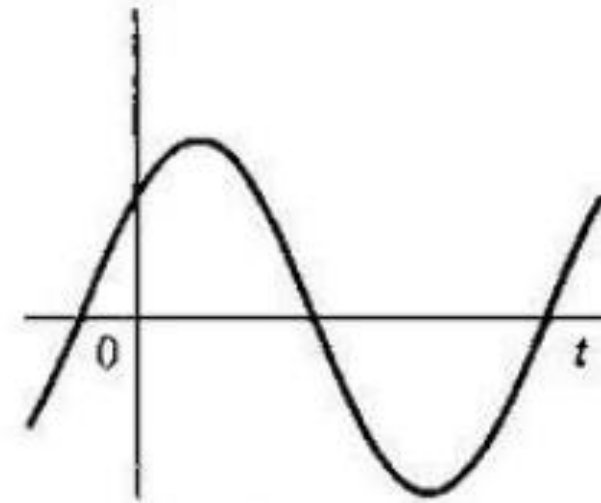

(f) Sinusoidal


Exponential Signals

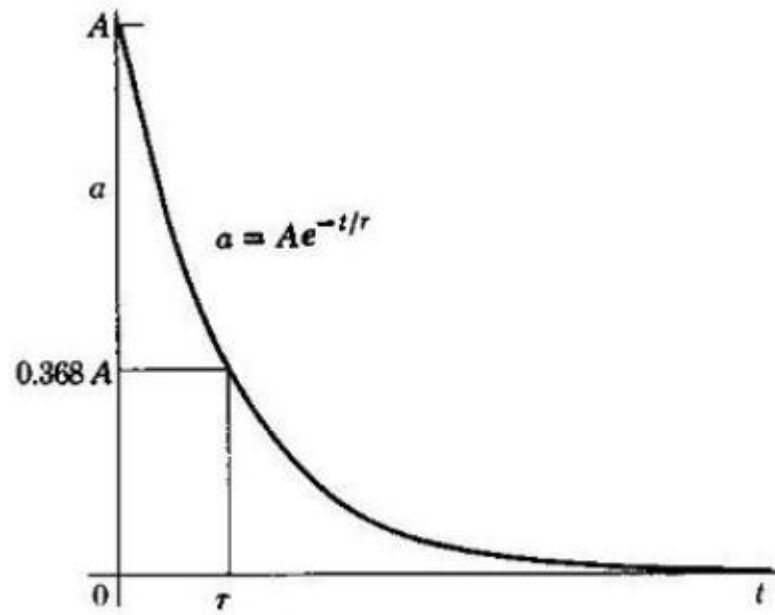

The decaying exponential.

$$a = A e^{-\frac{t}{\tau}}$$

Exponential Signals

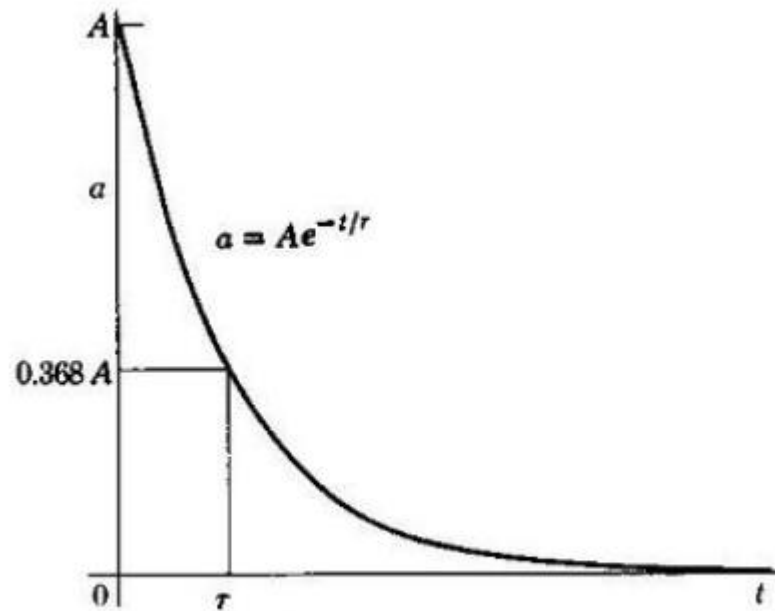

The decaying exponential.

$$a = A e^{-\frac{t}{\tau}}$$

Time constant

When $t = \tau = \text{Time Constant}$

$$e^{-\frac{t}{\tau}} = e^{-1} = 0.368$$


Normalized Exponentials

$$\frac{a}{A} = e^{-\frac{t}{\tau}}$$

For $t = 2\tau$, $a/A = 0.135$ and for $t = 5\tau$, $a/A = 0.0067$ i.e. practically negligible

Example 1

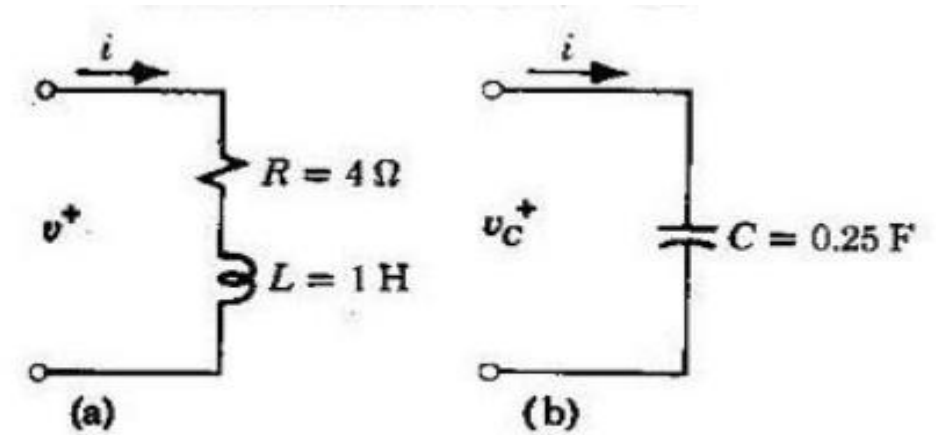- (a) Determine the voltage $v(t)$.
- (b) If the current $i = 5 e^{-2t}$ A flows in an initially uncharged 0.25-F capacitance ($v_C = 0$ at $t = 0$ in Fig. 3.5b), determine the voltage $v_C(t)$.




Response to exponentials.


Example 1

- (a) Determine the voltage $v(t)$.
- (b) If the current $i = 5 e^{-2t}$ A flows in an initially uncharged 0.25-F capacitance ($v_C = 0$ at $t = 0$ in Fig. 3.5b), determine the voltage $v_C(t)$.

the current $i = 5 e^{-2t}$ A

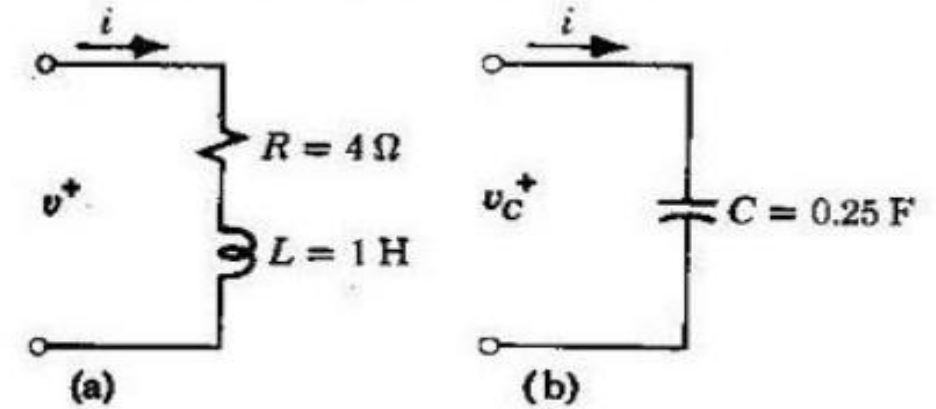


Response to exponentials.

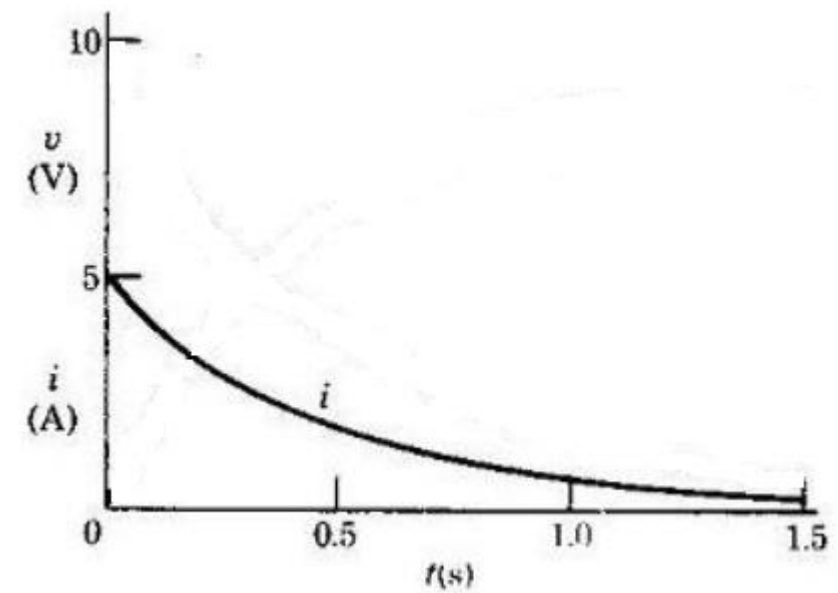

Example 1

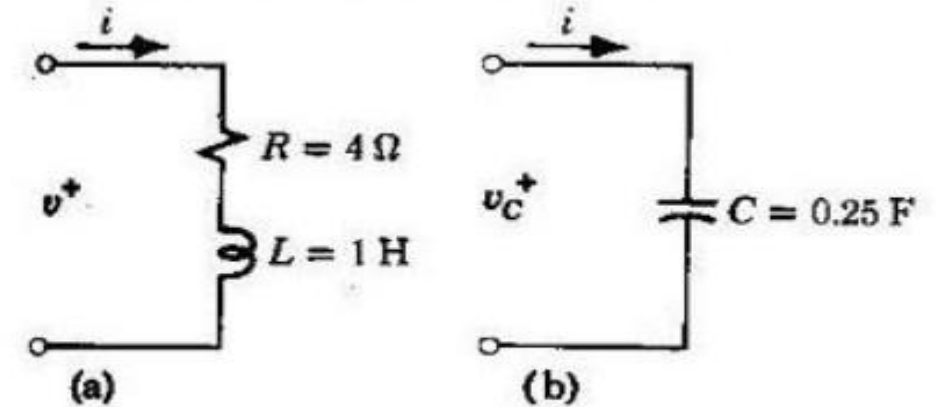- (a) Determine the voltage $v(t)$.
- (b) If the current $i = 5 e^{-2t}$ A flows in an initially uncharged 0.25-F capacitance ($v_C = 0$ at $t = 0$ in Fig. 3.5b), determine the voltage $v_C(t)$.
- the current $i = 5 e^{-2t}$ A.




Response to exponentials.

Solution

Step 1: Calculate V_R

$$v_R = Ri = 4 \times 5 e^{-2t} = 20 e^{-2t} \text{ V}$$

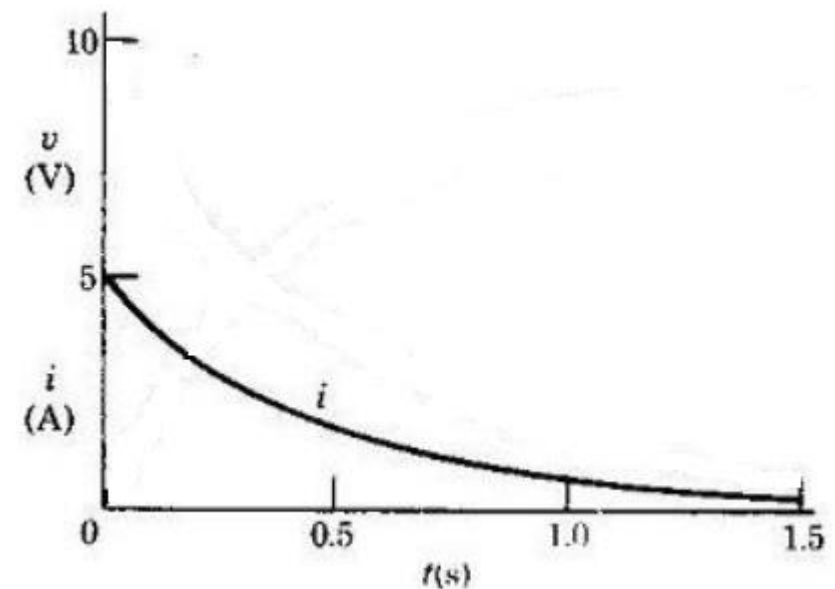


Example 1

(a) Determine the voltage $v(t)$.

(b) If the current $i = 5 e^{-2t}$ A flows in an initially uncharged 0.25-F capacitance ($v_C = 0$ at $t = 0$ in Fig. 3.5b), determine the voltage $v_C(t)$.

the current $i = 5 e^{-2t}$ A.

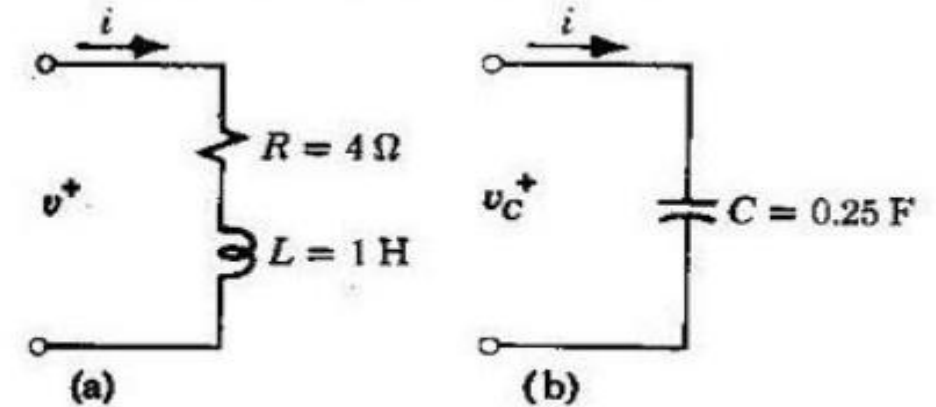

Response to exponentials.


Solution

Step 1: Calculate V_R

$$v_R = Ri = 4 \times 5 e^{-2t} = 20 e^{-2t} \text{ V}$$

Step 2: Calculate V_L

$$v_L = L \frac{di}{dt} = 1(-2)5 e^{-2t} = -10 e^{-2t} \text{ V}$$

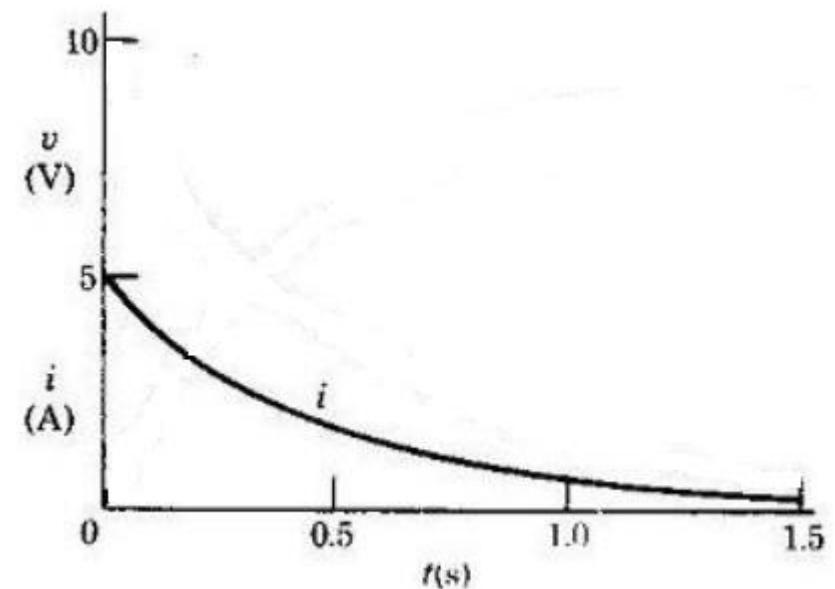

Example 1

Solution

Step 3: Calculate V_{RL}


$$v = v_R + v_L = 20 e^{-2t} - 10 e^{-2t} = +10 e^{-2t} \text{ V}$$

Example 1

Solution

Step 3: Calculate V_{RL}

$$v = v_R + v_L = 20 e^{-2t} - 10 e^{-2t} = +10 e^{-2t} \text{ V}$$

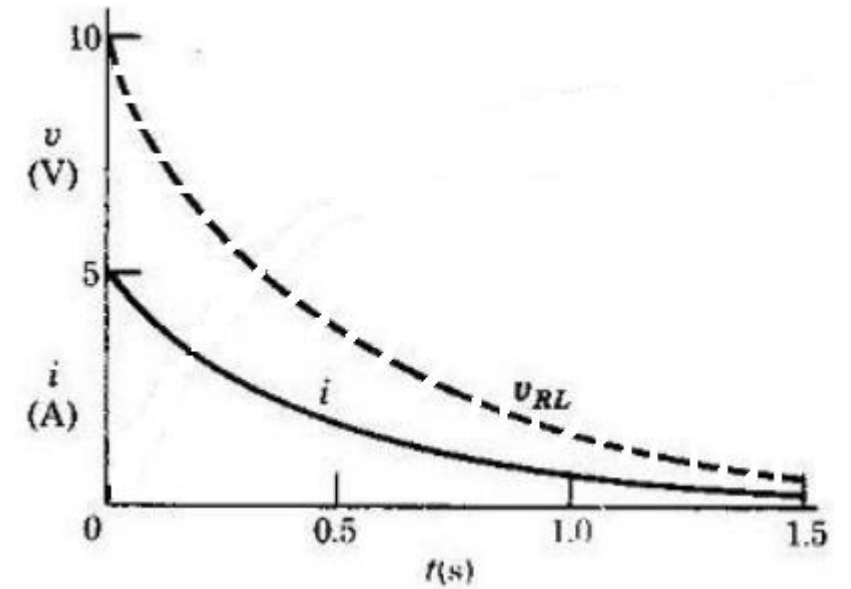

Example 1

Solution


Step 3: Calculate V_{RL}

$$v = v_R + v_L = 20 e^{-2t} - 10 e^{-2t} = +10 e^{-2t} \text{ V}$$

Step 4: Calculate V_C

$$v_C(t) = \frac{1}{C} \int_0^t i \, dt + V_O = \frac{1}{0.25} \int_0^t 5 e^{-2t} \, dt + 0$$

$$= \frac{5}{0.25(-2)} e^{-2t} \Big|_0^t = 10 - 10 e^{-2t} \text{ V}$$

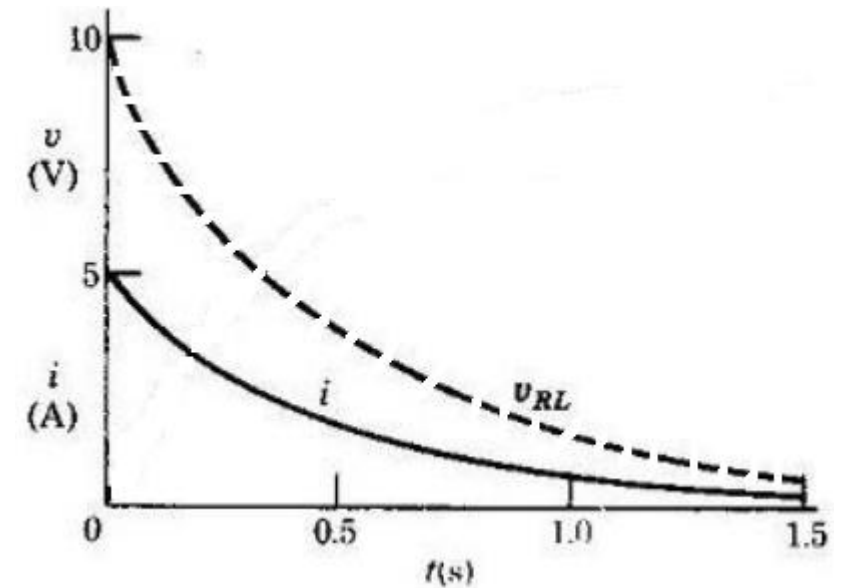

Example 1

Solution



Step 3: Calculate V_{RL}

$$v = v_R + v_L = 20 e^{-2t} - 10 e^{-2t} = +10 e^{-2t} \text{ V}$$

Step 4: Calculate V_C

$$v_C(t) = \frac{1}{C} \int_0^t i \, dt + V_O = \frac{1}{0.25} \int_0^t 5 e^{-2t} \, dt + 0$$


$$= \frac{5}{0.25(-2)} e^{-2t} \Big|_0^t = 10 - 10 e^{-2t} \text{ V}$$

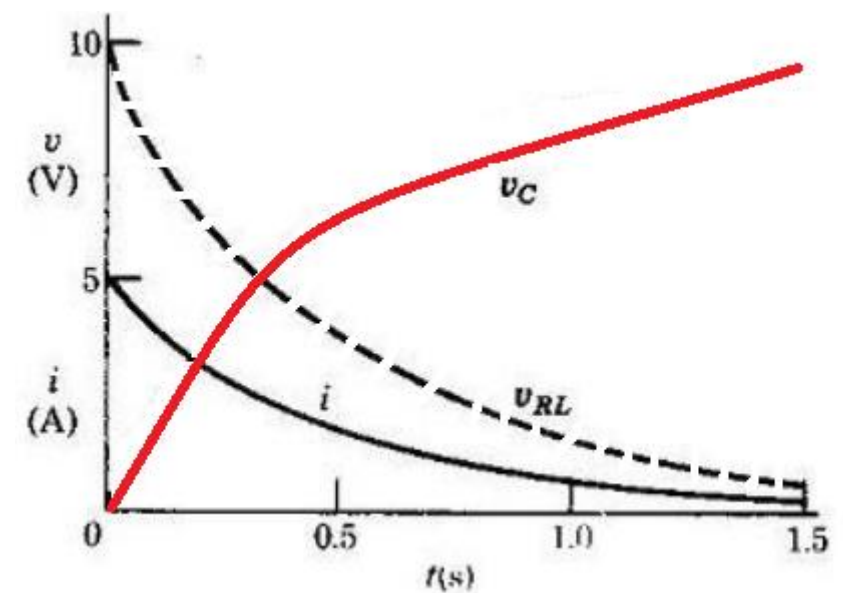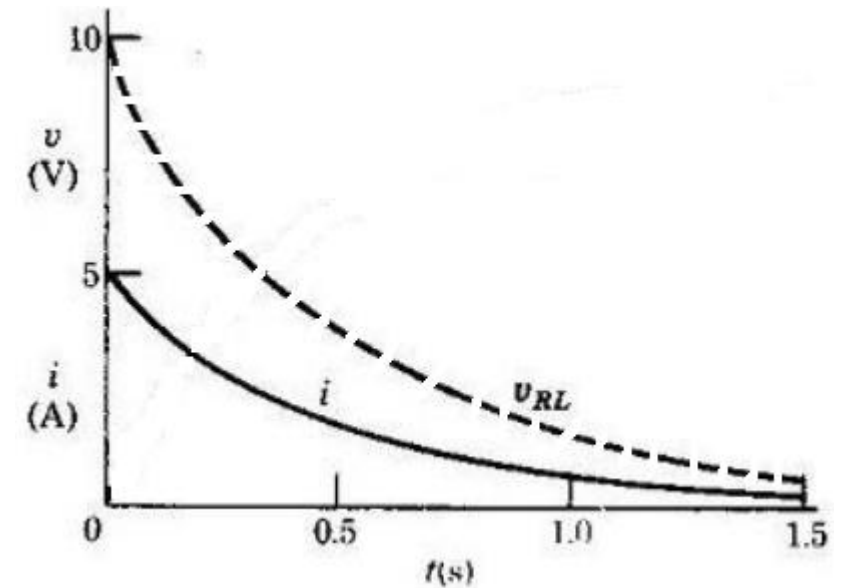

Sinusoids


Eg. Current in oscillating circuit, vibration of a string

$$a = A \cos(\omega t + \alpha) \quad , \quad f = \frac{\omega}{2\pi}$$
$$a = A \sin\left(\omega t + \alpha + \frac{\pi}{2}\right) \quad , \quad T = \frac{1}{f}$$

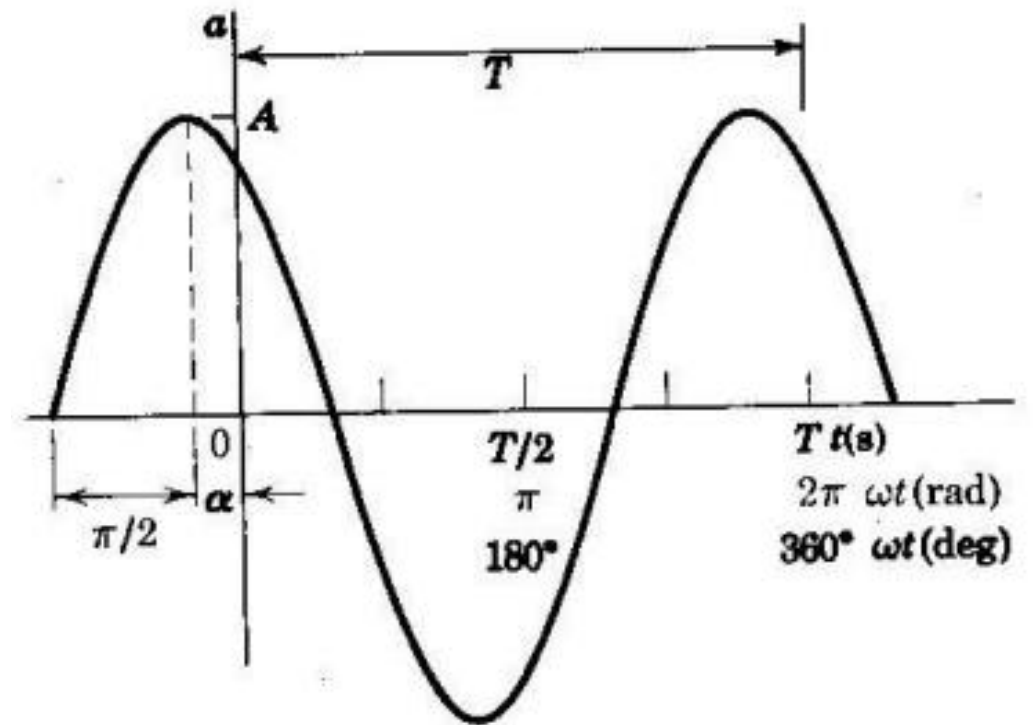

Example 2

A sinusoidal current with a frequency of 60 Hz reaches a positive maximum of 20 A at $t = 2$ ms. Write the equation of current as a function of time.

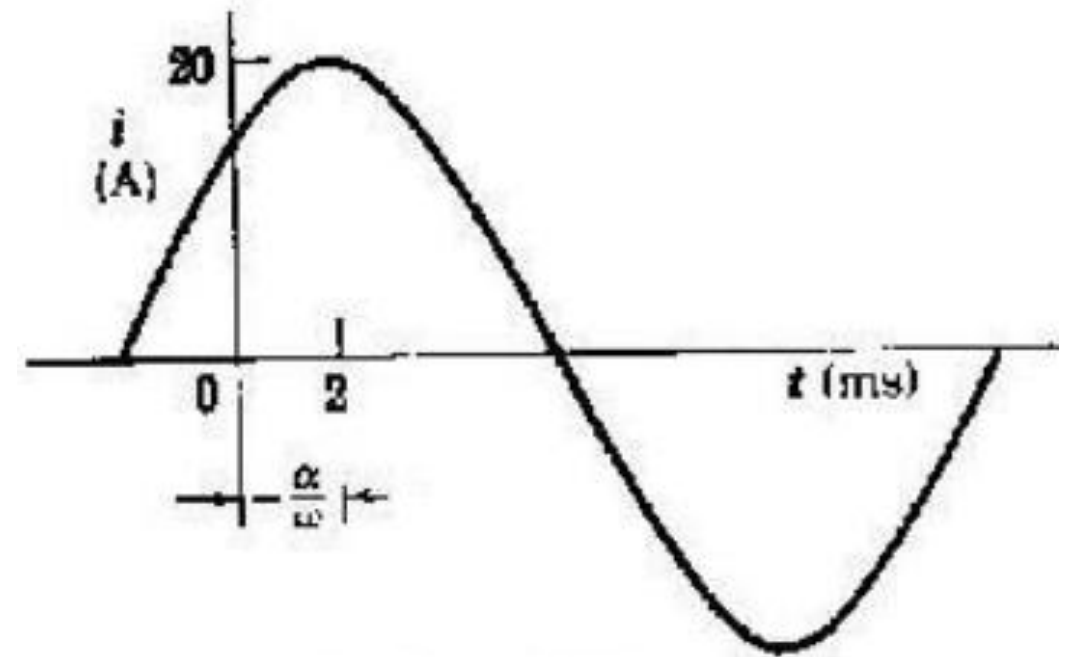


Example 2

A Sinusoidal current with a frequency of 60 Hz reaches a positive maximum of 20 A at $t = 2$ ms. Write the equation of current as a function of time.

As per Cosine wave equation,

$$A = 20 \text{ A}$$

$$\omega = 2\pi f = 2\pi (60) = 377 \text{ rad/s}$$

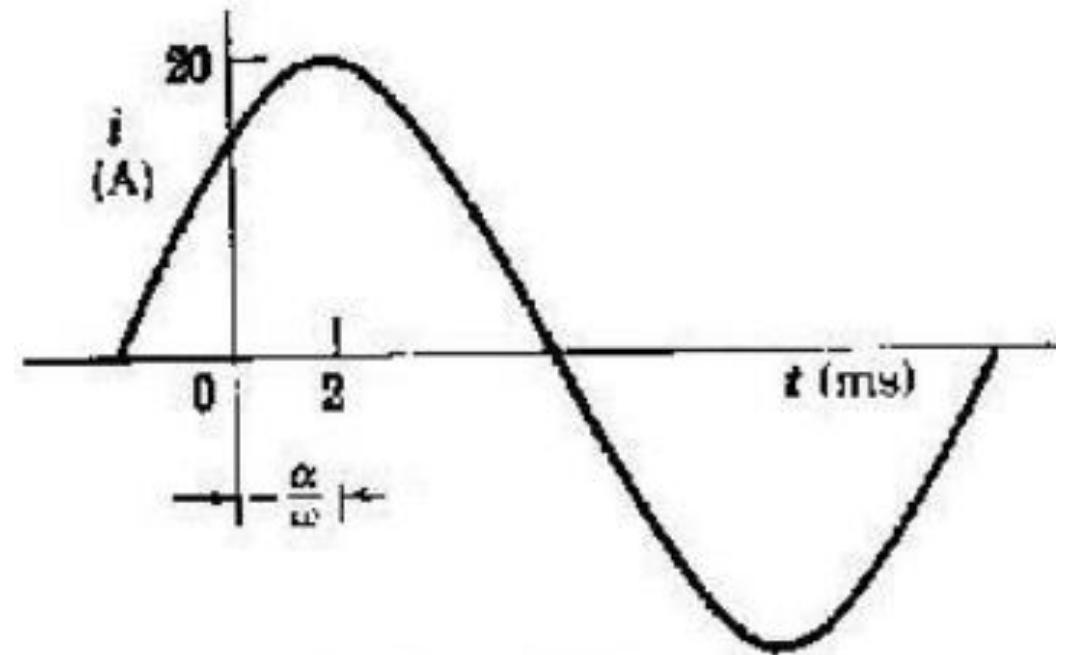

Example 2

A Sinusoidal current with a frequency of 60 Hz reaches a positive maximum of 20 A at $t = 2$ ms. Write the equation of current as a function of time.

As per Cosine wave equation,

$$A = 20 \text{ A}$$


$$\omega = 2\pi f = 2\pi (60) = 377 \text{ rad/s}$$

The positive maximum is reached when $(\omega t + \alpha) = 0$ or any multiple of 2π . Letting $(\omega t + \alpha) = 0$,

$$\begin{aligned}\alpha &= -\omega t \\ &= -377 * 2 * 10^{-3} \\ &= (-) 0.754 \text{ rad}\end{aligned}$$


Or

$$\begin{aligned}\alpha &= -0.754 * (360^\circ / 2\pi) \\ &= -43.2^\circ\end{aligned}$$

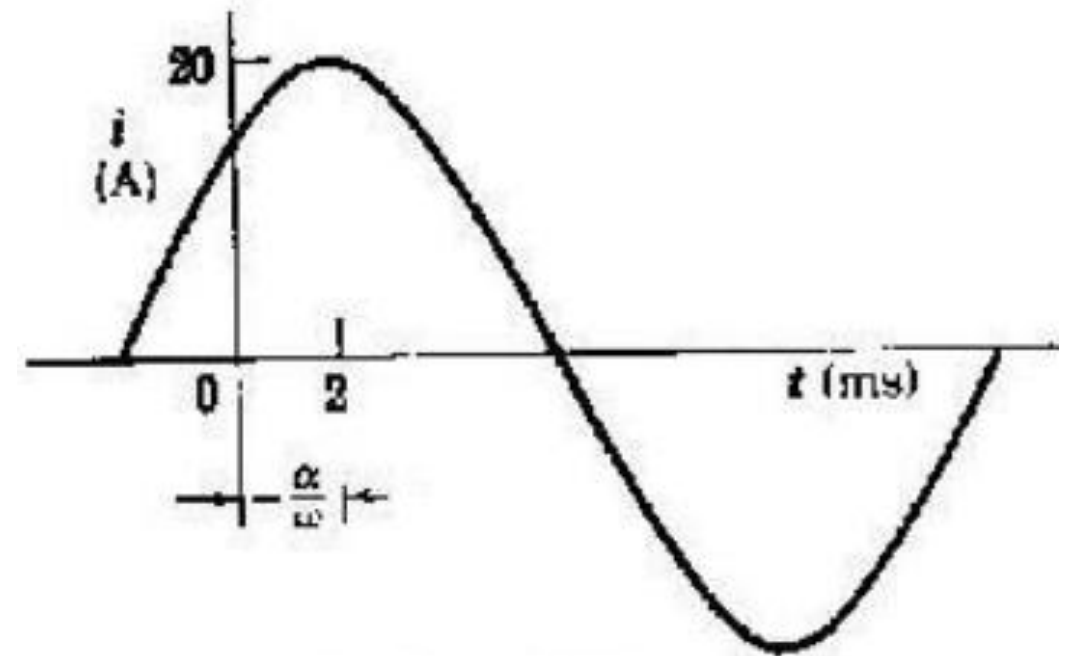

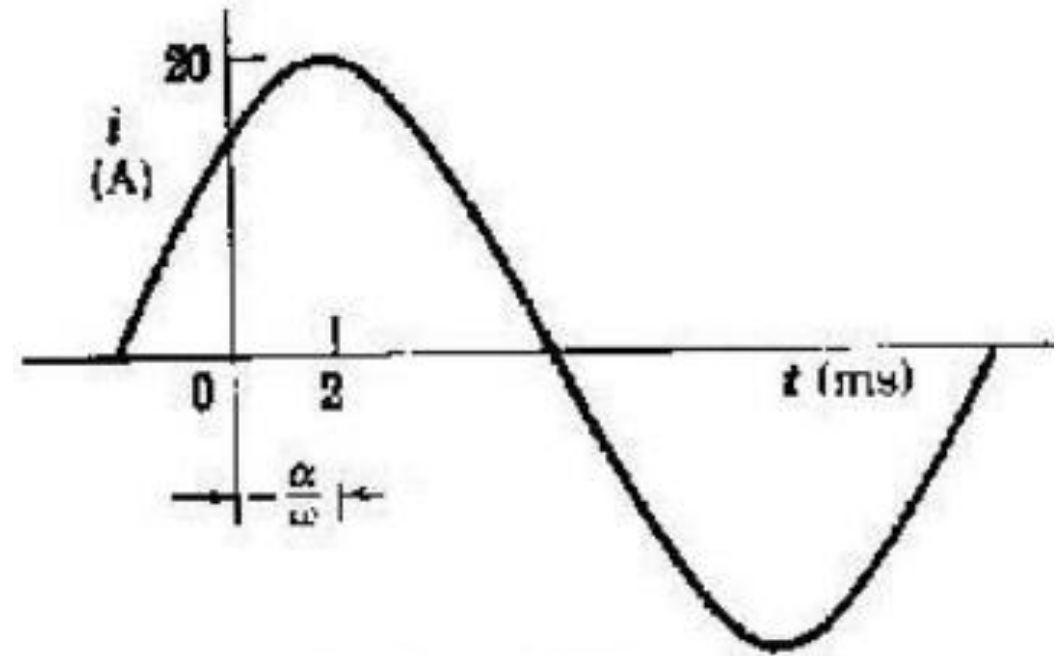Example 2

A Sinusoidal current with a frequency of 60 Hz reaches a positive maximum of 20 A at $t = 2$ ms. Write the equation of current as a function of time.




Therefore, the current equation is

$$i = 20 \cos(377t - 43.2^\circ) \text{ A}$$

Note that the angle in parentheses is a convenient hybrid; to avoid confusion, the degree symbol is essential.

Projections of a Rotating Line

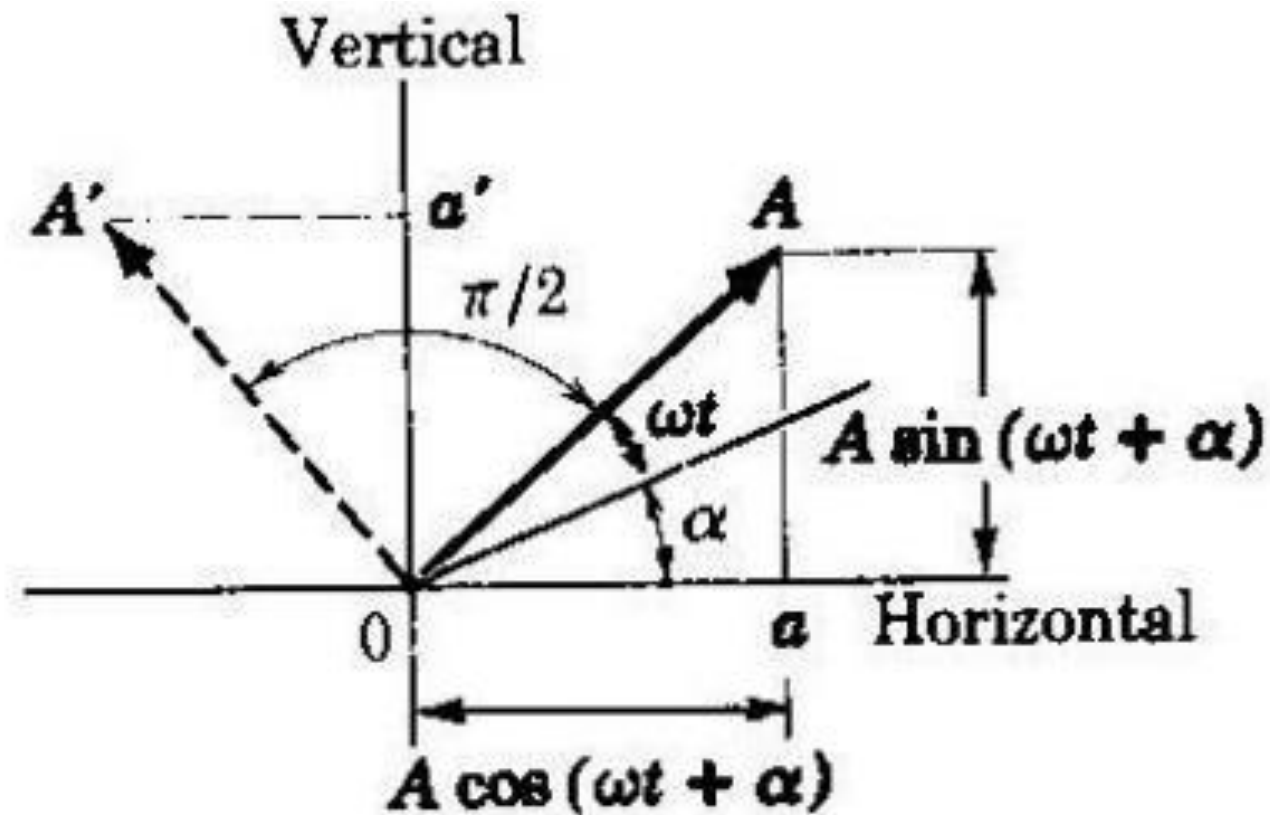


Horizontal projection : $a = A \cos(\omega t + \alpha)$


Vertical projection : $a' = A' \sin(\omega t + \alpha + \frac{\pi}{2})$

Periodic Waveforms

$$f(t + nT) = f(t)$$

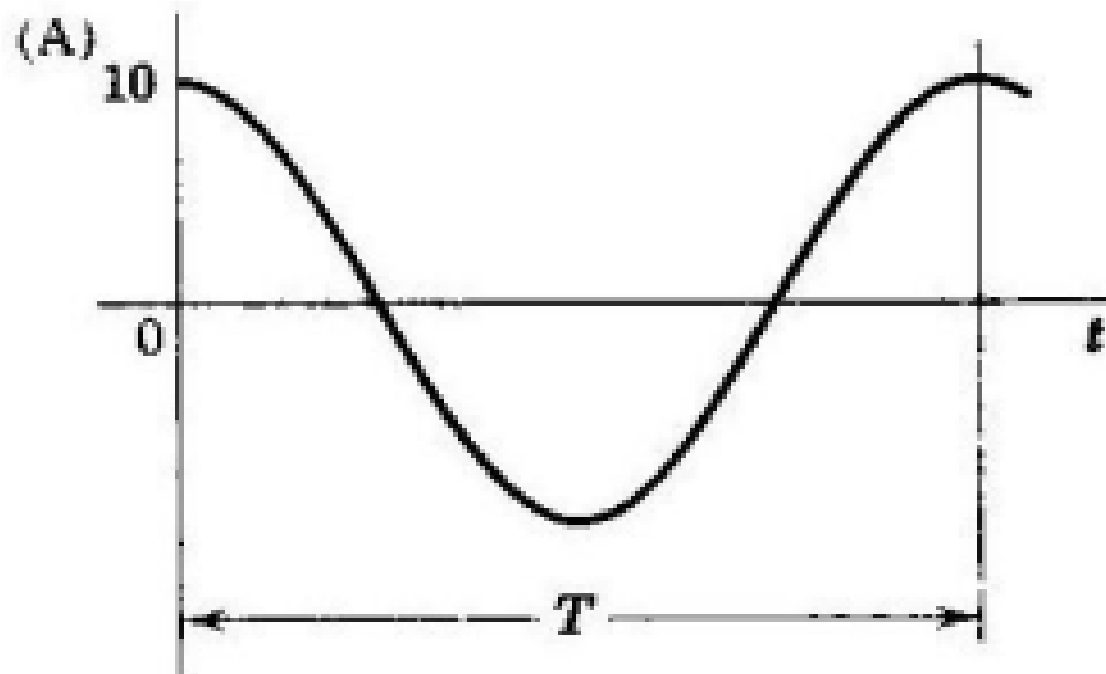

(a) Sinusoidal

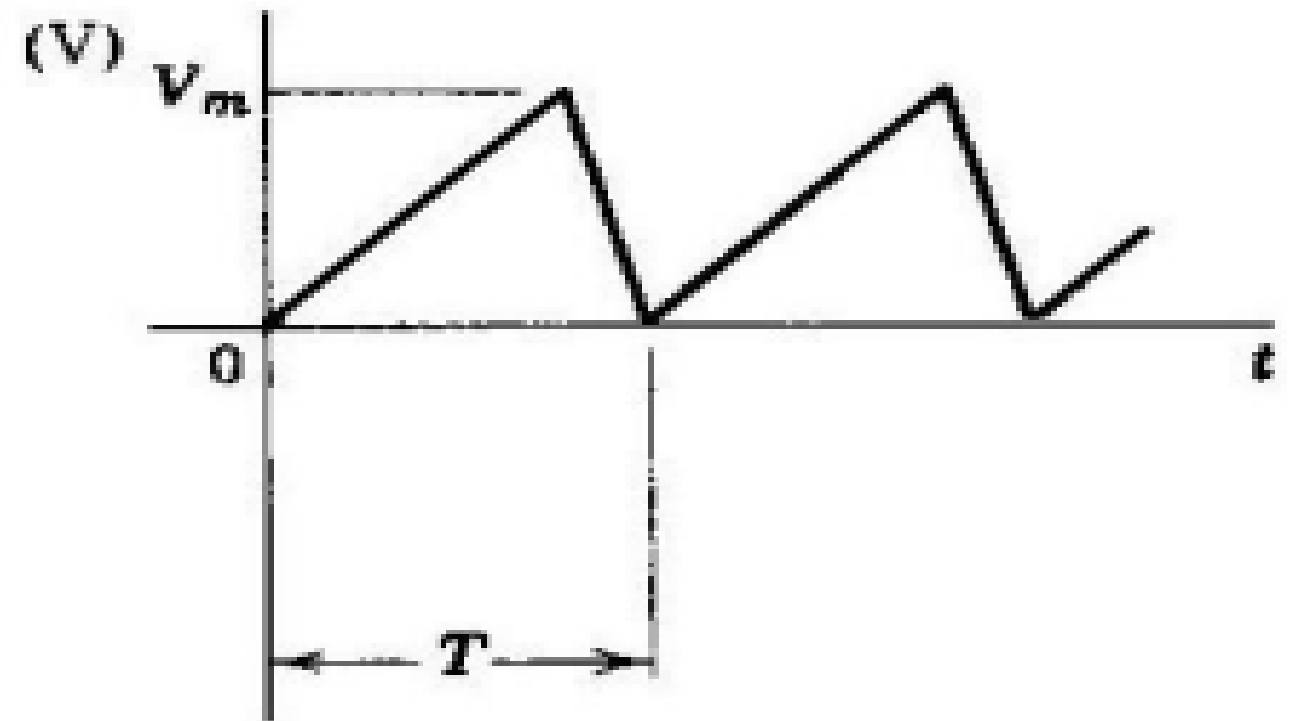

(b) Triangular

Periodic Waveforms

Average Value

The average value of a varying current $i(t)$ over the period T is the steady value of current I_{av} that in the period T would transfer the same charge Q

Periodic Waveforms

Average Value

The average value of a varying current $i(t)$ over the period T is the steady value of current I_{av} that in the period T would transfer the same charge Q

$$I_{av} T = Q = \int_t^{t+T} i(t) dt = \int_0^T i dt$$


or

$$I_{av} = \frac{1}{T} \int_0^T i(t) dt$$

Similarly,

$$V_{av} = \frac{1}{T} \int_0^T v(t) dt$$


Half-Cycle Average

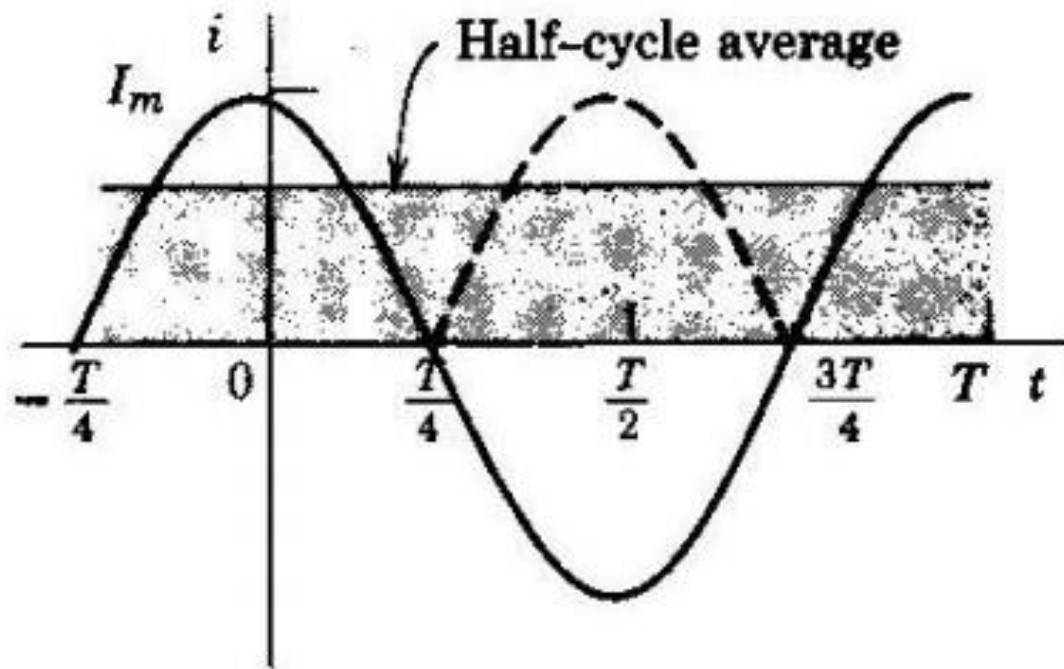

The half-cycle average.

Periodic Waveforms

Half cycle average

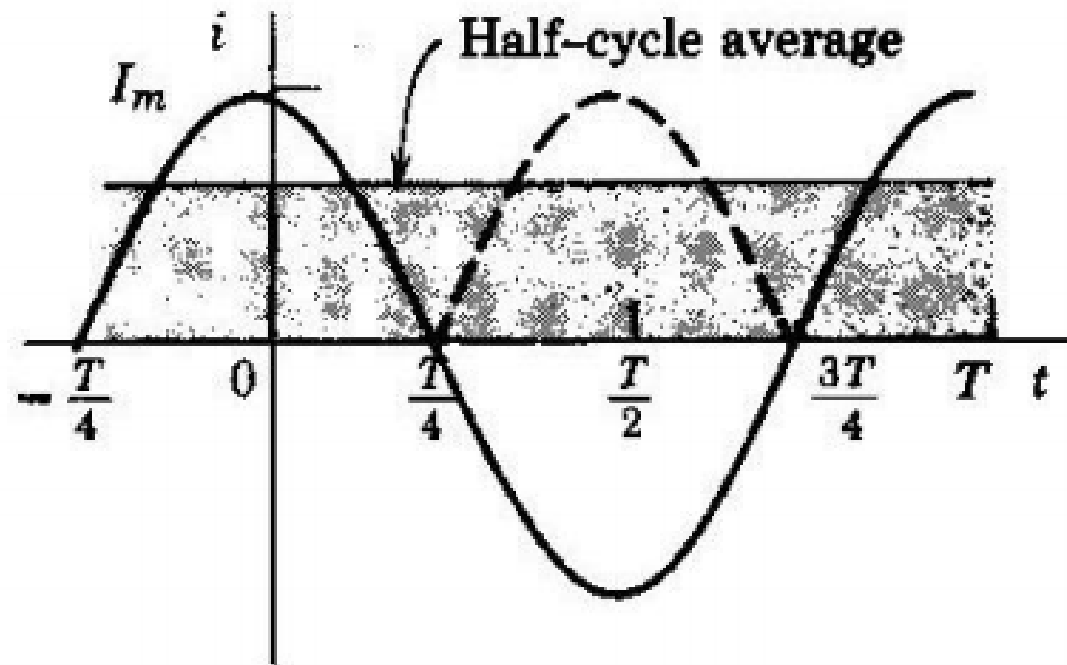

The half-cycle average.

$$\begin{aligned} I_{\text{half-cycle}} &= \frac{1}{\frac{1}{2}T} \int_{-T/4}^{+T/4} I_m \cos \frac{2\pi t}{T} dt \\ &= \frac{2I_m}{T} \left(\frac{T}{2\pi} \right) \sin \frac{2\pi t}{T} \Big|_{-T/4}^{+T/4} \\ &= \frac{I_m}{\pi} \left[\sin \left(\frac{\pi}{2} \right) - \sin \left(-\frac{\pi}{2} \right) \right] \\ &= \frac{2}{\pi} I_m = 0.637 I_m \end{aligned}$$

Effective Value

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt$$

Effective Value

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt$$

For a resistance case,

$$P = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T i^2 R dt = I_{eff}^2 R$$

where

$$I_{eff} = \left[\frac{1}{T} \int_0^T i^2 dt \right]^{1/2} = I_{rms}$$

Effective Value

For a sinusoidal current

$$\begin{aligned} I_{eff}^2 &= \frac{1}{T} \int_0^T I_m^2 \cos^2\left(\frac{2\pi t}{T}\right) dt \\ &= \frac{1}{T} \frac{I_m^2}{2} \int_0^T \left(1 + \cos\left(\frac{4\pi t}{T}\right)\right) dt = \frac{I_m^2}{2} \end{aligned}$$

$$\text{or } I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$